



# Industrial Electronics

Prepared By:  
Ajit Singh, Lecturer


# The p-n Junction

- ▶ A p-n junction is formed when p-type semiconductor is brought in metallurgical or physical contact with n-type semiconductor.
  - ▶ p-region has more holes concentration.
  - ▶ n- region has more electrons concentration.
- 


# The p-n Junction

- ▶ In p-region holes are majority carriers and electrons are minority carriers.
  - ▶ In n-region electrons are majority carriers and holes are minority carriers.
- 

# Depletion Layer

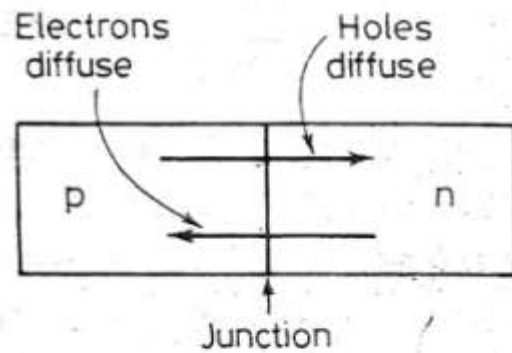


(a)

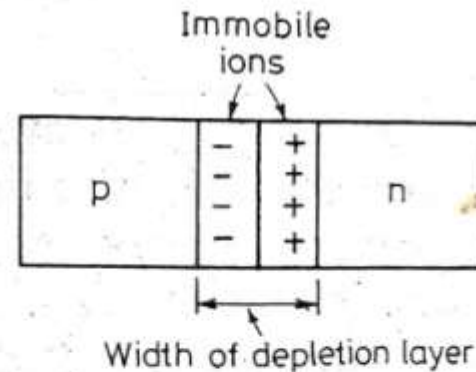


(b)

Depletion-layer width decreases

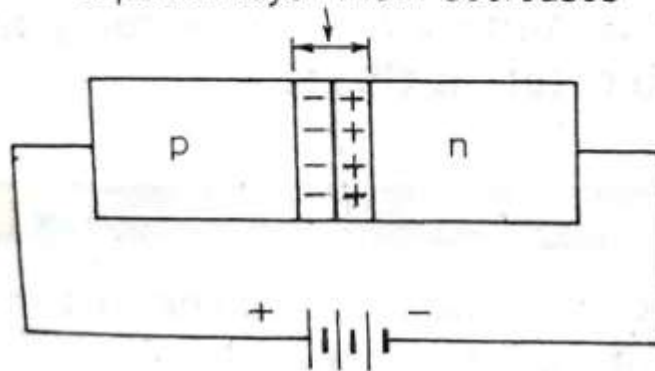


(c)


Depletion-layer width increases

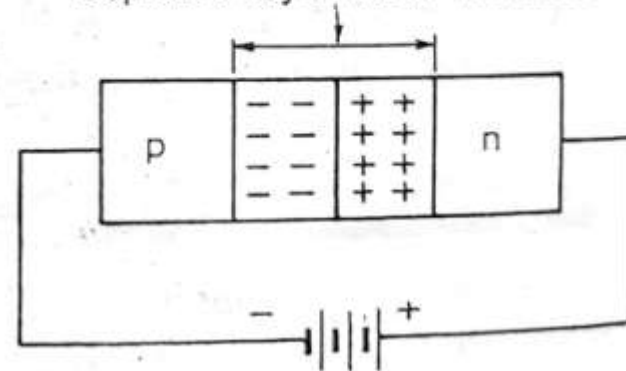

(d)

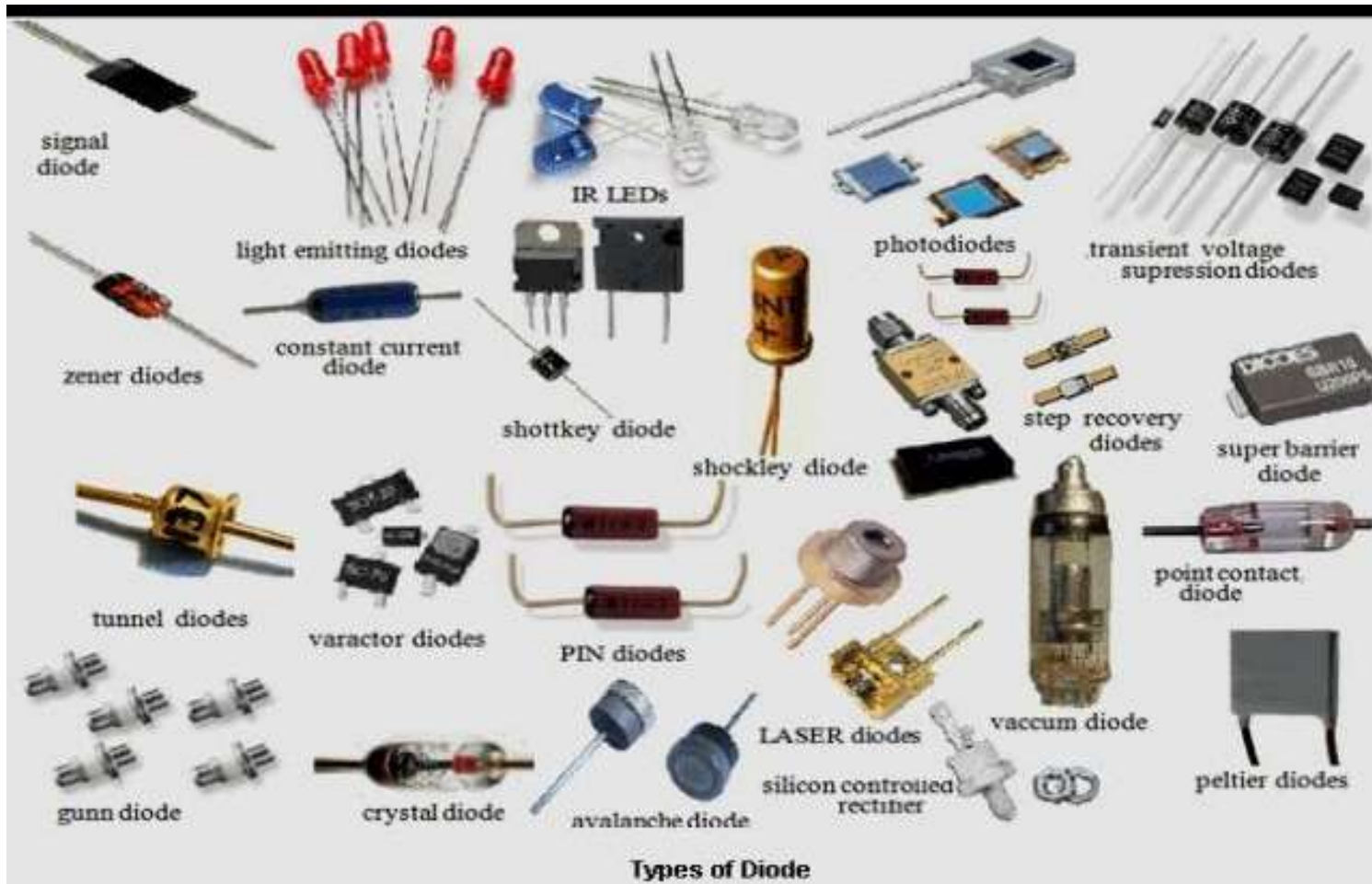


# Thyristor

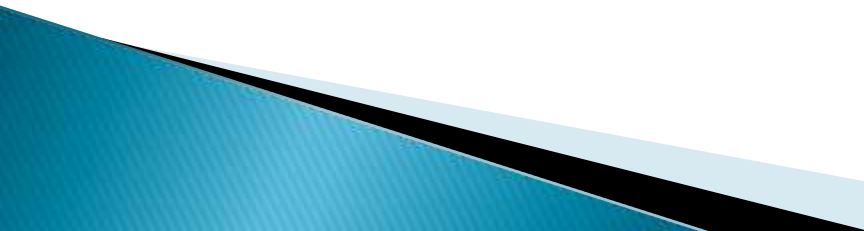- ▶ The term Thyristor denotes a family of semiconductor devices used for power control in DC and AC system.
  - ▶ Thyristor is a family of semiconductor devices like SCR, TRIAC, Diac, Silicon controlled Switch (SCS), Programmable Unijunction Transistor (PUT) etc.
  - ▶ The use of SCR is so vast that over the years, the word thyristor has become synonymous with SCR.
- 

# Thyristor


- ▶ Thyristor has characteristics similar to a thyatron tube.
- ▶ The name Thyristor is derived from combination of THYRatron and transISTOR.
- ▶ Thyristor:
  - Constitutes three or more p–n junctions.
  - Has two stable states, an ON state and an OFF state.
  - Can change its state from one to another.

# SCR (Silicon Controlled Rectifier)

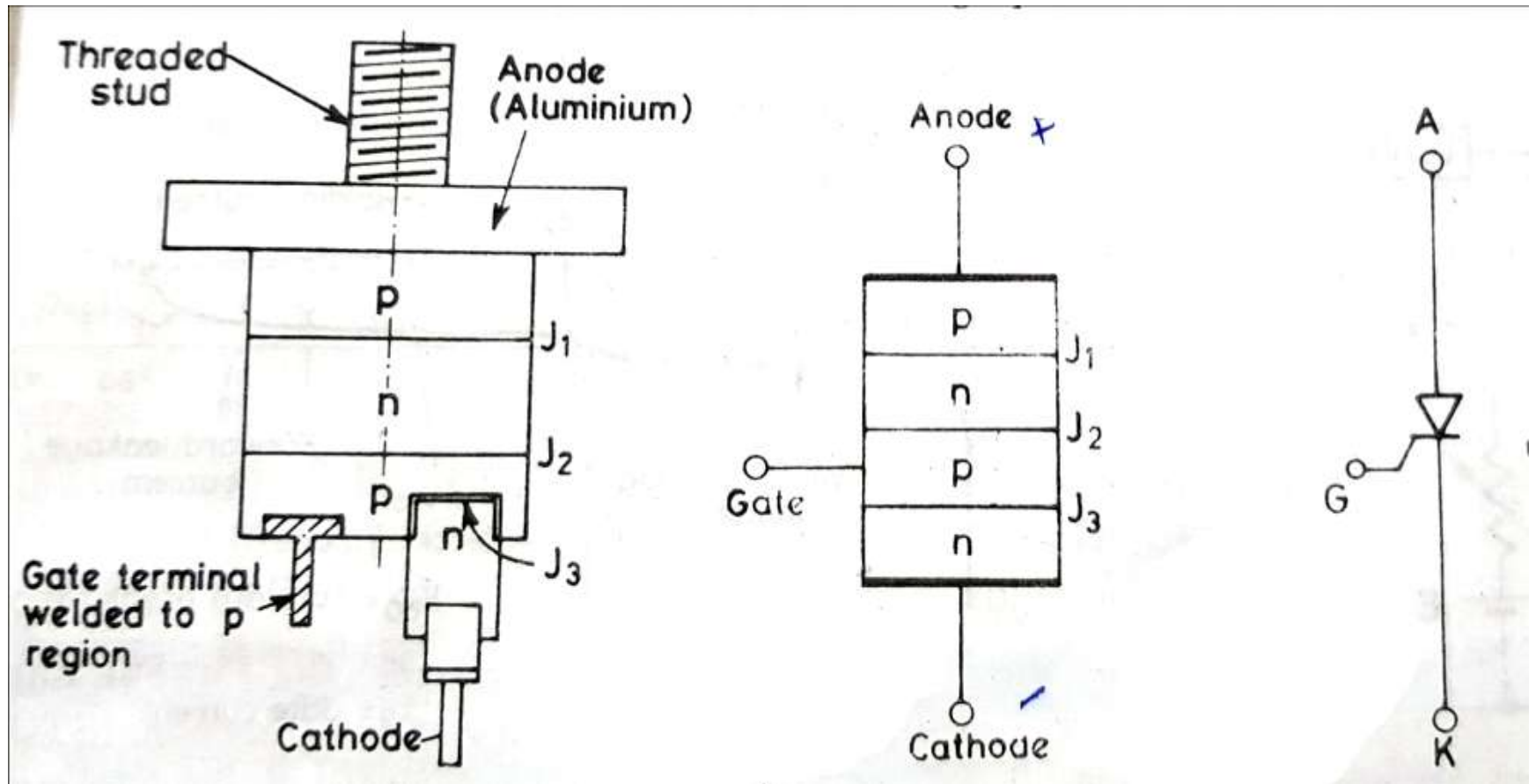






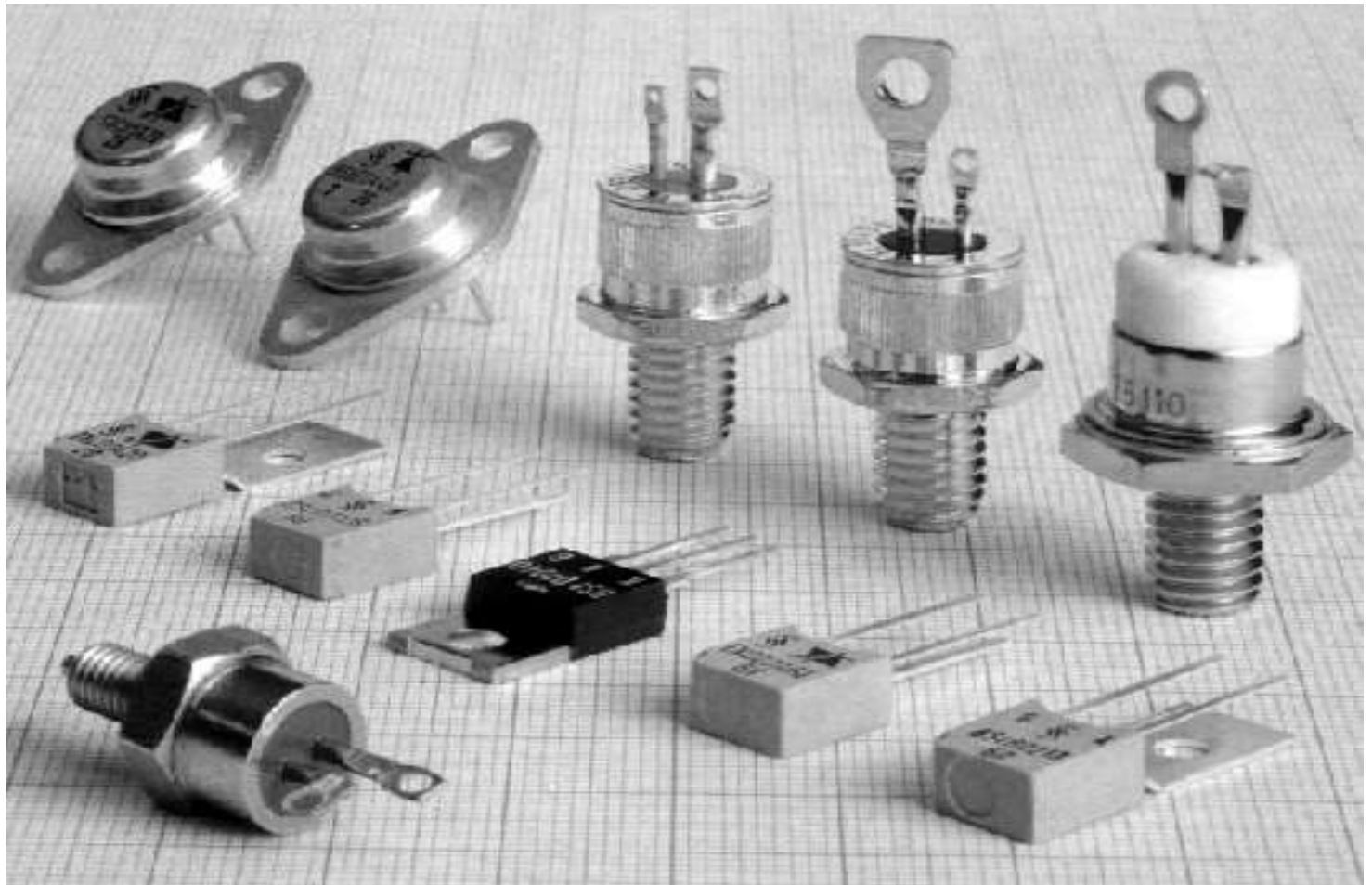

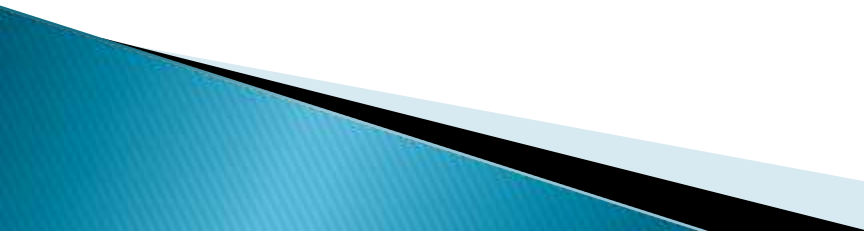
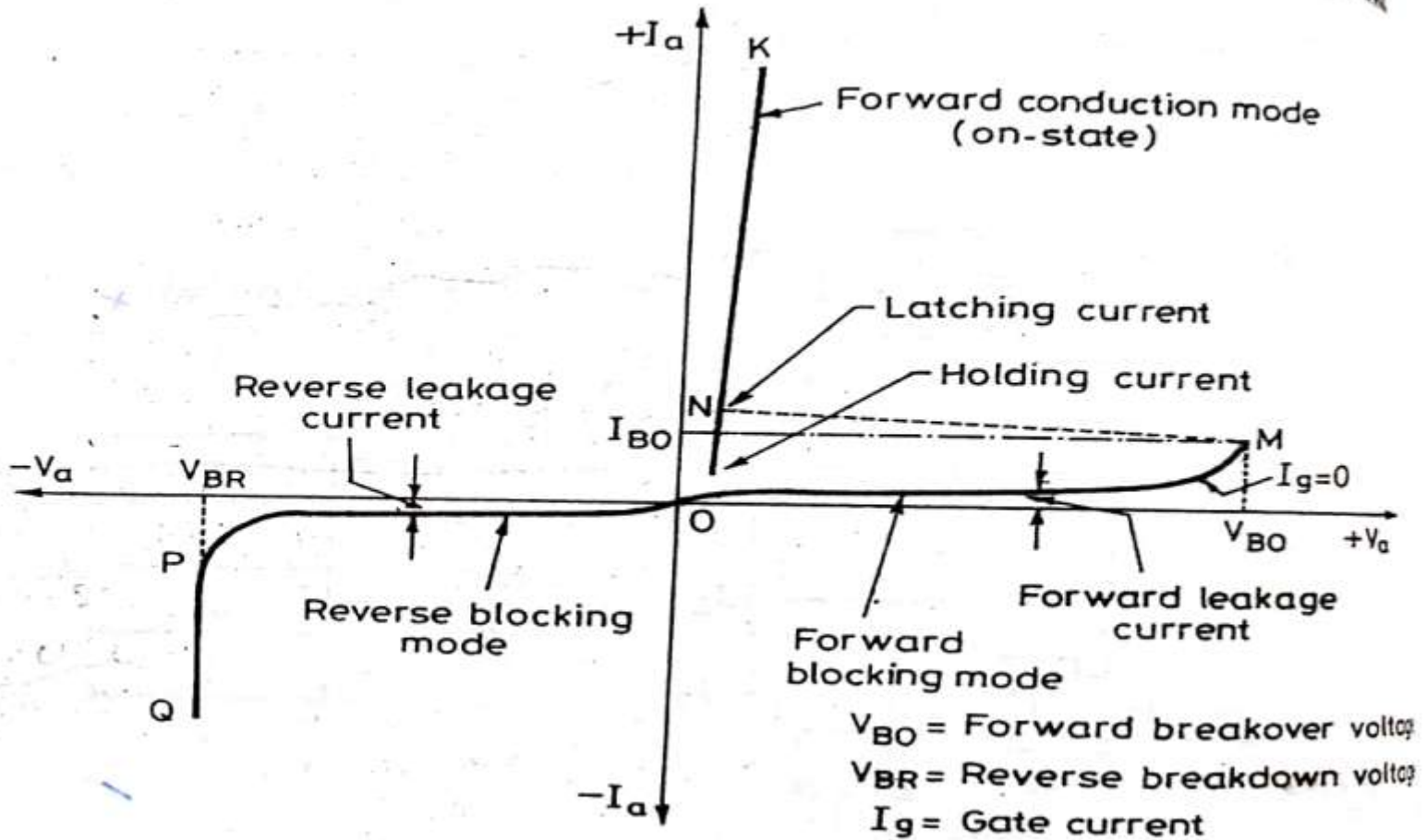
# Thyristor (SCR)

- ▶ It is four layer, three junction, p-n-p-n semiconductor switching device.
  - ▶ It has three terminals; Anode, Cathode and Gate.
  - ▶ Gate terminal is usually kept near cathode terminal.
  - ▶ SCRs of voltage rating 10 kV and rms current rating of 3000A with corresponding power handling capacity of 30MW are available.
- 

# Thyristor (SCR)

- ▶ SCR is so called because silicon is used for its construction and used as controlled rectifier.
  - ▶ Unlike diode, a thyristor also blocks the current flow from anode to cathode until it is triggered by gate signal.
- 

# SCR Characteristics



# SCR Characteristics

- ▶ Forward Blocking Mode
  - Anode is made +ve w.r.t. Cathode , Gate open.
  - $J_1, J_3$  are forward biased,  $J_2$  is reverse biased.
  - Forward leakage current flows.
  - SCR offers high impedance.
  - It can be treated as an open switch.

# SCR Characteristics

- ▶ Forward Conduction Mode
  - When anode to cathode forward voltage is increased, Junction  $J_2$  will have an avalanche breakdown at Forward Break over Voltage  $V_{BO}$ .
  - Voltage drop across the thyristor is of the order of 1 to 2 V, depending on SCR rating.
  - Anode current is limited by load impedance.
  - Thyristor acts as a closed switch.

# SCR Characteristics

## ▶ Reverse Blocking Mode

- Cathode is made +ve w.r.t. Anode, Gate open.
- $J_1, J_3$  are reverse biased,  $J_2$  is forward biased.
- Device behaves as two diodes connected in series with reverse voltage applied.
- Reverse leakage current of few milli amperes flow.
- At reverse breakdown voltage  $V_{BR}$ , an avalanche occurs at  $J_1$  and  $J_3$ .
- Reverse current increases rapidly.
- Large current with  $V_{BR}$  gives rise to more losses.
- This may lead to damage of SCR.




# SCR Characteristics

## ▶ Gate Triggering

- Simple, reliable and efficient method to turn on the SCR and is mostly used.
- Positive gate voltage between gate and cathode is applied.
- Charges are injected in to inner p layer
- The voltage at which forward break over occurs, is reduced.
- Higher the gate current, lower is the forward break over voltage.
- Typical gate current is 20 to 200 mA.

- ▶ Gate Triggering Continued...
  - With positive gate current, p layer is flooded with electrons from cathode as n layer is heavily doped as compared to gate p layer.
  - Some of these electrons reach junction  $J_2$ .
  - Due to this, width of depletion layer near junction  $J_2$  is reduced and it breaks down at lower voltage.
  - Reverse biased junction  $J_2$  no longer exists.
  - If gate current is removed, anode to cathode current remains unaffected.

# SCR Characteristics

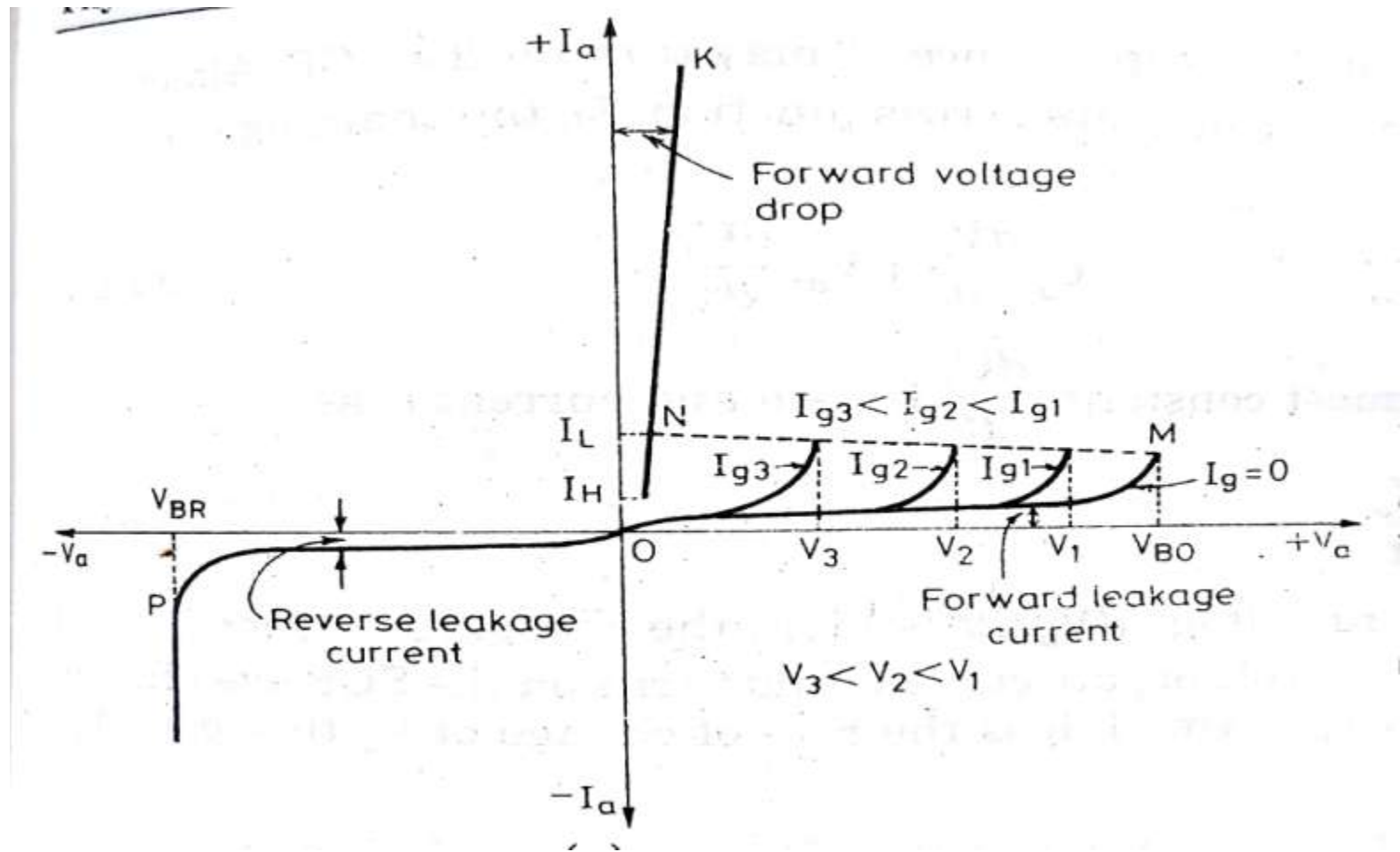


▶ **Latching Current:**

- Minimum value of anode current which SCR must attain during turn on process, to maintain conduction when gate signal is removed.


▶ **Holding Current:**

- Minimum value of anode current below which it must fall for turning off the thyristor.
- Latching current is associated with turn on process and Holding current with turn off process


# Two Transistor Analogy

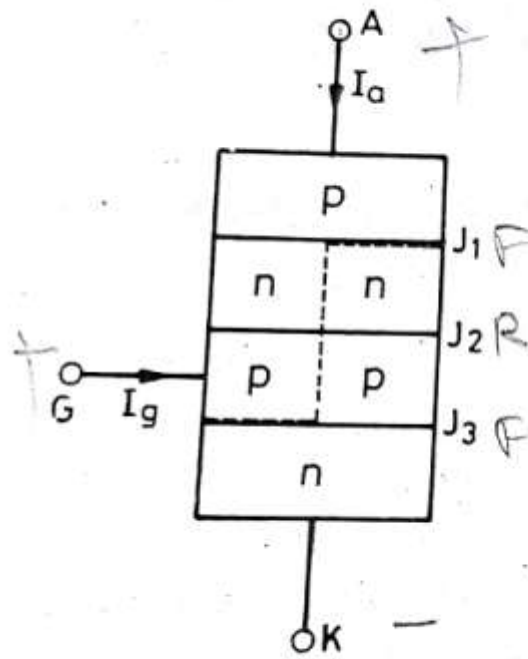

(a)

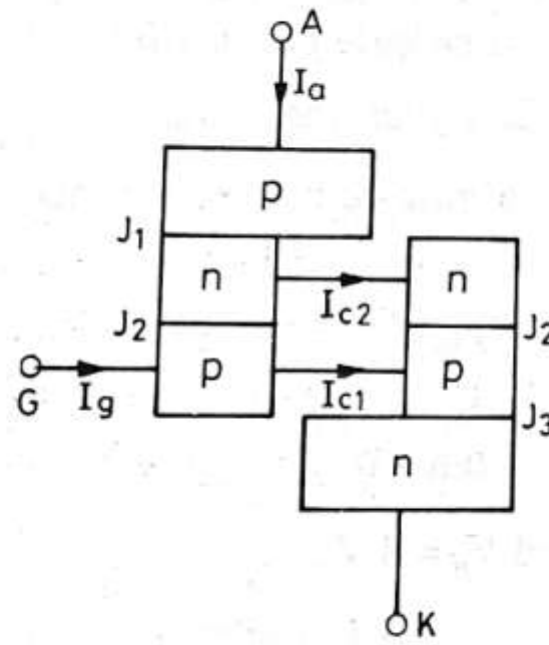

(b)

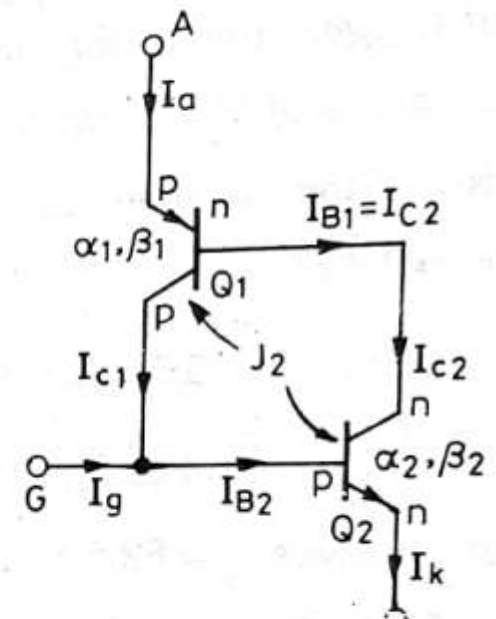

(c)

# Two Transistor Analogy

In the off-state of a transistor, collector current  $I_C$  is related to emitter current  $I_E$  as

$$I_C = \alpha I_E + I_{CBO}$$

where  $\alpha$  is the common-base current gain and  $I_{CBO}$  is the common-base leakage current of collector-base junction of a transistor.

For transistor  $Q_1$  in Fig. , emitter current  $I_E =$  anode current  $I_a$  and  $I_C =$  collector current  $I_{C1}$ . Therefore, for  $Q_1$ ,

$$I_{C1} = \alpha_1 I_a + I_{CBO1} \quad \dots(i)$$

where

$\alpha_1 =$  common-base current gain of  $Q_1$

and

$I_{CBO1} =$  common-base leakage current of  $Q_1$ .

# Two Transistor Analogy

Similarly, for transistor  $Q_2$ , the collector current  $I_{C2}$  is given by

$$I_{C2} = \alpha_2 I_k + I_{CBO2} \quad \dots (ii)$$

where

$\alpha_2$  = common-base current gain of  $Q_2$

$I_{CBO2}$  = common-base leakage current of  $Q_2$

and

$I_k$  = emitter current of  $Q_2$ .

The sum of two collector currents given by Eqs. ( i ) and ( ii ) is equal to the external circuit current  $I_a$  entering at anode terminal A.

$$\therefore I_a = I_{C1} + I_{C2}$$

or

$$I_a = \alpha_1 I_a + I_{CBO1} + \alpha_2 I_k + I_{CBO2} \quad \dots (iii)$$

When gate current is applied, then  $I_k = I_a + I_g$ . Substituting this value of  $I_k$  in Eq. (iii) gives

$$I_a = \alpha_1 I_a + I_{CBO1} + \alpha_2 (I_a + I_g) + I_{CBO2}$$

or




$$I_a = \frac{\alpha_2 I_g + I_{CBO1} + I_{CBO2}}{1 - (\alpha_1 + \alpha_2)}$$

# Two Transistor Analogy


- ▶ For a silicon transistor, current gain  $\alpha$  is very low at low emitter current.
- ▶ With an increase in emitter current,  $\alpha$  builds up rapidly.
- ▶ With  $I_g=0$ ,  $(\alpha_1 + \alpha_2)$  is very low.
- ▶ If emitter current is increased so that  $(\alpha_1 + \alpha_2)$  approaches unity,  $I_a$  would tend to become infinity.




# DIAC

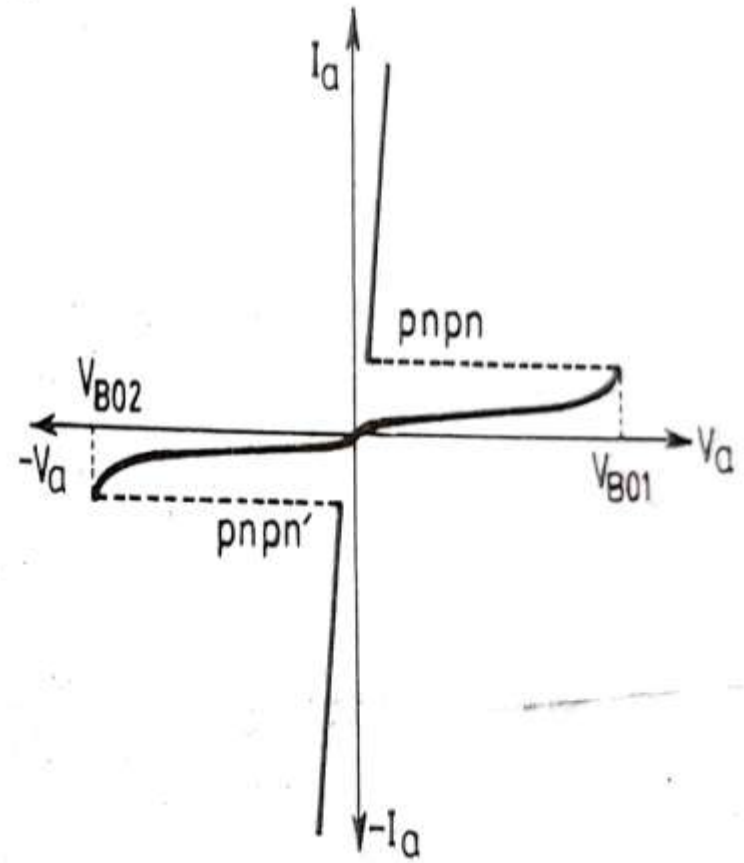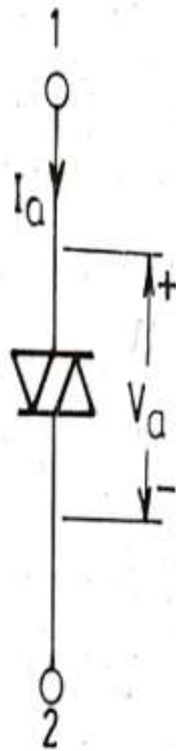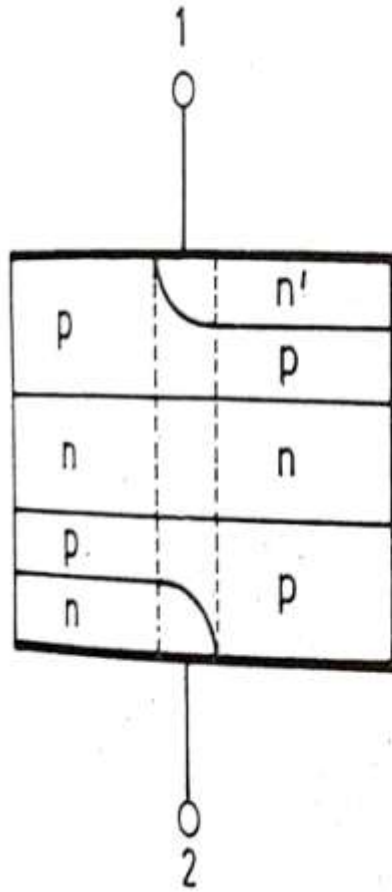


# DIAC

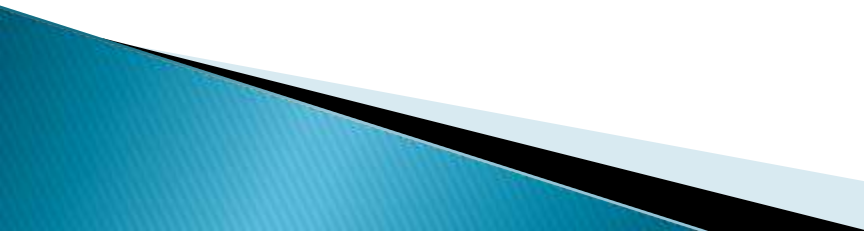- ▶ When voltage across the terminals exceeds the breakover voltage, the four out of five layers conduct.
  - ▶ Name is derived from **Diode** that can work on **AC**.
  - ▶ It's terminals are interchangeable.
  - ▶ Turn on voltage is around 30 V.
  - ▶ While conducting, voltage drop across it is around 3 V
- 

# TRIAC

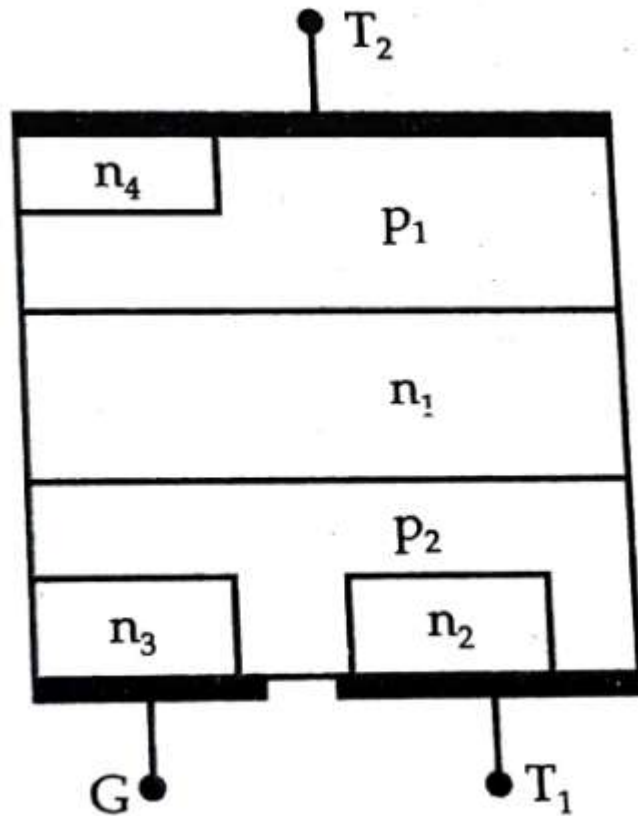

(a)

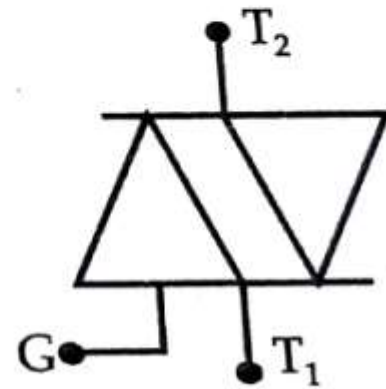


(b)


# Modes of Operation




# $T_2$ Positive and Gate Positive

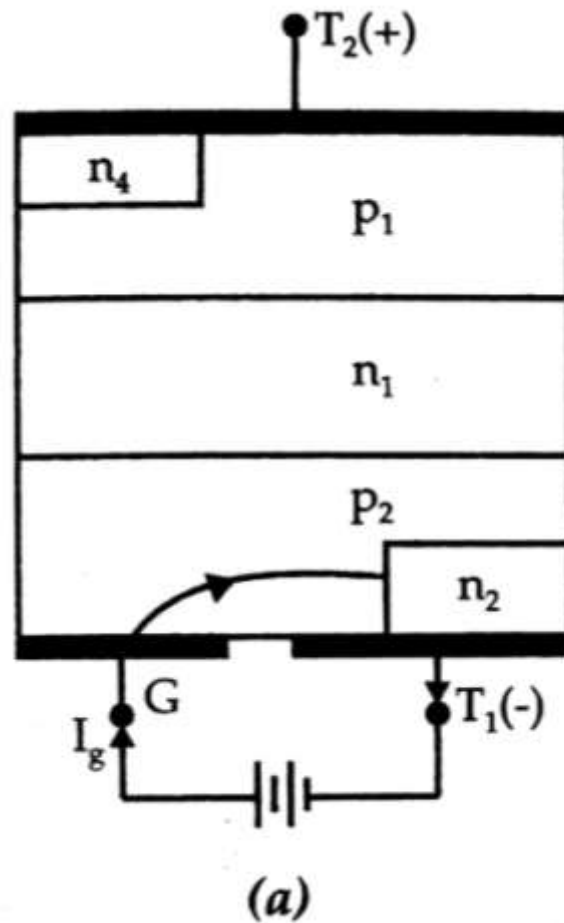

# $T_2$ Positive and Gate Positive

- ▶ Junction  $p_1 - n_1$  and  $p_2 - n_2$  are forward biased.
  - ▶ Junction  $n_1 - p_2$  is reverse biased.
  - ▶ Gate current injects sufficient carriers in  $p_2$  layer and Junction  $n_1 - p_2$  breaks down.
  - ▶ Device is more sensitive in this mode.
- 

# $T_2$ Positive and Gate Negative

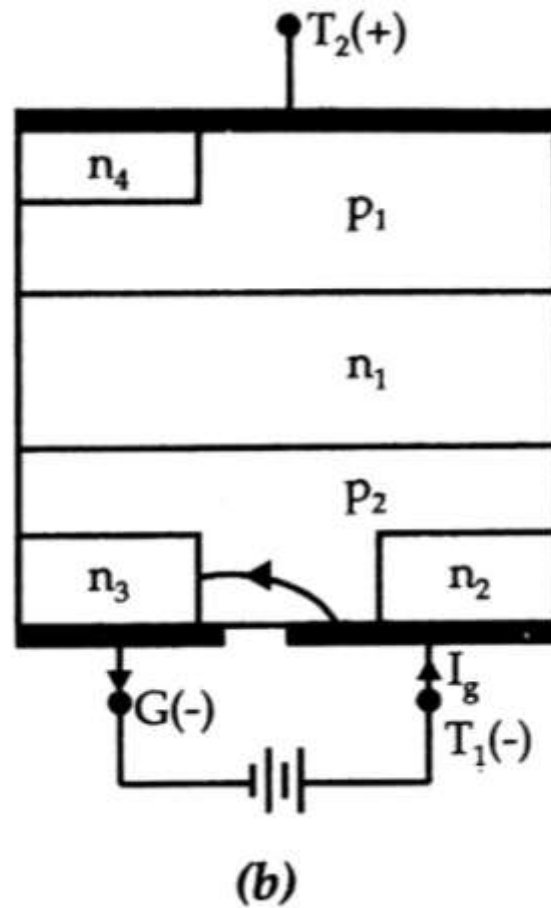

# T<sub>2</sub> Positive and Gate Negative


- ▶ Junction p<sub>1</sub> n<sub>1</sub> and p<sub>2</sub> n<sub>2</sub> are forward biased.
- ▶ Junction n<sub>1</sub> p<sub>2</sub> is reverse biased.
- ▶ Gate current flows through p<sub>2</sub> n<sub>3</sub> junction.
- ▶ Initially TRIAC current flows through p<sub>1</sub> n<sub>1</sub> p<sub>2</sub> n<sub>3</sub>.
- ▶ Due to conduction of p<sub>1</sub> n<sub>1</sub> p<sub>2</sub> n<sub>3</sub>, the potential of left side of the layer p<sub>2</sub> rises towards anode potential of T<sub>2</sub>.



# T<sub>2</sub> Positive and Gate Negative

- ▶ Potential gradient exists between across the layer p<sub>2</sub>.
- ▶ Left side being at higher potential, the current is established in p<sub>2</sub> layer from left to right.
- ▶ p<sub>1</sub> n<sub>1</sub> p<sub>2</sub> n<sub>2</sub> start conducting like normal SCR.
- ▶ p<sub>1</sub> n<sub>1</sub> p<sub>2</sub> n<sub>3</sub> may be regarded as pilot SCR.
- ▶ Device is less sensitive in this mode, so require more gate current.


# $T_2$ Negative and Gate Positive

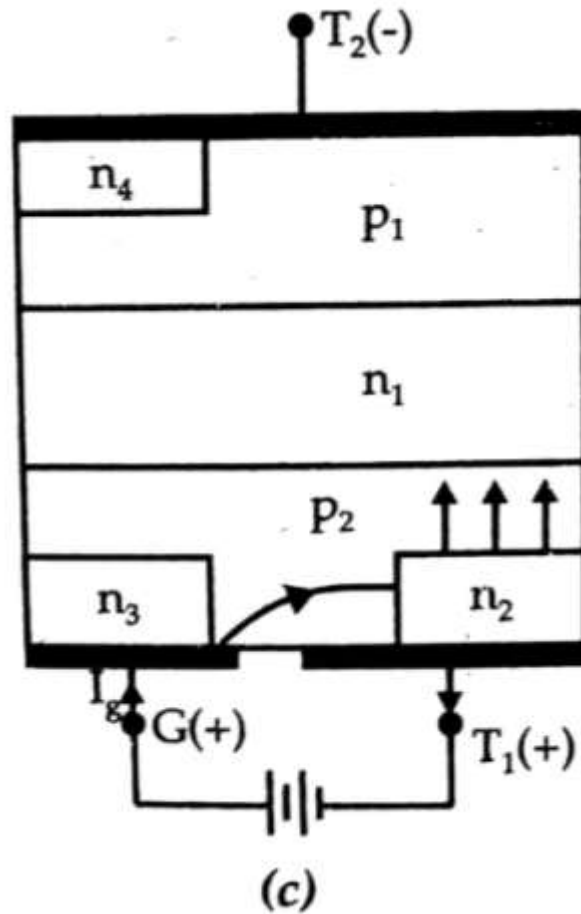


# T<sub>2</sub> Negative and Gate Positive

- ▶ Gate current forward biases the p<sub>2</sub> n<sub>2</sub> junction.
- ▶ Layer n<sub>2</sub> injects electrons in p<sub>2</sub> layer.
- ▶ Reverse biased junction n<sub>1</sub> p<sub>1</sub> breaks down.
- ▶ P<sub>2</sub> n<sub>1</sub> p<sub>1</sub> n<sub>4</sub> is completely turned on.
- ▶ As the TRIAC is turned on by remote gate n<sub>2</sub> the device is less sensitive.


# T2 and Gate is Negative

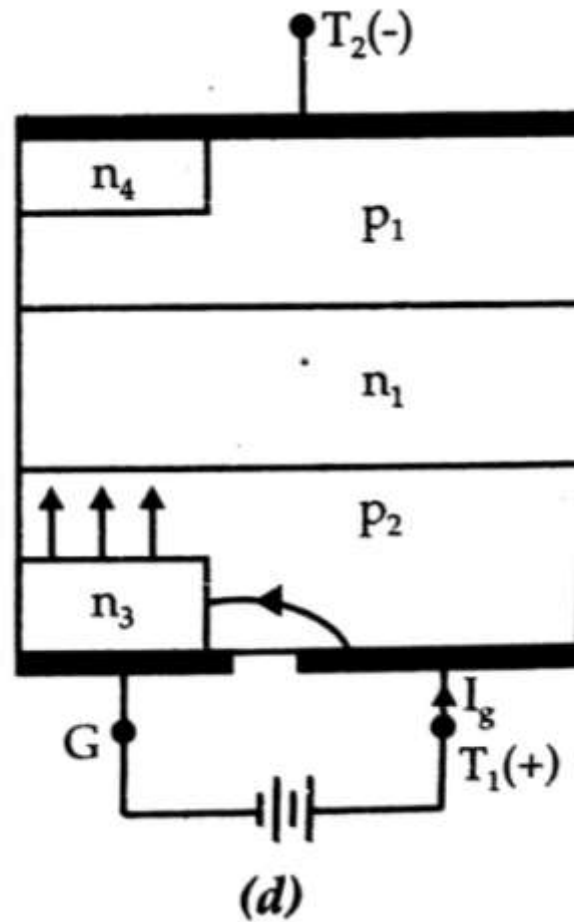


# T2 and Gate is Negative

- ▶  $n_3$  acts as remote gate.
  - ▶ Gate current flows from  $p_2$  to  $n_3$  as in normal Thyristor.
  - ▶ Reverse biased junction  $n_1 p_1$  breaks down.
  - ▶ Structure  $p_2 n_1 p_1 n_4$  is turned on.
  - ▶ Device is more sensitive.
- 

# Quadracs

- ▶ Quadracs are a special type of thyristor which combines a "diac" and a "triac" in a single package.
  - ▶ The diac is the triggering device for the triac.
  - ▶ Quadracs eliminate the need to buy and assemble discrete parts.
  - ▶ Quadracs are used in lighting control, speed control, and temperature modulation control applications.
- 

# Heat Sinks

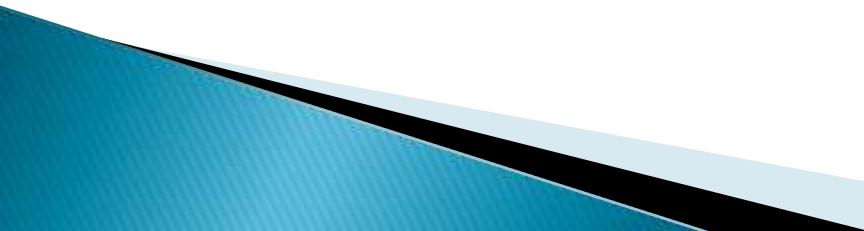- ▶ Small voltage drop exists at Thyristor Junctions.
  - ▶ With flow of current, heat is developed at junctions.
  - ▶ Junction temperature may increase beyond permissible limits.
  - ▶ It may damage the Thyristor.
  - ▶ To keep junction temperature within limits, Thyristor are mounted on Heat Sinks.
- 


# Thermal Ohm's Law

$$P_{21} = \frac{T_2 - T_1}{\theta_{21}}$$

- ▶  $\Theta_{21}$  = Thermal Resistance between point 2 and 1
- ▶  $P_{21}$  = Heat flow from point 2 and 1, W
- ▶  $T_2$  = Temperature of point 2, °C
- ▶  $T_1$  = Temperature of point 1, °C



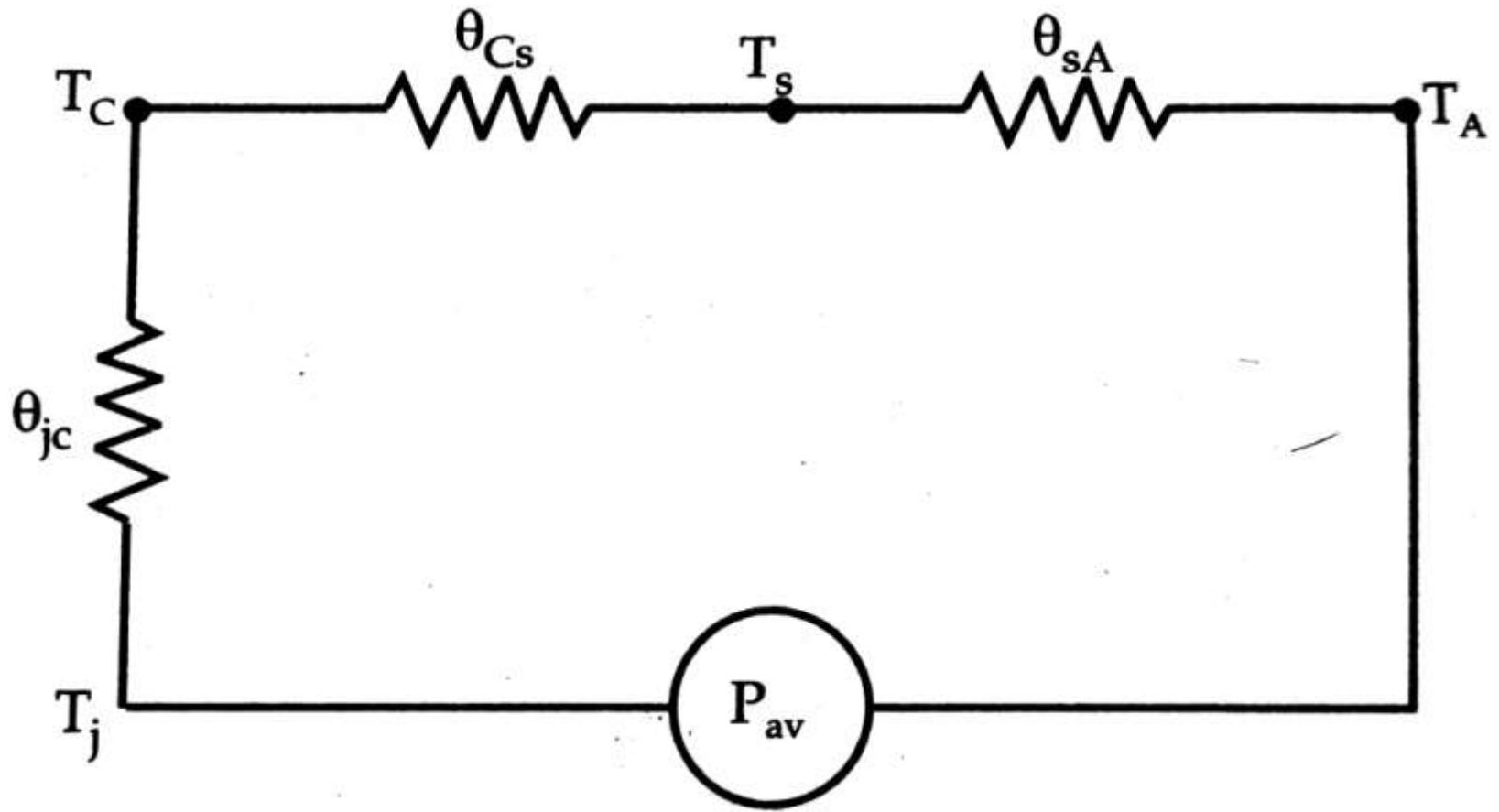
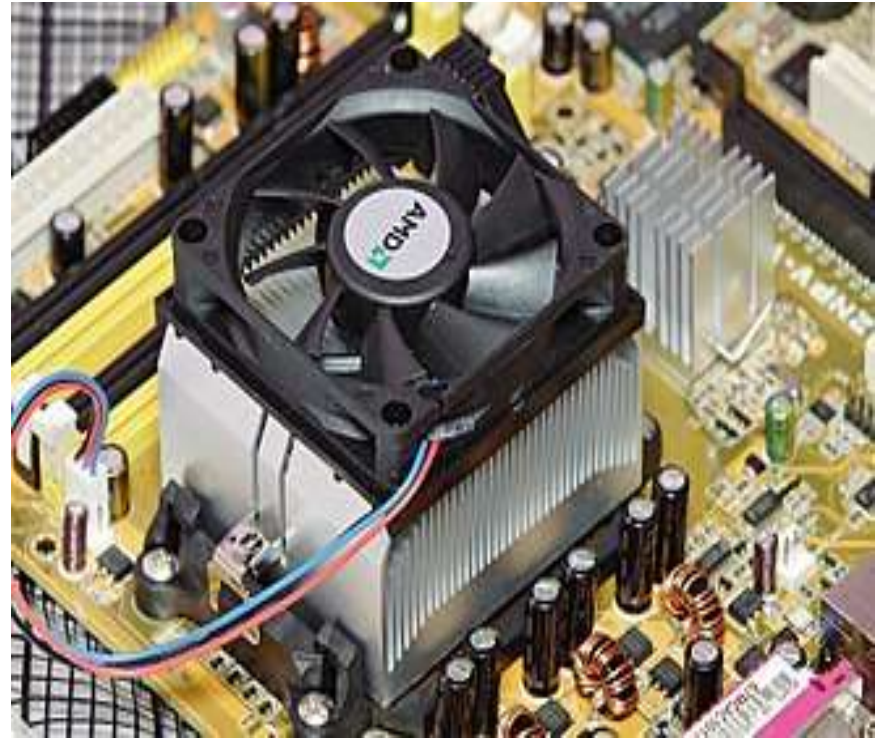
# Thermal Equivalent Circuit




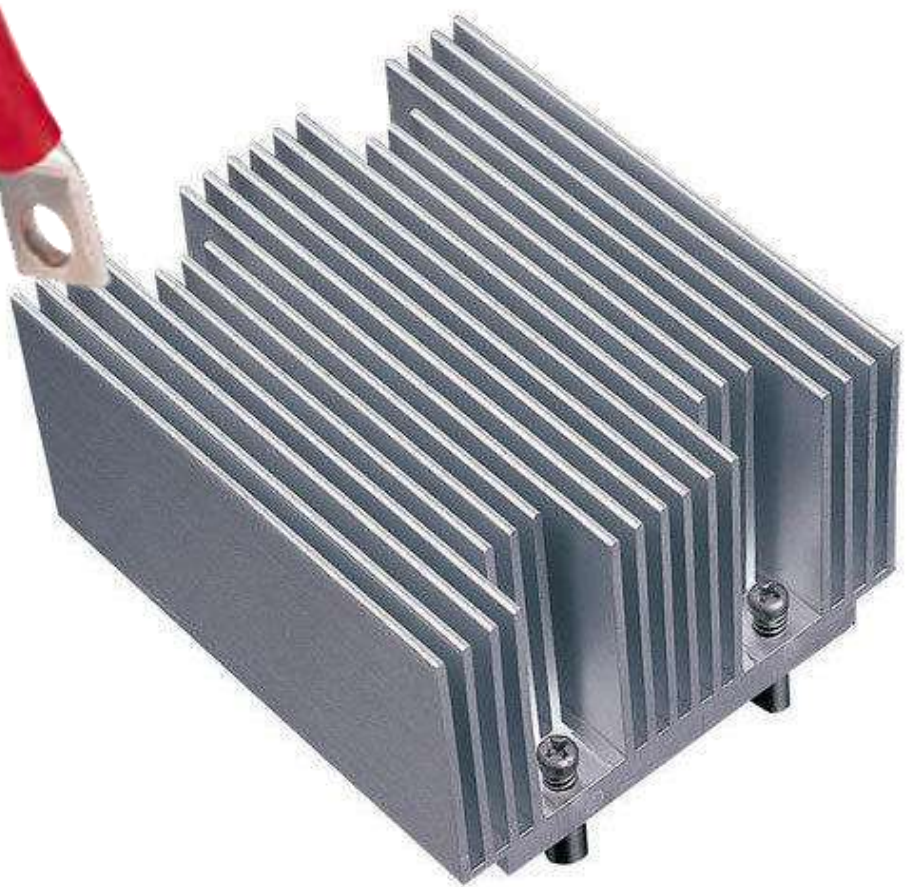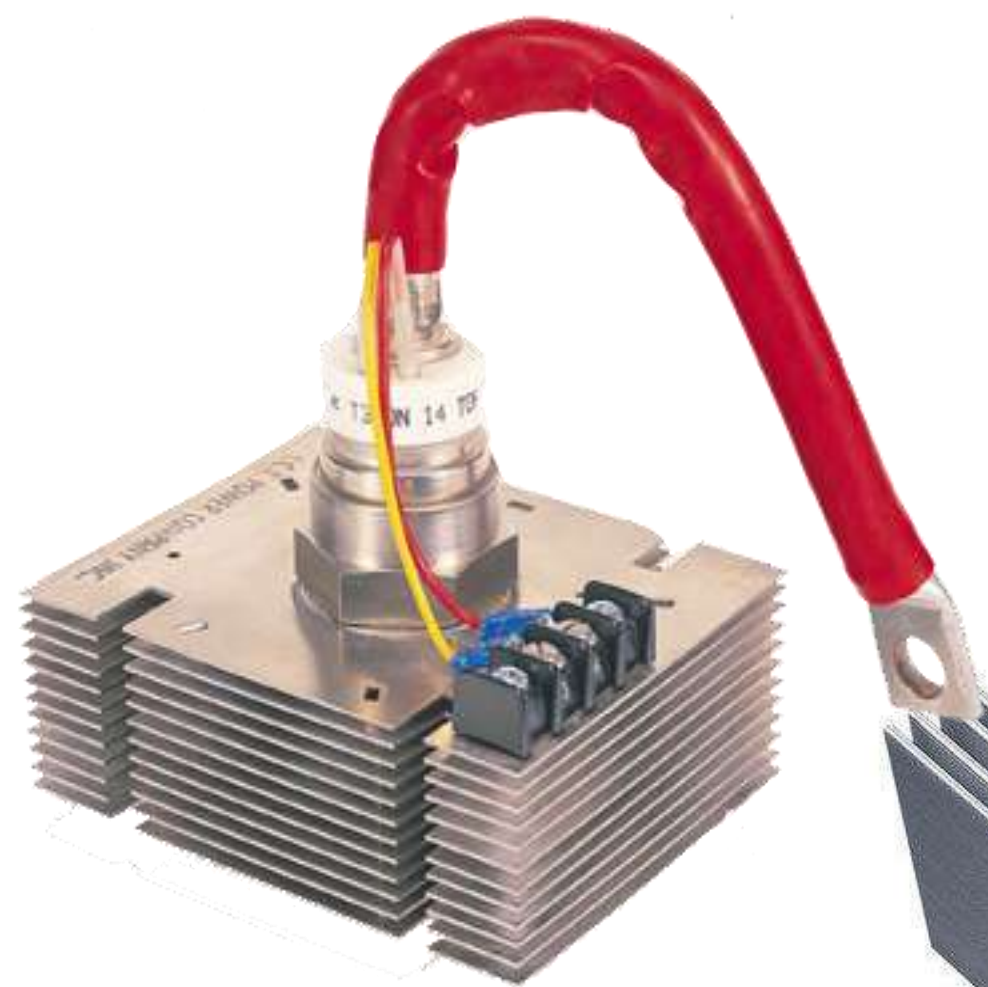
# Thermal Equivalent Circuit

- ▶  $P_{av}$  : average power loss in the device
- ▶  $T_j$  : Temperature of Junction
- ▶  $T_c$  : Temperature of Case
- ▶  $T_s$  : Temperature of Sink
- ▶  $T_a$  : Ambient Temperature
- ▶  $\Theta_{jc}$  : Thermal Resistance from junction to case
- ▶  $\Theta_{cs}$  : Thermal Resistance from case to sink
- ▶  $\Theta_{sA}$  : Thermal Resistance from sink to atmosphere

- ▶ Normally  $\Theta_{jc}$  and  $\Theta_{cs}$  are specified by the manufacturer.
  - ▶ Once  $P_{av}$  is known, the required  $\Theta_{sA}$  is calculated for known  $T_a$ .
  - ▶ Next step is to choose a heat sink and its size which would meet the thermal resistance requirement.
  - ▶ Copper and Aluminum heat sinks are preferred.
- 








# Thyristor Tiggering

# Forward Voltage Triggering


- ▶ When anode - cathode increases beyond the forward break over voltage  $V_{BO}$ , reverse biased junction  $J_2$  breaks down due to Avalanche breakdown.
- ▶ Anode current is limited by load impedance only.

# Gate Triggering

- ▶ Simple, reliable and efficient method to turn on the SCR and is mostly used.
  - ▶ Positive gate voltage between gate and cathode is applied.
  - ▶ Charges are injected in to inner p layer
  - ▶ The voltage at which forward break over occurs, is reduced.
  - ▶ Higher the gate current, lower is the forward break over voltage.
  - ▶ Typical gate current is 20 to 200 mA.
- 



# Gate Triggering

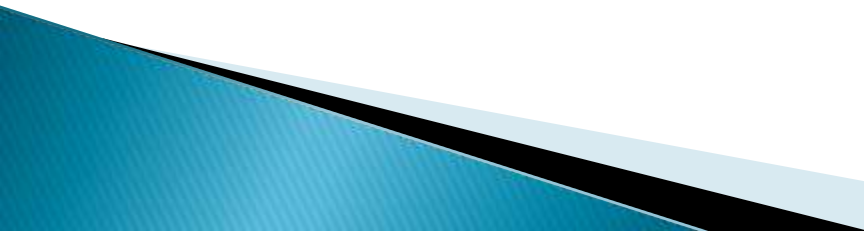
- ▶ With positive gate current, p layer is flooded with electrons from cathode as n layer is heavily doped as compared to gate p layer.
  - ▶ Some of these electrons reach junction J2.
  - ▶ Due to this, width of depletion layer near junction J2 is reduced and it breaks down at lower voltage.
  - ▶ Reverse biased junction J2 no longer exists.
  - ▶ If gate current is removed, anode to cathode current remains unaffected.
- 

# dv/dt Triggering


- ▶ Reverse biased junction  $J_2$  has characteristics similar to capacitor due to charges existing across the junction.
- ▶ If forward voltage is suddenly applied, the charging current through junction capacitance may turn on the SCR.

$$i_c = \frac{dQ}{dt} = C \frac{dv}{dt}$$

# dv/dt Triggering

- ▶ If rate of rise of forward voltage  $dv/dt$  is high, the charging current  $i_c$  would be more.
  - ▶ This charging current plays the role of gate current.
  - ▶ It may turn on the SCR even though gate signal is zero, at lower anode voltages.
- 


# Temperature Triggering

- ▶ Applied voltage, associated with leakage current raises the temperature of the junction  $J_2$ .
  - ▶ With increase in temperature, width of depletion layer decreases.
  - ▶ This further leads to more leakage current and therefore more junction temperature.
- 


# Temperature Triggering

- ▶ With the cumulative process, at some high temperature (Within the safe limits), depletion layer of reverse biased junction vanishes and device gets turned on.

# Light Triggering

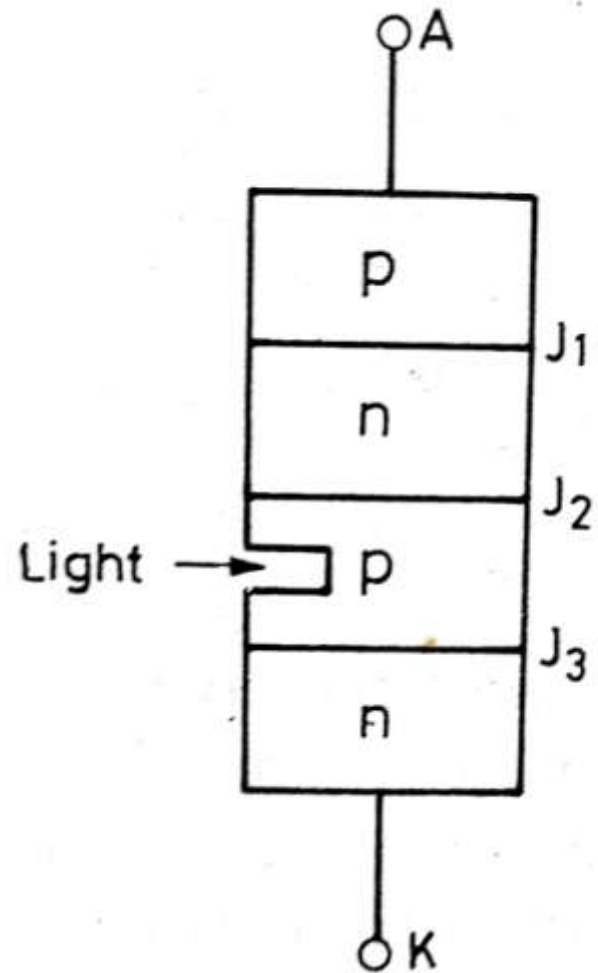


# Light Triggering

- ▶ Light triggered SCRs has a recess made in the inner p-layer.
  - ▶ When this recess is irradiated, free charge carriers are generated.
  - ▶ With sufficient light at recess, the forward biased SCR is turned on.
  - ▶ Such a thyristor is called Light Activated SCR (LASCR).
  - ▶ LASCR may be triggered with a light source or with gate signal.
- 

# Triggering Circuits





# Resistance Triggering

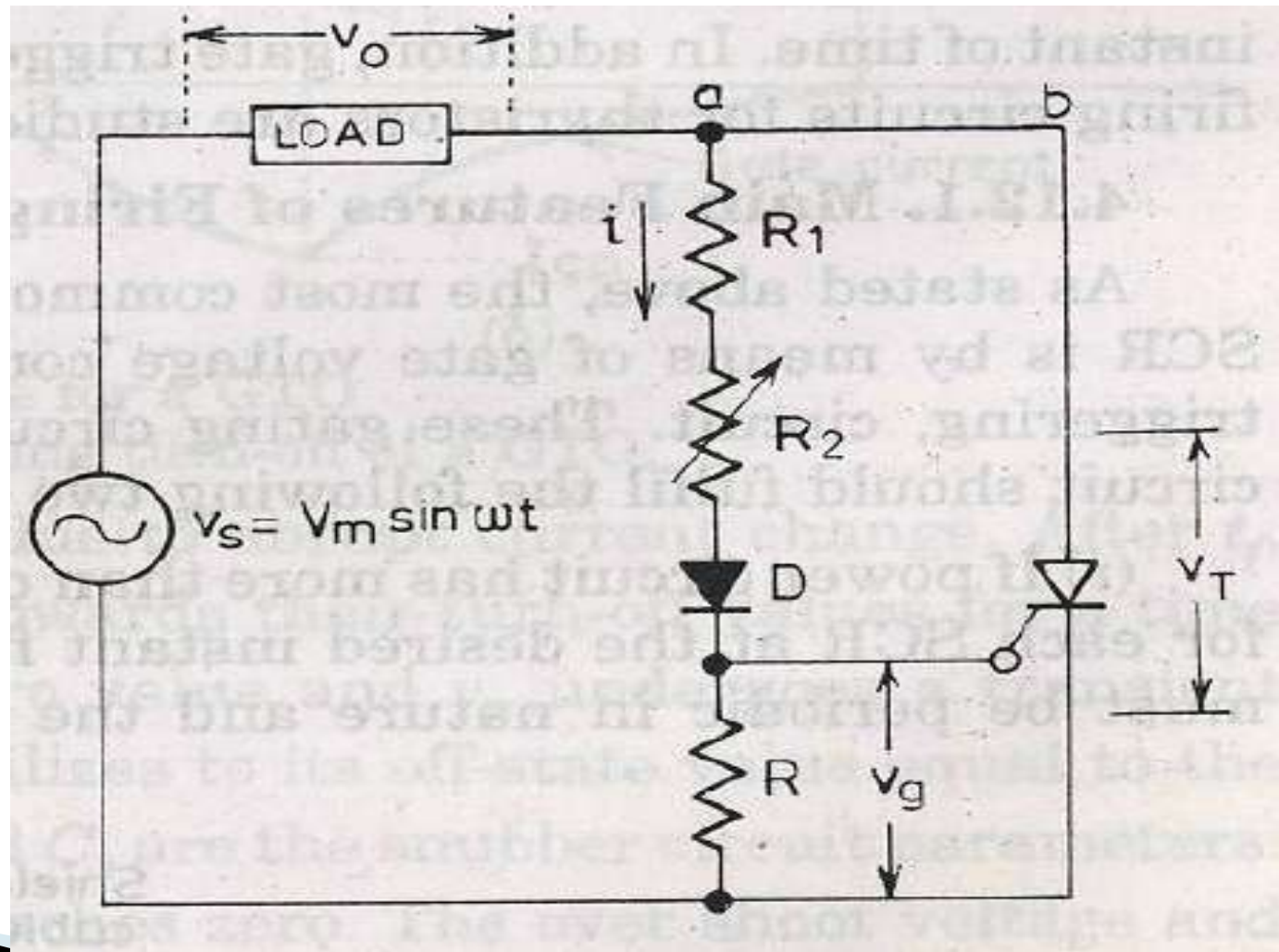

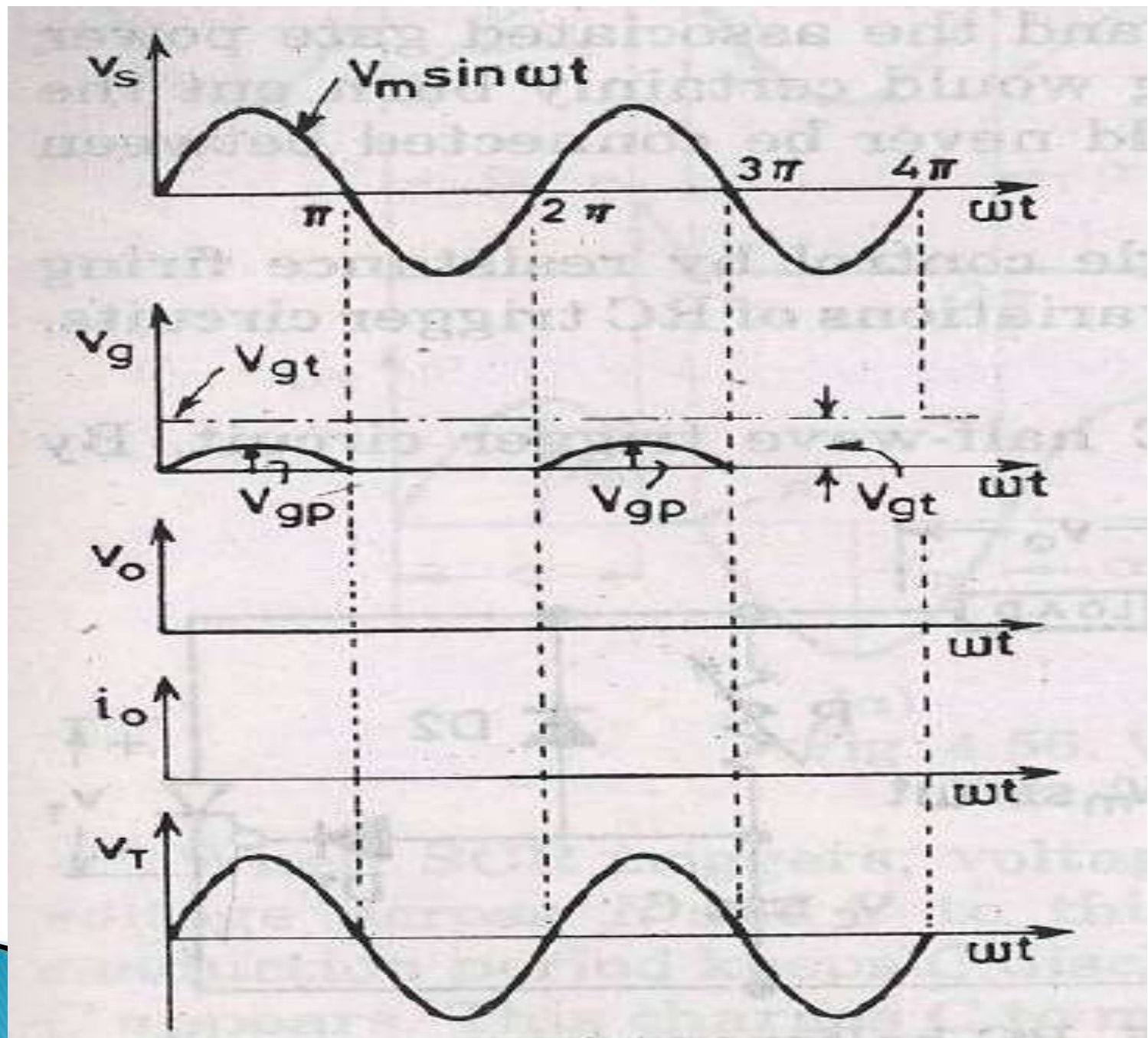
# Resistance Triggering

- ▶ Simplest and most economical.
- ▶ Limited firing angle control (0–90°).
- ▶ The function of  $R_1$  is to limit the gate current to safe value, as  $R_2$  is varied.
- ▶  $R_1$  should be greater than or equal to  $V_m/I_{gm}$ .  
Where  $V_m$  is maximum source voltage and  $I_{gm}$  is maximum permissible gate current.




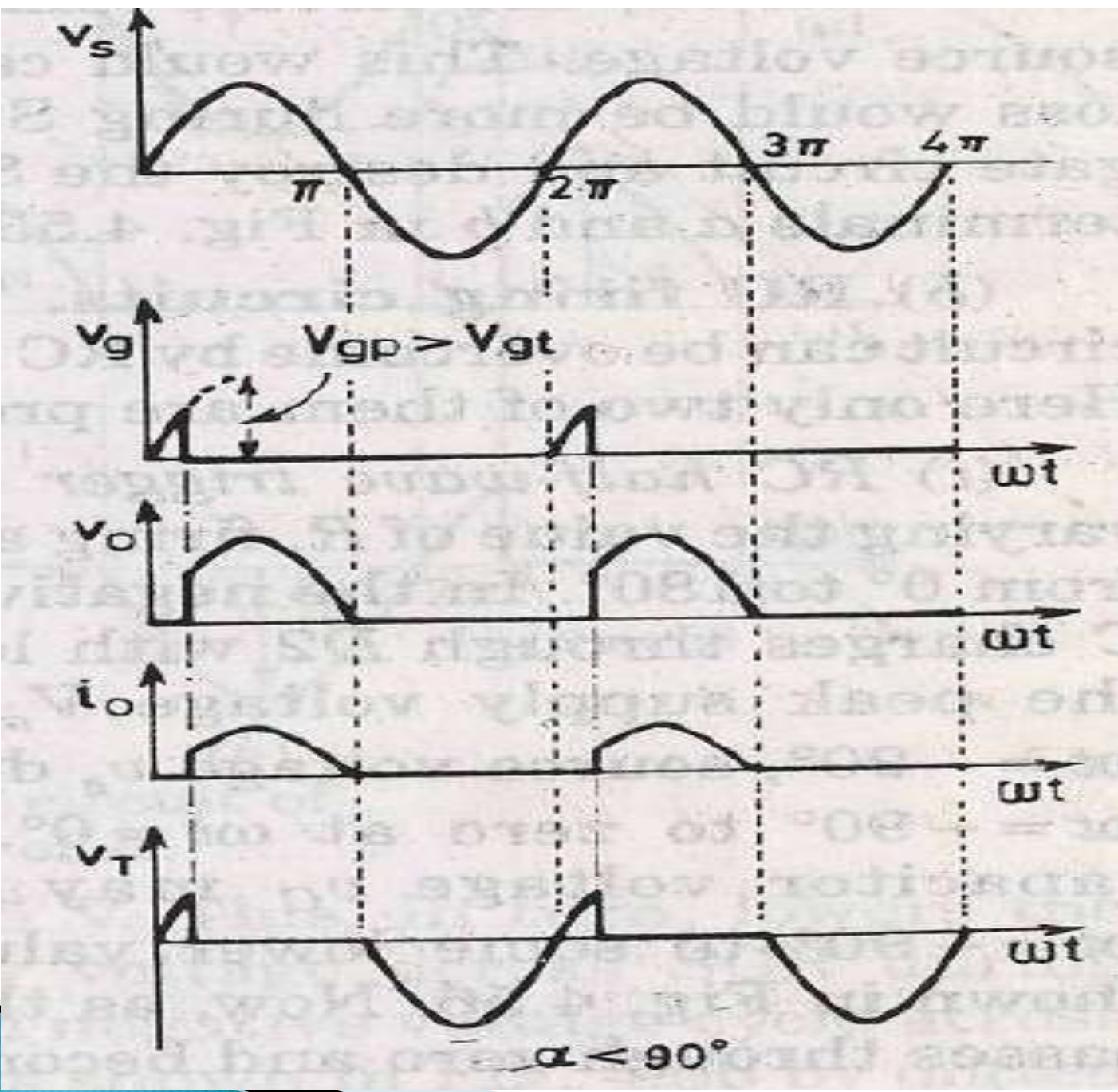



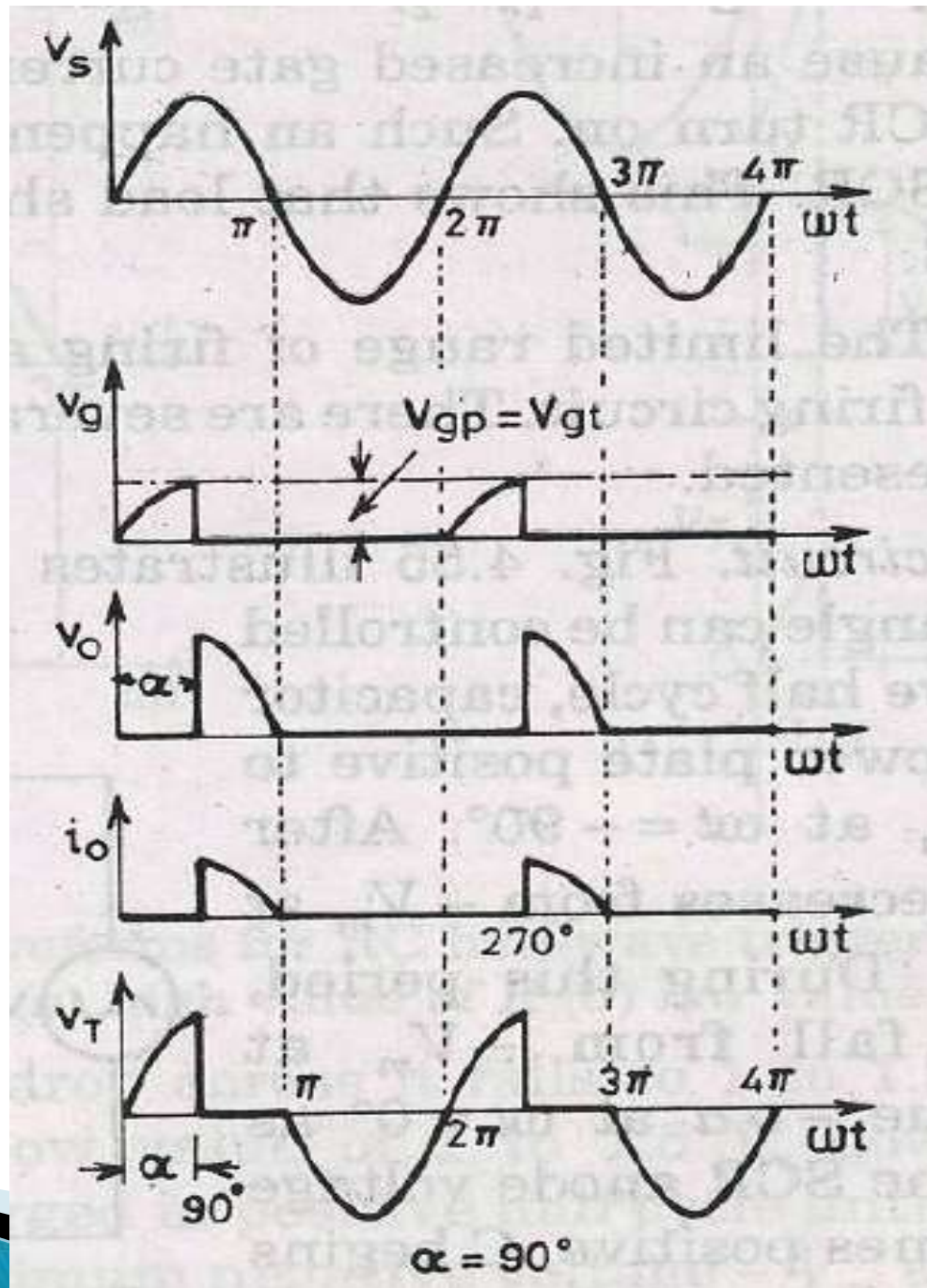

# RC Half Wave Triggering Circuit

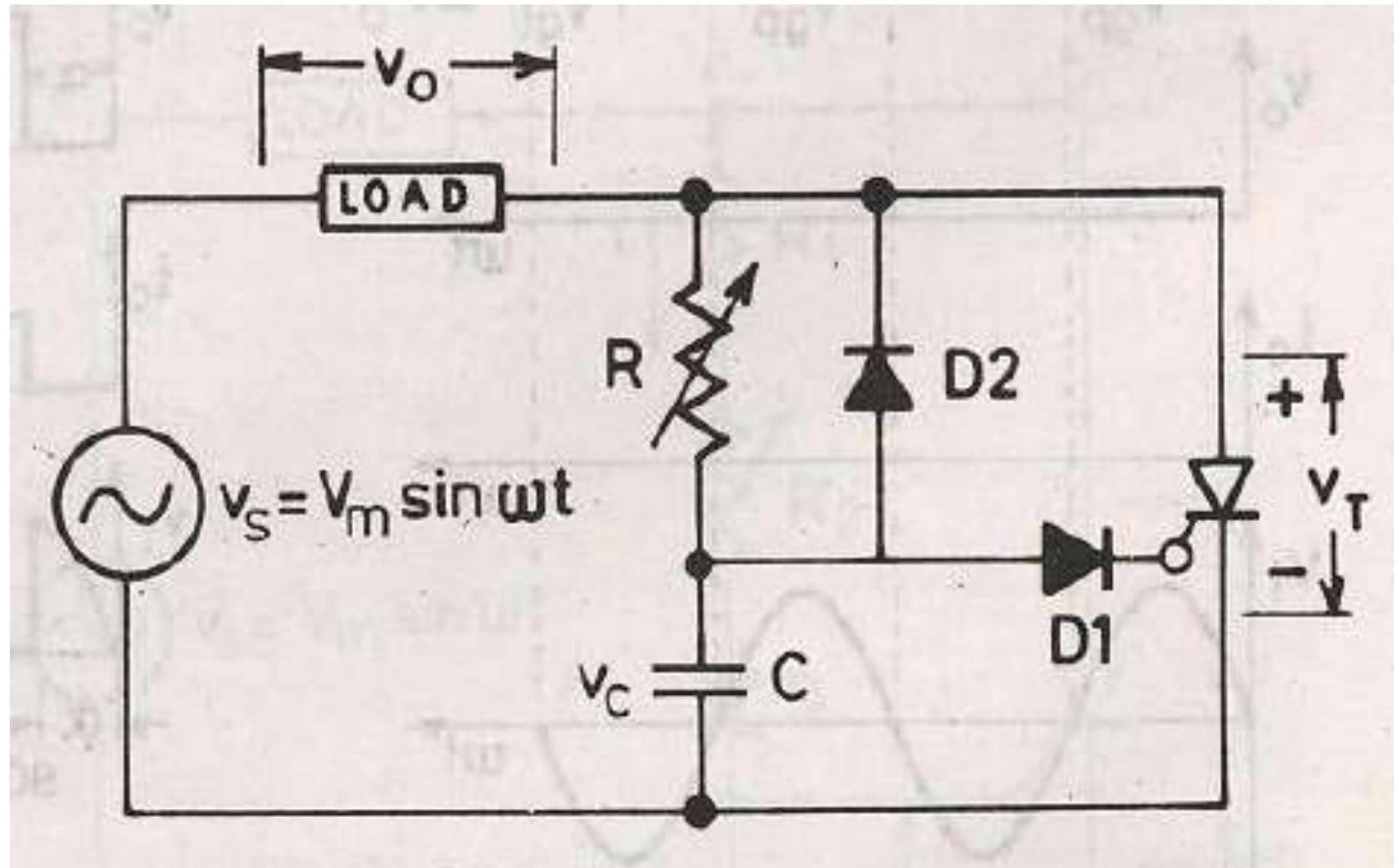


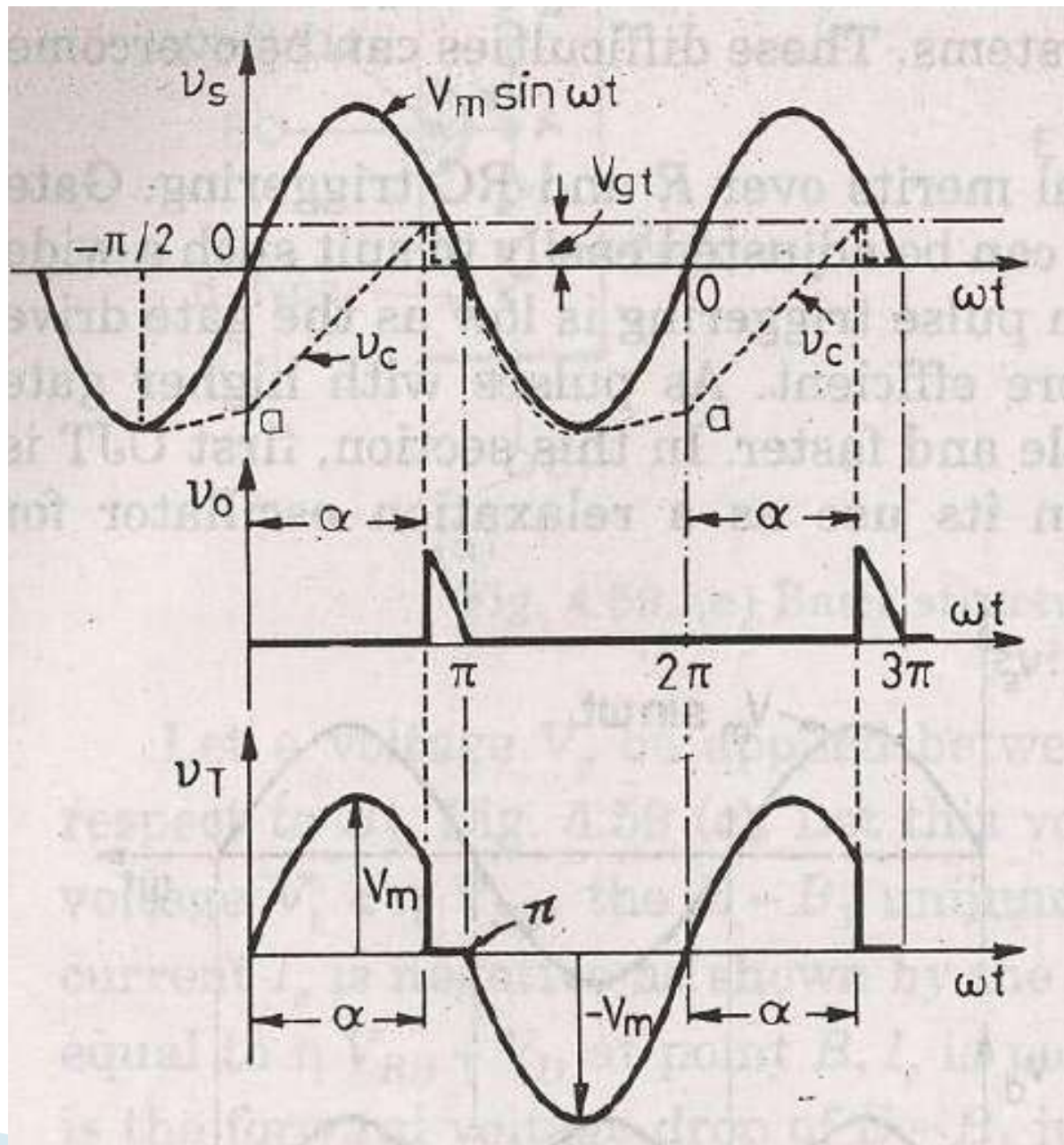
# RC Half Wave Triggering Circuit

- ▶ By varying the value of R, firing angle can be controlled from 0 – 180°.
- ▶ In negative half, the capacitor charges through D2 with lower plate positive to voltage  $V_m$ .
- ▶ In positive half, capacitor C begins to charge through resistance R.
- ▶ When capacitor voltage reaches  $V_{gt}$ , SCR is fired.
- ▶  $[V_c = V.(1 - e^{(-t/RC)})]$


- ▶ Diode  $D_1$  is used to prevent the breakdown of cathode to gate junction through  $D_2$ , during negative half cycle.






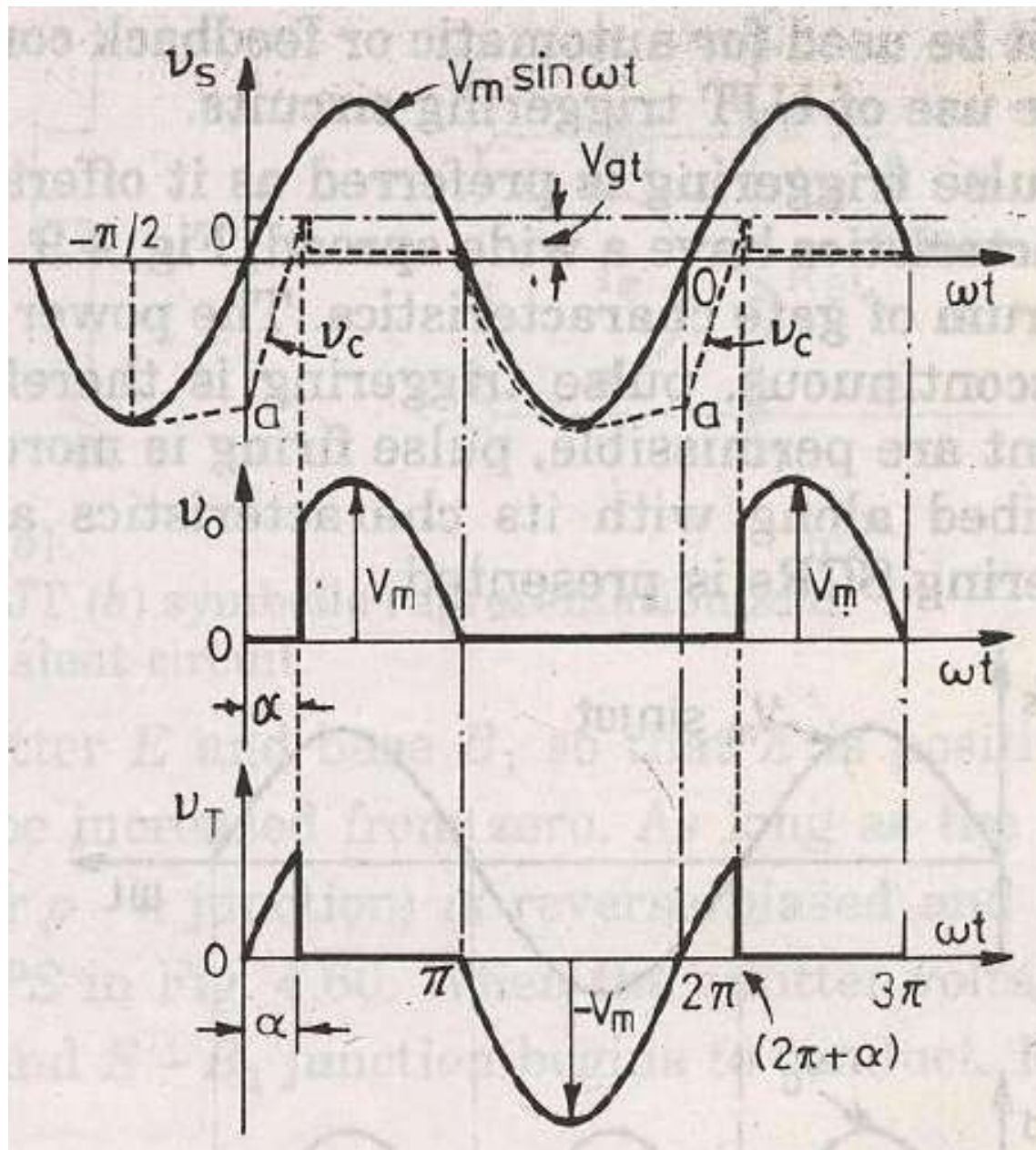


# RC Full Wave Triggering Circuit

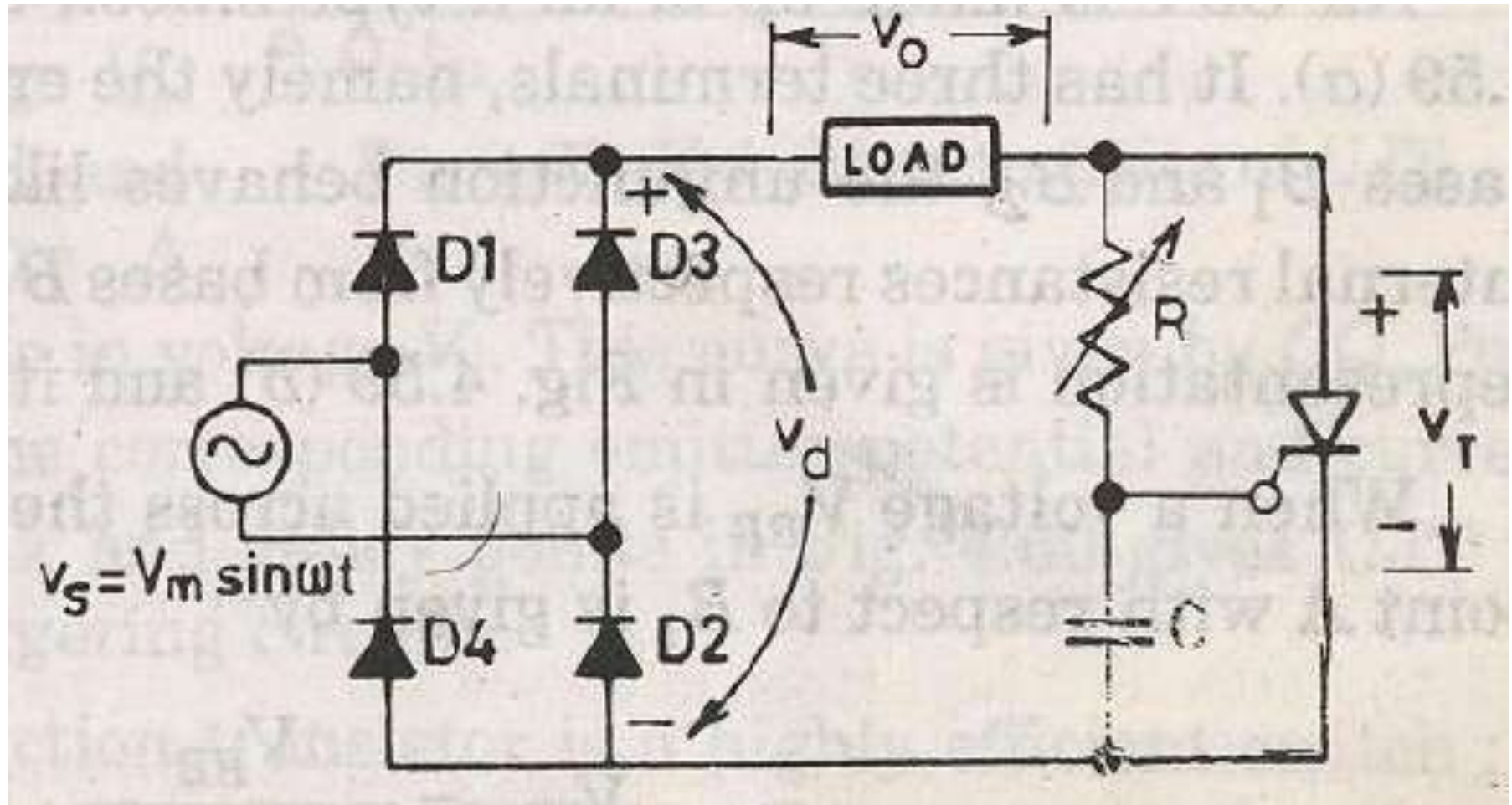




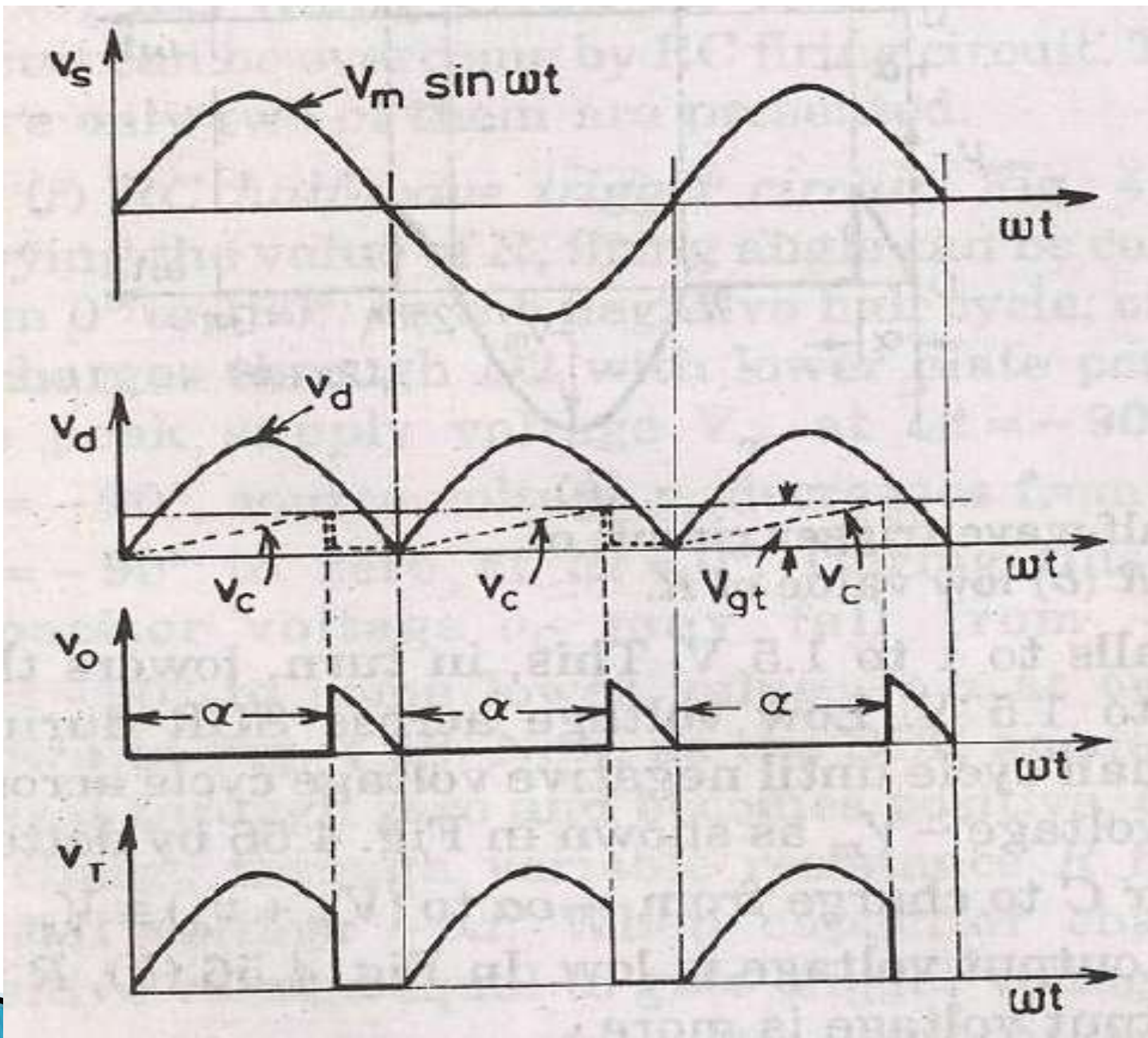

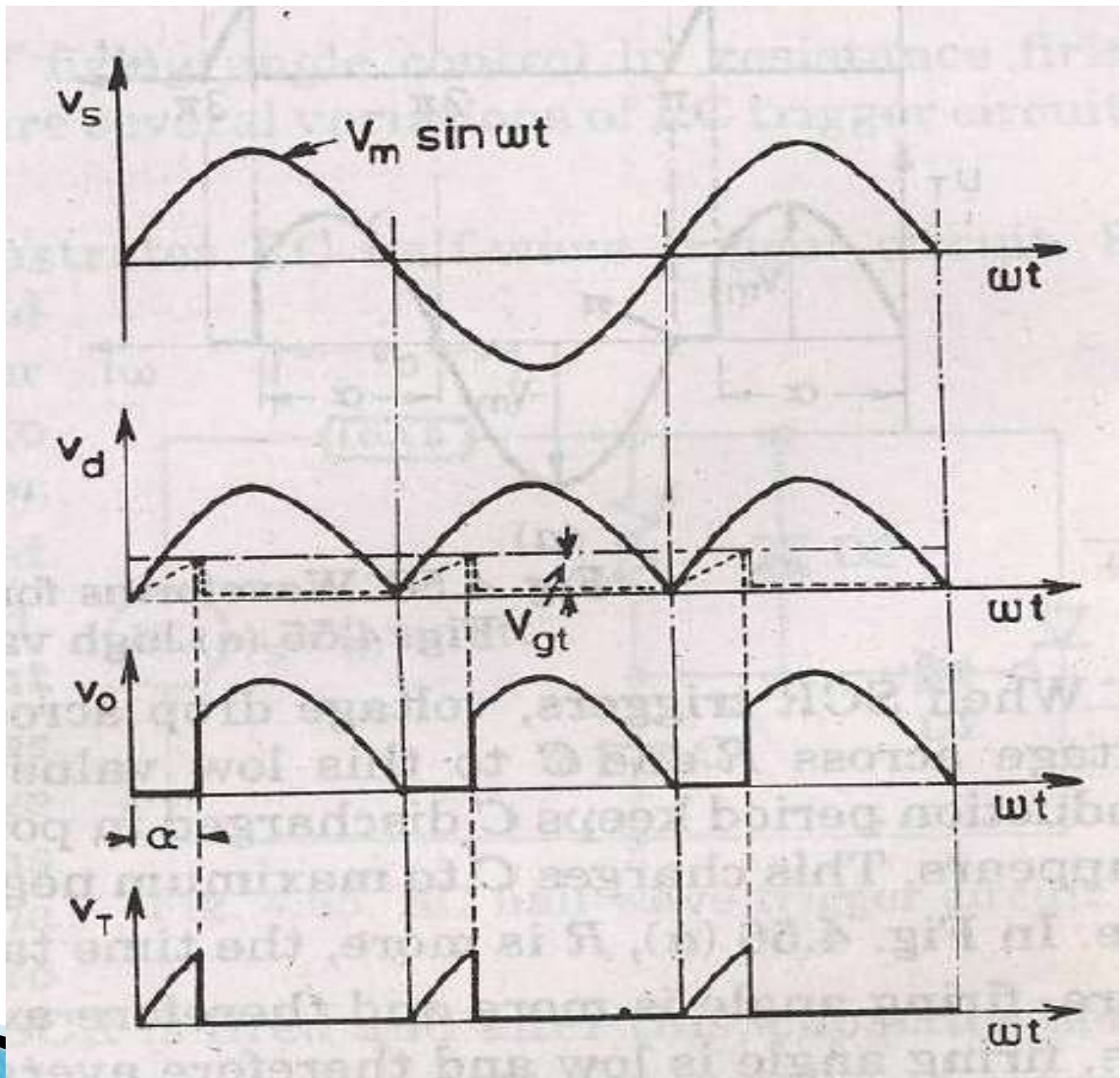

# Unijunction Transistor (UJT)

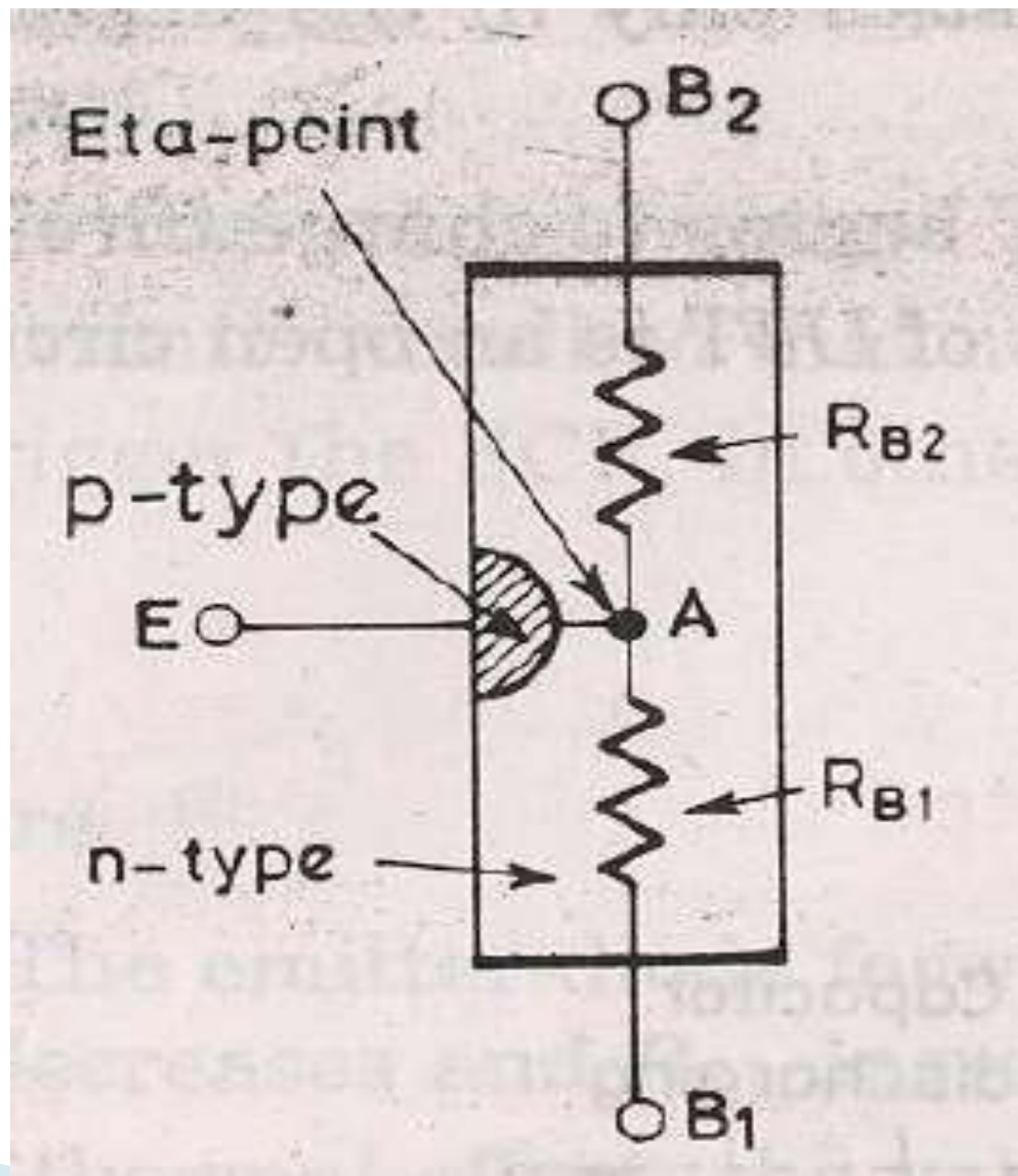





- ▶ UJT is made of an n-type silicon base to which p-type emitter is embedded.
- ▶ n-type base is lightly doped, whereas p-type emitter is heavily doped.
- ▶ Between bases  $B_1$  and  $B_2$ , unijunction behaves like an ordinary resistance.
- ▶ When  $V_{BB}$  is applied between  $B_1$  and  $B_2$


$$V_{AB1} = \frac{V_{BB}}{R_{B1} + R_{B2}} \cdot R_{B1} = \frac{R_{B1}}{R_{B1} + R_{B2}} \cdot V_{BB} = \eta V_{BB}$$



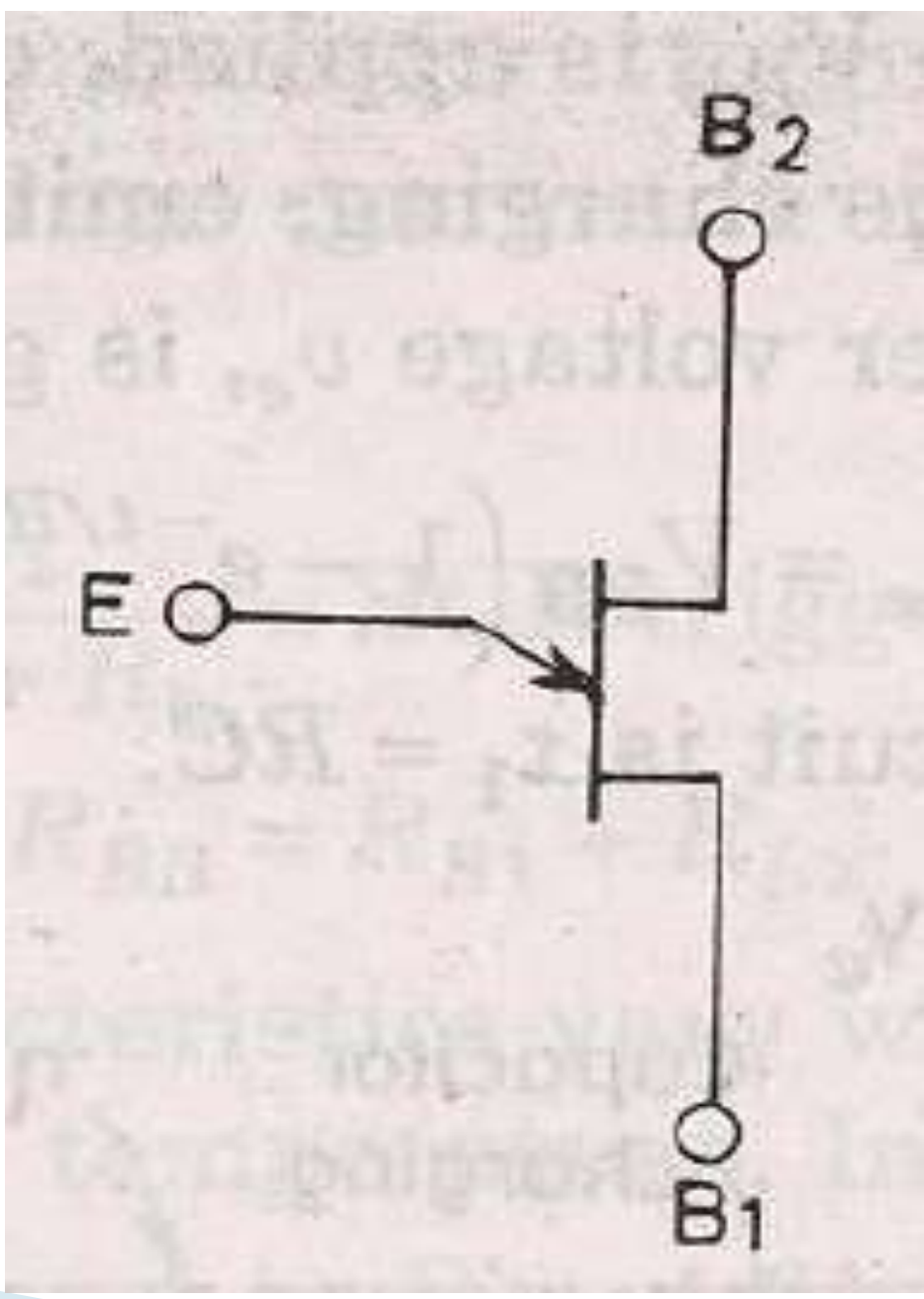
- ▶  $\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$  is called the intrinsic standoff ratio.
- ▶ Typical values of  $\eta$  are 0.51 to 0.82.
- ▶ Inter base resistance  $R_{BB} = R_{B1} + R_{B2}$  is of the order of 5 – 10 K $\Omega$ .
- ▶ Emitter is nearer to  $B_2$ , resistance  $R_{B2}$  is less than  $R_{B1}$ .



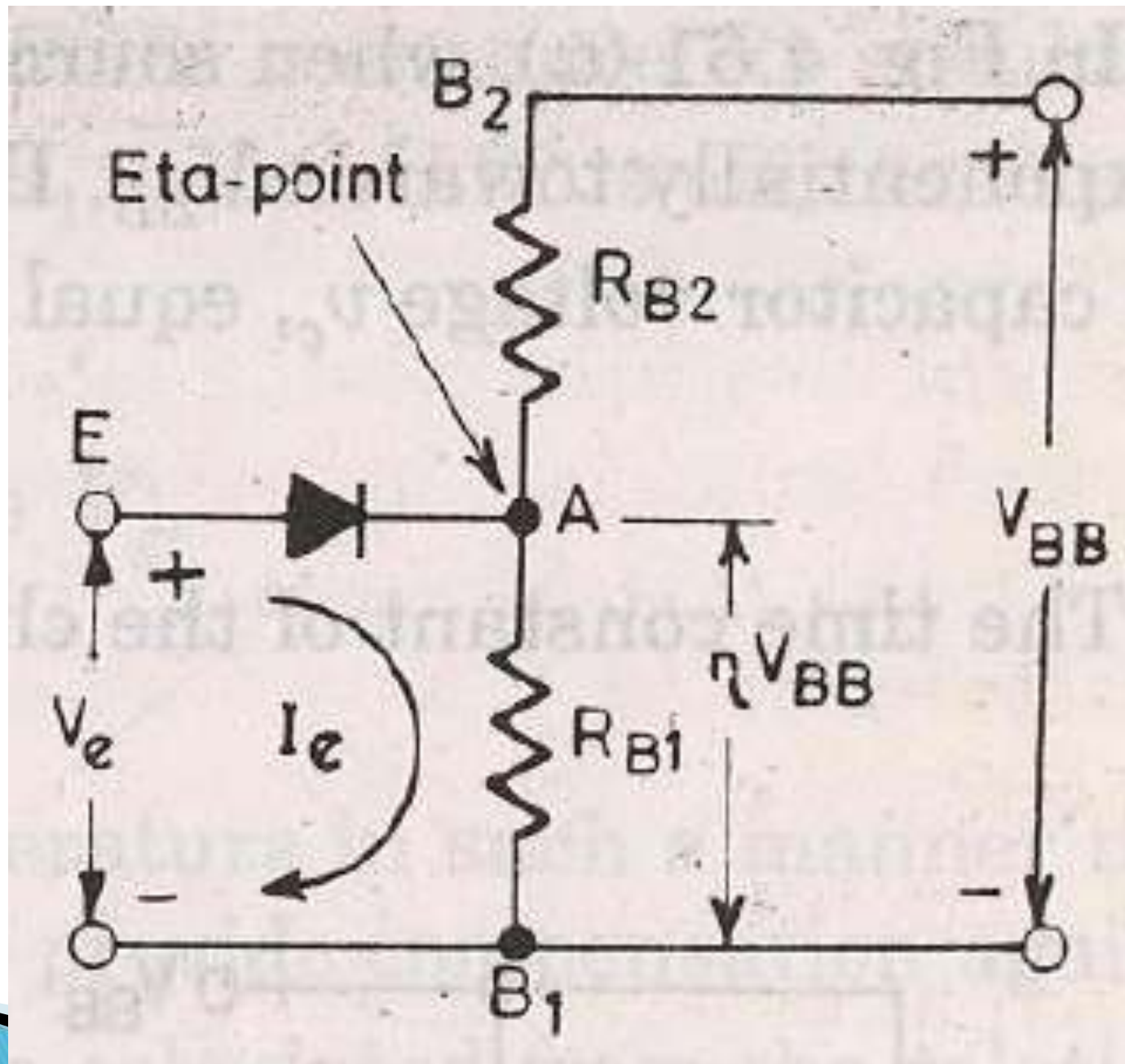

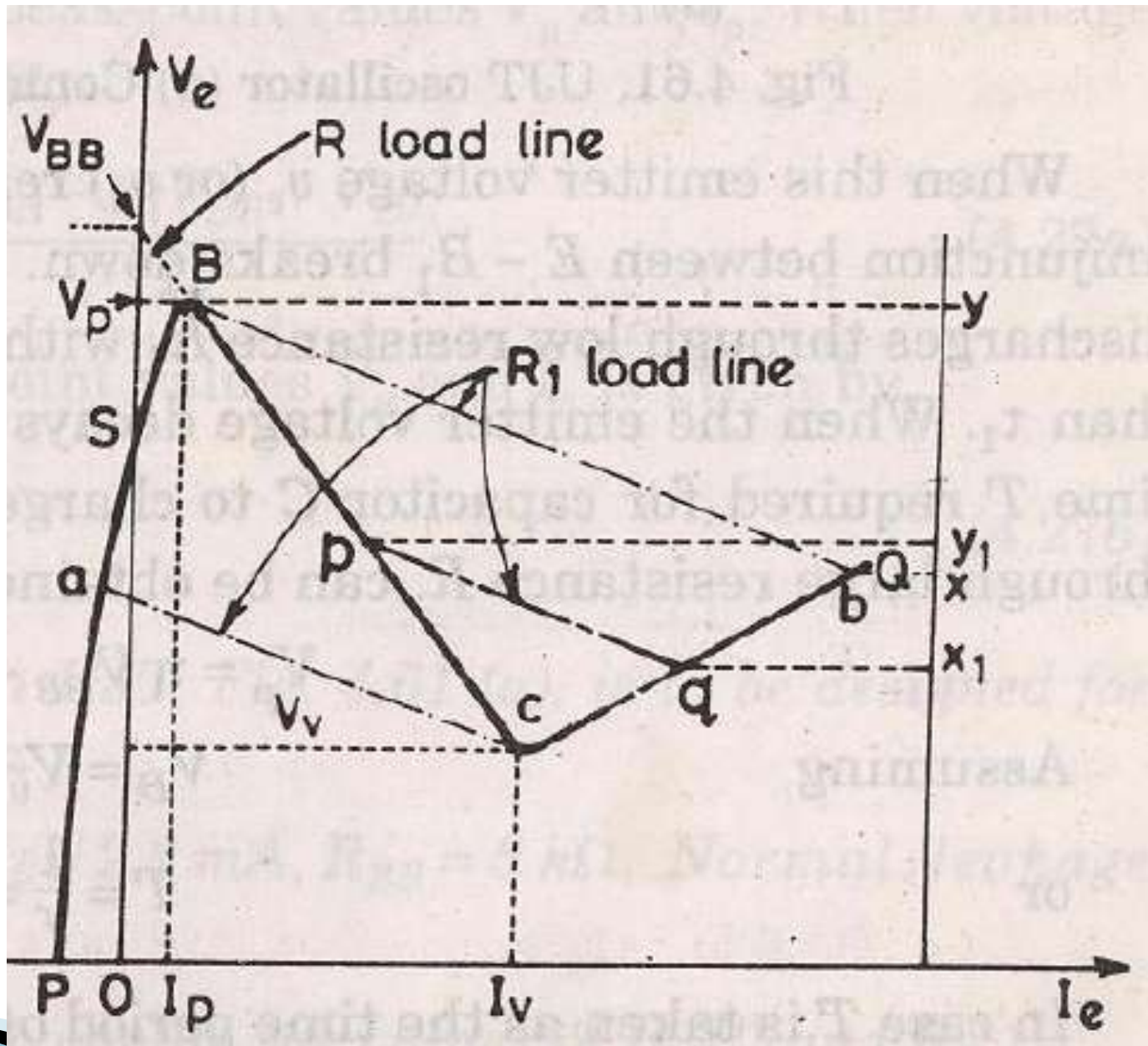


- ▶ As long as emitter voltage  $V_e < \eta V_{BB}$ , the E-B<sub>1</sub> junction is reverse biased and emitter current  $I_e$  is negative.
- ▶ At point S, drop across  $R_E$  is zero and  $I_e = 0$ .
- ▶ When  $V_e = \eta \cdot V_{BB} + V_D$  at point B, E-B<sub>1</sub> junction gets forward biased.
- ▶  $V_D$  is forward voltage drop across the junction E-B<sub>1</sub> (usually 0.5V).
- ▶  $V_p$  and  $I_p$  are called peak voltage and peak current respectively.

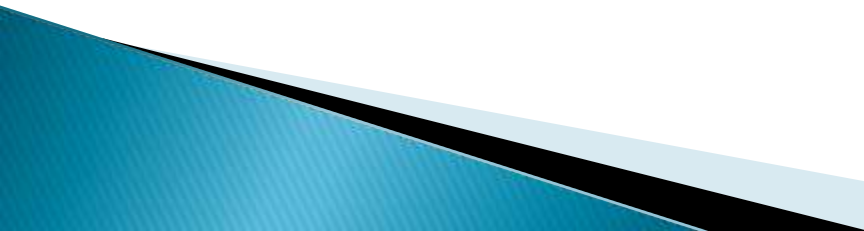- ▶ At peak point B, the p-emitter begins to inject holes in to lower base region  $B_1$ .
  - ▶ Resistance  $R_{B_1}$  suddenly decreases.
  - ▶ Potential of eta point A drops.
  - ▶ As  $V_{EE}$  is constant, fall of  $V_e$  gives rise to more emitter current  $I_e$  ( $= (V_{EE} - V_e) / R_E$ ).
  - ▶ Increased  $I_e$  injects more holes, further reducing  $R_{B_1}$  and so on.
- 


- ▶ Regenerative effect continues till  $R_{B1}$  has dropped to small value (from about  $4K\Omega$  to around  $2$  to  $25\Omega$ ).
- ▶ Emitter current is limited by external resistance  $R_E$  only.
- ▶ At valley point (point C), UJT reaches the on state.
- ▶ At point C, entire base region is saturated and  $R_{B1}$  can not decrease any more.




- ▶ Any increase in  $V_e$  is accompanied by increase in  $I_e$ .
  - ▶ Between point B and C,  $V_e$  Falls and  $I_e$  increases.
  - ▶ UJT, therefore, exhibits negative resistance between point B and C.
- 

# UJT Relaxation Oscillator




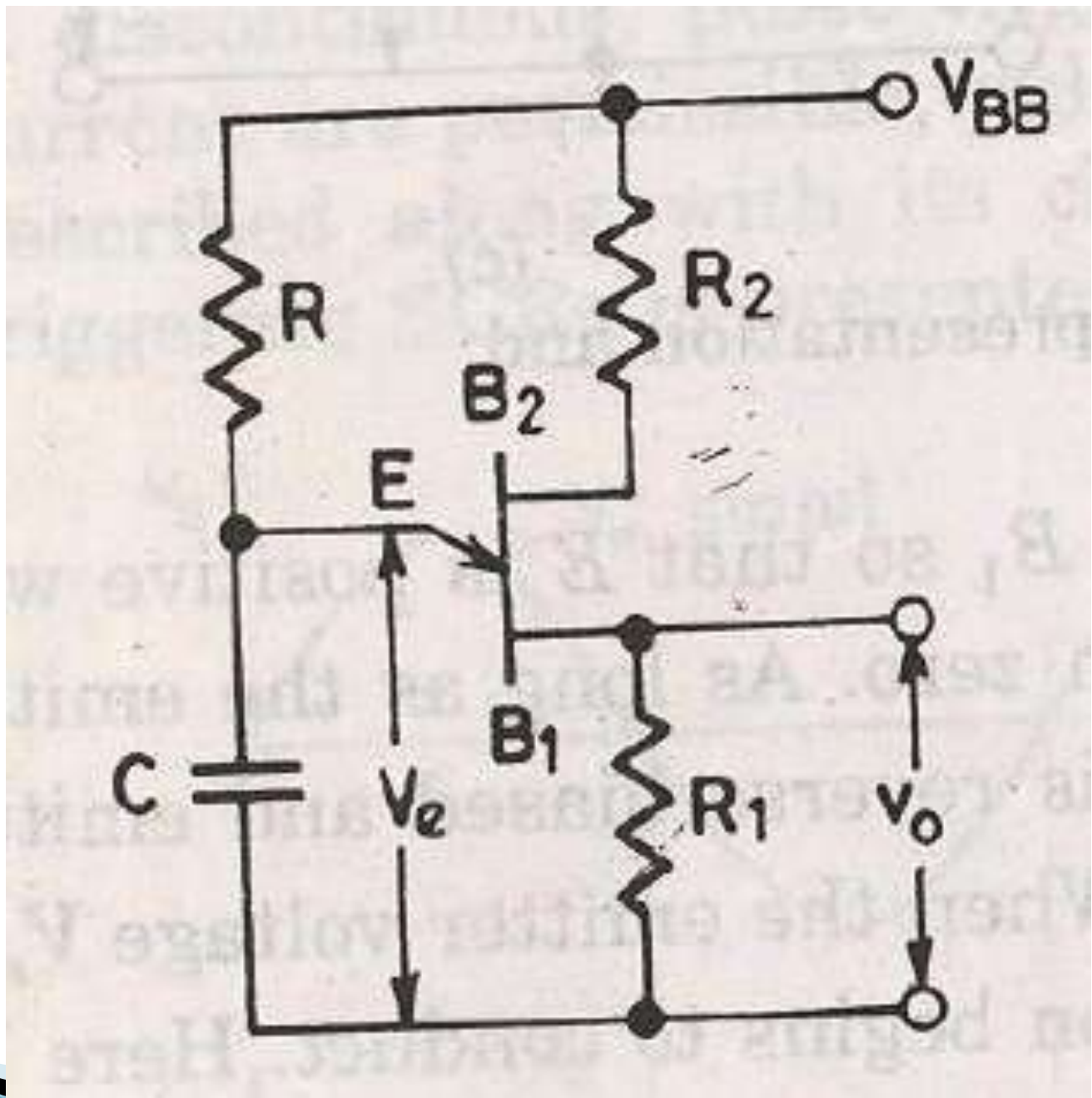

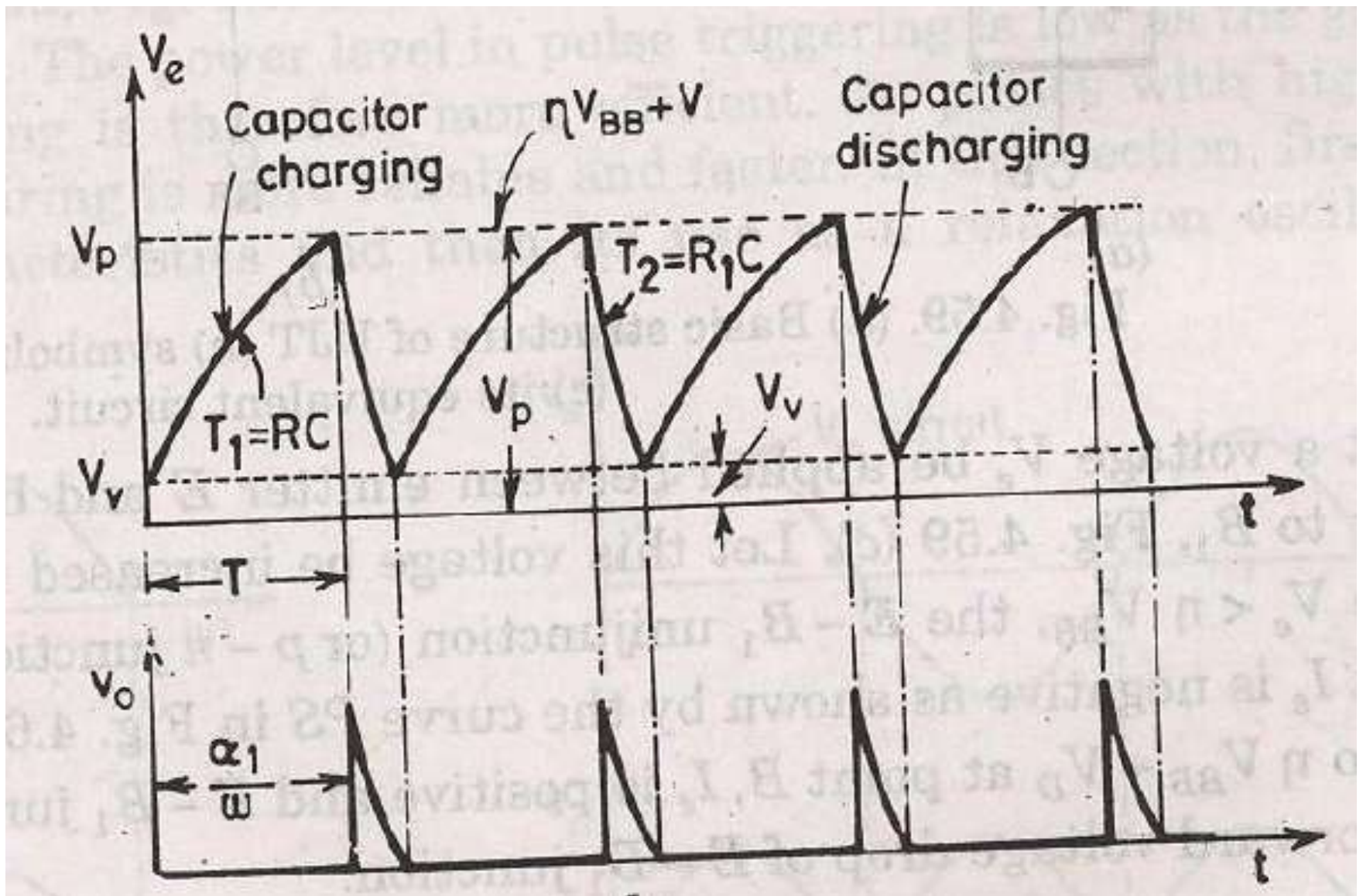


- ▶ UJT is highly efficient switch.
- ▶ Switching time is of the range of nano seconds.
- ▶ Because of negative resistance characteristics, UJT can be used as relaxation oscillator.
- ▶ External resistance  $R_1$  and  $R_2$  are small as compared to internal resistances  $R_{B1}$  and  $R_{B2}$ .
- ▶ On application of  $V_{BB}$ , capacitor  $C$  begins to charge through  $R$ , exponentially towards  $V_{BB}$ .

# Commutation of Thyristor

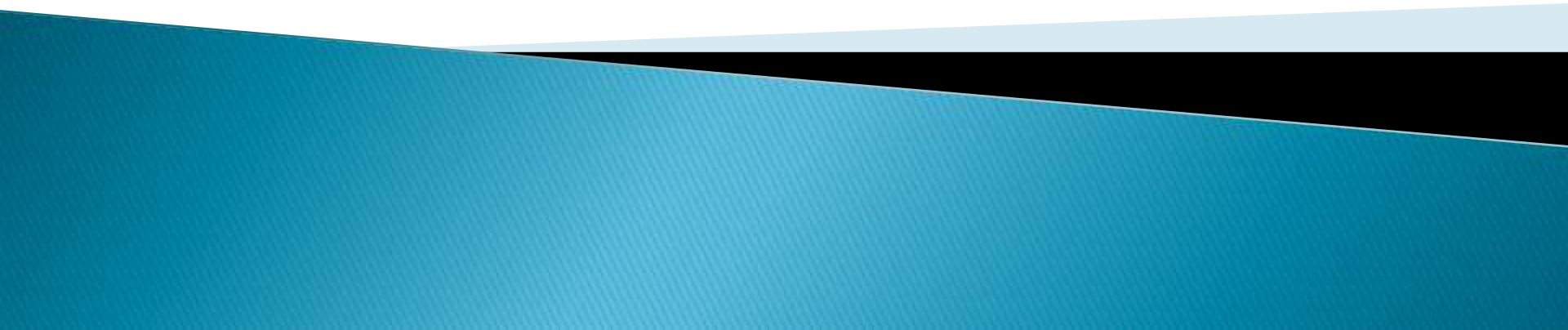






# Class A Commutation (Load Commutation)

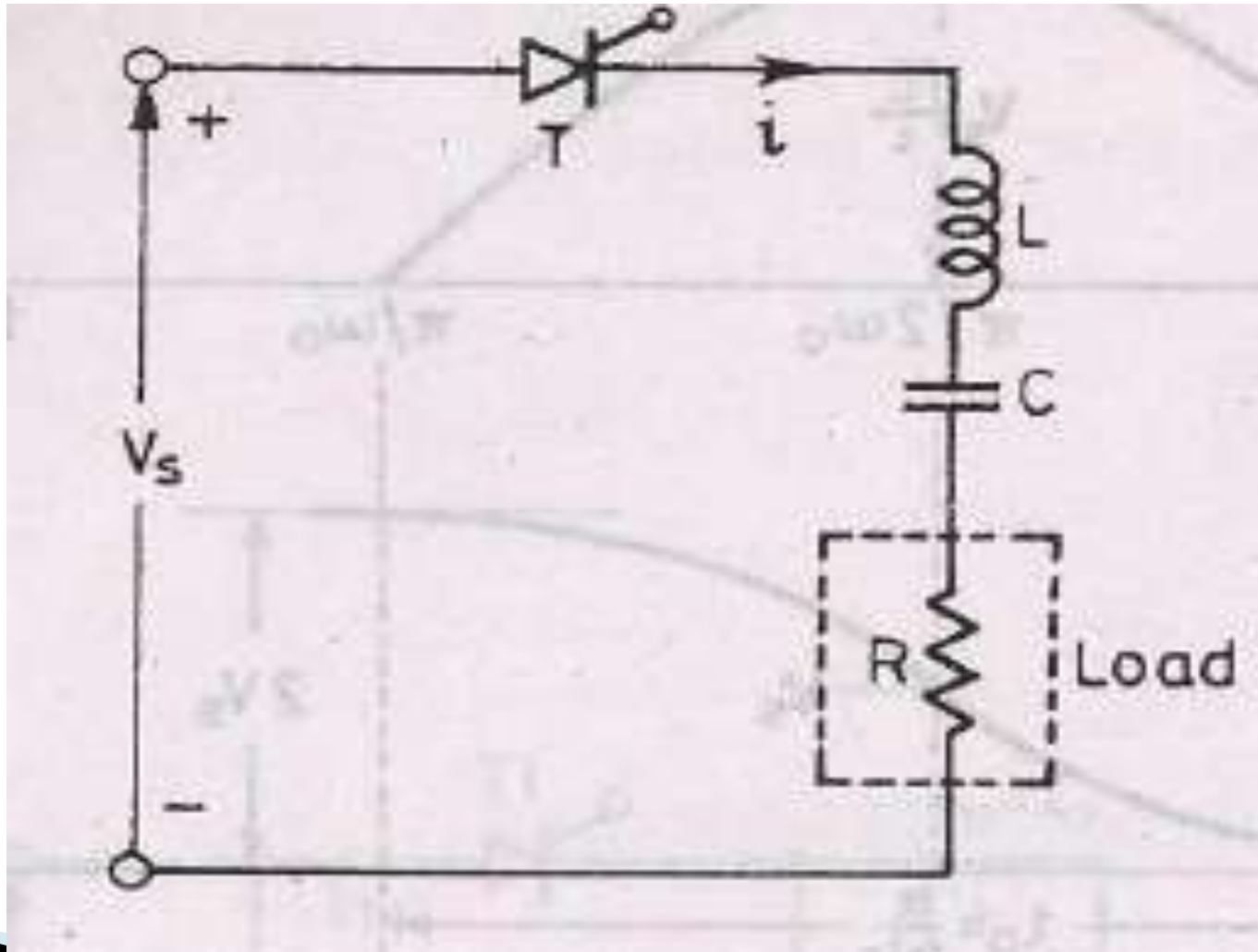




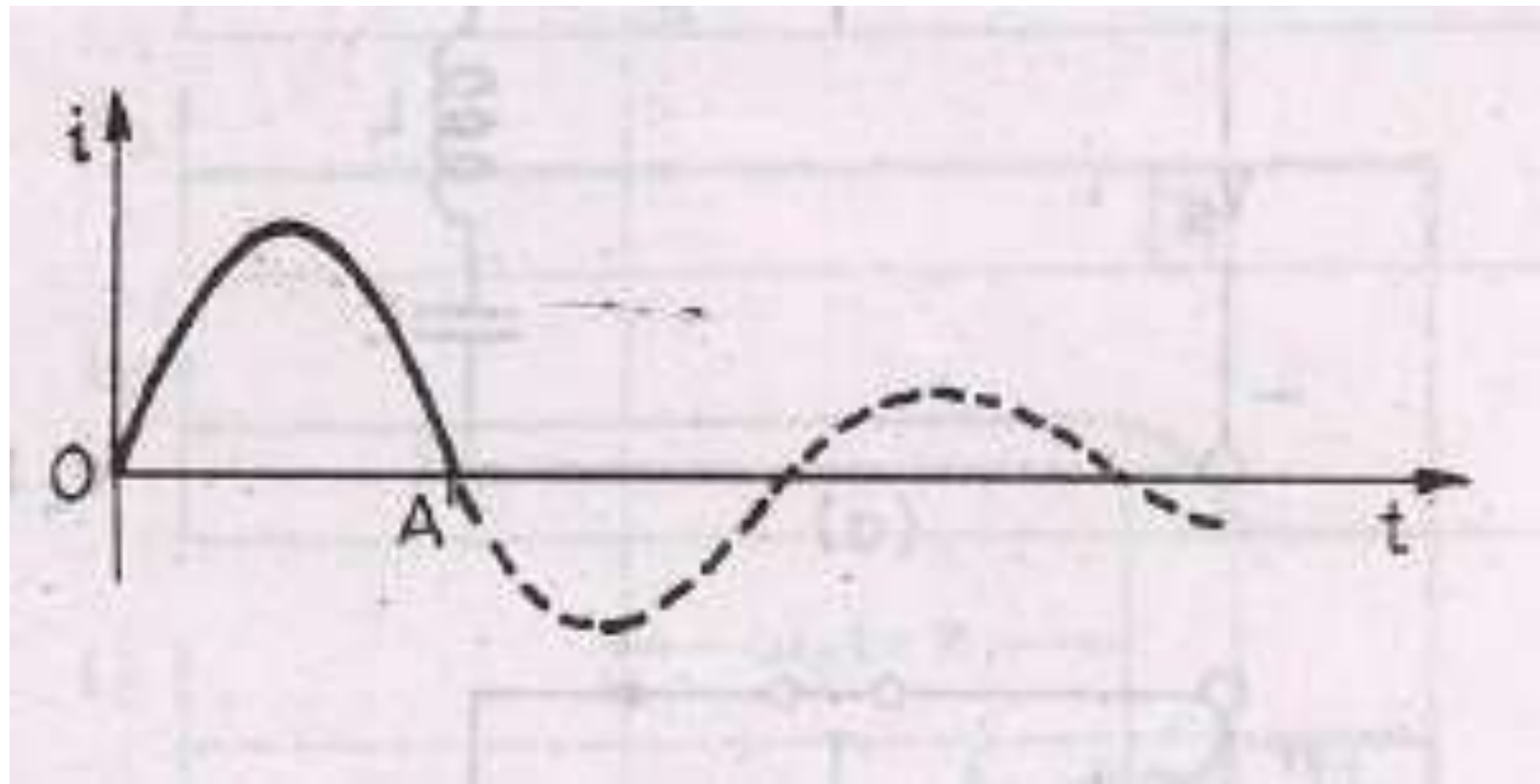

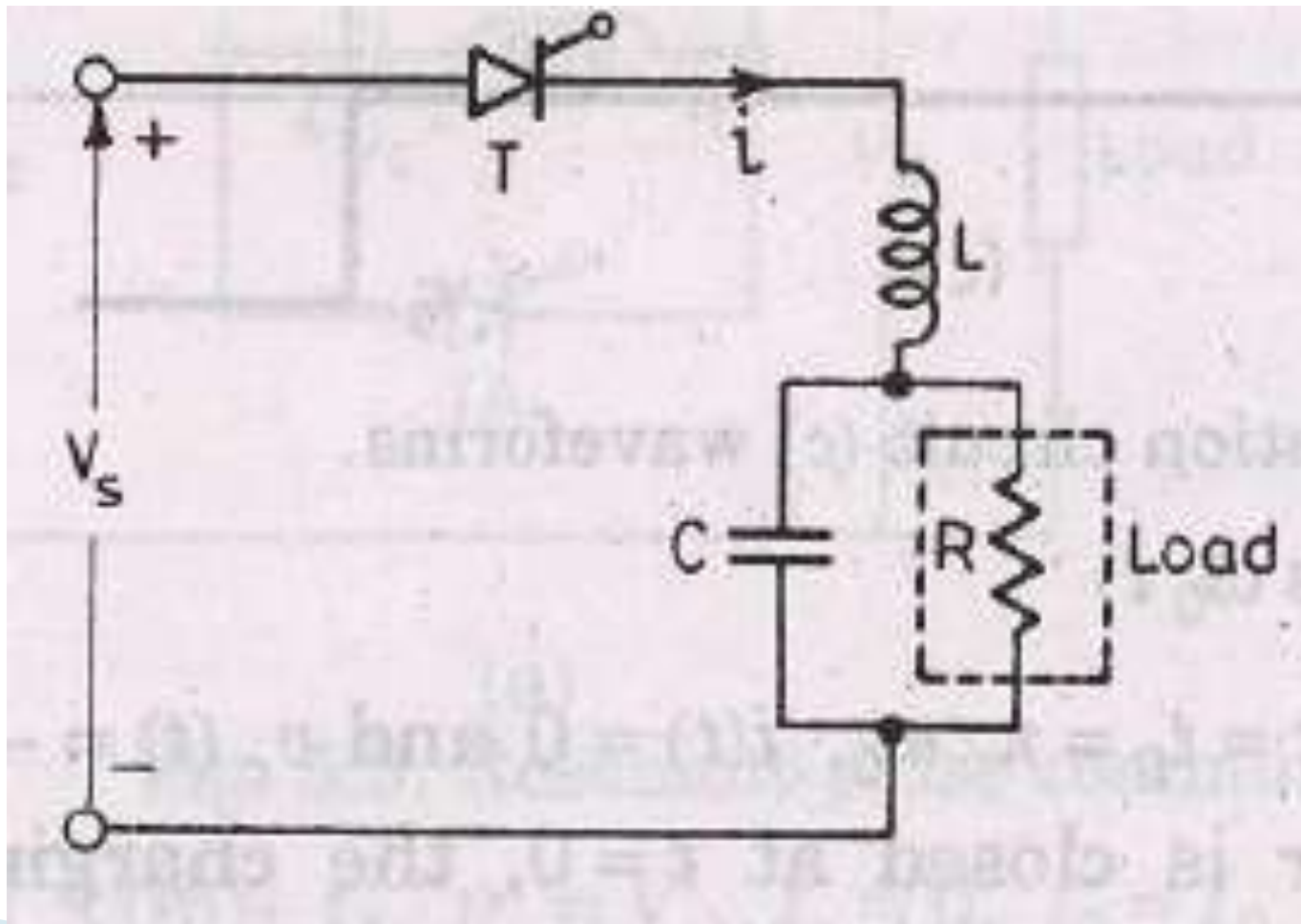


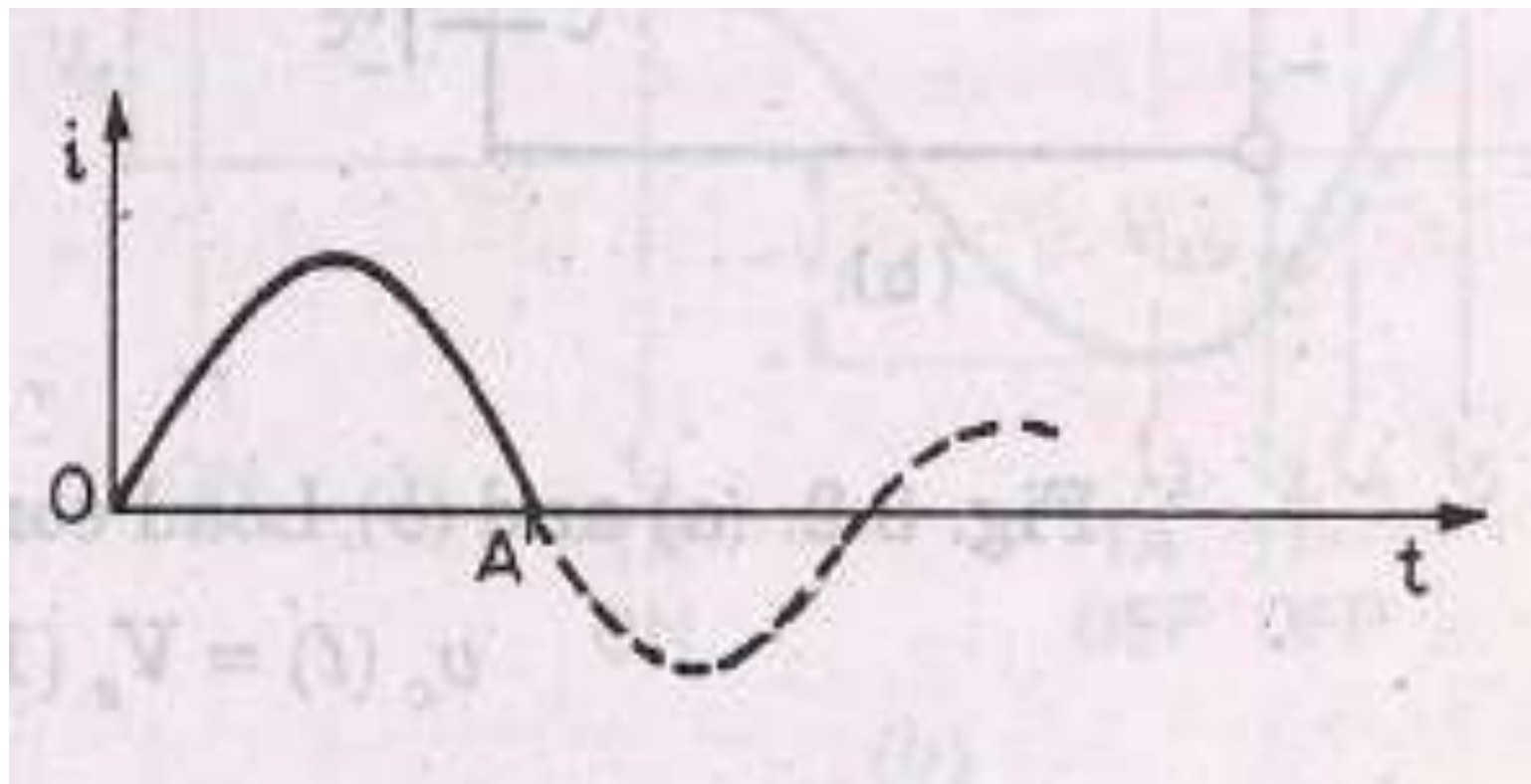

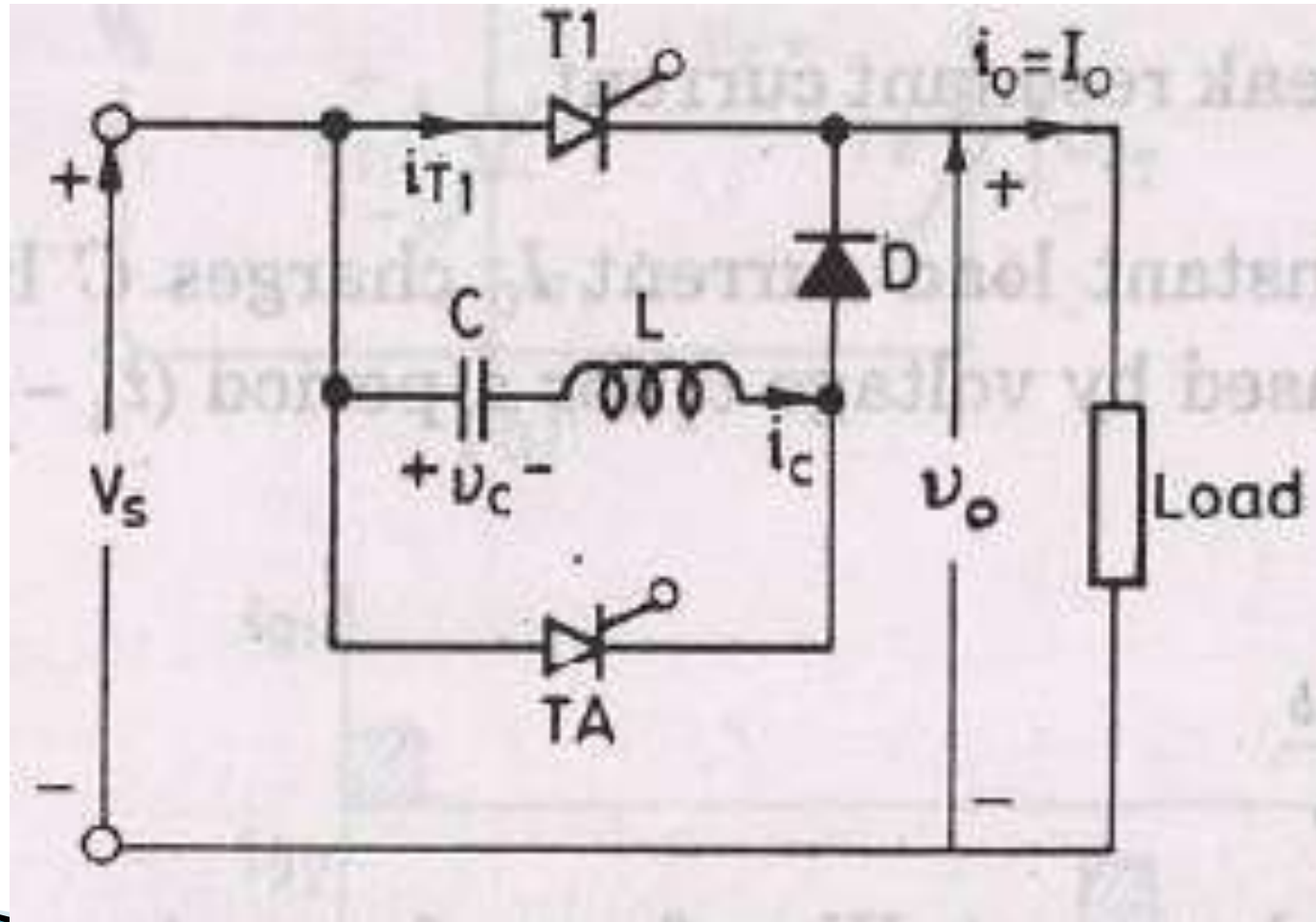
# Class B Commutation (Resonant Pulse Commutation)


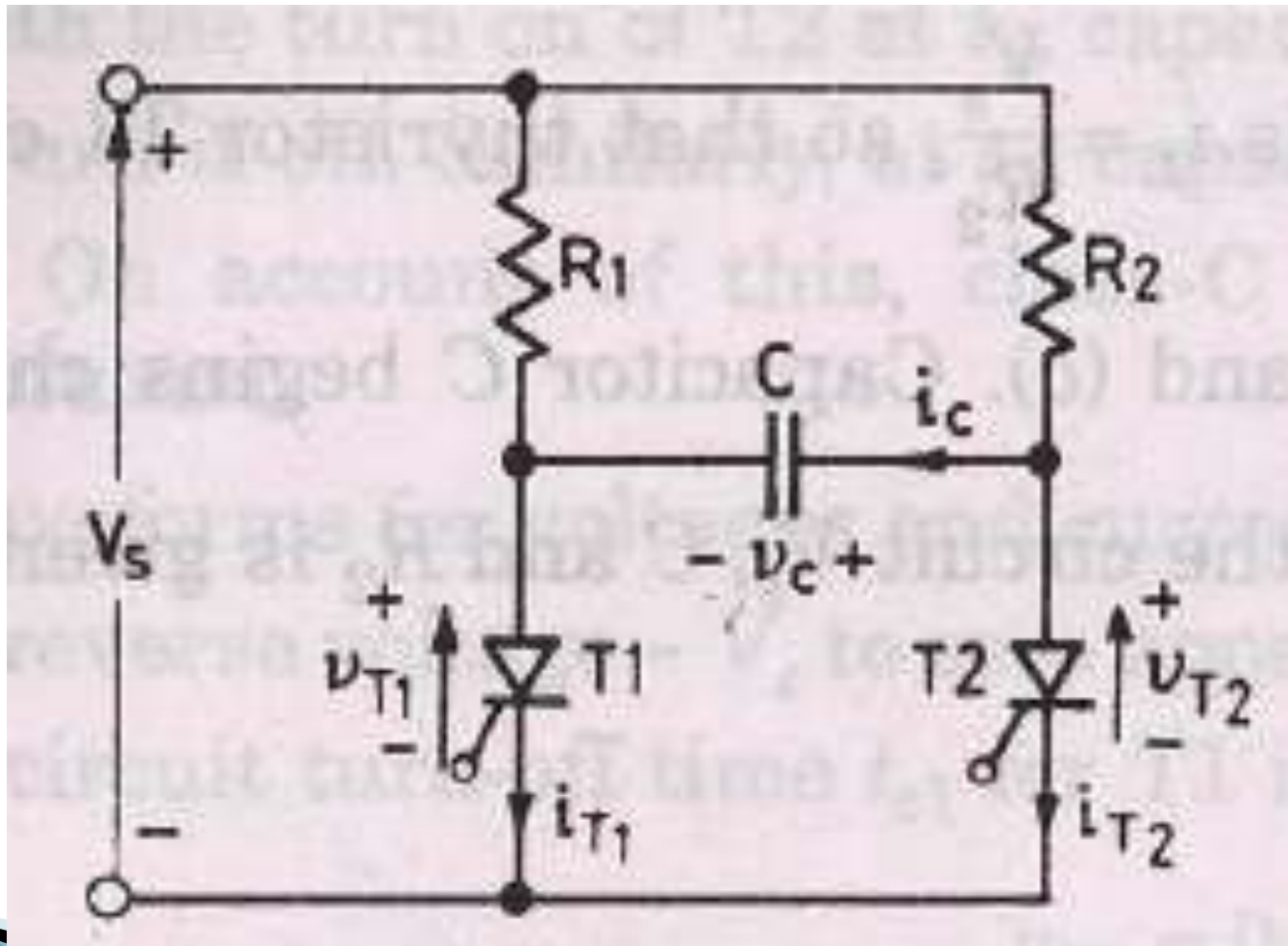
# Class C Commutation (Complementary Commutation)



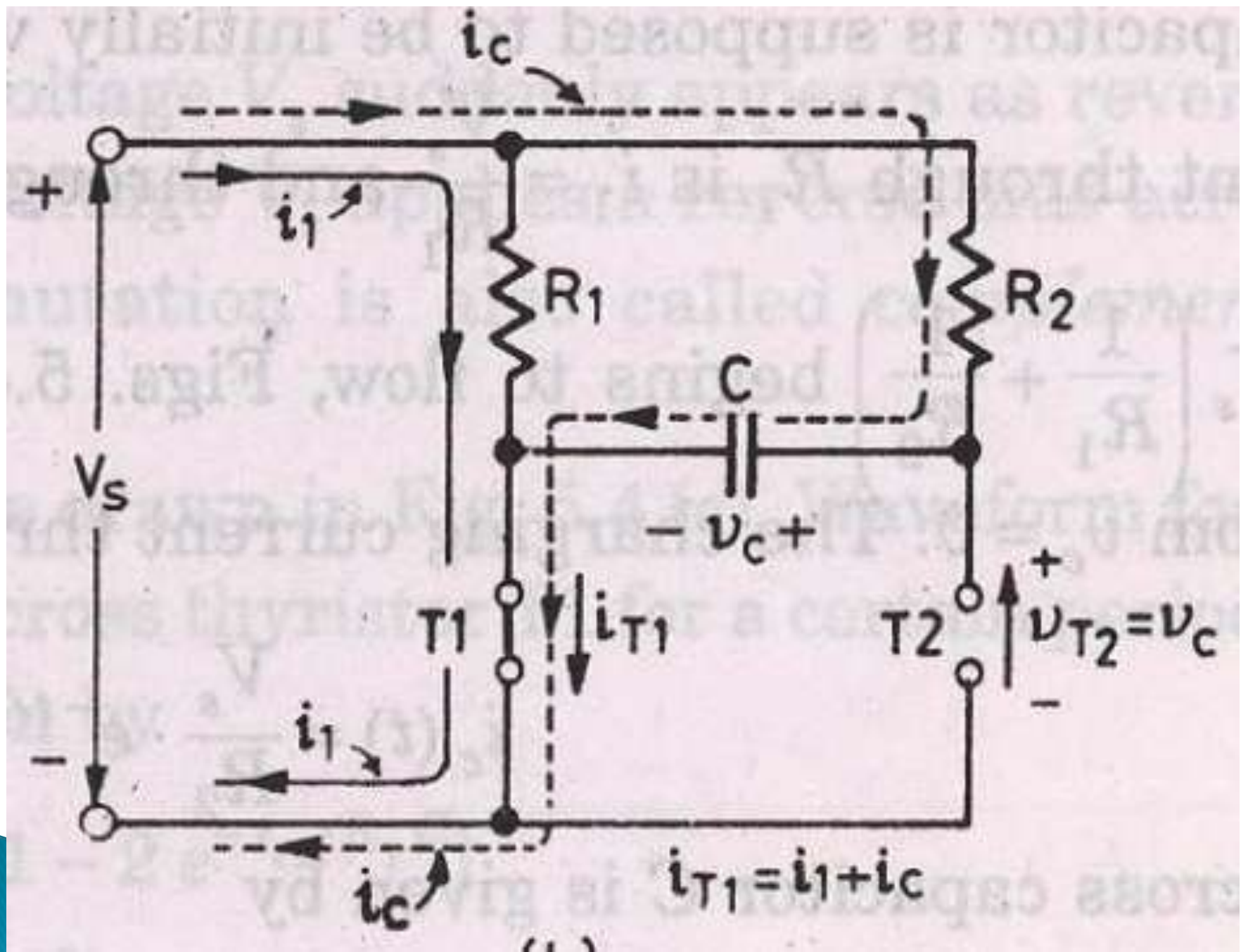



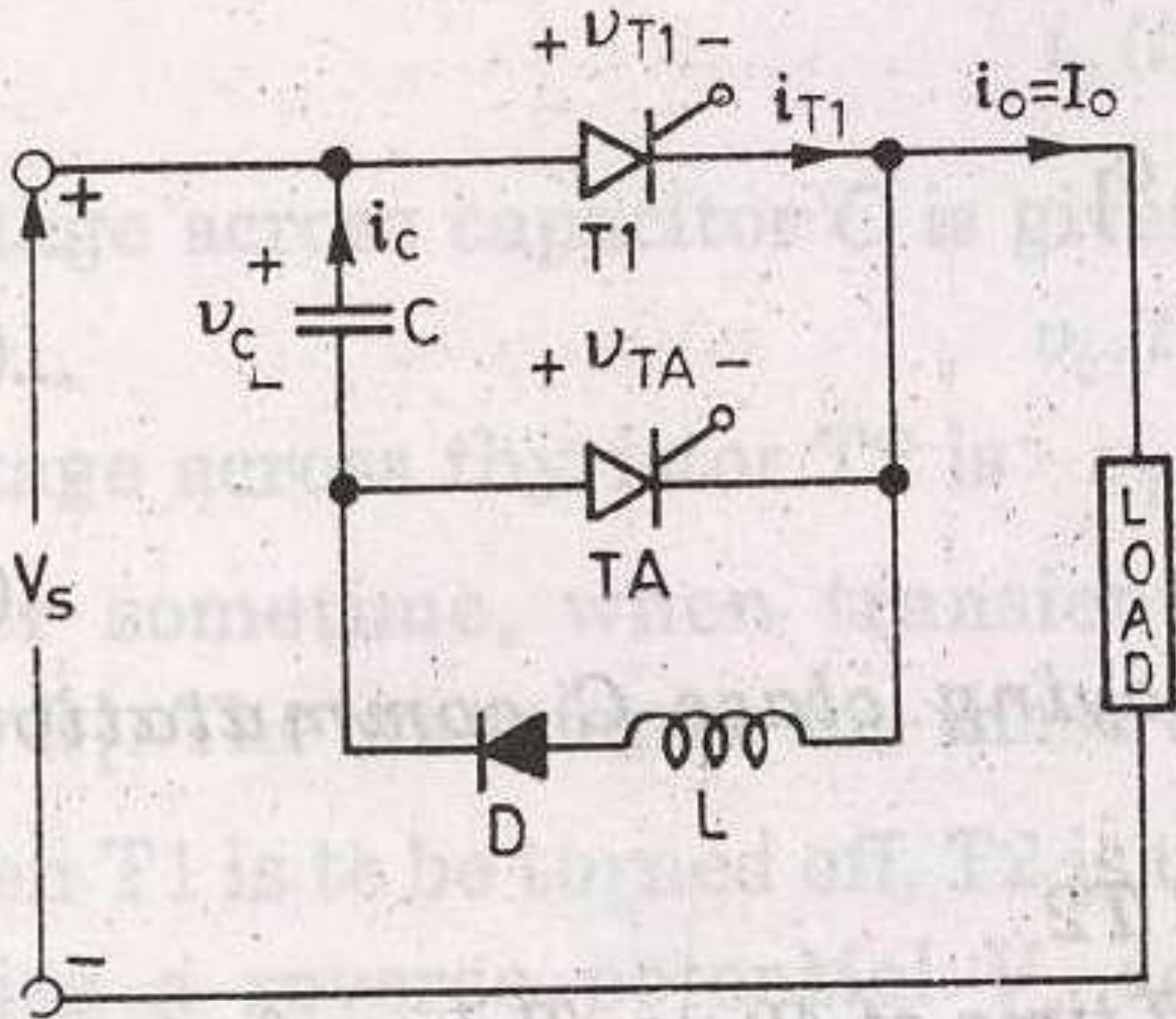
# Class D Commutation: Impulse Commutation








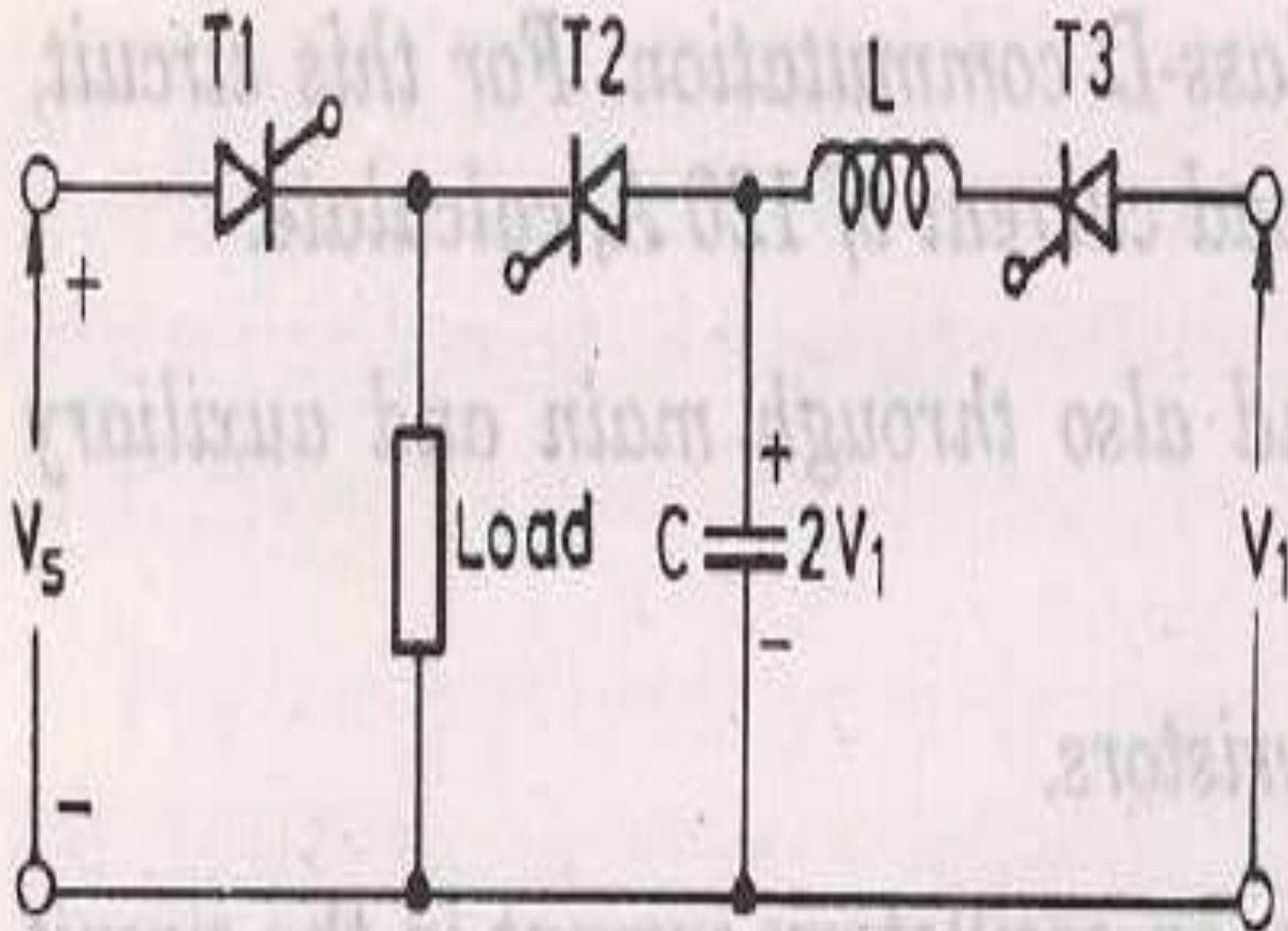
# Class E Commutation: External Pulse Commutation






# Class F or Line Commutation



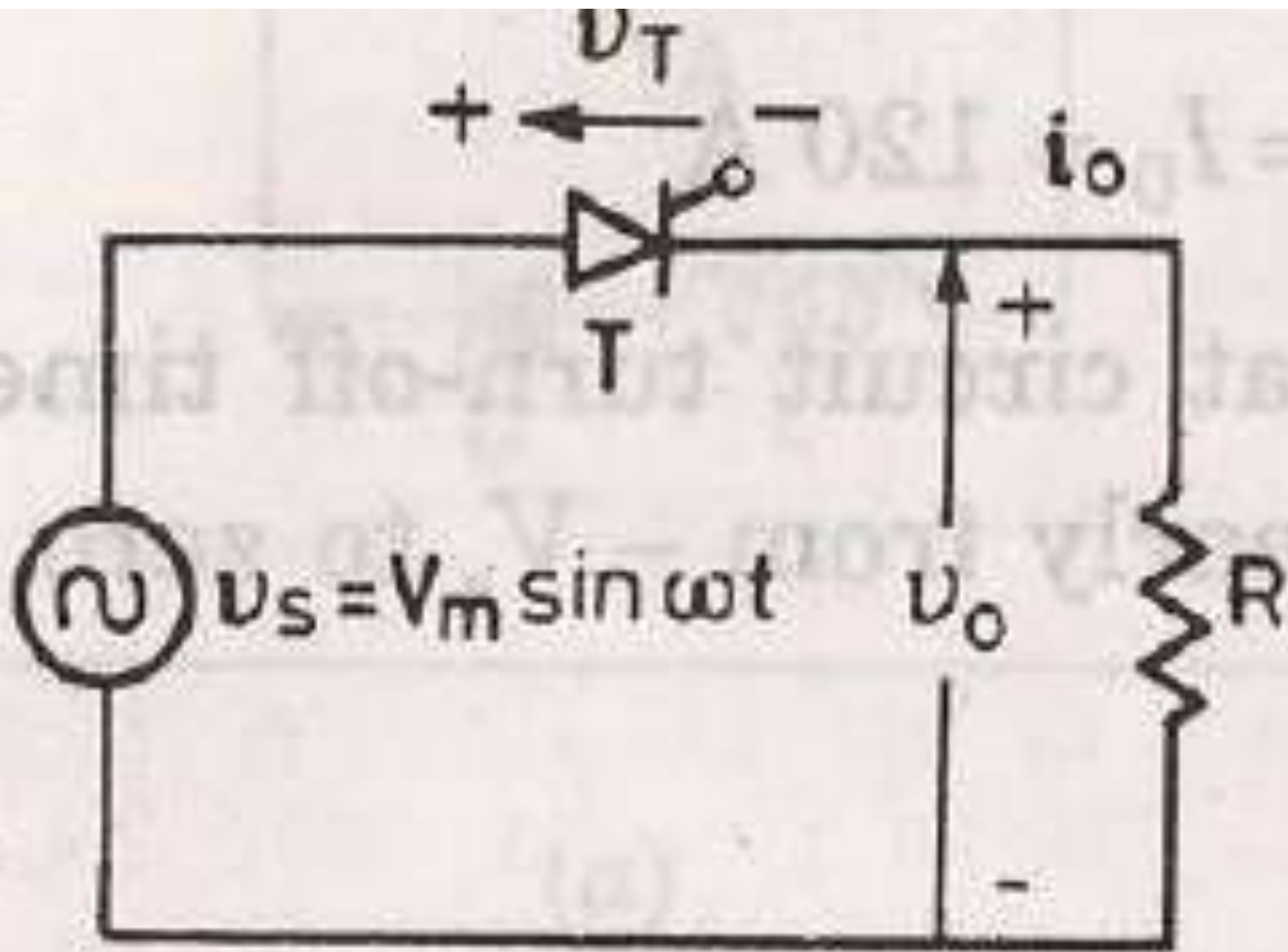

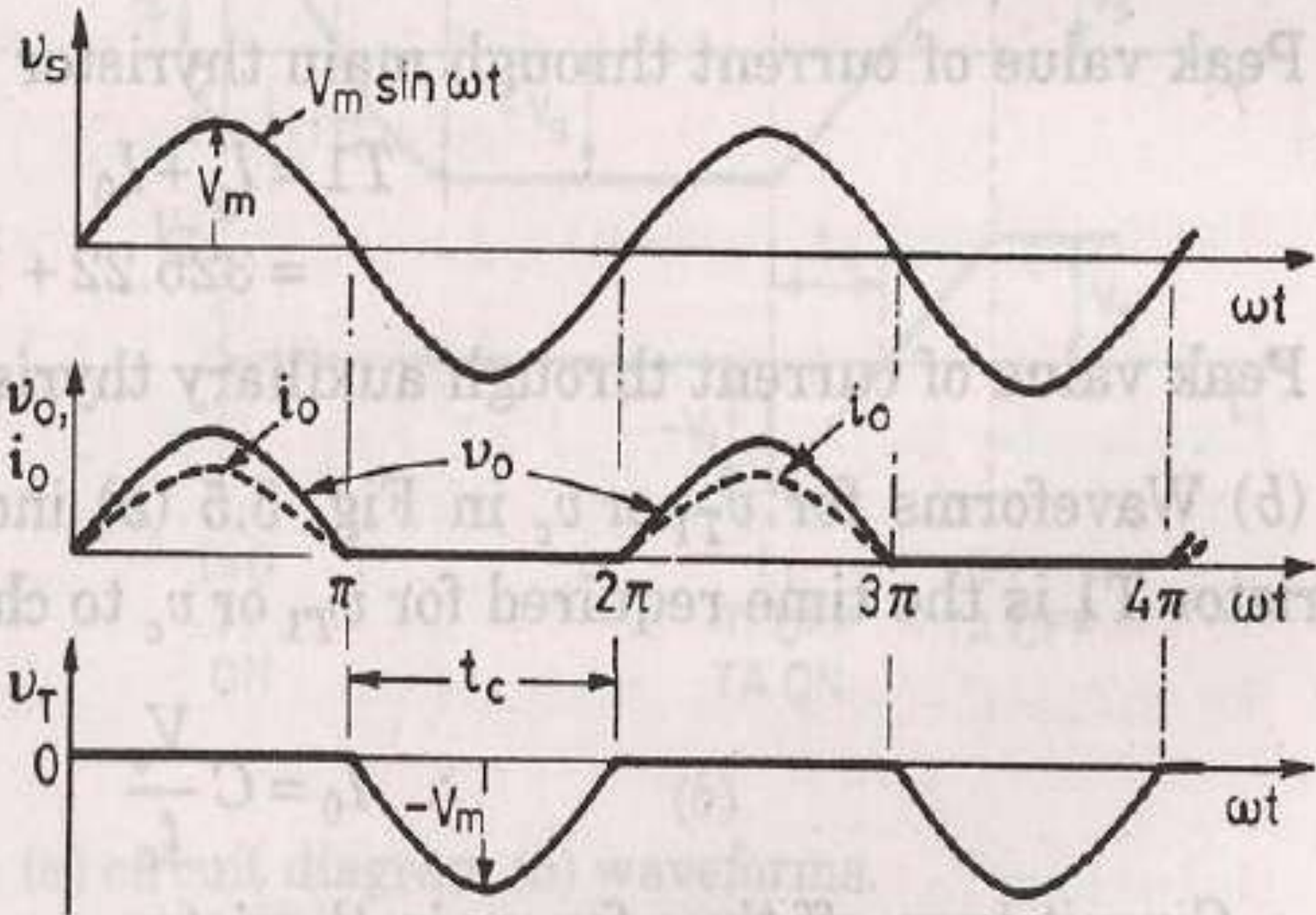



# Series and Parallel Operation


string efficiency


$$= \frac{\text{Actual voltage/current rating of the whole string}}{[\text{Individual voltage/current rating of one SCR}] [\text{Number of SCRs in the string}]}$$

$$DRF = 1 - \text{string efficiency}$$




# Series Operation

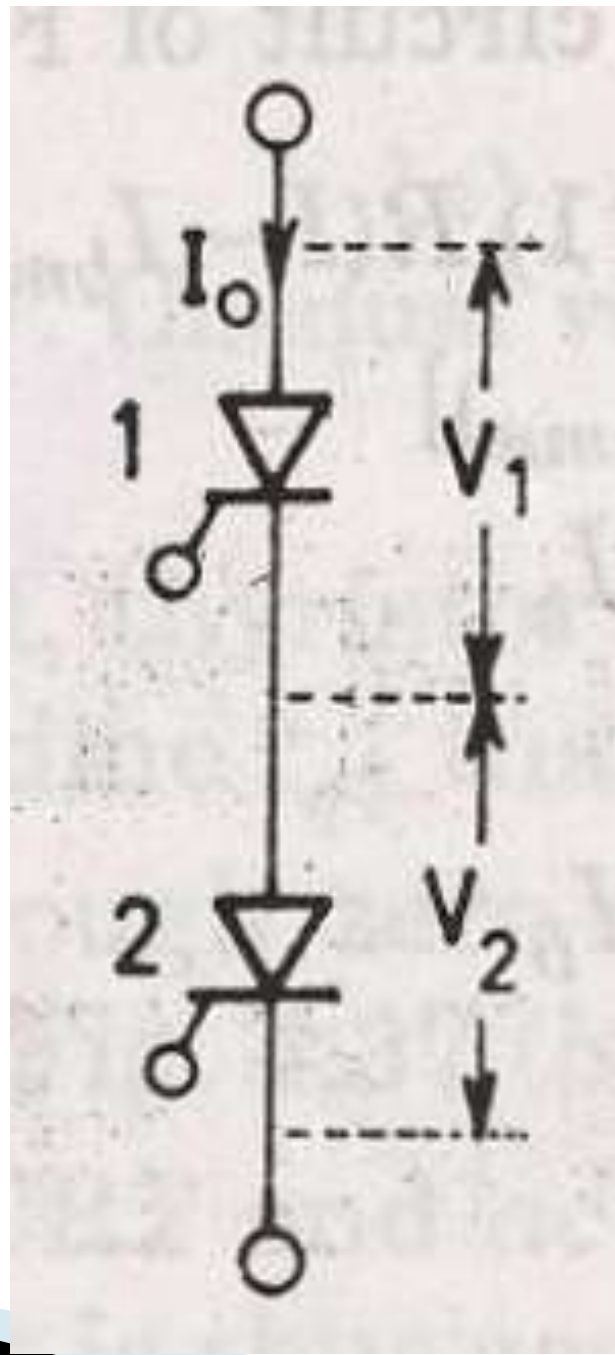


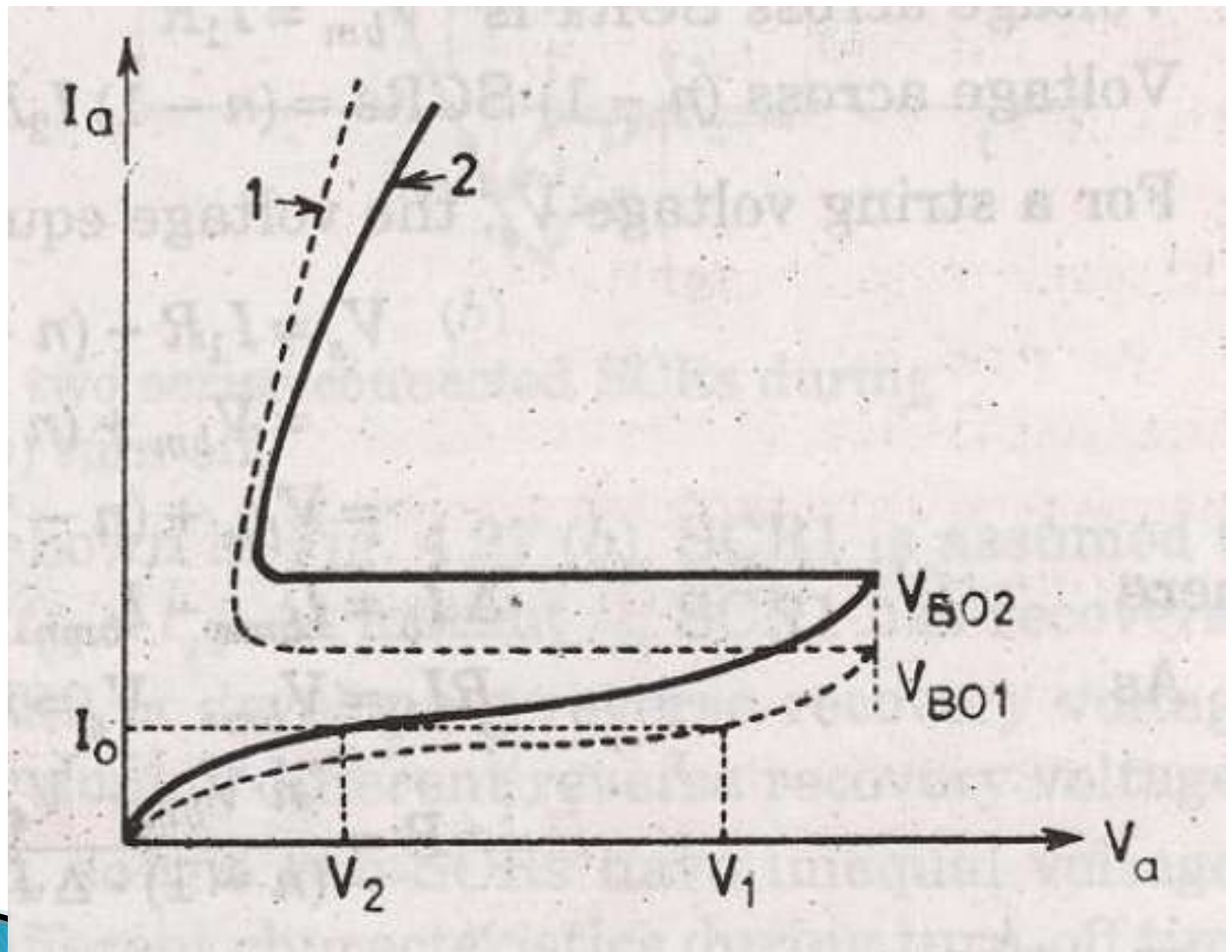

# Parallel Operation



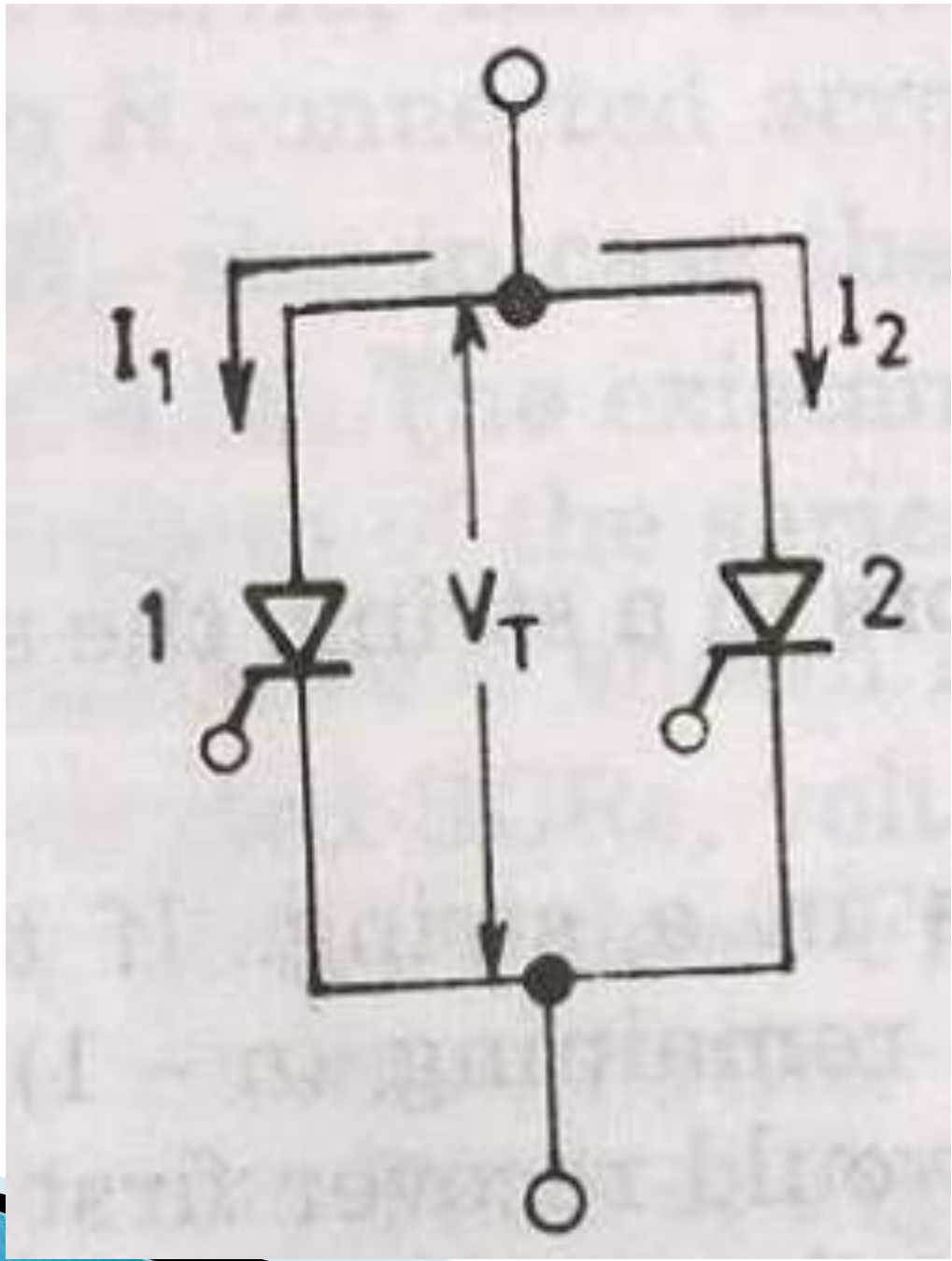

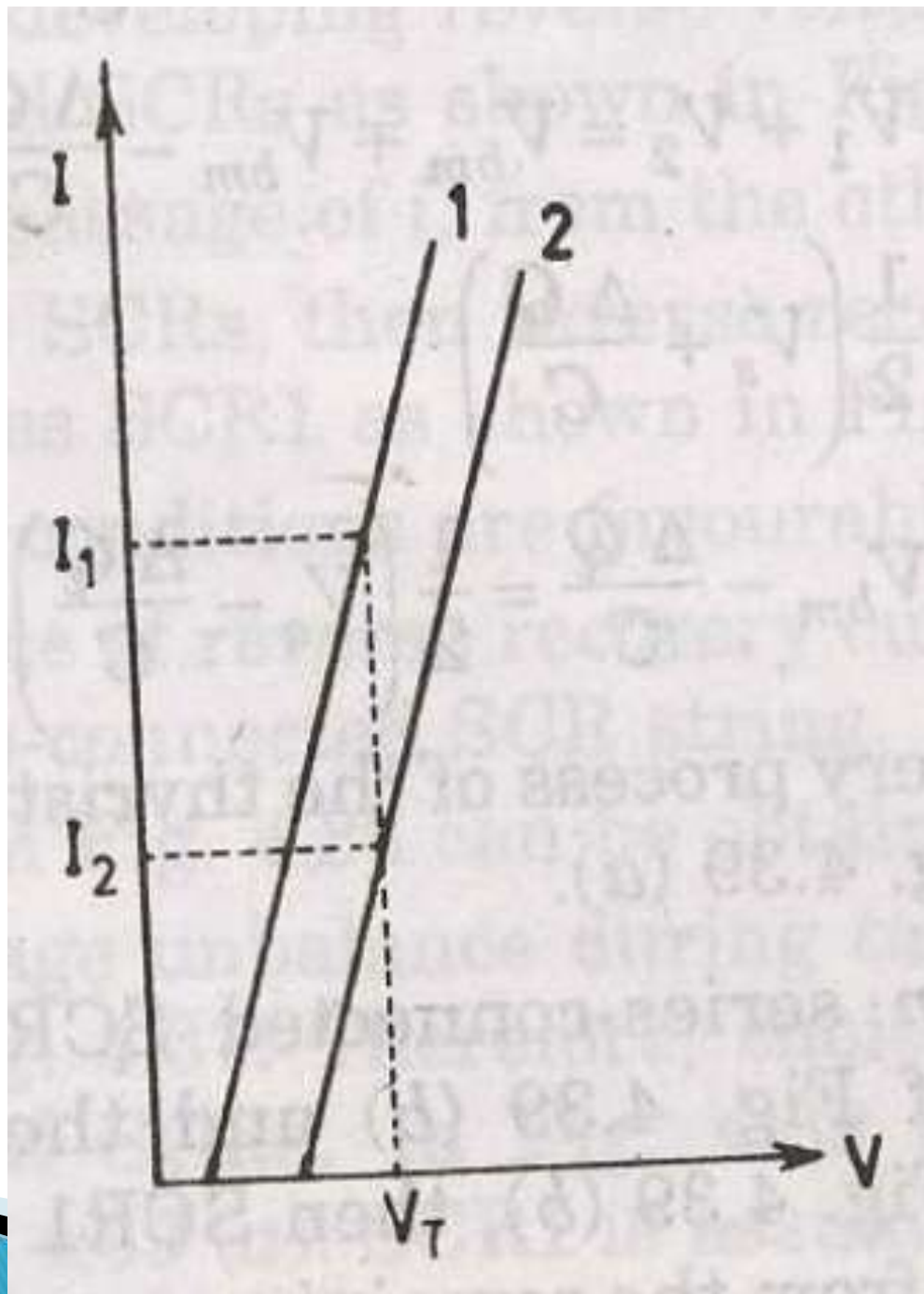


# Applications of Thyristor






# Light intensity Control



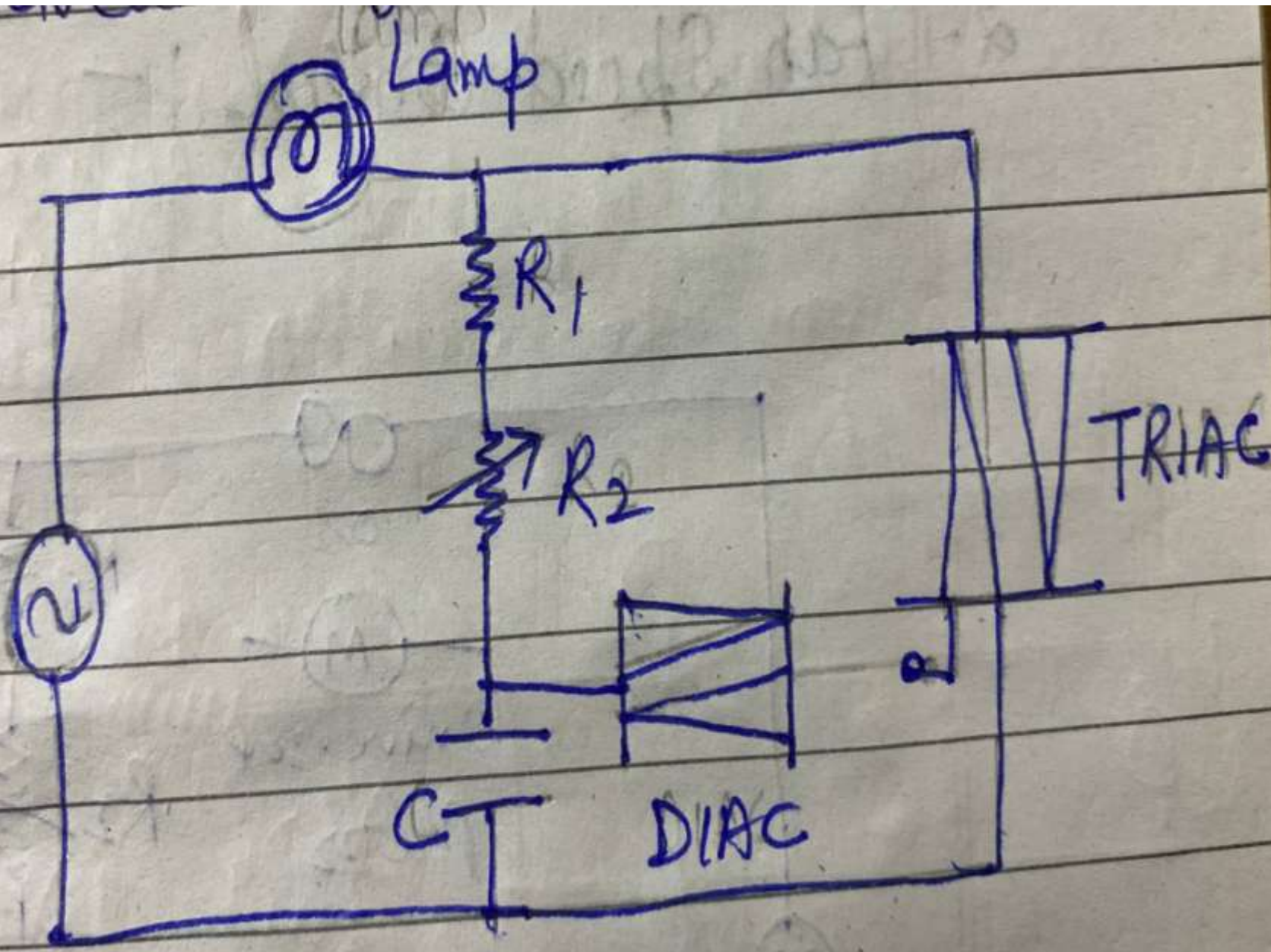

# Fan Speed Control



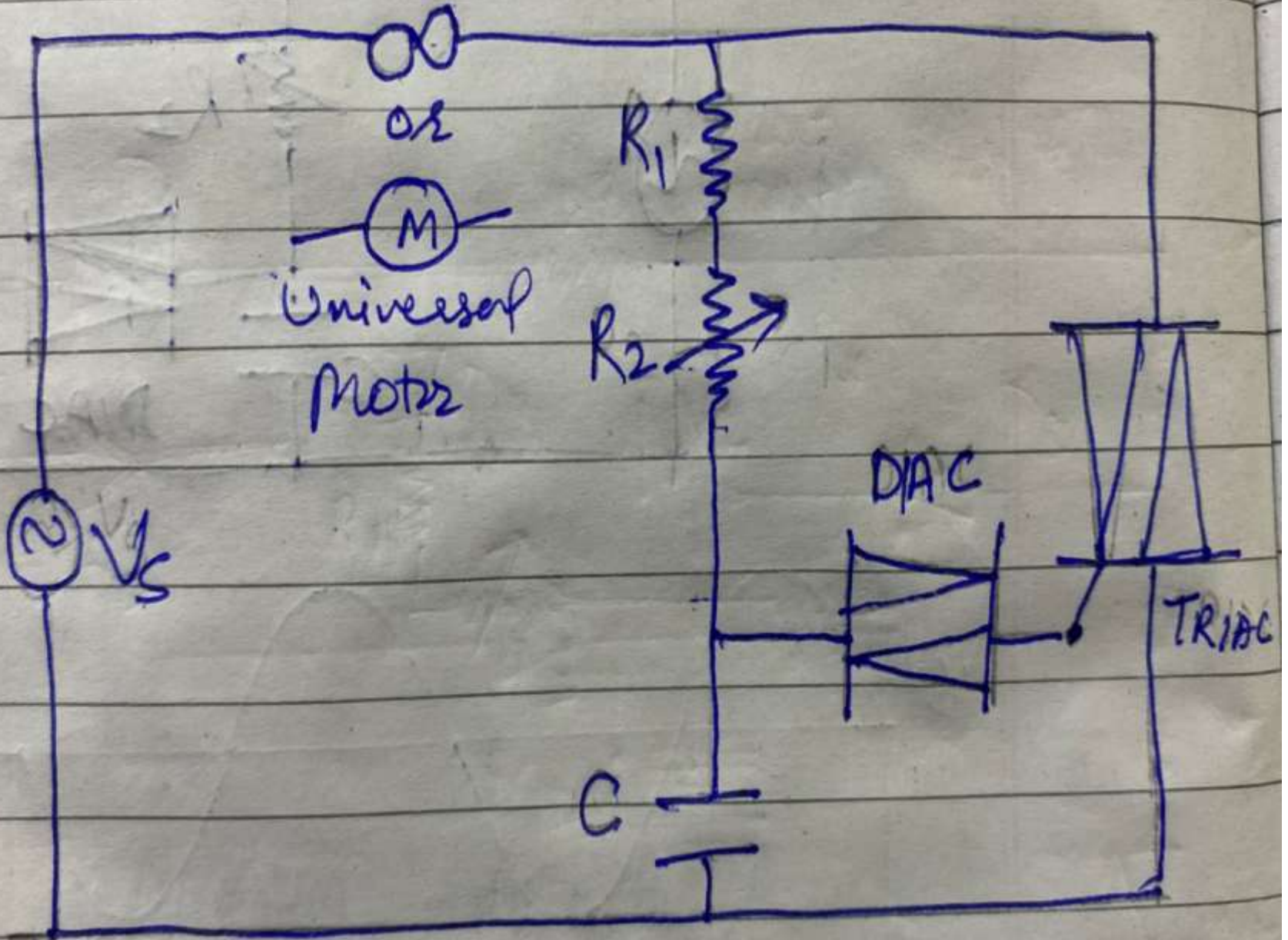


# Speed Control of DC Motor






Armature.

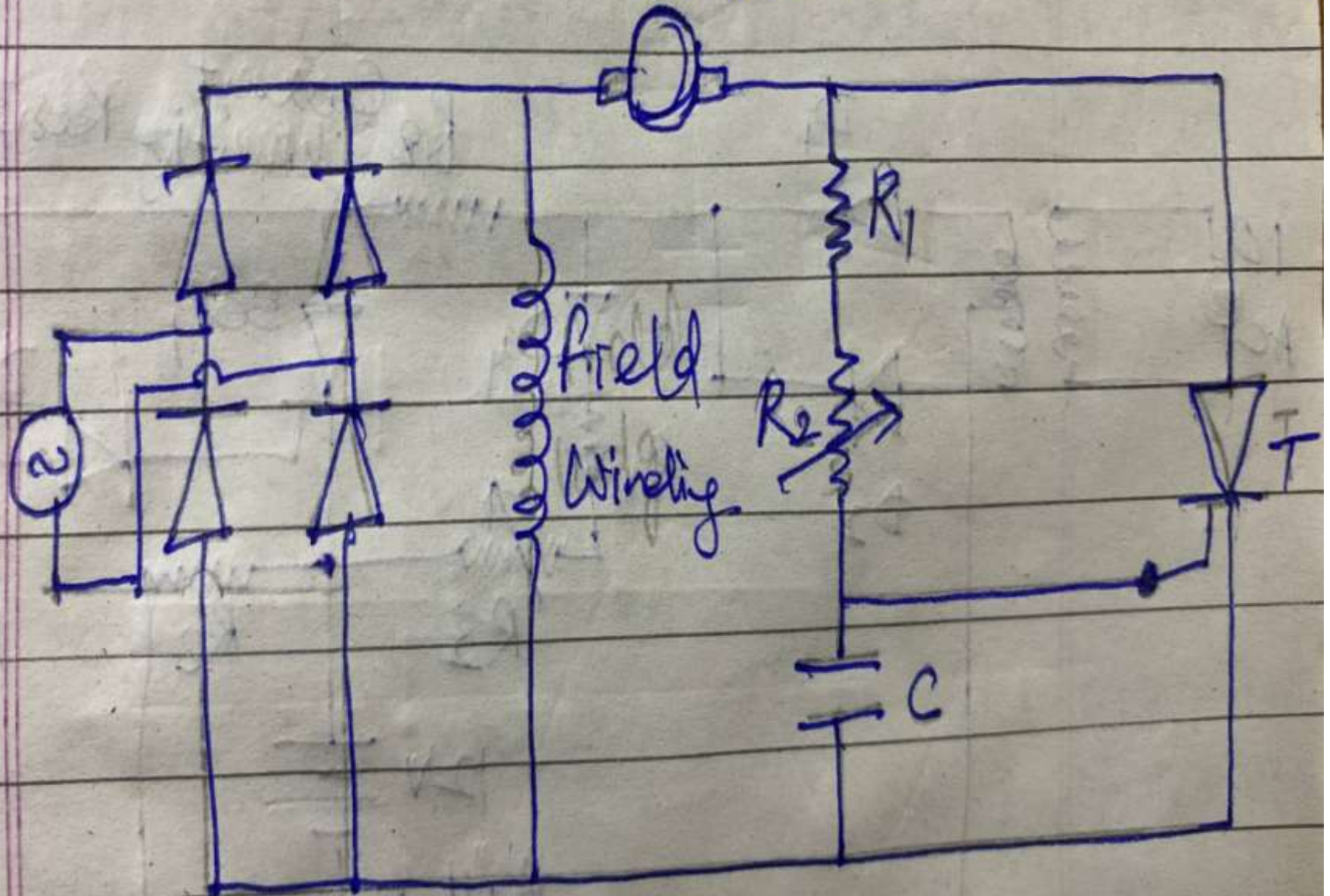

# Battery Charger






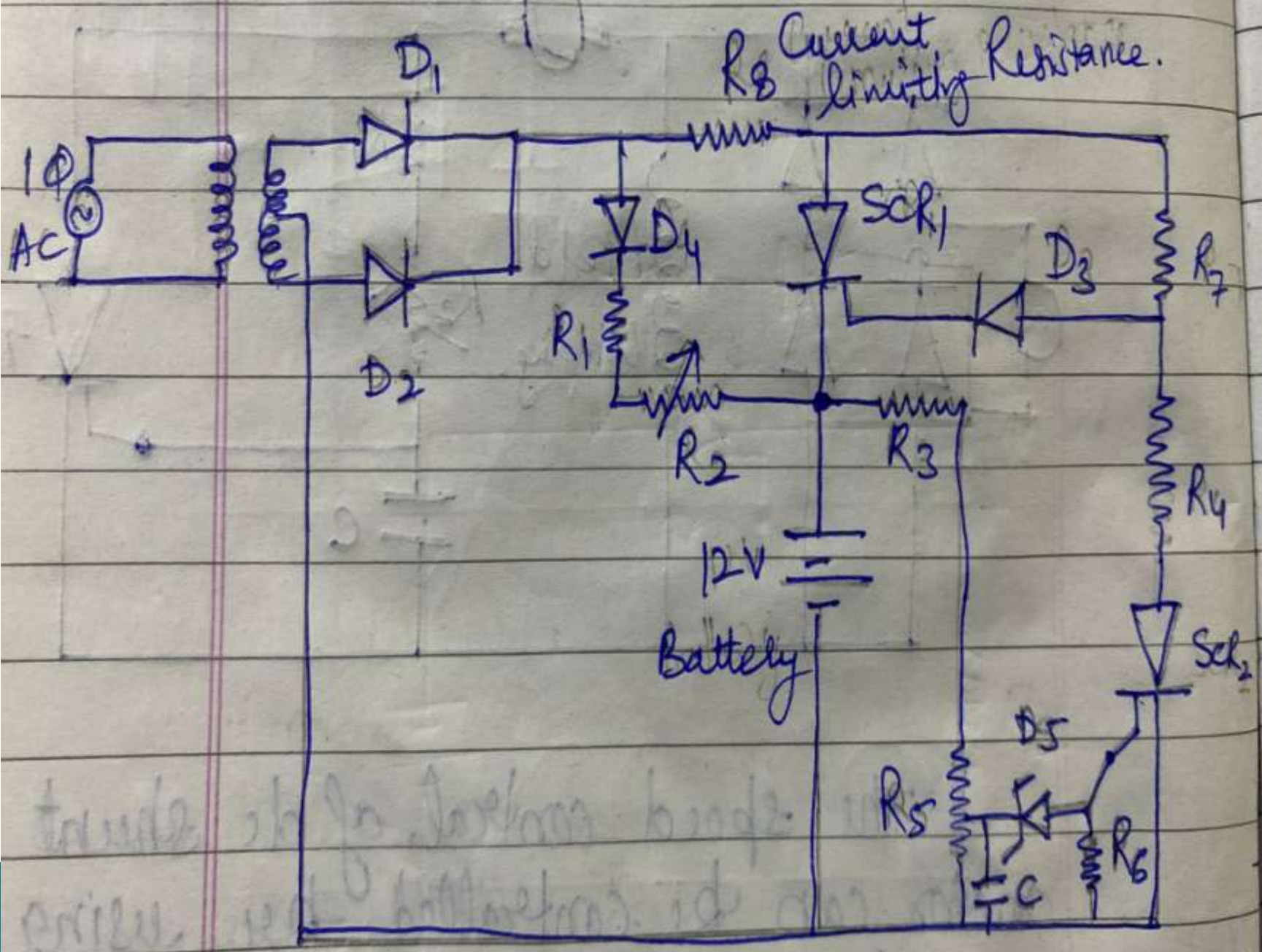

# Automatic Street Light



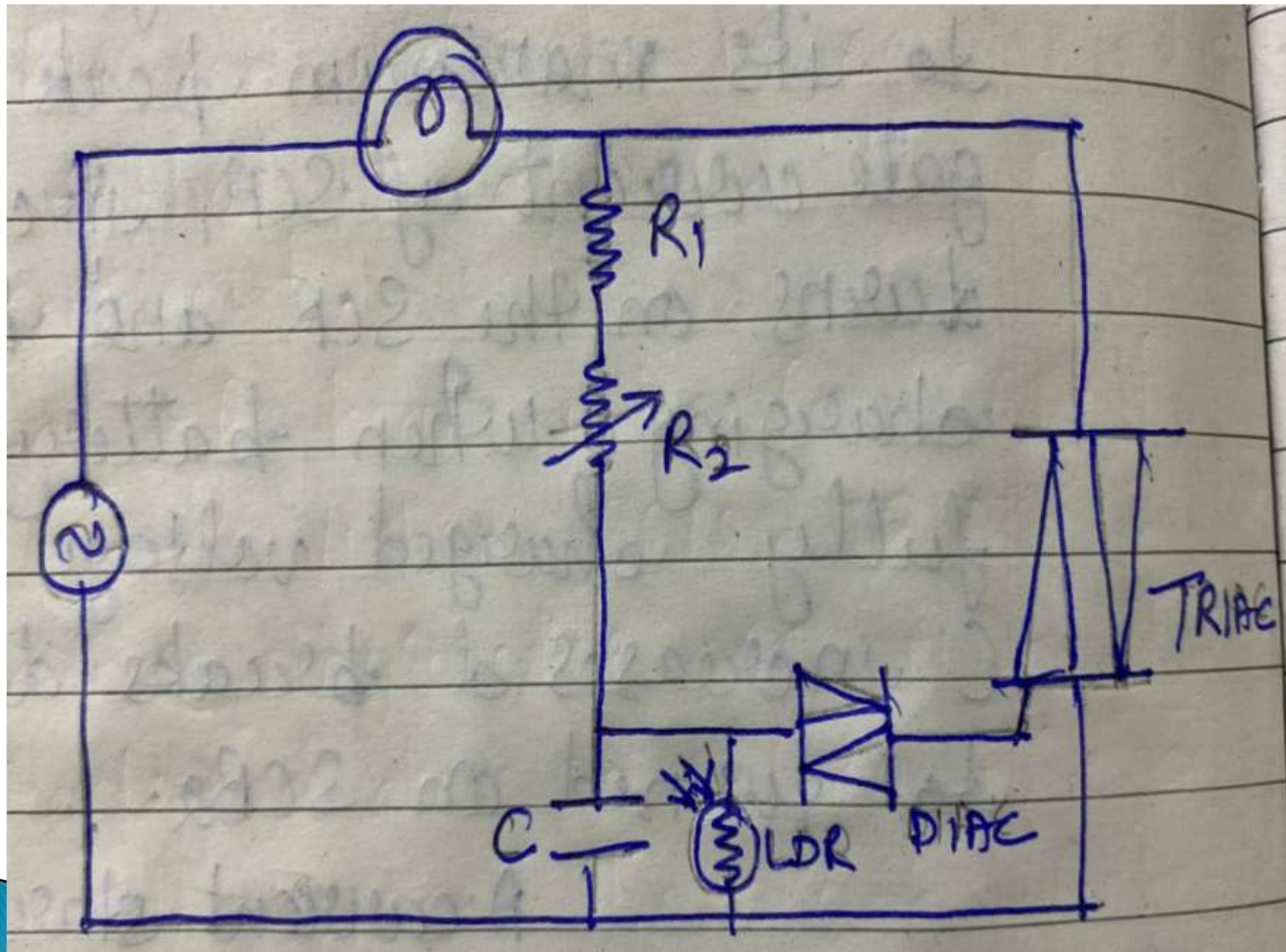


# SCR Protection







# dv/dt Protection (Snubber Ckt)

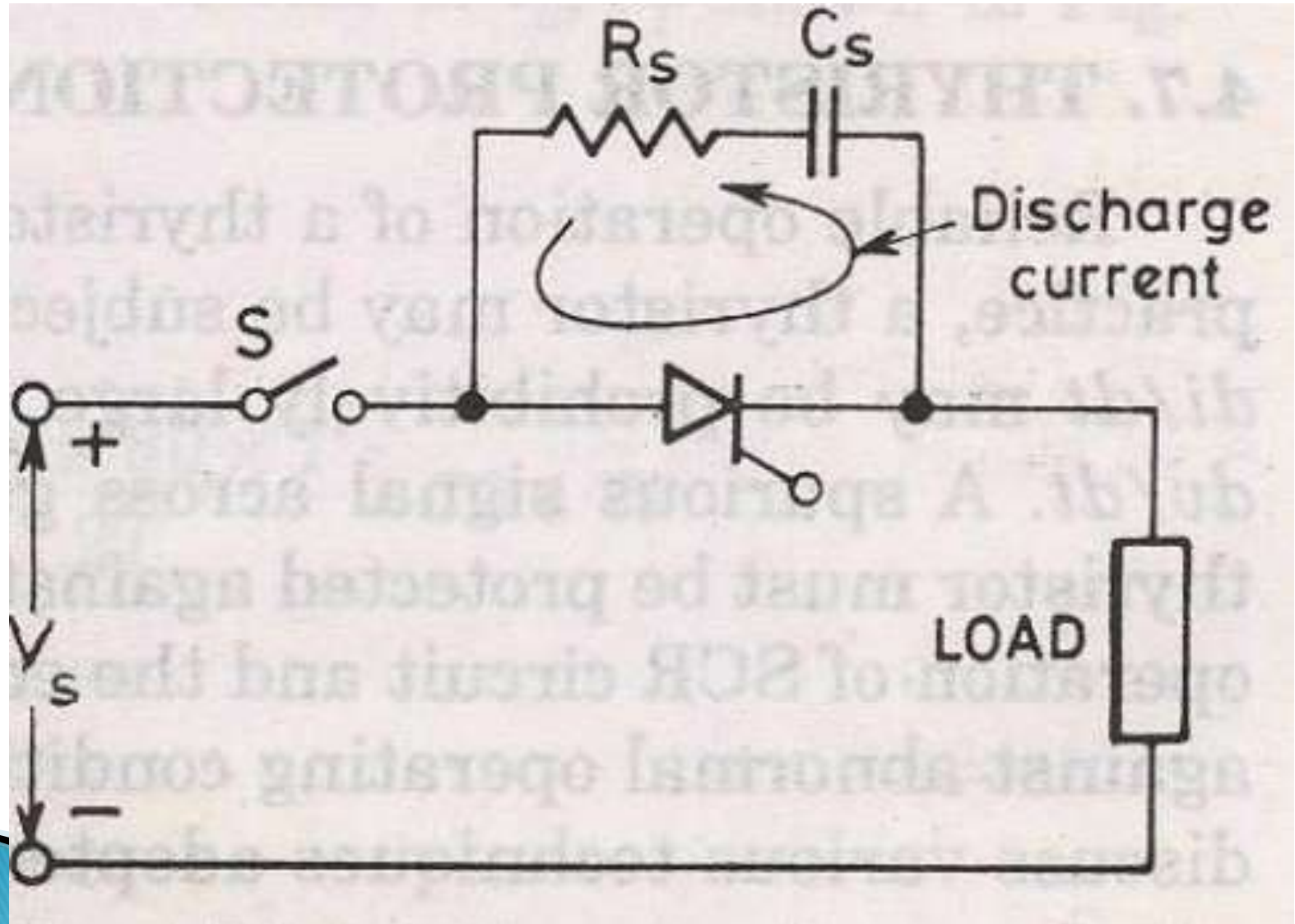

# di/dt Protection

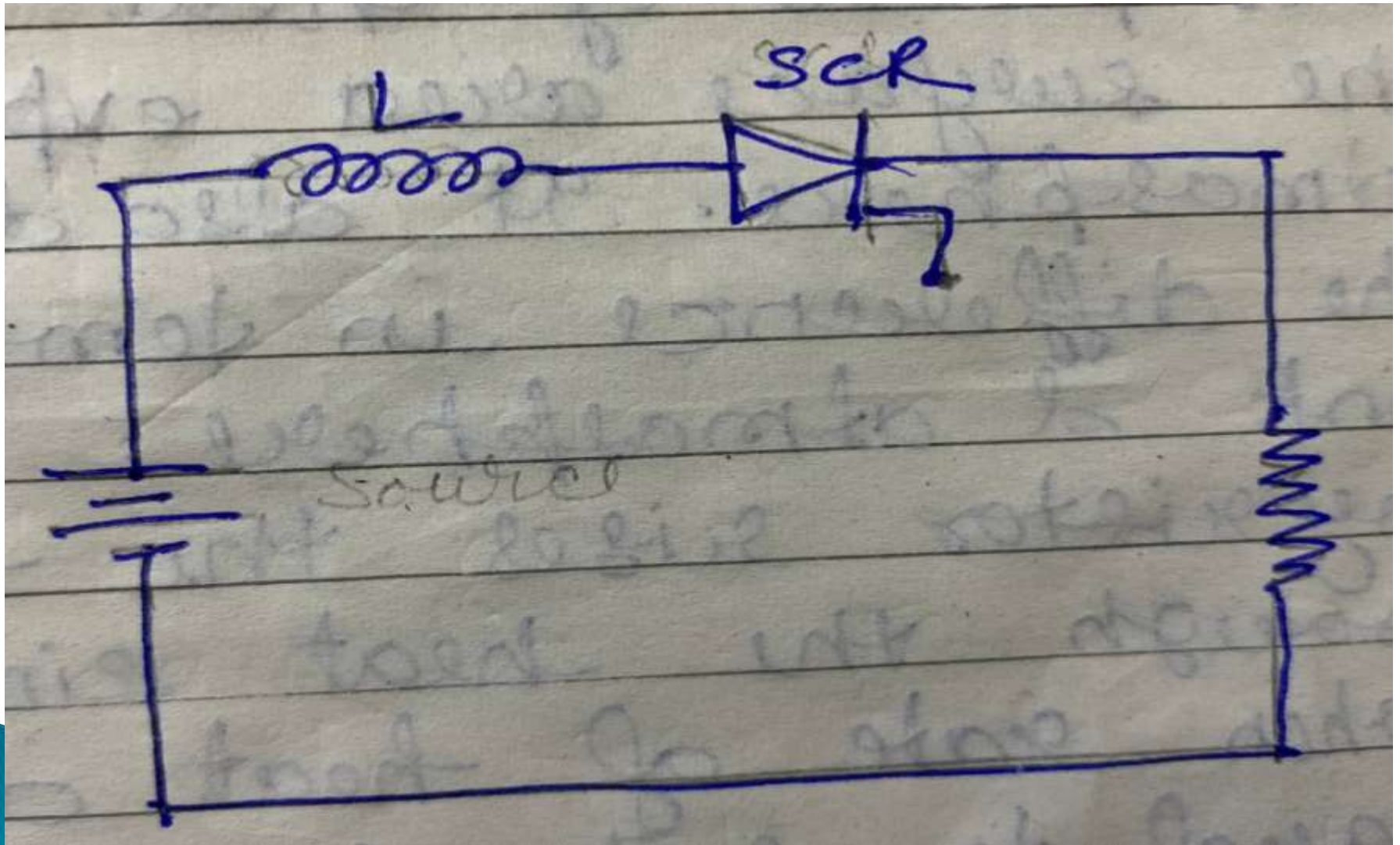


# di/dt Protection

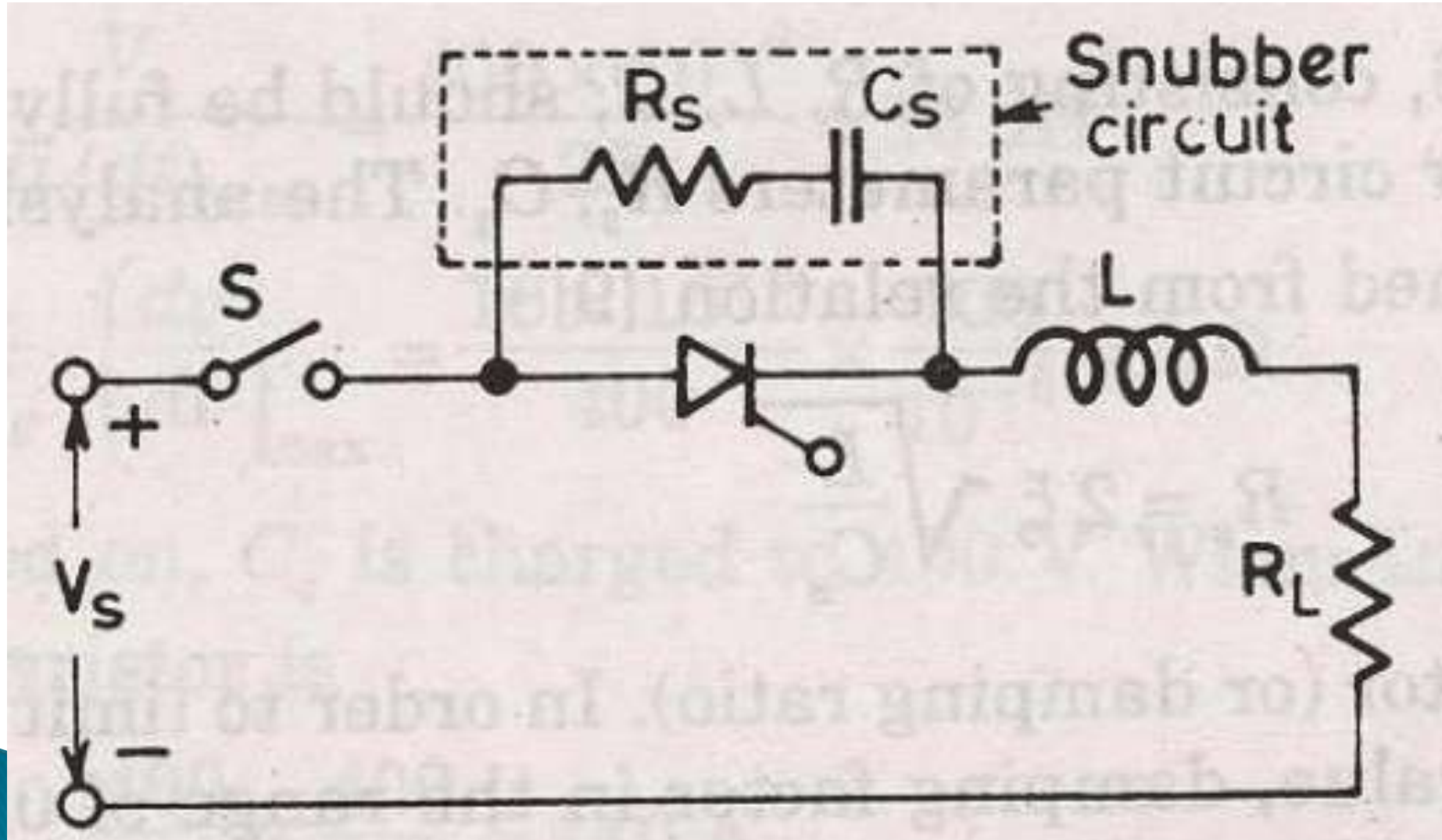



# Complete Protection Ckt.

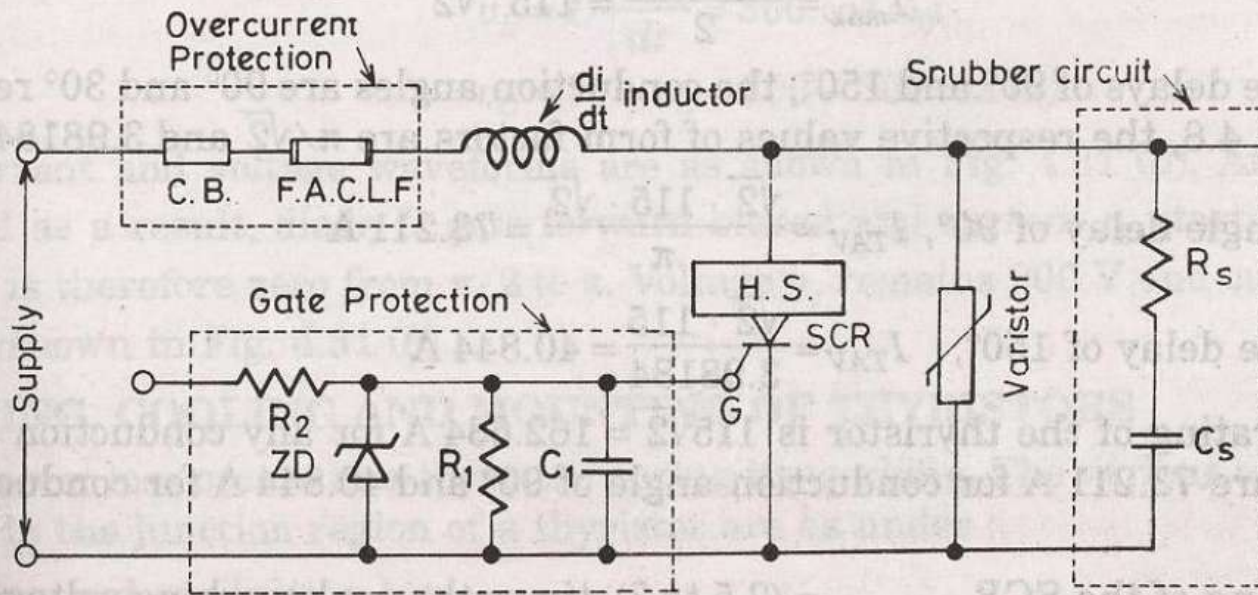

C.B.—Circuit breaker ; F.A.C.L.F.—Fast acting current limiting fuse ; H.S.—Heat sink ; ZD—Zener diode.





