

Industrial Electronics and control of Drives

Prepared By:
Ajit Singh, Lecturer

Inverters



Inverter

- ▶ A device that converts DC power in to AC power at desired output voltage and frequency.
 - ▶ These are used for adjustable speed ac drives, induction heating, aircraft power supplies, UPS, HVDC transmission lines etc.
- 

Classification

- ▶ **According to output:**
 - Single phase Inverter
 - Three phase Inverter
- ▶ **According to Input Source:**
 - Voltage Source Inverter
 - Current Source Inverter

Classification

- ▶ **According to Method of Commutation:**
 - Line Commutated Inverter
 - Forced Commutated Inverter
- ▶ **According to Connections of Commutating Components:**
 - Bridge Inverter
 - Series Inverter
 - Parallel Inverter


- ▶ **Voltage Source Inverters:** In these, DC source has small or negligible impedance.
- ▶ **Current Source Inverters:** In these, DC source has high impedance.

Bridge Inverters




Half Bridge Inverters




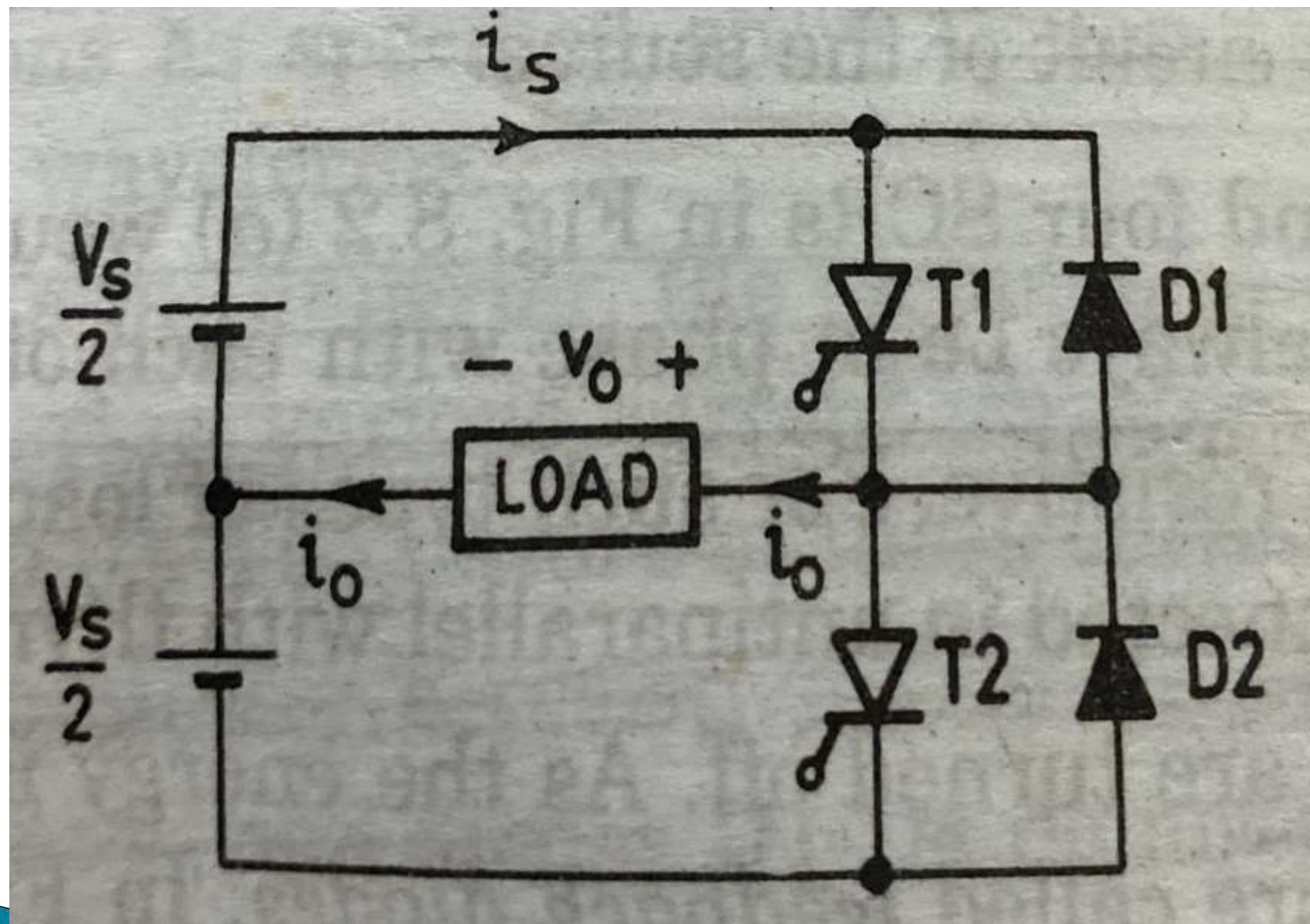

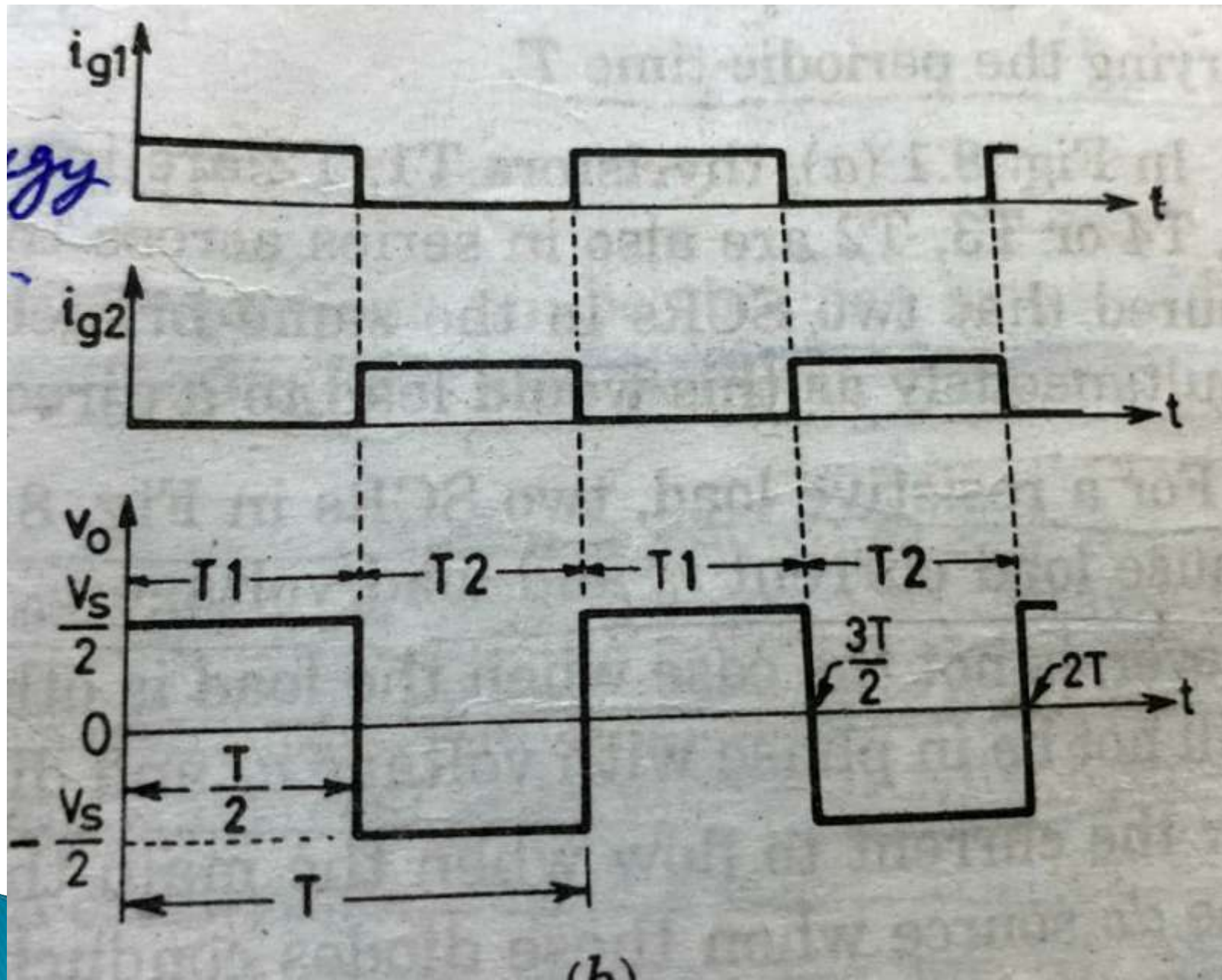- ▶ D1 and D2 are **Feedback diodes**, as they feed the stored energy back to source.
- ▶ Main drawback is that 3 wire DC supply is required.



Full Bridge Inverters

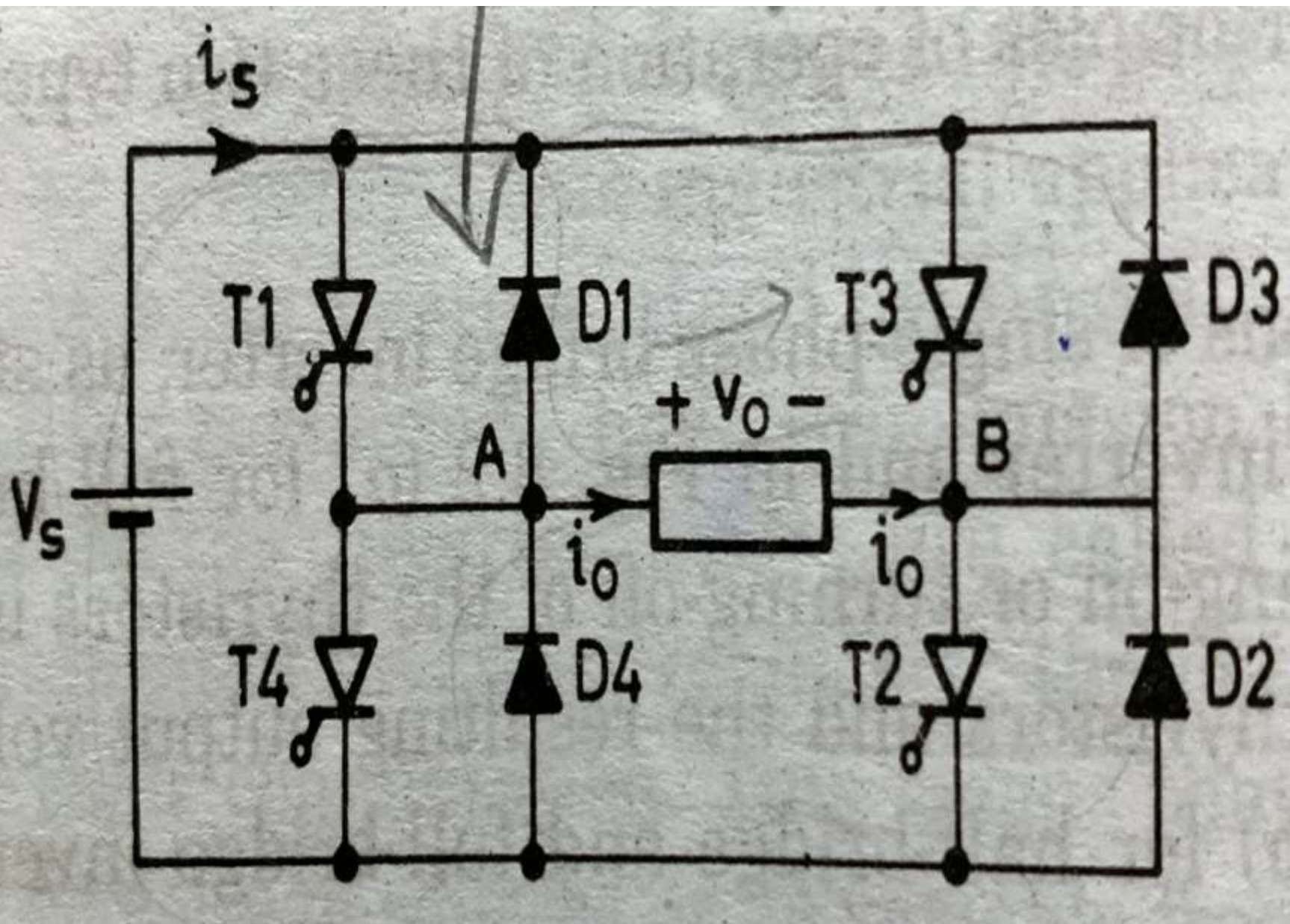


i_{g1}, i_{g2}




i_{g3}, i_{g4}



v_o

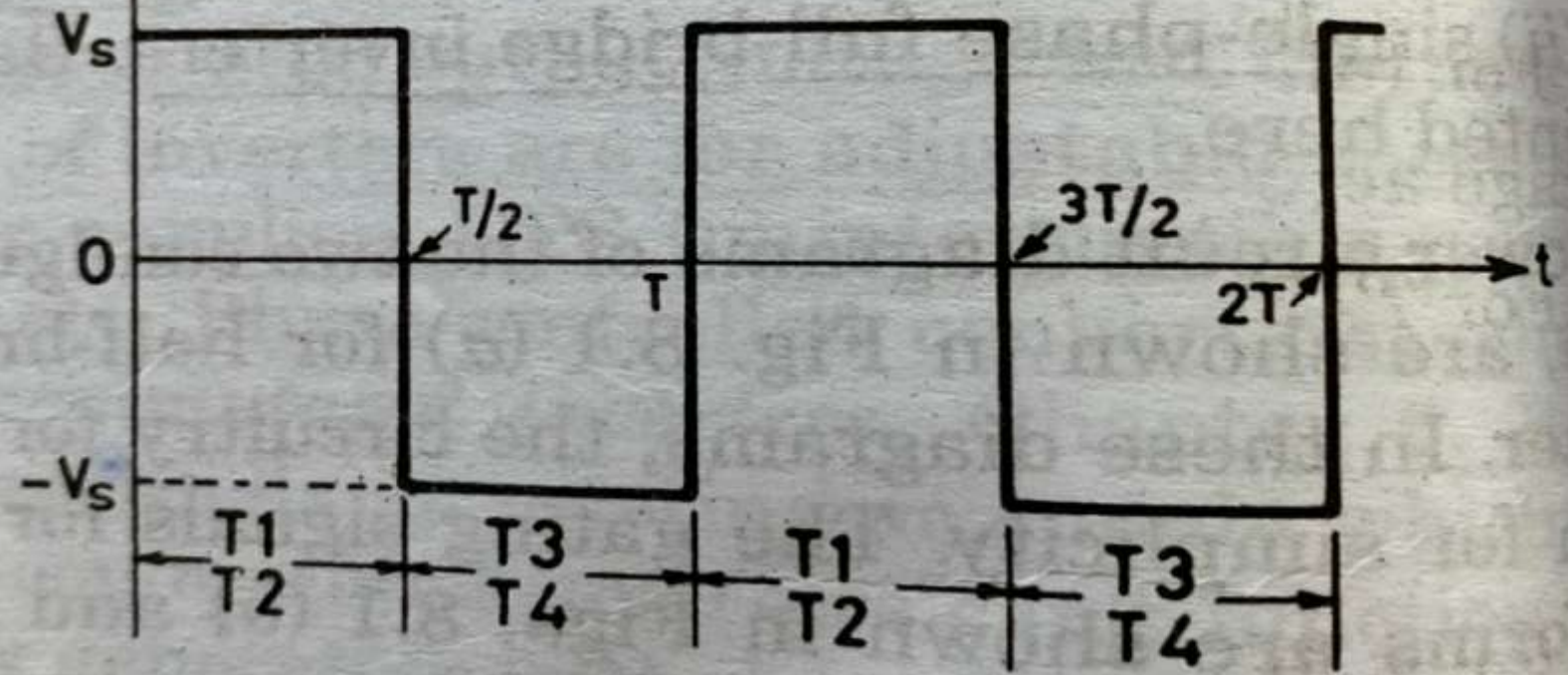


Series Inverter

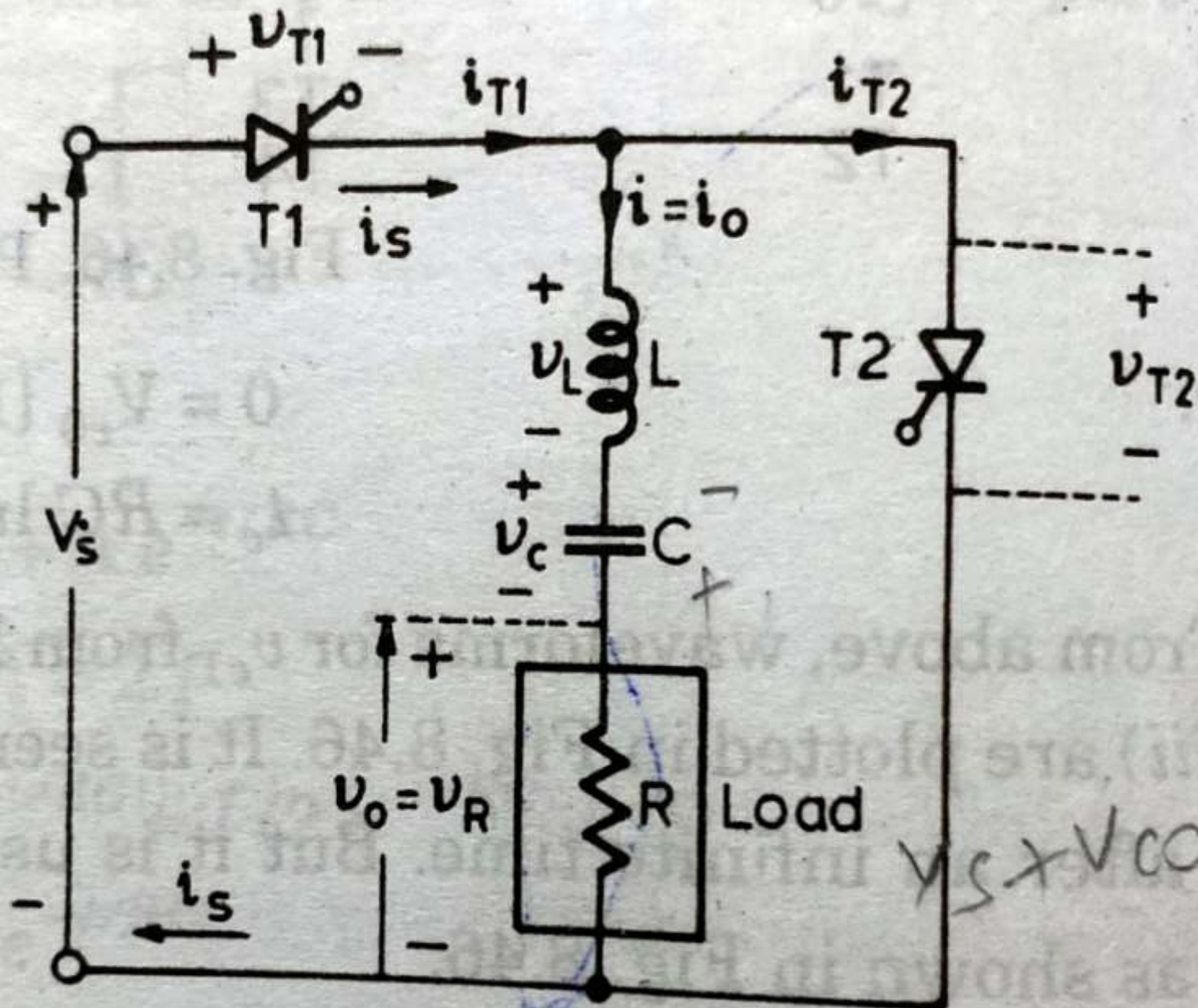



- ▶ Inverters in which commutating components are permanently connected in series with the load are called series inverters.
 - ▶ The value of R , L and C is so chosen that the series RLC circuit forms an underdamped circuit.
 - ▶ On turning on of T_1 , current I starts building up in RLC circuit.
- 

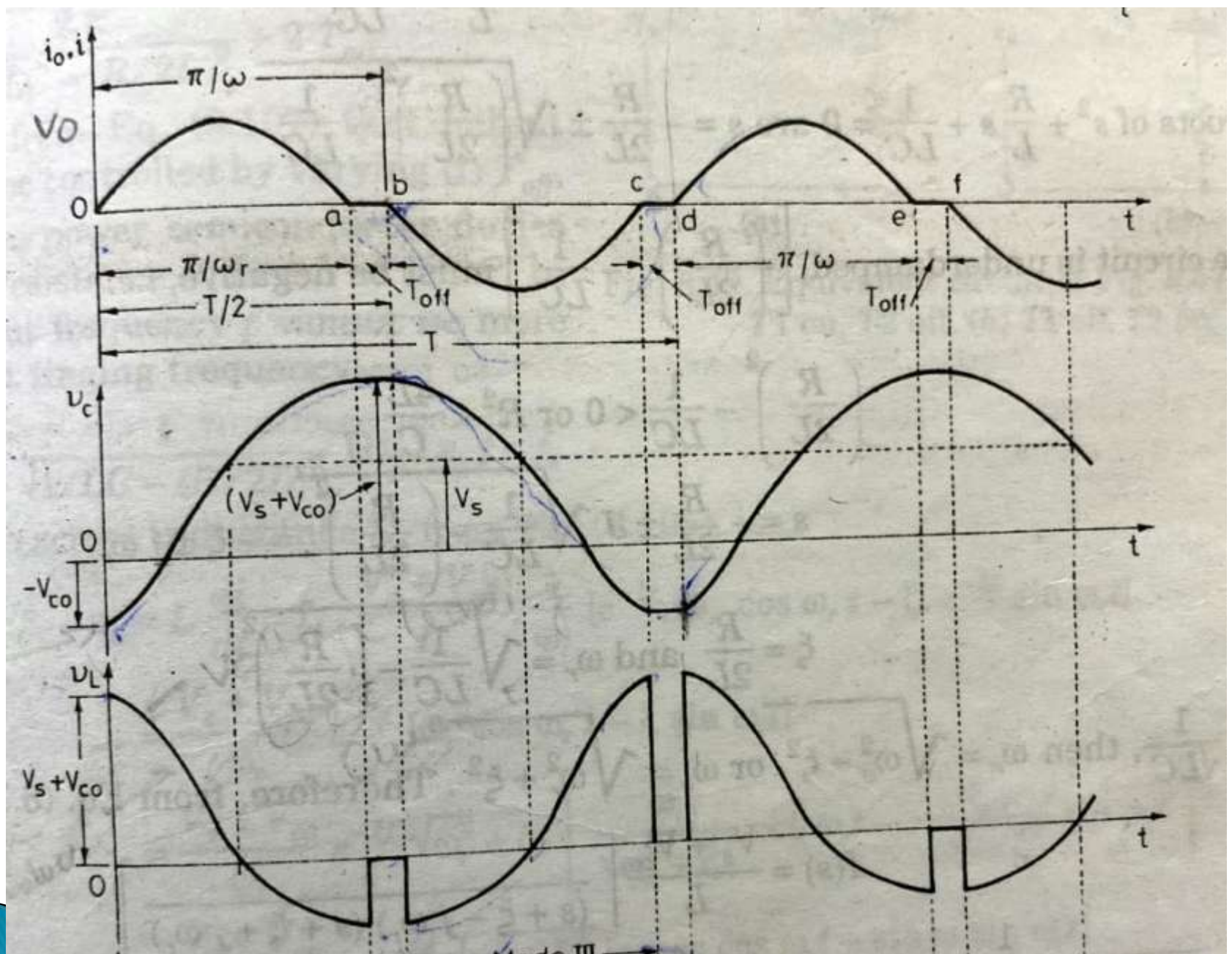- ▶ As the circuit is underdamped, current decays to zero and tends to reverse.
 - ▶ SCR T_1 turns off.
 - ▶ SCR T_2 is turned ON.
 - ▶ Capacitor begins to discharge and load current is reversed.
 - ▶ Load current decays to zero, after some time.
- 




Parallel Inverter

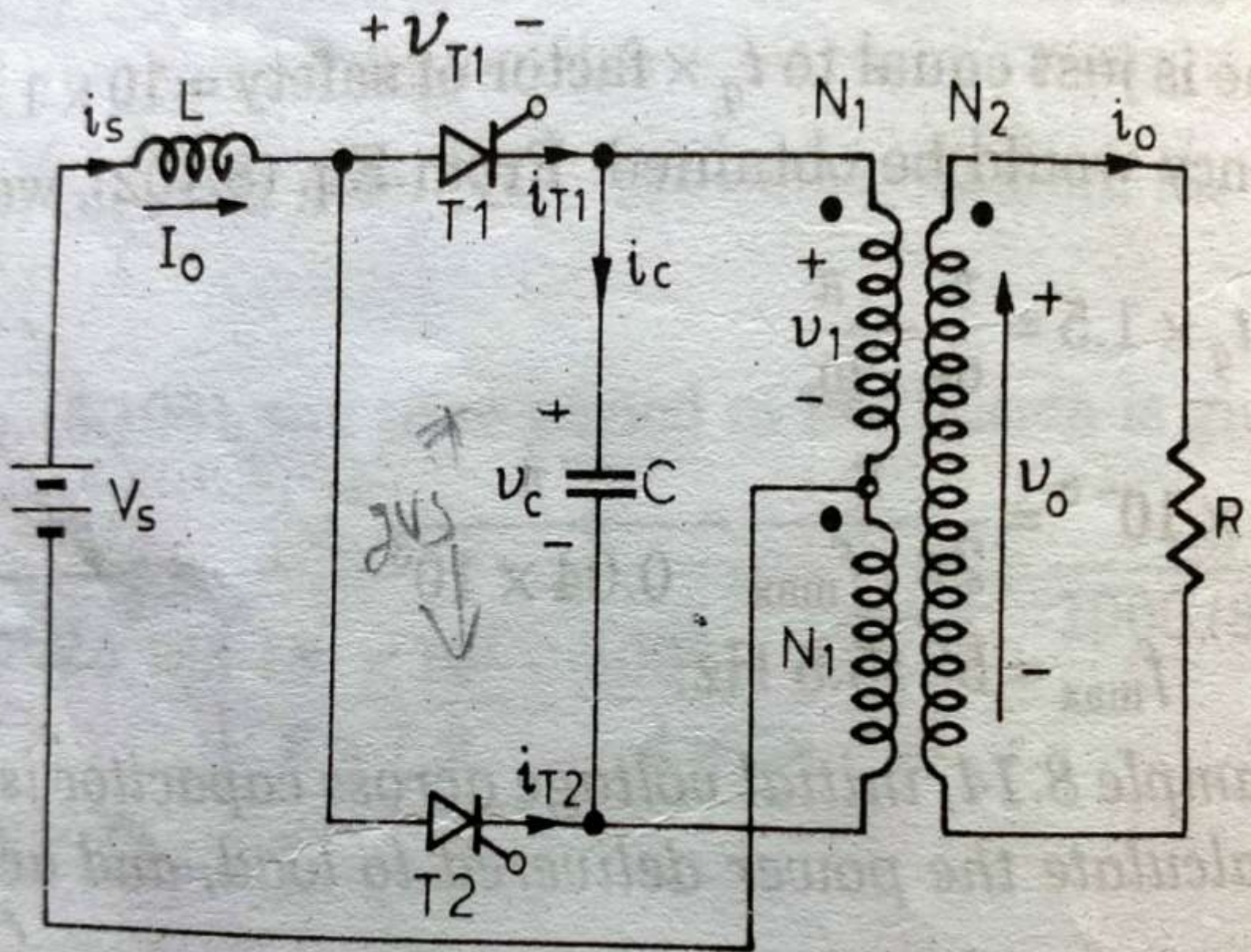

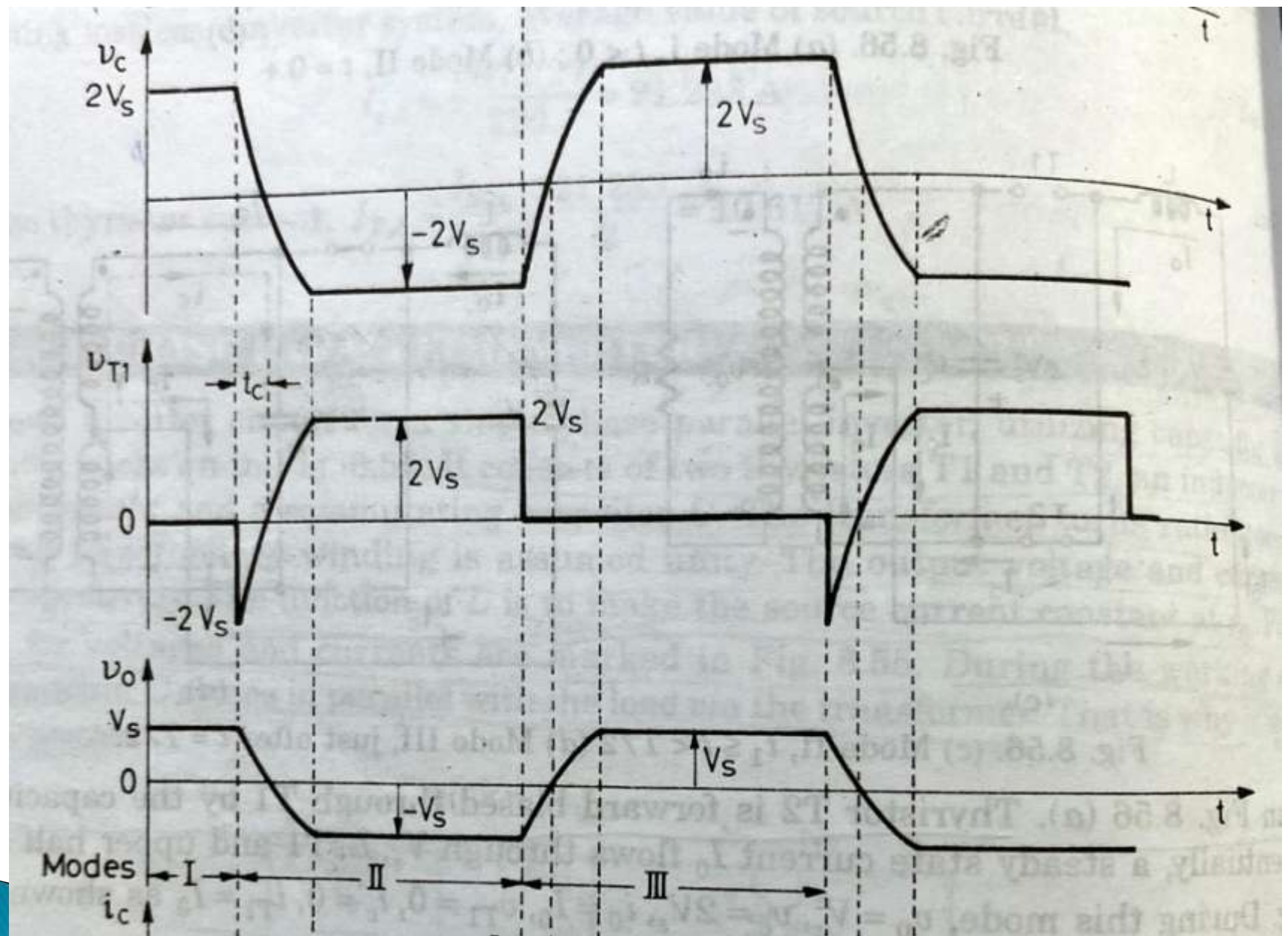

Current Source Inverter

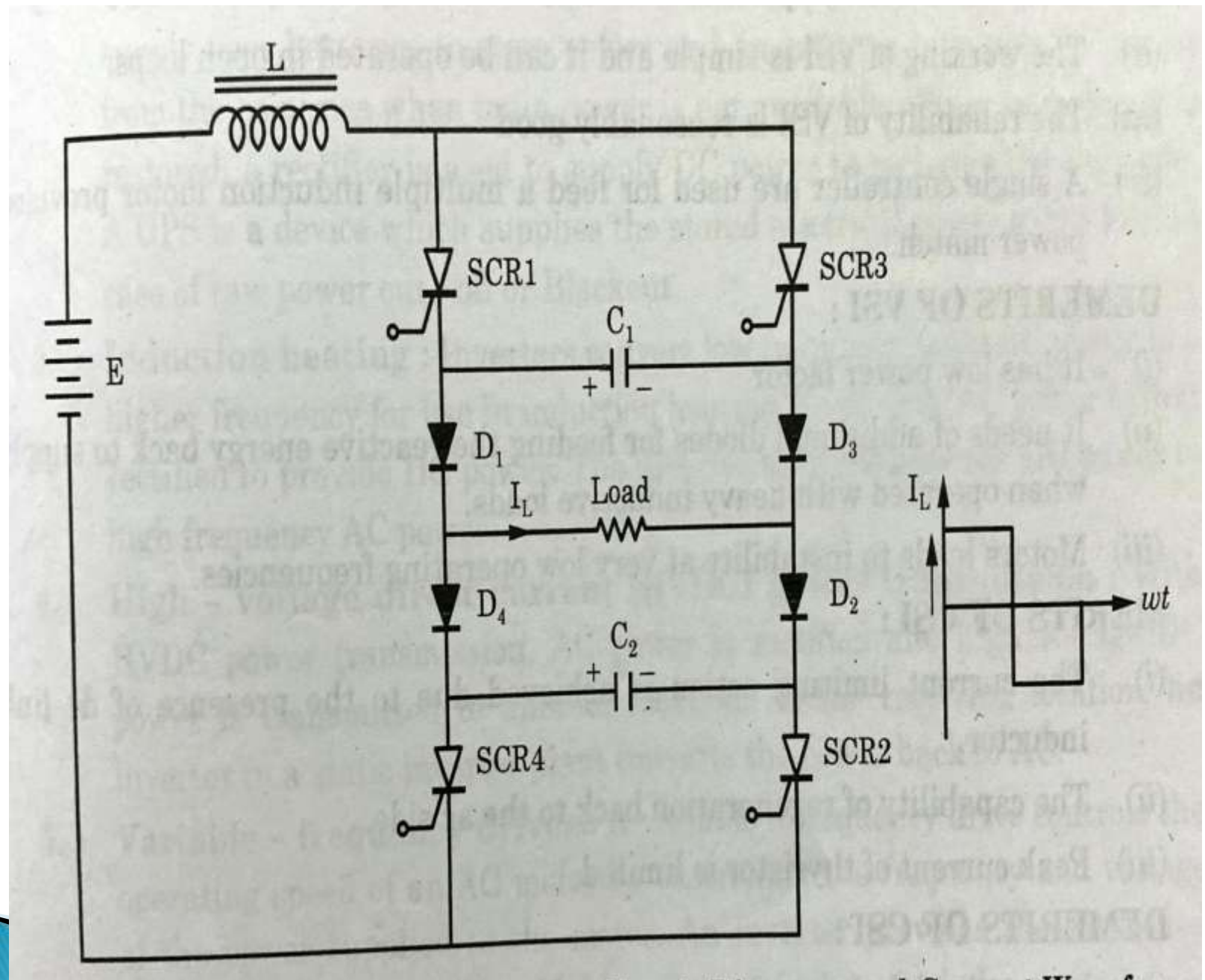



Choppers




Chopper

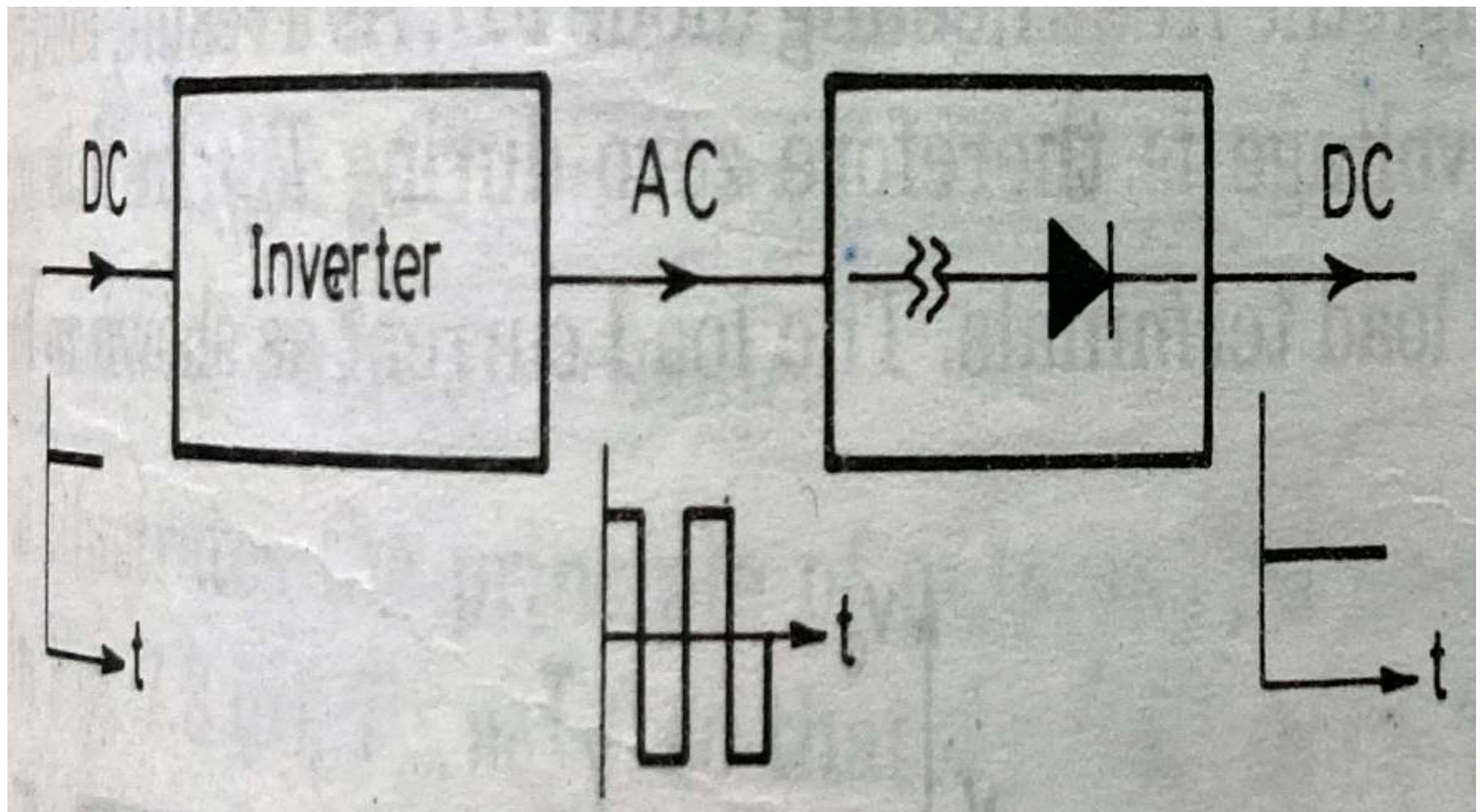
- ▶ Chopper is a static device that converts fixed DC input voltage to a variable DC output voltage.
 - ▶ Chopper may be thought as a DC equivalent of an AC transformer.
 - ▶ These involve one stage conversion.
 - ▶ These are more efficient.
- 



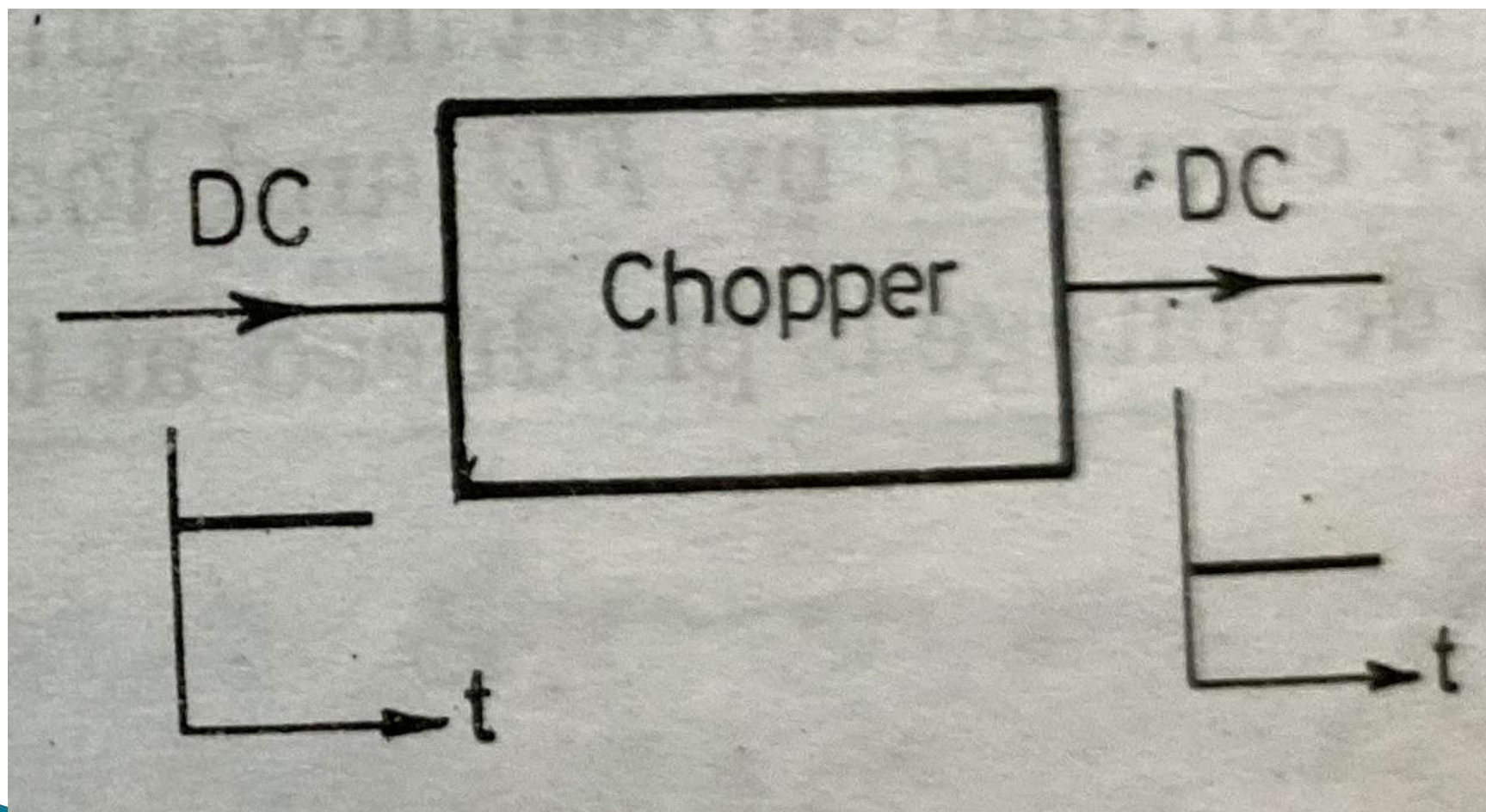

Principle of Operation

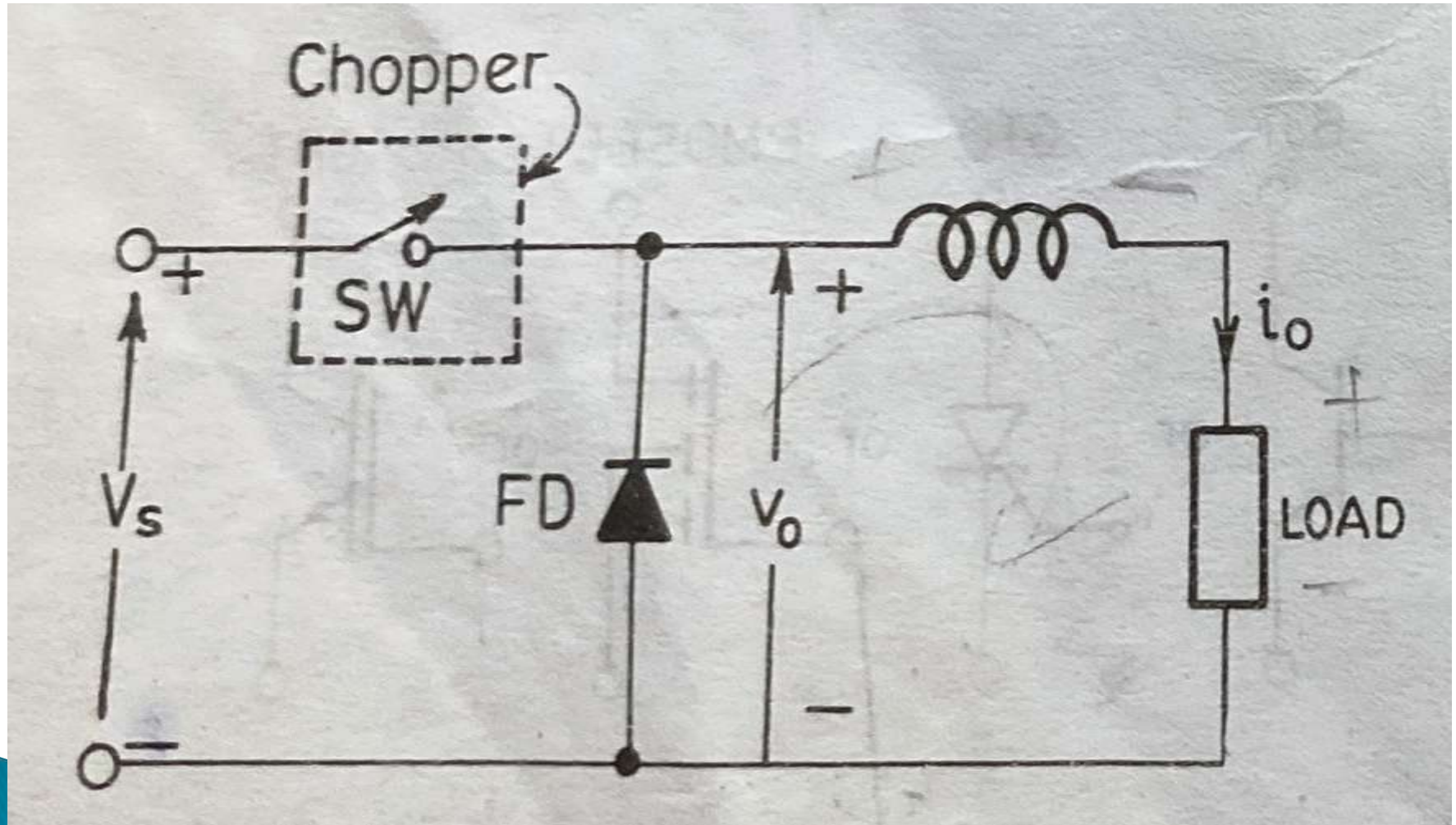

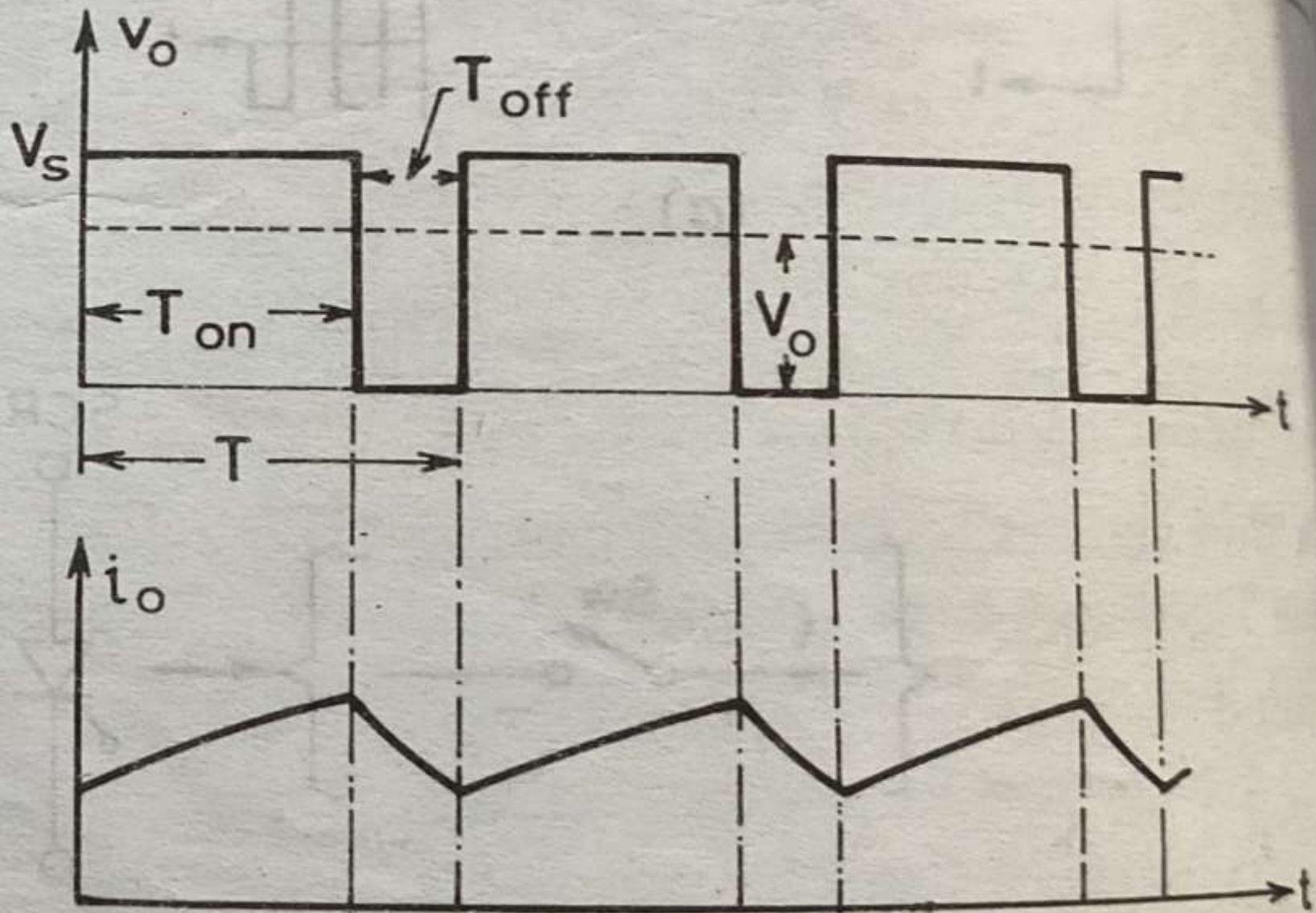

$$V_0 = \frac{T_{on}}{T_{on} + T_{off}} V_s = \frac{T_{on}}{T} V_s = \alpha V_s$$

T_{on} = on-time ; T_{off} = off-time

$T = T_{on} + T_{off}$ = chopping period


$$\alpha = \frac{T_{on}}{T} = \text{duty cycle}$$

$$V_0 = f \cdot T_{on} \cdot V_s$$


$$f = \frac{1}{T} = \text{chopping frequency}$$

Methods of Controlling Output Voltage

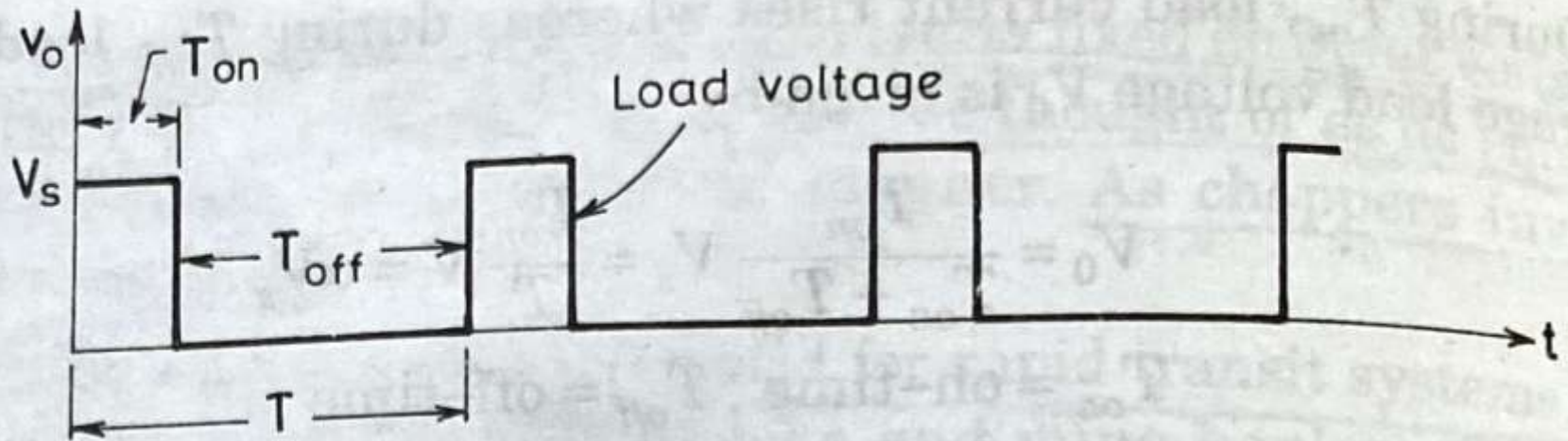- ▶ **Constant Frequency Control:**
 - On Time T_{on} is varied but chopping Frequency is kept constant.





(a)


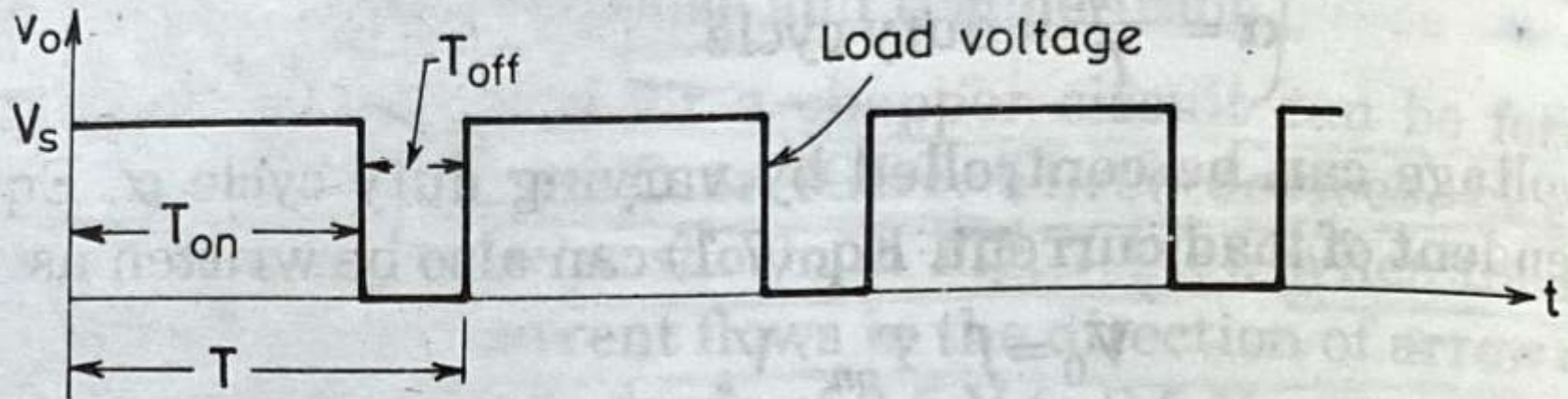


Methods of Controlling Output Voltage

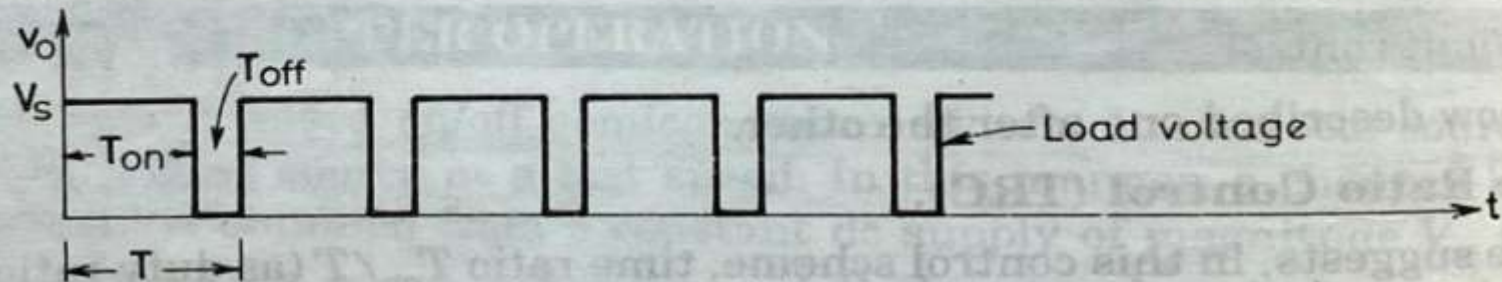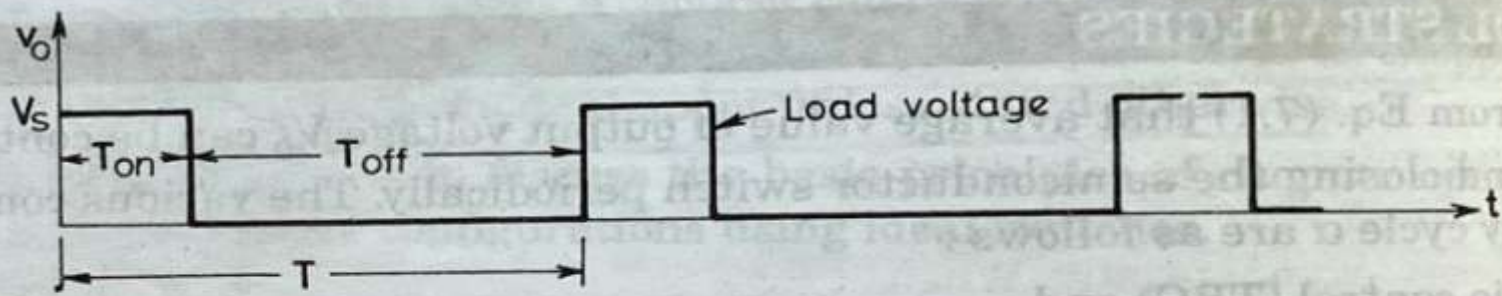
- ▶ **Variable Frequency Control:**
 - Either Time T_{on} or T_{off} is kept constant but chopping Frequency is varied.





(a)

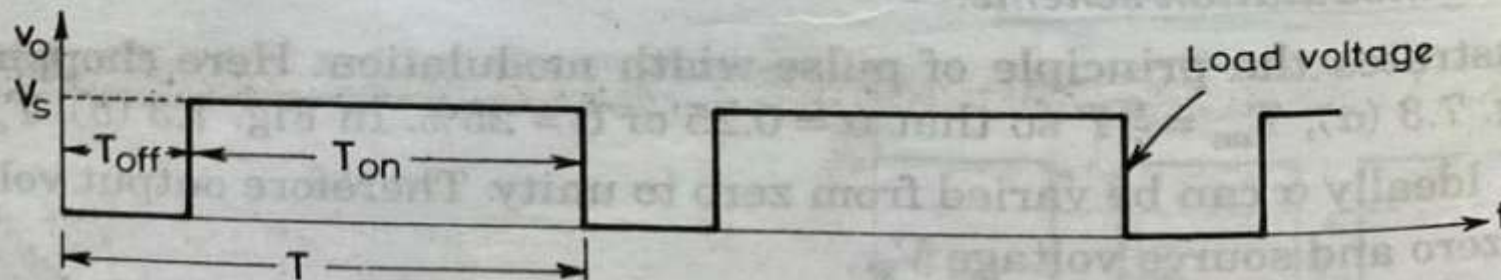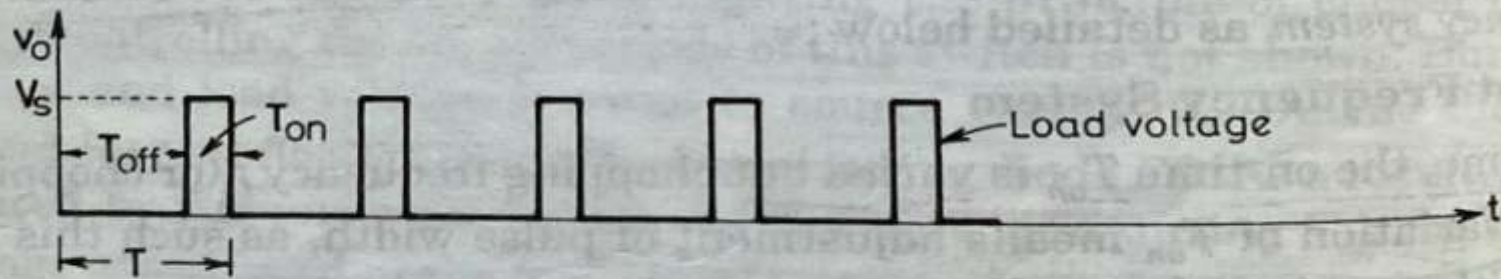


Step Up Chopper

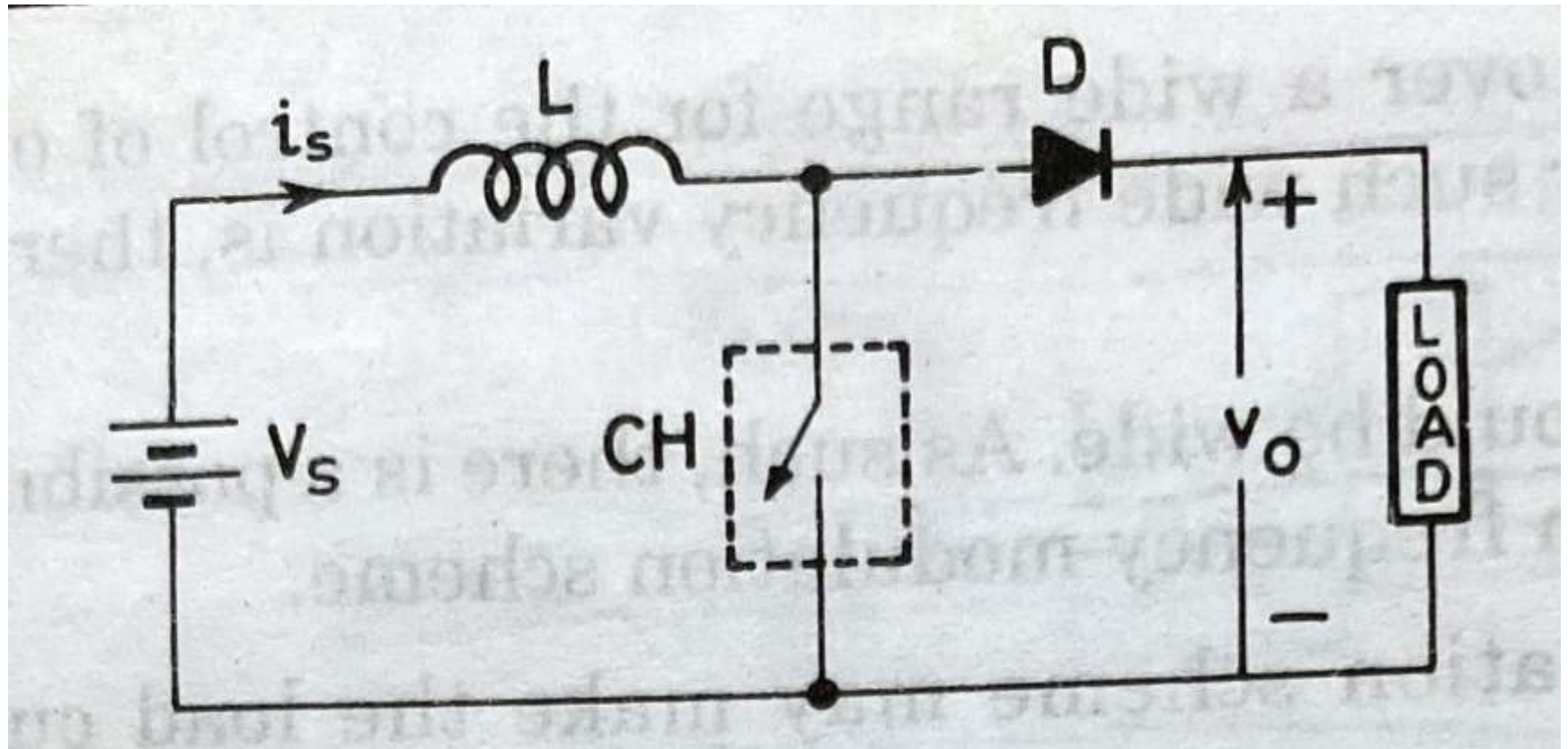


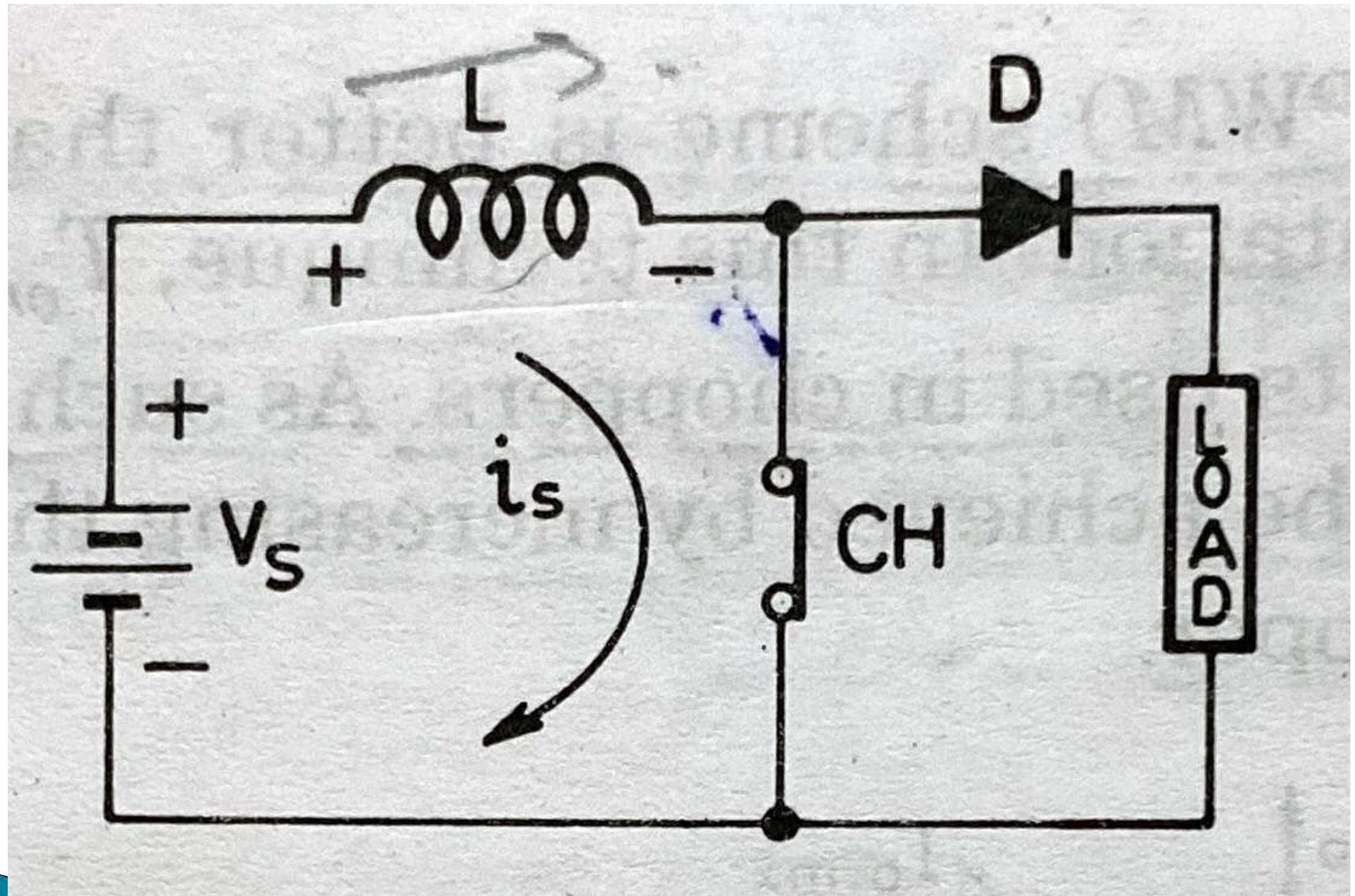


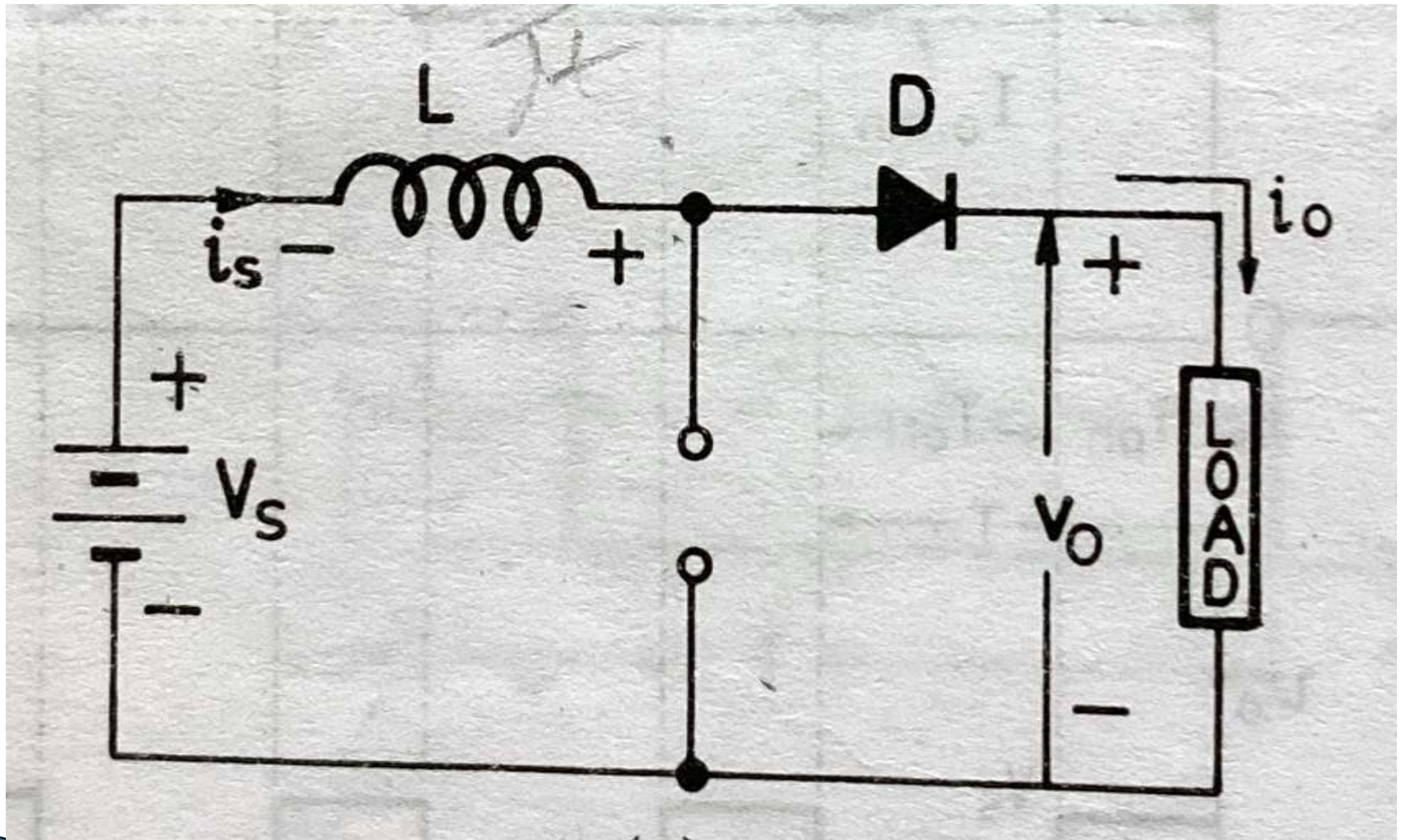



First Quadrant or Type A Chopper

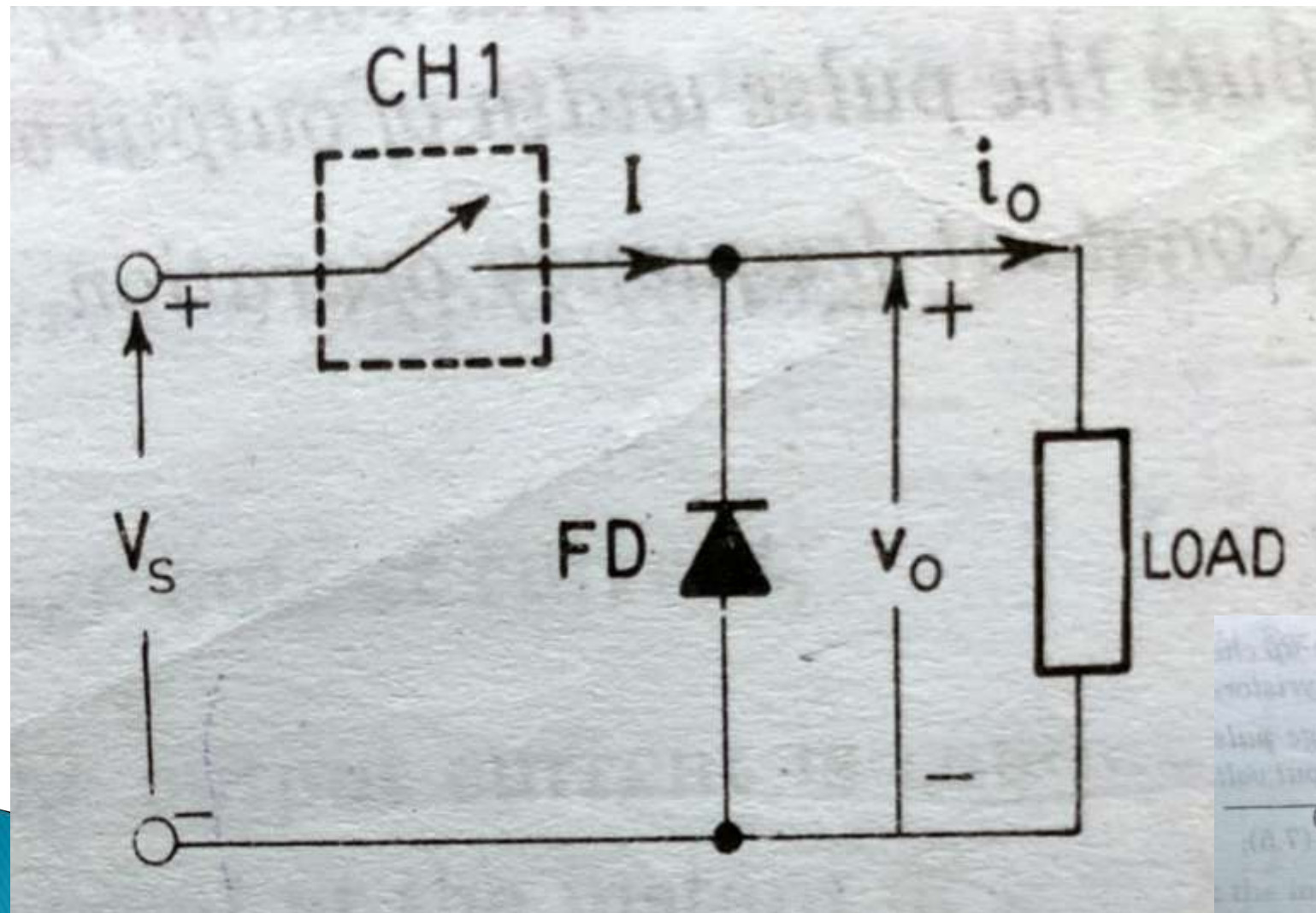



Second Quadrant or Type B Chopper

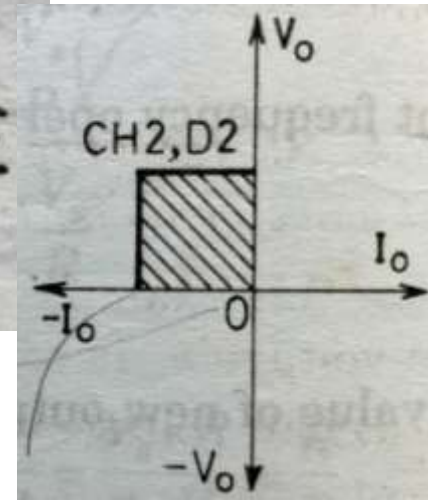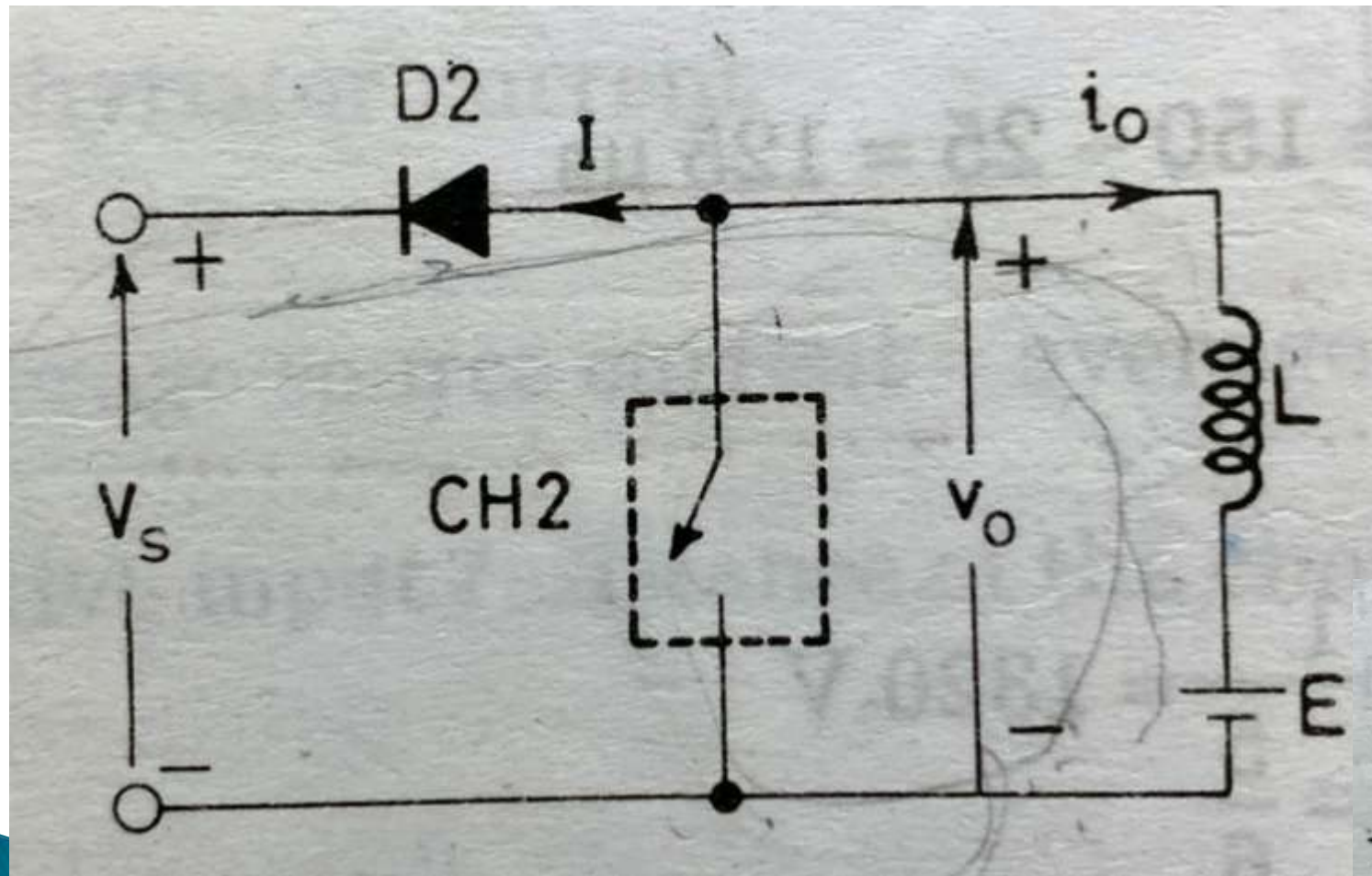


Type C Chopper

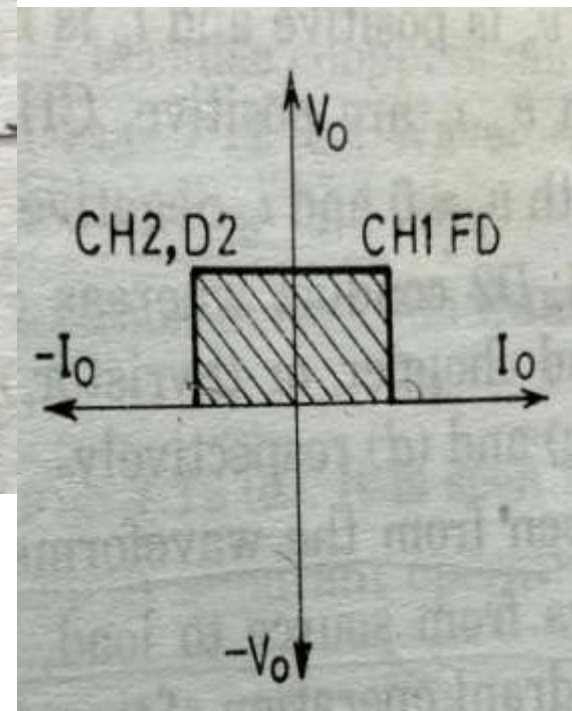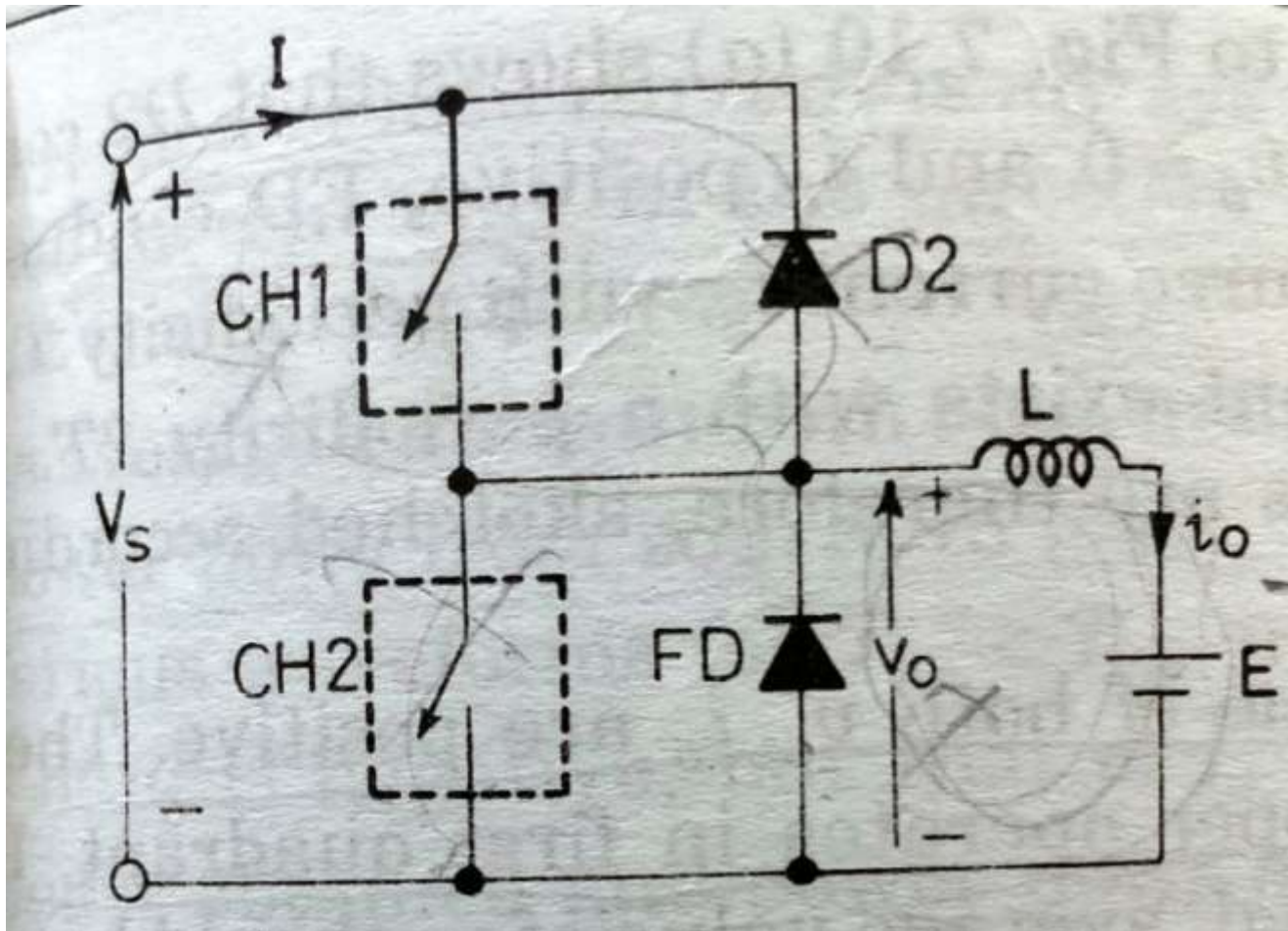


Type D Chopper

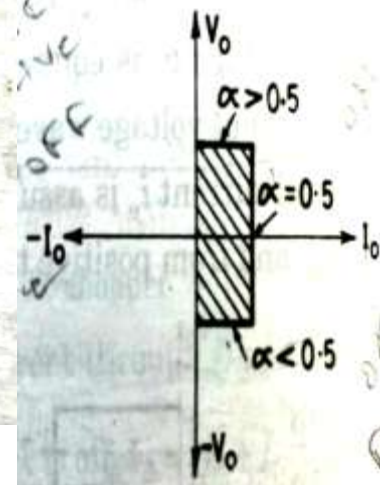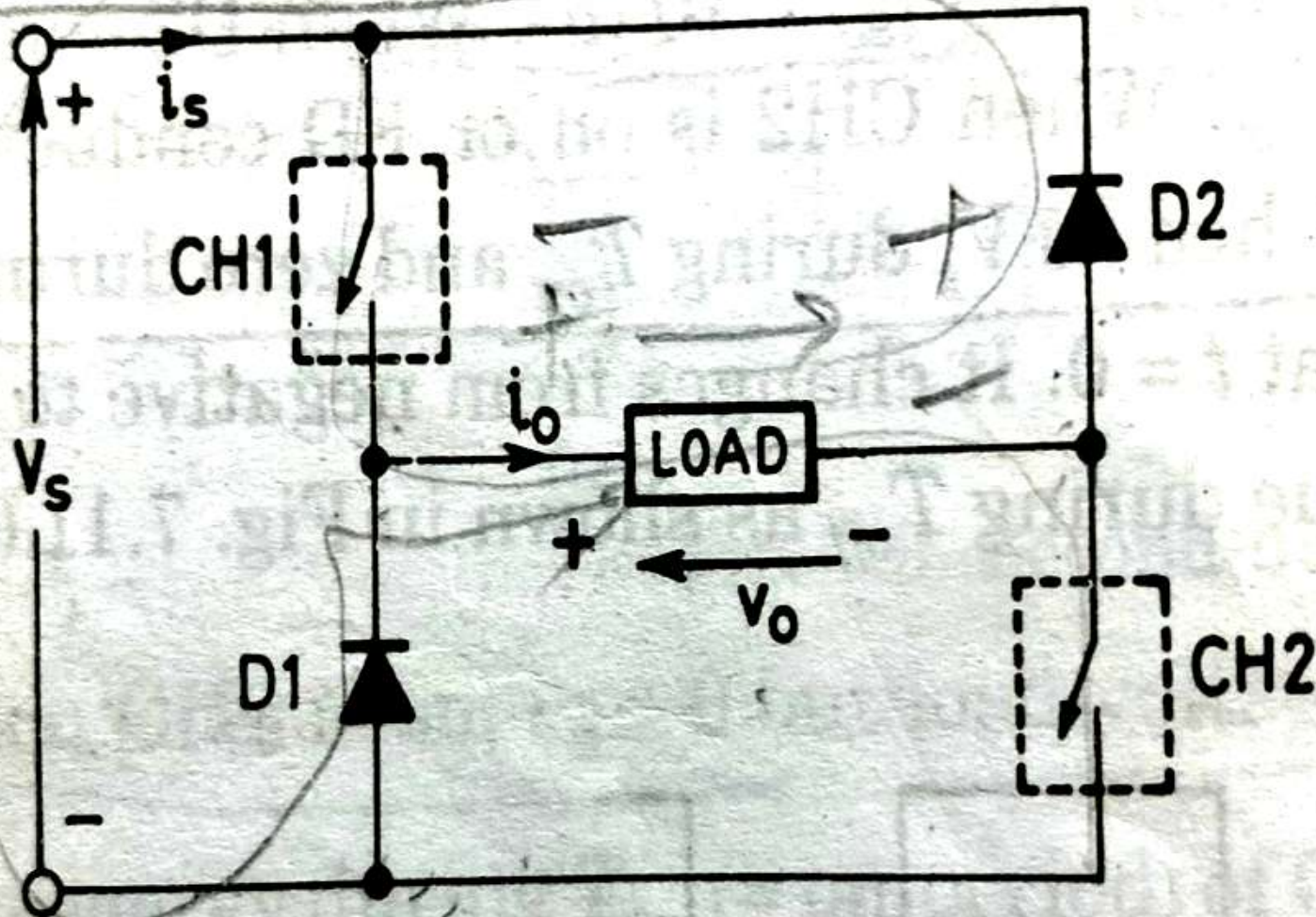


Four Quadrant or Type E Chopper

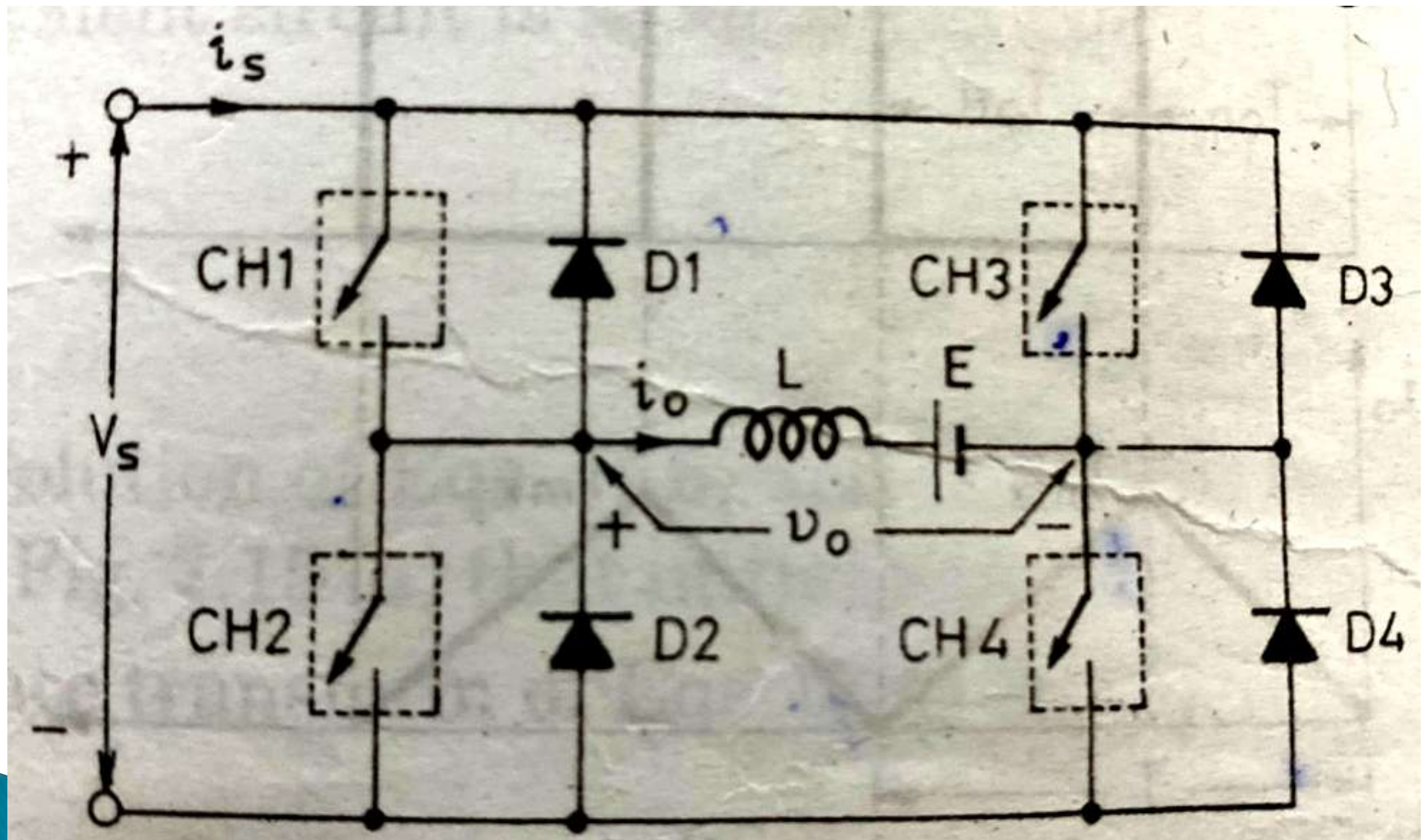

EMF E Reversed

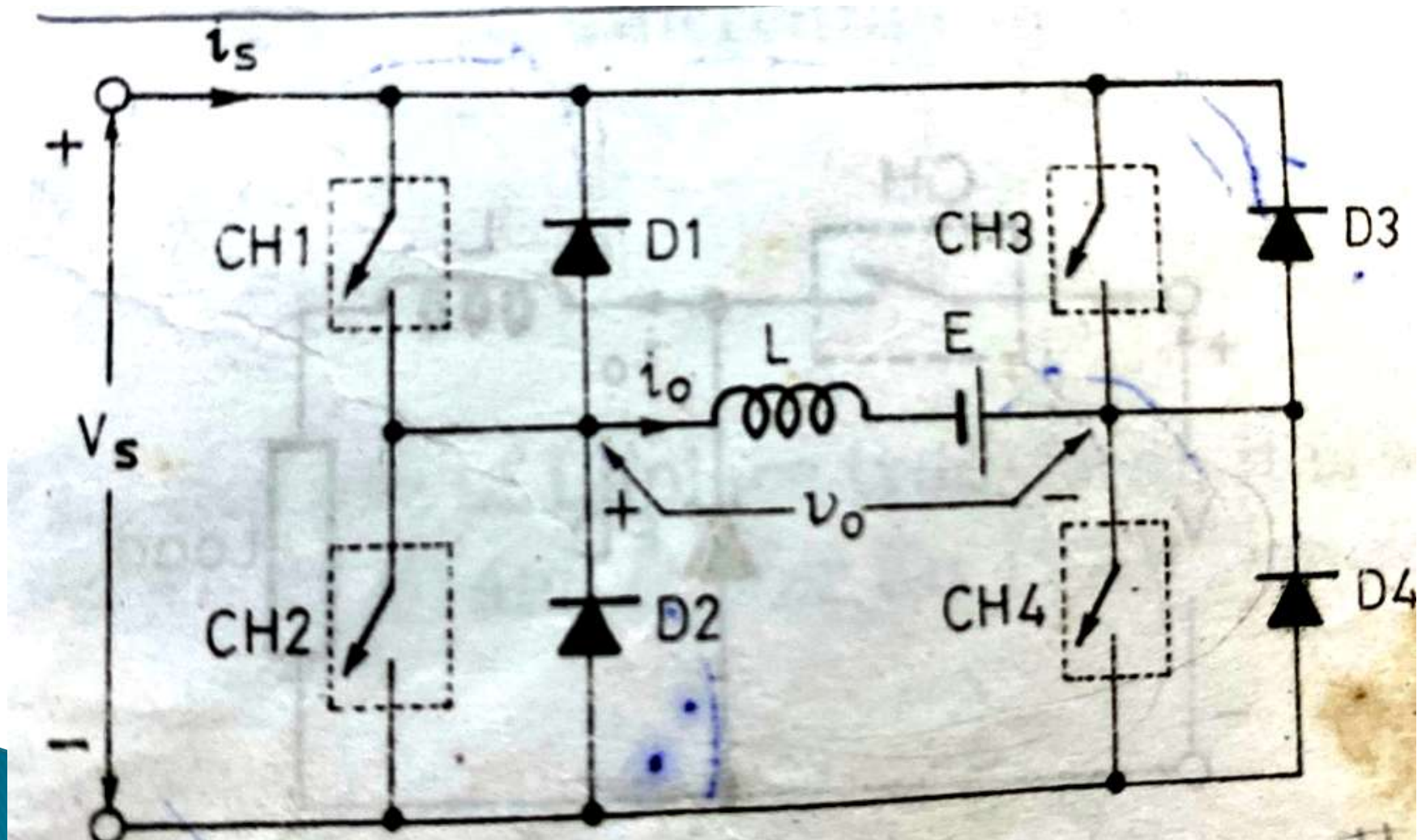


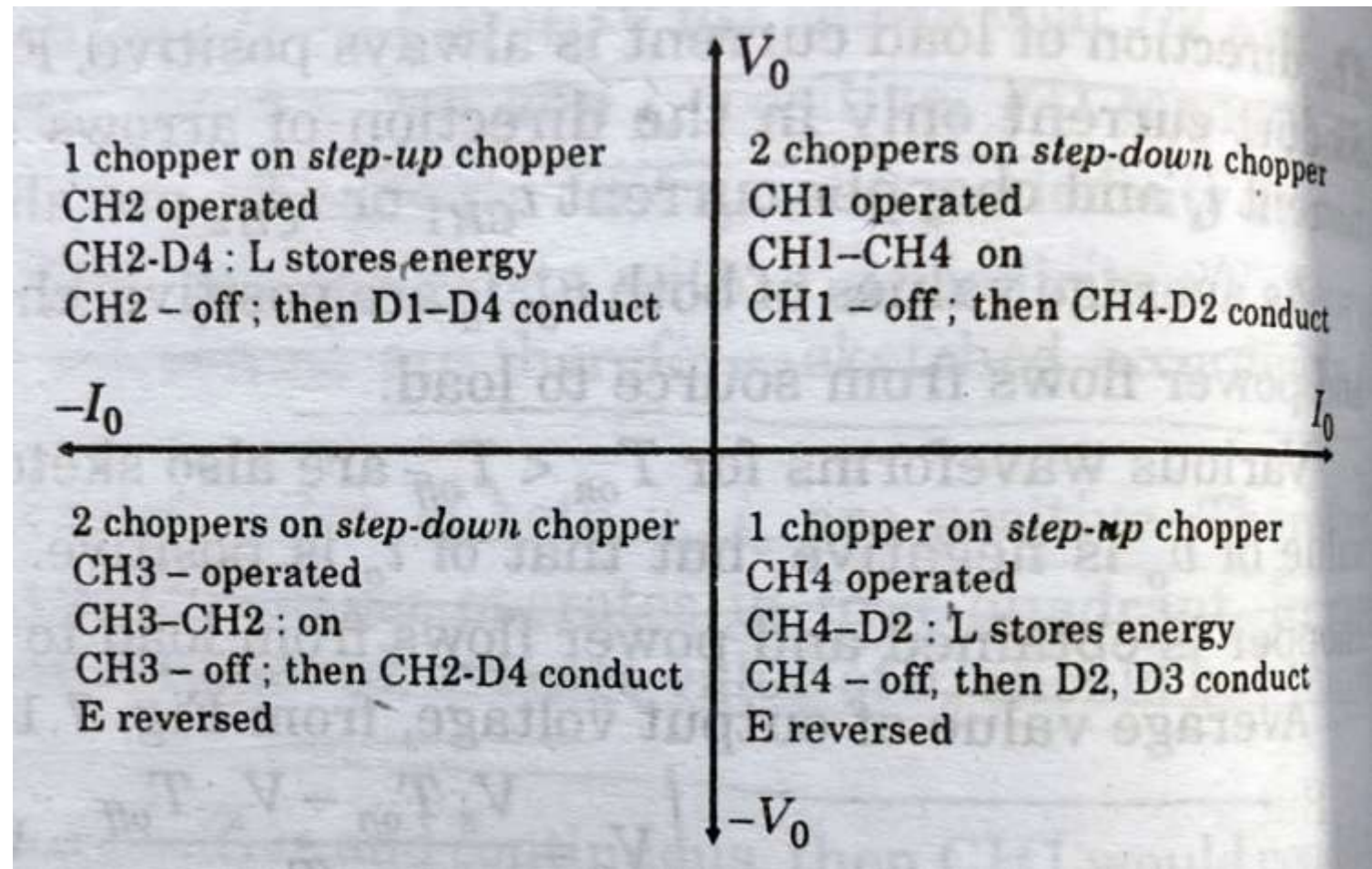



Dual Converters

Dual Converter

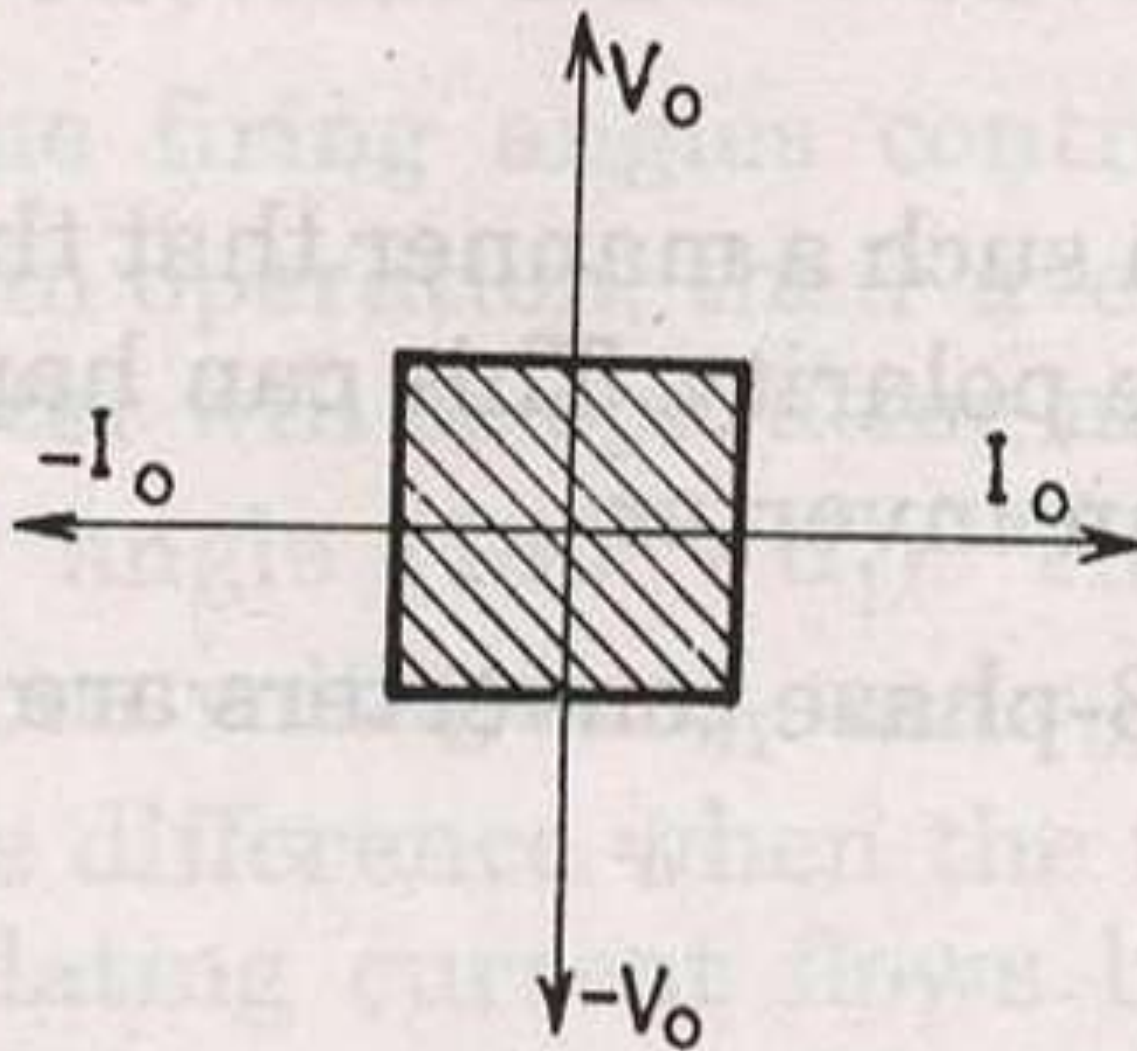- ▶ A Full converter can operate in Two quadrants.
 - ▶ If four Quadrant operation is required, without any mechanical changeover switch, two full converters can be connected back to back to load circuit.
 - ▶ Such an arrangement using two full converters in anti parallel and connected to the same dc load is called a Dual Converter.
- 



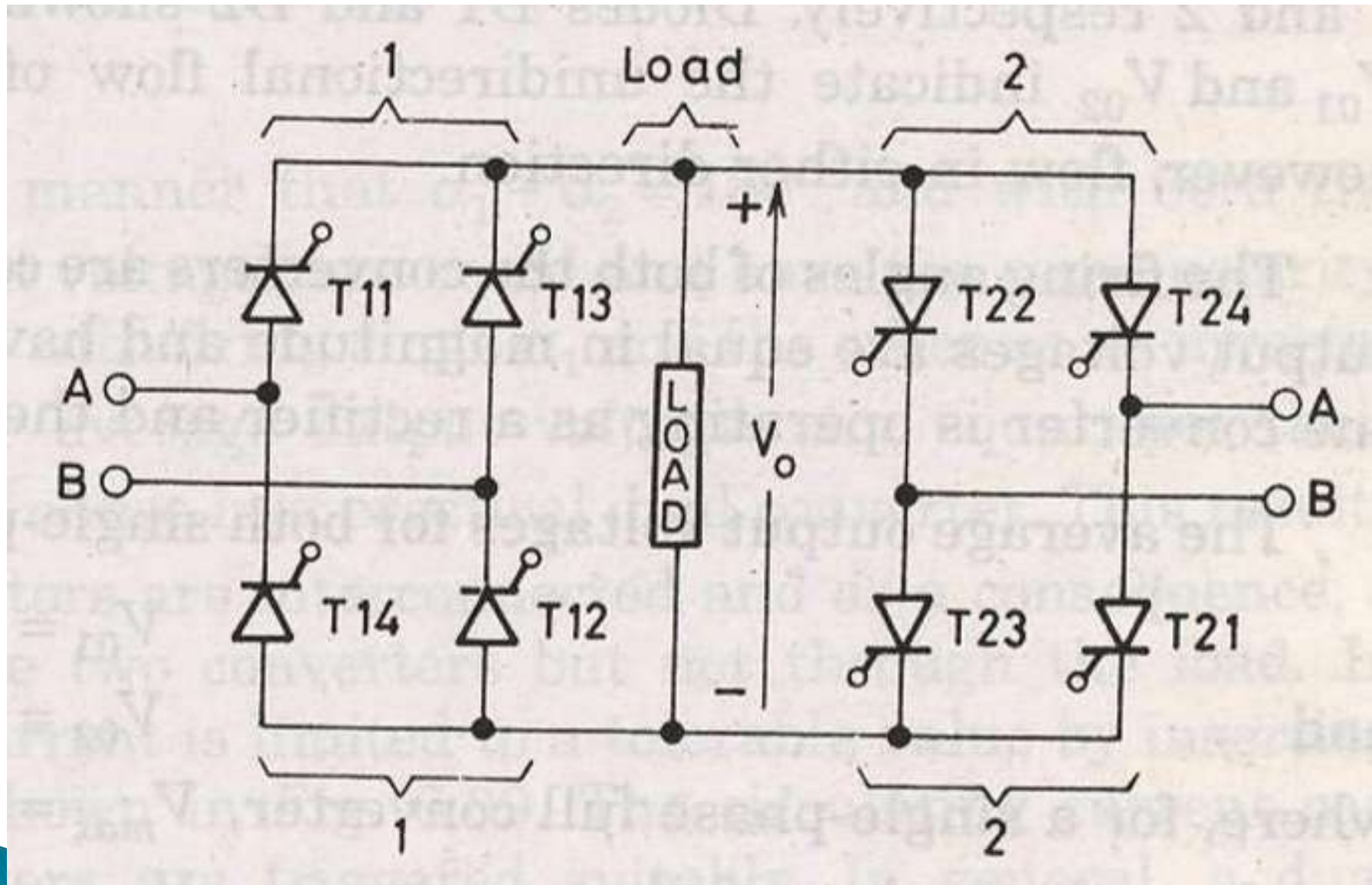

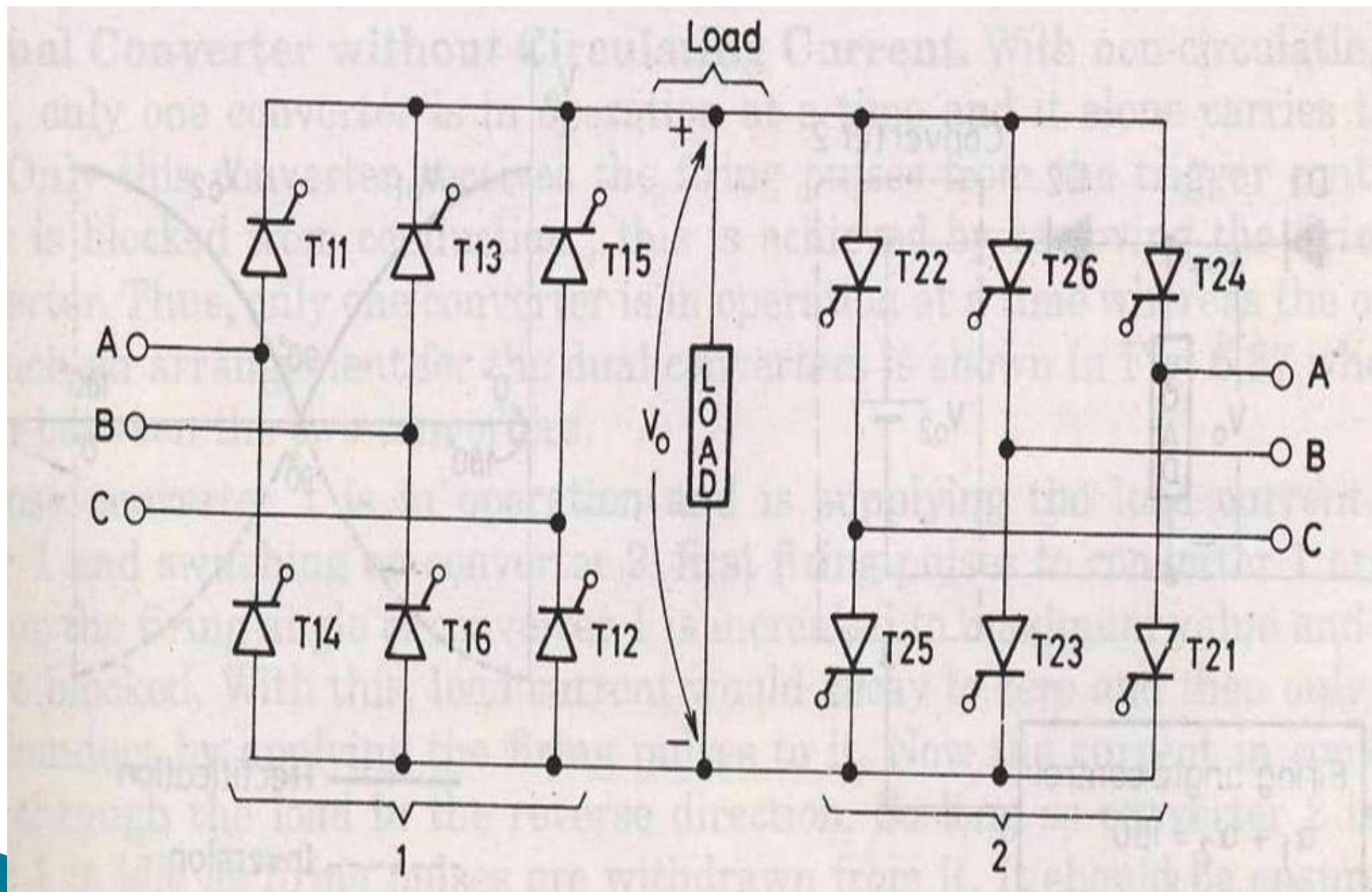

$$V_0 = V_{01} = -V_{02}$$


$$V_{max} \cos \alpha_1 = -V_{max} \cos \alpha_2$$


$$\cos \alpha_1 = -\cos \alpha_2 = \cos (180 - \alpha_2)$$

$$\alpha_1 + \alpha_2 = 180^\circ$$

$$V_{o1} = V_{max} \cos \alpha_1$$

$$V_{o2} = V_{max} \cos \alpha_2$$

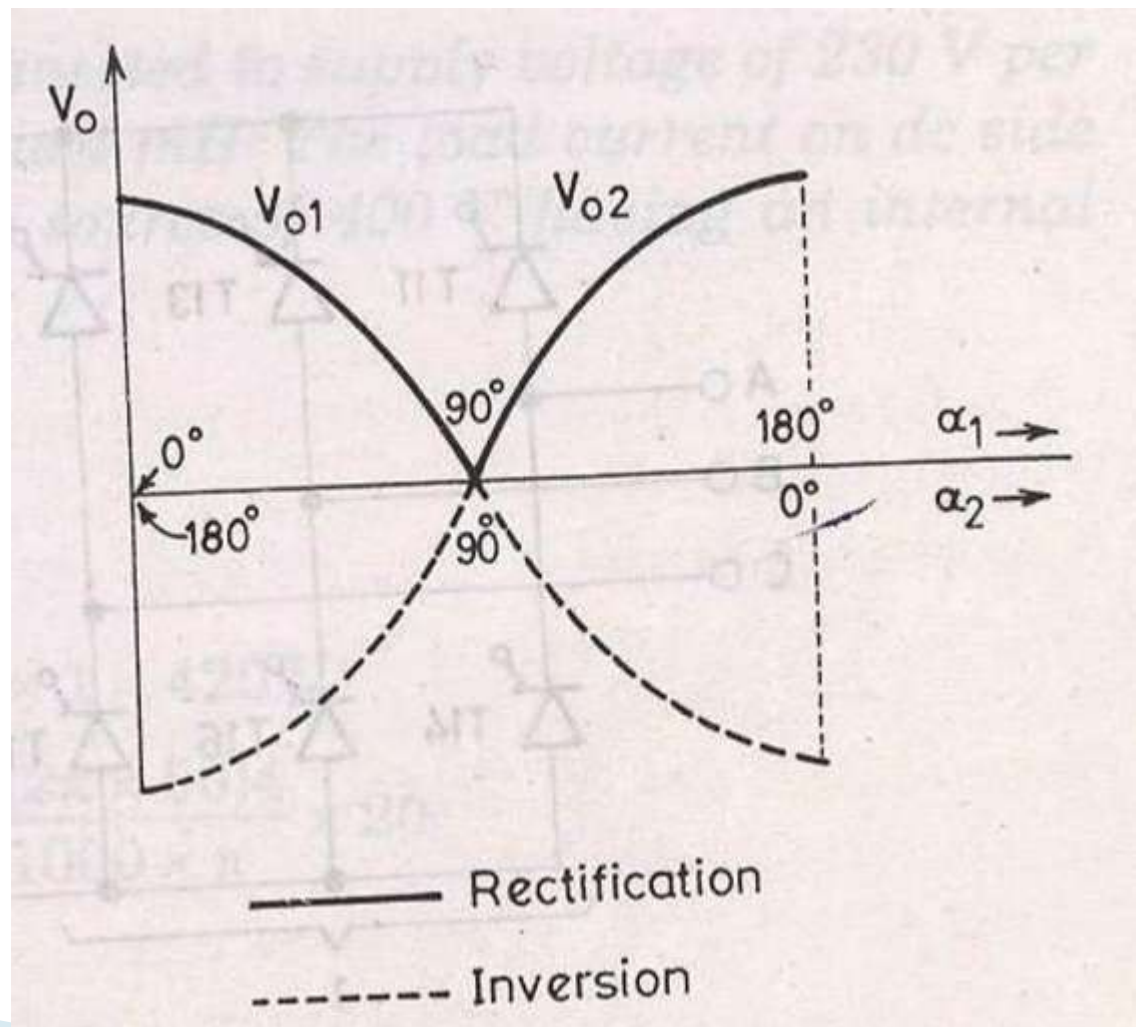

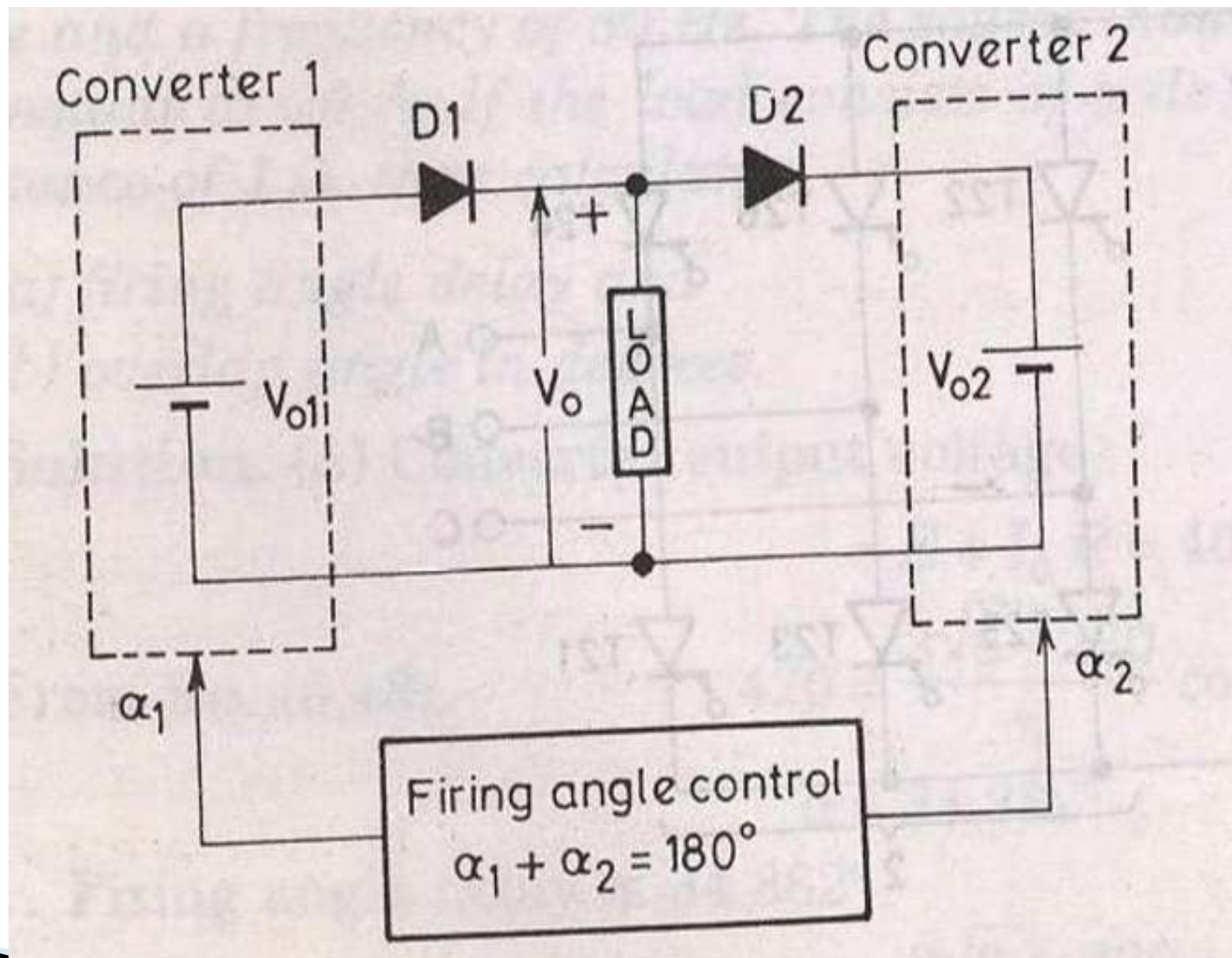

Types of Dual Converters

- ▶ Non Circulating Current Type
- ▶ Circulating Current Type


Non Circulating Current Type


- ▶ Only one converter operates at a time and carries the load current.
- ▶ Before second converter is triggered, it is necessary to make load current zero.

Circulating Current Type

- ▶ Both the converters are operated simultaneously
 - ▶ As the instantaneous output voltage of both converters is out of phase, therefore circulating current flows between them.
 - ▶ Inductors are used to limit the circulating current.
- 

Circulating Current Type

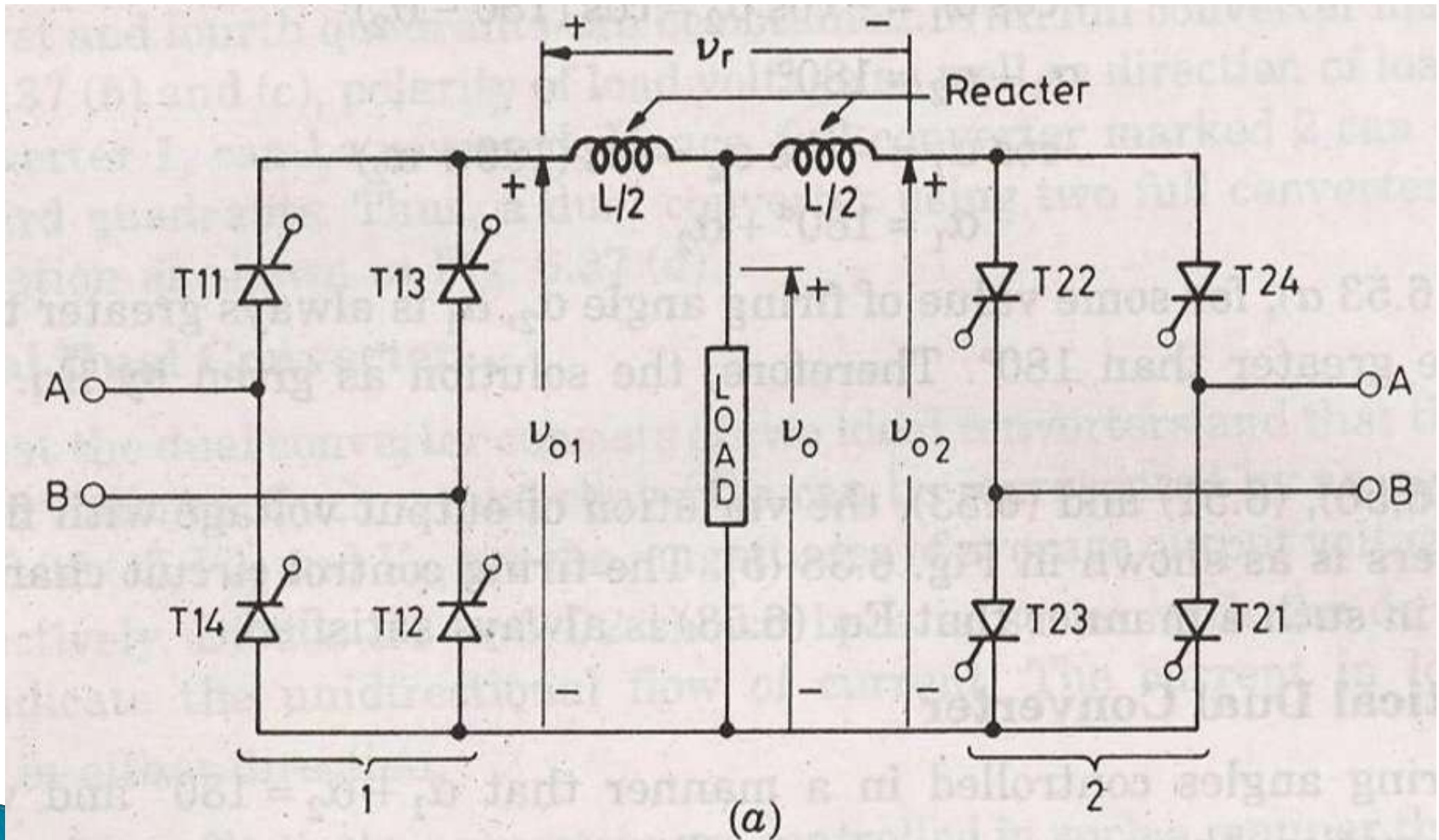

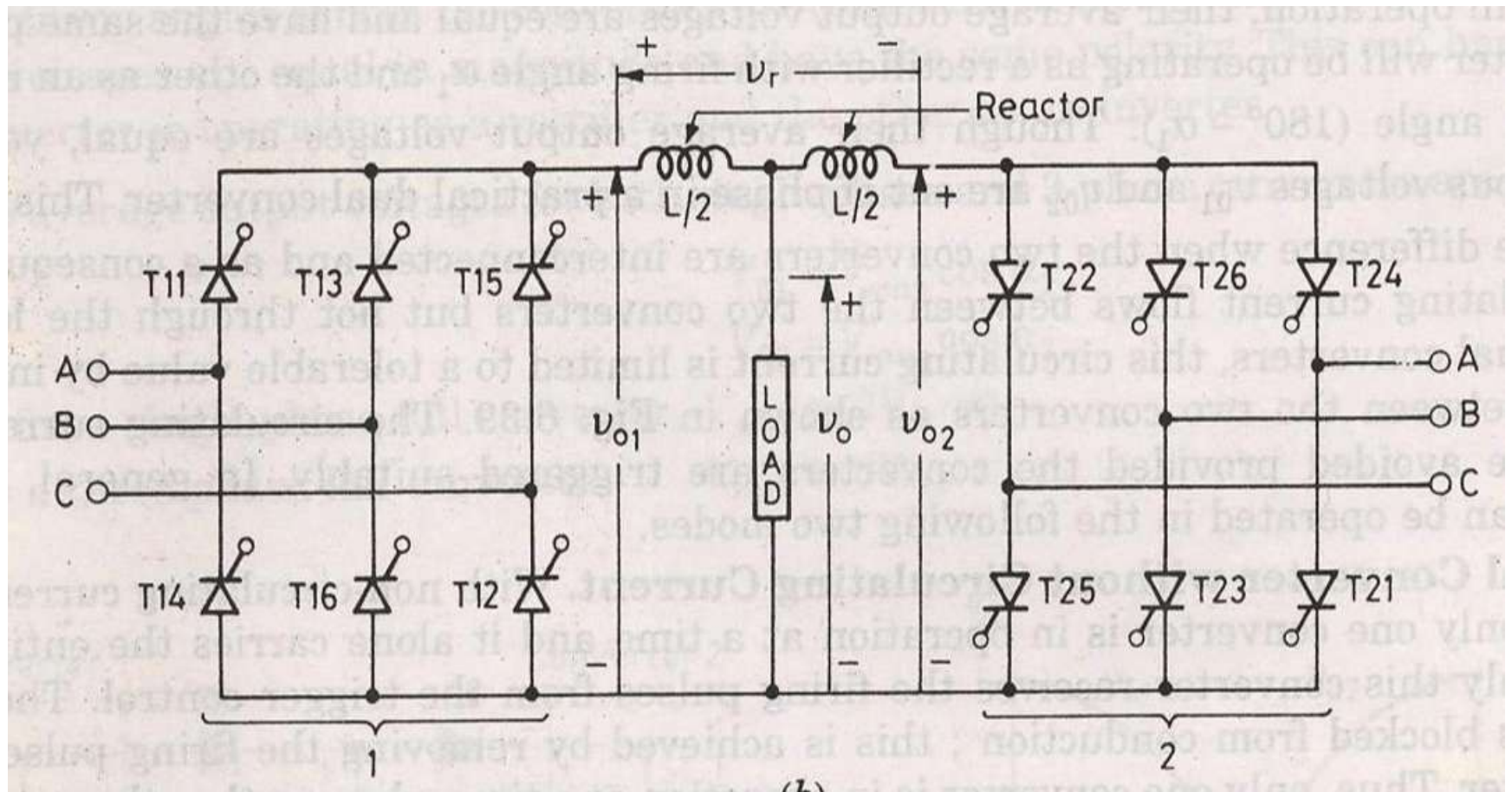

Cycloconverters

Cycloconverter

- ▶ A device which converts input power at one frequency to output power at different frequency, with one stage conversion is called cycloconverter.
 - ▶ Cycloconverter is a one stage frequency changer.
- 


Types of Cycloconverters

- ▶ Step Down Cycloconverters
 - Output frequency is lower than supply frequency
- ▶ Step Up Cycloconverters
 - Output frequency is higher than supply frequency


Applications of Cycloconverters

- ▶ Speed control of high power ac drives
 - ▶ Induction Heating
 - ▶ Static Var Compensation
 - ▶ For converting variable speed alternator voltage to constant frequency output voltage for use as power supply in aircraft or shipboards.
- 


Principle of Operation

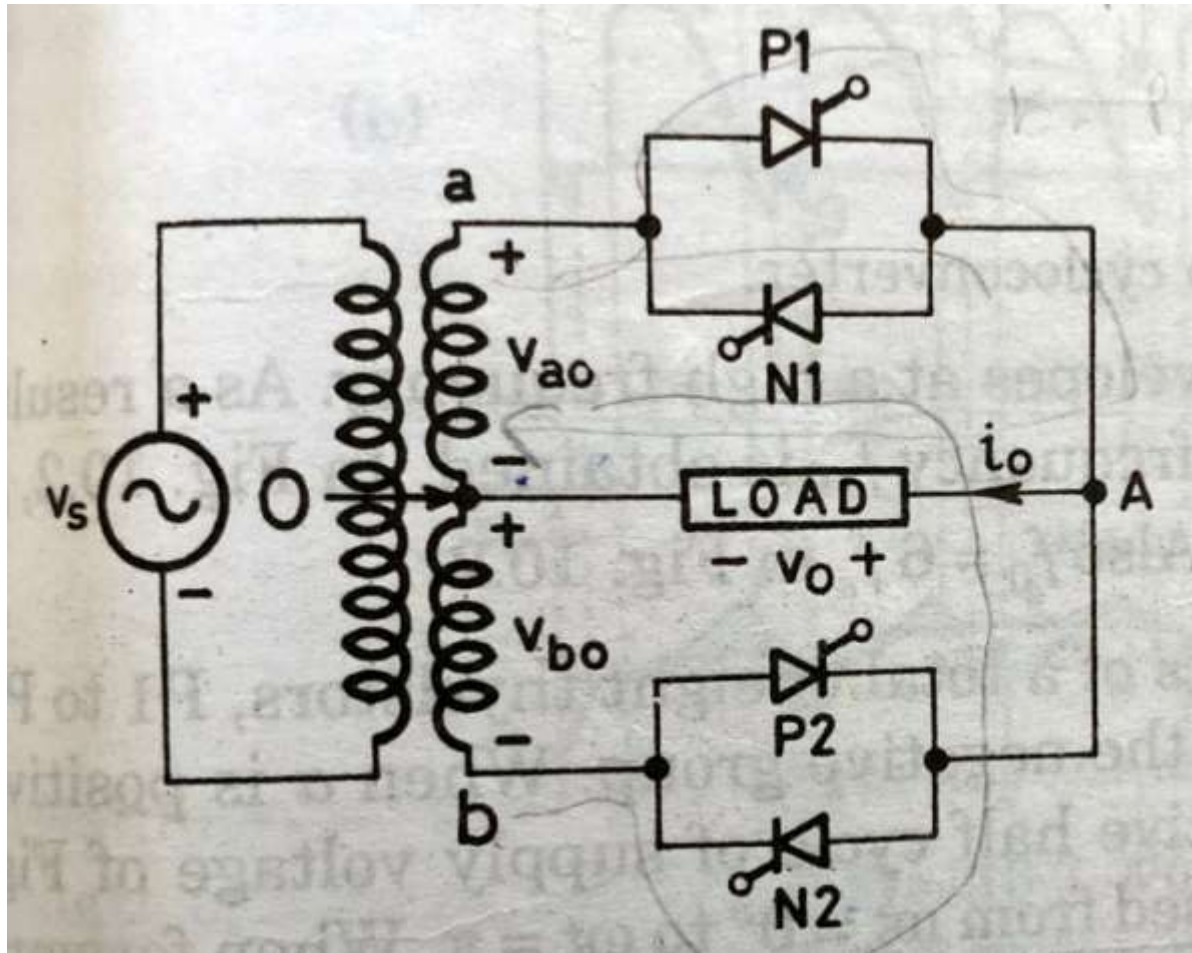


Output of Step Down Cycloconverter

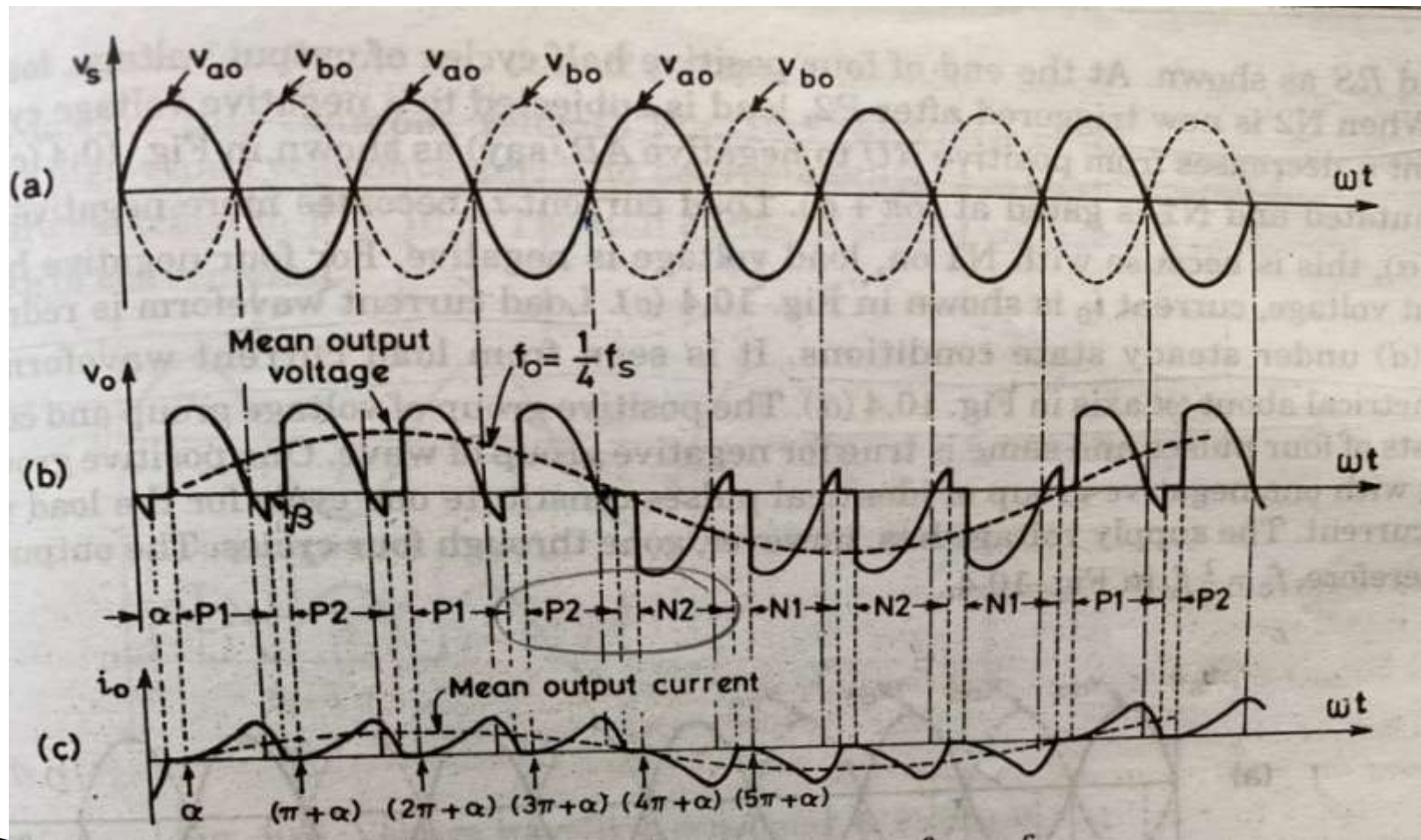


Output of Step Up Cycloconverter

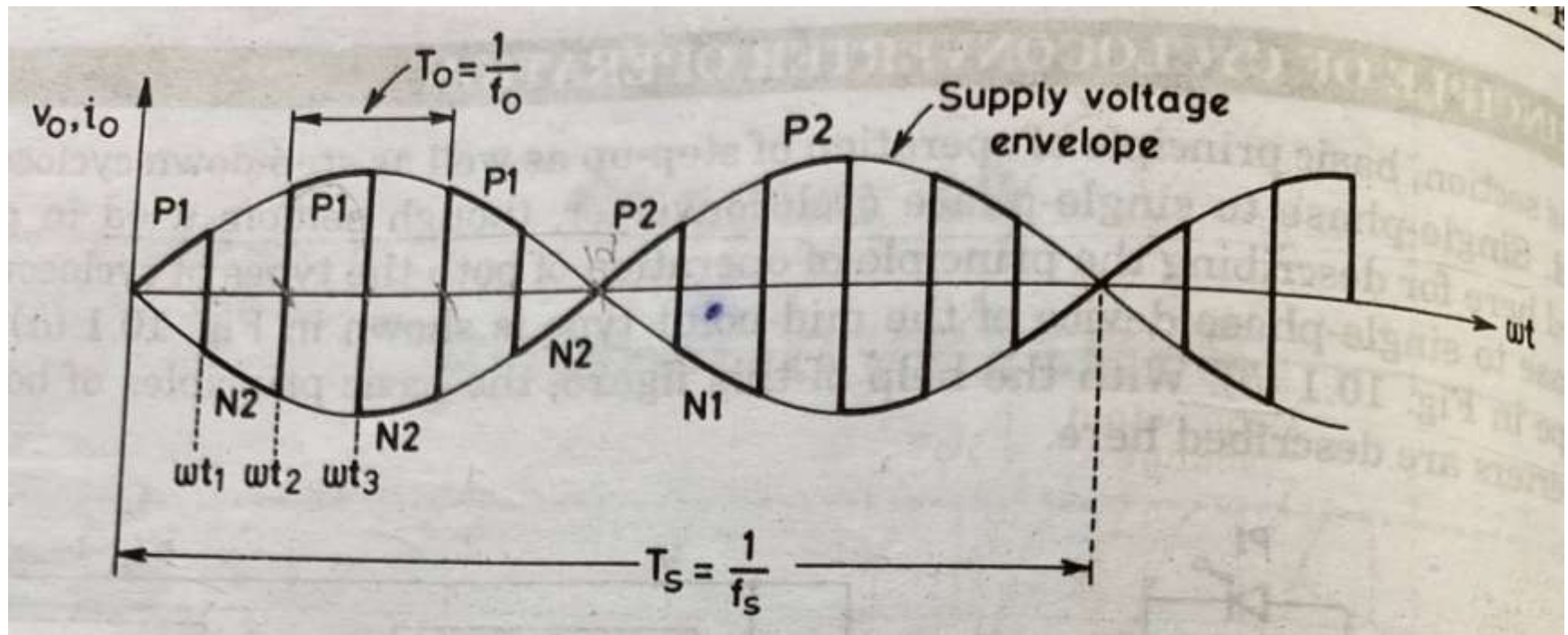


Principle of Operation

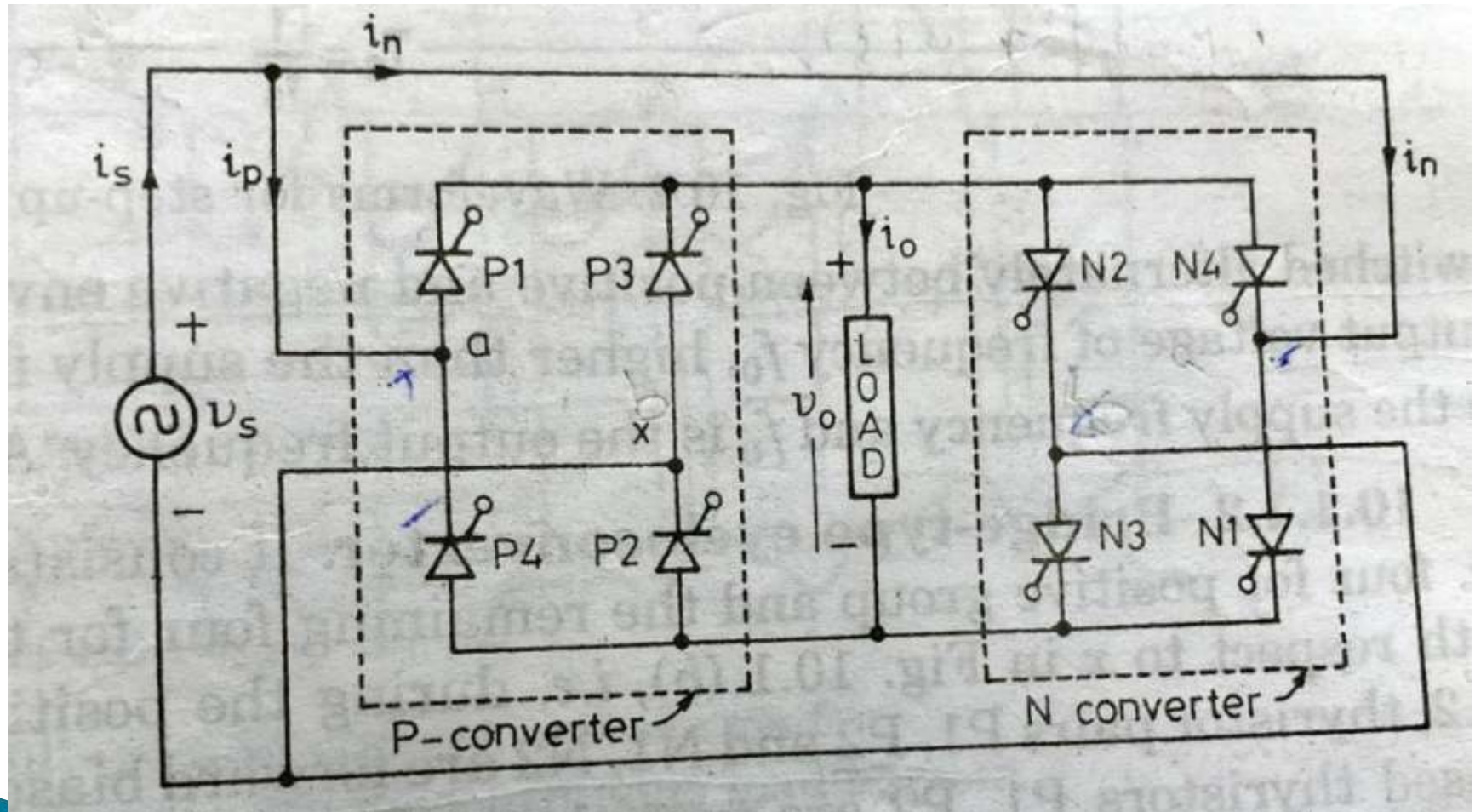


3 Phase, Half Wave Cycloconverter

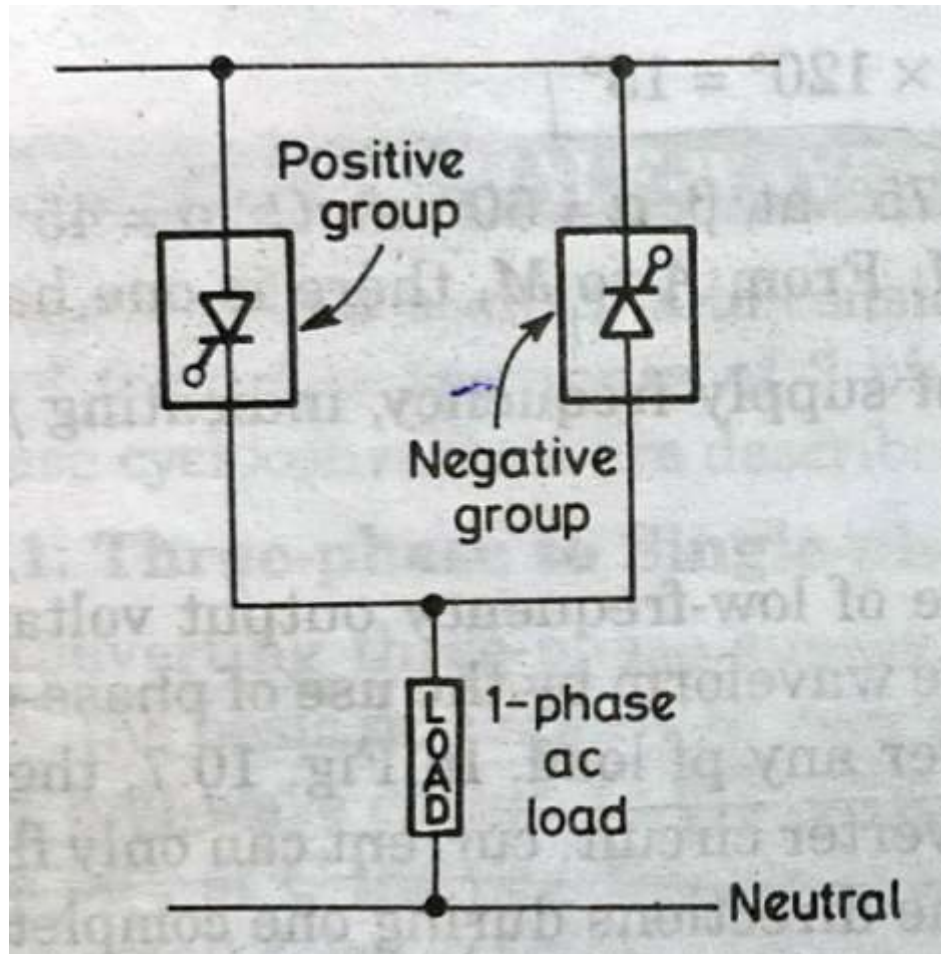


3 Phase, Half Wave Cycloconverter

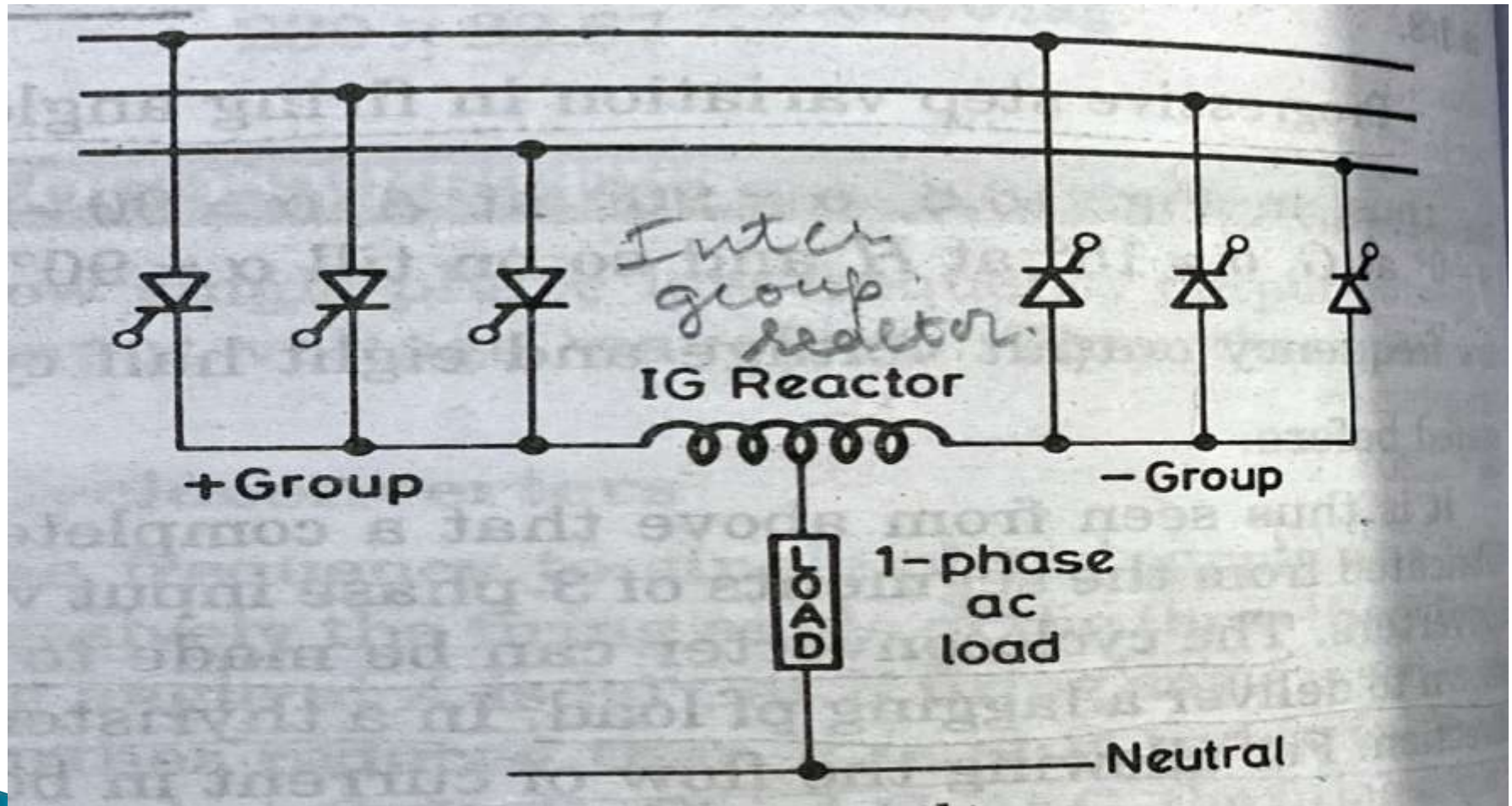


3 Phase, Half Wave Cycloconverter

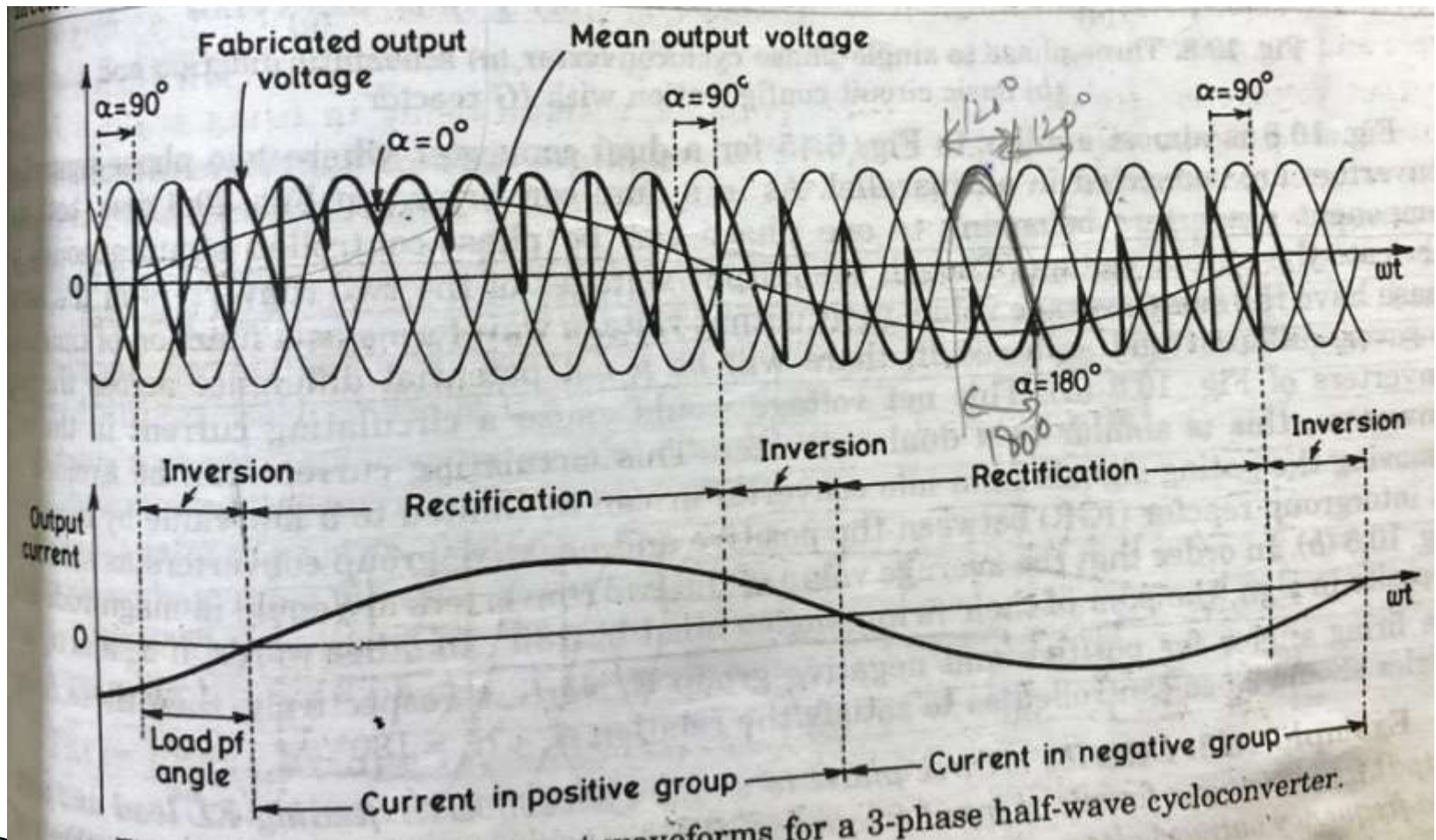

3 Phase, Full Wave Cycloconverter

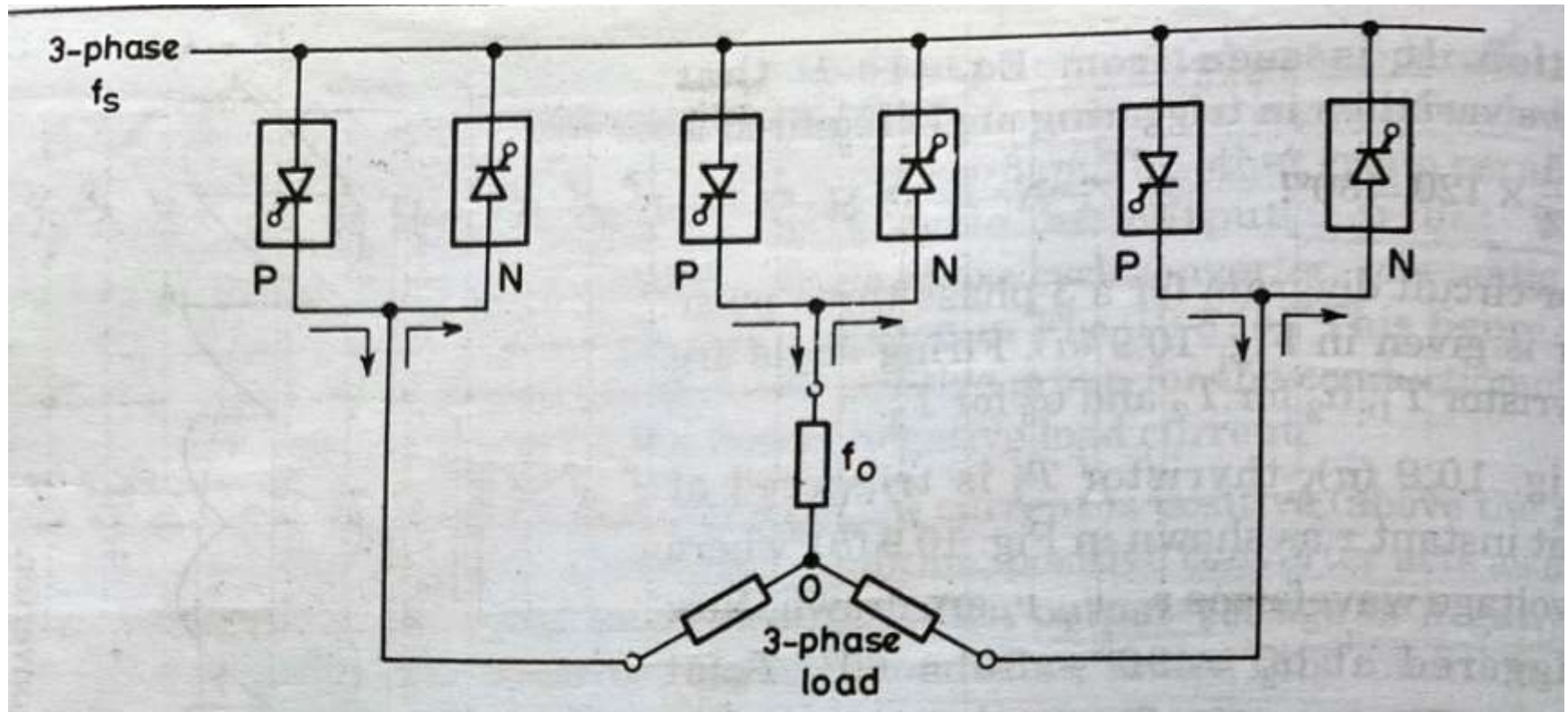

3 Phase, Full Wave Cycloconverter

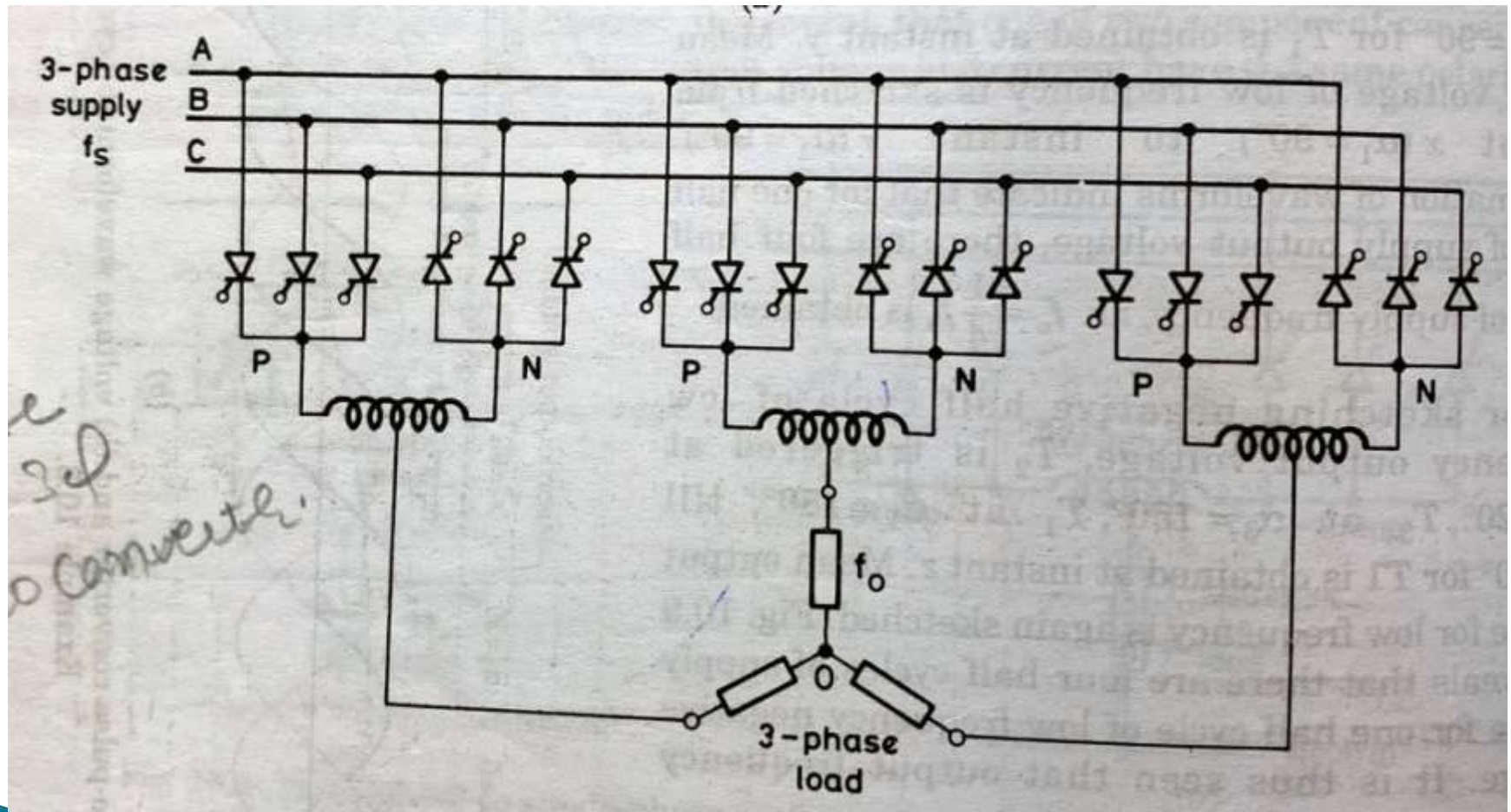

3 Phase, Full Wave Cycloconverter

