

UNIT-2

Attenuators

Attenuators in Network Analysis:

In various transmission equipments, it is many times required to suppress or reduce the levels of the currents and voltages at certain points. To fulfill the need of attenuation, a four terminal resistive network called attenuator is used. Attenuators in Network Analysis are designed to provide a known amount of attenuation between input and output terminals without changing the matching of the impedance at a given value. Attenuators are resistive networks, so all frequencies are attenuated by same degree of amount preventing attenuation distortion. As all the components are resistive in the attenuator networks, no phase shift will be introduced by such networks. Hence the phase constant (β) will be zero and the propagation constant (γ) will be equal to only the attenuation constant (α).

Attenuators in Network Analysis are either symmetrical or asymmetrical networks. Attenuators are either of fixed value or adjustable value type. Generally fixed attenuators providing constant attenuation are called **pads**. The variable attenuators are generally used in radio broadcasting stations as volume controls. Attenuation is usually expressed in neper or decibel.

Power Ratios, Voltage Ratios and Current Ratios:

In line communication, when AC power from one point (generally sending end) to another point (generally receiving end) is considered, various elements in the communication system introduce gains or losses of power at various points.

Consider a four terminal network between a generator and a load as shown in the Fig. 10.1.

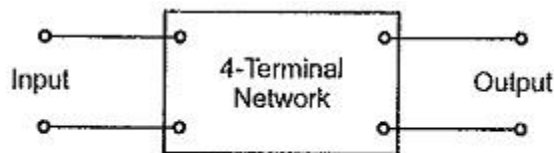


Fig. 10.1 4 Terminal network between generator and load

Let input and output powers be P_1 and P_2 respectively. The network introduced in between generator and load may provide loss or gain in power. Let the ratio of input power to output power i.e. P_1/P_2 be M .

If M is greater than unity, then the network introduces loss. If M is less than unity, then the network introduces gain.

If 'n' number of such networks are connected in cascade or tandem, then the overall power ratio of cascade connection can be obtained by multiplying individual power ratios of networks.

Let M_1 to M_{n-1} be individual input power to output power ratios for (n — 1) number of networks respectively connected in cascade. Then overall power ratio M can be written as,

$$\frac{P_1}{P_n} = \frac{P_1}{P_2} \times \frac{P_2}{P_3} \times \frac{P_3}{P_4} \times \dots \times \frac{P_{n-1}}{P_n}$$

$$M = M_1 \times M_2 \times M_3 \times \dots \times M_{n-1}$$

From above expression it is clear that in the complex systems, calculation of overall power ratio is very tedious. To simplify this calculation the individual power ratios are expressed in logarithmic scale. This enables addition of power ratios in the logarithmic scale instead of multiplication. The logarithmic unit employed is "BELL".

Hence, we can express power ratio in bell as follows,

$$\text{Power ratio in bell} = \log_{10} \left| \frac{P_1}{P_2} \right|$$

But in practice, it is observed that the unit bell is too large. Hence instead of bell a smaller unit called as decibel is introduced, where,

$$1 \text{ bell} = 10 \text{ decibel.}$$

The power ratio expressed in decibel is given by

$$\text{Power ratio in decibel} = D = 10 \log_{10} \left| \frac{P_1}{P_2} \right|$$

Thus, if ratio (P_1/P_2) is greater than unity, then D will be positive which indicates power loss. Similarly if ratio (P_1/P_2) less than unity, then D will be negative which indicates power gain.

The power ratio can be expressed in decibel as follows,

$$D = 10 \log_{10} \left| \frac{P_1}{P_2} \right|$$

$$\log_{10} \left| \frac{P_1}{P_2} \right| = \frac{D}{10}$$

$$\frac{P_1}{P_2} = \text{Antilog} \left| \frac{D}{10} \right|$$

Thus using this conversion we can express any power (either input or output) in watt.

Consider again the network shown in the Fig. 10.1. Assume that two equal resistors of value R are connected at generator and load side. Let the current and voltage at source side be I_1 and E_1 and current and voltage at load side be I_2 and E_2 . The power developed across resistors at source and load side can be written as,

$$P_1 = E_1 I_1 = (R I_1) (I_1) = R I_1^2 \quad \dots (1-a)$$

$$= (E_1) \left(\frac{E_1}{R} \right) = \frac{E_1^2}{R} \quad \dots (1-b)$$

$$P_2 = E_2 I_2 = (R I_2) (I_2) = R I_2^2 \quad \dots (2-a)$$

$$= (E_2) \left(\frac{E_2}{R} \right) = \frac{E_2^2}{R} \quad \dots (2-b)$$

Then input to output power ratio can be given by

$$\frac{P_1}{P_2} = \frac{E_1 I_1}{E_2 I_2} = \left(\frac{I_1}{I_2}\right)^2 = \left(\frac{E_1}{E_2}\right)^2 \quad \dots (3)$$

Expressing all the ratios in decibel as follows,

$$D = 10 \log_{10} \left| \frac{P_1}{P_2} \right| = 10 \log_{10} \left| \frac{I_1}{I_2} \right|^2 = 20 \log_{10} \left| \frac{I_1}{I_2} \right| \quad \dots (4)$$

$$D = 10 \log_{10} \left| \frac{P_1}{P_2} \right| = 10 \log_{10} \left| \frac{E_1}{E_2} \right|^2 = 20 \log_{10} \left| \frac{E_1}{E_2} \right| \quad \dots (5)$$

Expression of Attenuation in Neper and Decibel:

Attenuation is defined as loss of power in a transmission line or an electrical network. Attenuation is expressed either in neper (N) or decibel (dB) notations.

Usually power ratios are expressed in decibel. But it is possible to express voltage and current ratios in decibel if the resistive components of generator and [load impedances](#) are equal.

Similarly neper is usually used to express current ratios. But it is possible to express power ratio in neper if the resistive components of generator and load impedances are equal.

Consider a four terminal network as shown in the Fig. 10.2 between generator and load.

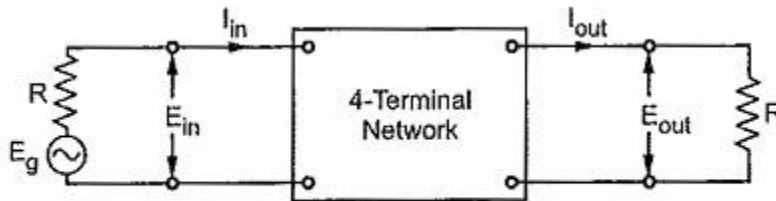


Fig. 10.2

If the power entering a network is P_{in} and that leaving the network is P_{out} , then the attenuation in decibel is defined as,

$$\text{Attenuation (in decibel)} = 10 \log_{10} \left| \frac{P_{in}}{P_{out}} \right| \quad \dots (1)$$

If the current entering a network is I_{in} and that leaving the network is I_{out} , then the attenuation in neper is defined as,

$$\text{Attenuation (in neper)} = \ln \left| \frac{I_{in}}{I_{out}} \right| \quad \dots (2)$$

Under the condition of equal resistive components at generator and load side, we can write,

$$\begin{aligned}
\text{Attenuation (in decibel)} &= 10 \log_{10} \left| \frac{P_{in}}{P_{out}} \right| \\
&= 10 \log_{10} \left| \frac{I_{in}^2 R}{I_{out}^2 R} \right| \\
&= 20 \log_{10} \left| \frac{I_{in}}{I_{out}} \right| \quad \dots (3) \\
&= 20 \log_{10} \left| \frac{E_{in}}{E_{out}} \right| \quad \dots (4)
\end{aligned}$$

Similarly,

$$\begin{aligned}
\text{Attenuation (in neper)} &= \ln \left| \frac{I_{in}}{I_{out}} \right| \\
&= \ln \left| \frac{E_{in}}{E_{out}} \right| \\
&= \frac{1}{2} \ln \left| \frac{P_{in}}{P_{out}} \right| \quad \dots (5)
\end{aligned}$$

If the resistive components of the impedances at input (i.e. generator) and output (i.e. load) of the network are equal, we can convert attenuation in any notation as follows

$$[\text{Attenuation in decibel}] = 8.686 \times [\text{Attenuation in neper}]$$

$$\text{and } [\text{Attenuation in neper}] = 0.1151 \times [\text{Attenuation in decibel}]$$

Attenuator Network:

An attenuator network must fulfil following conditions.

- **It must give correct input impedance,**
- **It must give correct output impedance and**
- **It must provide specified attenuation.**

In general, attenuation is expressed in decibel as follows,

$$D = 10 \log_{10} \left| \frac{P_{in}}{P_{out}} \right|$$

where D is the attenuation in decibel.

But we can express attenuation in neper as follows,

$$D = 20 \log_{10} \sqrt{\frac{P_{in}}{P_{out}}} = 20 \log_{10} N$$

where N is the attenuation in neper.

$$N = \text{Antilog}_{10} \left(\frac{D}{20} \right) \quad \dots (1)$$

In this topic, we shall study symmetrical attenuators such as symmetrical T type, symmetrical π type, 'L' type attenuator.

Any Attenuator Network is designed for specified characteristic resistance R_0 and attenuation.

Let us find design equations for various Attenuator Network one by one.

Symmetrical T Type Attenuator:

Consider properly terminated symmetrical T network as shown in the Fig. 10.3.

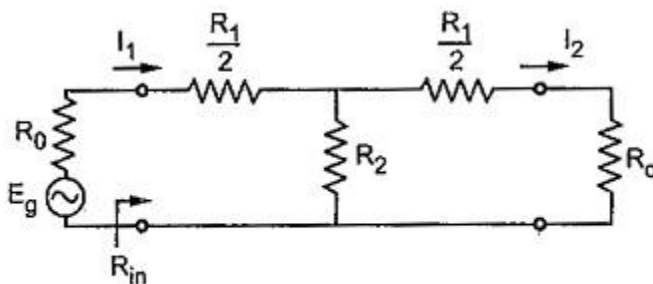


Fig. 10.3 Properly terminated symmetrical 'T' network

According to current divider rule,

$$I_2 = I_1 \left[\frac{R_2}{R_2 + \left(R_0 + \frac{R_1}{2} \right)} \right] \quad \dots (1)$$

But for symmetrical networks,

$$N = \frac{I_1}{I_2} = \frac{R_0 + R_2 + \frac{R_1}{2}}{R_2} \quad \dots (2)$$

For properly terminated network, input impedance R_{in} is given by,

$$R_{in} = R_0 = \left[\left(R_0 + \frac{R_1}{2} \right) \parallel R_2 \right] + \frac{R_1}{2}$$

$$R_0 = \frac{R_2 \left(R_0 + \frac{R_1}{2} \right)}{R_0 + R_2 + \frac{R_1}{2}} + \frac{R_1}{2}$$

From equation (2),

substituting $\frac{1}{N}$ for $\frac{R_2}{R_0 + R_2 + \frac{R_1}{2}}$

$$R_0 = \frac{R_0 + \frac{R_1}{2}}{N} + \frac{R_1}{2}$$

$$NR_0 = R_0 + \frac{R_1}{2} + N \frac{R_1}{2}$$

$$R_0(N-1) = \frac{R_1}{2}(N+1)$$

$$\frac{R_1}{2} = R_0 \left(\frac{N-1}{N+1} \right) \quad \dots (A)$$

From equation (2), we can write,

$$NR_2 = R_0 + R_2 + \frac{R_1}{2}$$

$$R_2(N-1) = R_0 + R_0 \left(\frac{N-1}{N+1} \right)$$

$$R_2(N^2 - 1) = R_0(N+1) + R_0(N-1)$$

$$R_2 = R_0 \left(\frac{2N}{N^2 - 1} \right) \quad \dots (B)$$

Equations (A) and (B) are called design equations of symmetrical T attenuator.

L Type Asymmetrical Attenuator:

An asymmetrical L type attenuator is as shown in the Fig. 10.12.

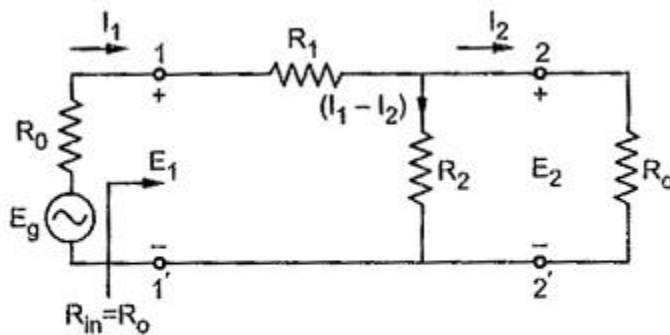


Fig. 10.12 Asymmetrical L type attenuator

$$\begin{aligned}
 E_2 &= (I_1 - I_2) R_2 = I_2 R_0 \\
 I_1 R_2 &= I_2 (R_0 + R_2) \\
 \frac{I_1}{I_2} &= N = \frac{R_0 + R_2}{R_2} \\
 N R_2 &= R_0 + R_2 \\
 R_2 &= R_0 \left[\frac{1}{N-1} \right] \quad \dots (A)
 \end{aligned}$$

Input resistance looking into network from terminals 1-1' is

$$R_{in} = R_0 = R_1 + \frac{R_2 R_0}{R_2 + R_0}$$

$$R_0 (R_2 + R_0) = R_1 (R_2 + R_0) + R_2 R_0$$

$$R_2 R_0 + R_0^2 = R_1 R_2 + R_1 R_0 + R_2 R_0$$

Putting value of R_2 from equation (A),

$$R_0^2 = R_1 \left[\frac{R_0}{N-1} \right] + R_1 R_0$$

$$R_0 = \frac{R_1}{N-1} + R_1$$

$$R_0 (N-1) = R_1 + N R_1 - R_1$$

$$R_1 = R_0 \left[\frac{N-1}{N} \right] \quad \dots (B)$$

equations (A) and (B) are called design equations of asymmetrical L type attenuator.