Microphones

Juan P Bello

Early recording

- Early recording and reproduction was entirely acoustic
- Sound was captured by a horn terminated on a diaphragm that vibrated in sympathy with the sound
- The diaphragm was attached to a stylus which cut grooves on foil or wax
- Performers had to clutter around the horn.
- Little control of individual levels




Sound in electrical form

- Sound in electrical form can be amplified, mixed and recorded.
- We can convert the acoustical waveform into an electrical waveform of the same shape
- Amplitude becomes voltage (V), and air particle motion becomes electrical current (I) electrons playing the role of air particles.
- The current's direction of flow changes with cycles of compression/rarefaction creating an alternating current (AC)
- The flow of electrons in a conductor is impeded by a certain amount of resistance (R)
- The relationship between V, I and R is regulated by Ohm's law: V = $I \times R$. Their relationship with Power (W) is: W = $I^2 \times R = V^2/R$
- In AC systems resistance is replaced by impedance (which also includes reactance). Impedance is frequency dependent

Electro-magnetic induction

- Electromagnetic transducers convert mechanical motion (as produced by, e.g., an acoustic wave) into an electrical signal
- An electrical current is induced (and voltage is produced) if: (i) a static conductor is situated in a changing magnetic field, or (ii) a conductor moves in a static magnetic field
- This phenomenon is characterized by Faraday's law of electromagnetic induction (<u>http://msdaif.googlepages.com/demo_faraday</u>)

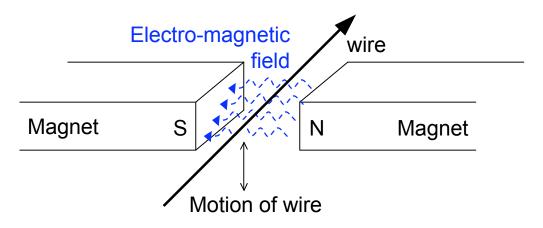

- The direction of motion (perpendicular to the lines of flux) controls the direction of current flow in the conductor (e.g. a wire).
- Back and forth movements result in an alternating current (AC) related in frequency and amplitude to the wire's motion

Microphones

- Microphones are transducers that convert acoustical energy into electrical energy.
- The three main types of microphones (according to their principles of operation) are:








Condenser

Dynamic (moving-coil)

Ribbon

Dynamic microphones

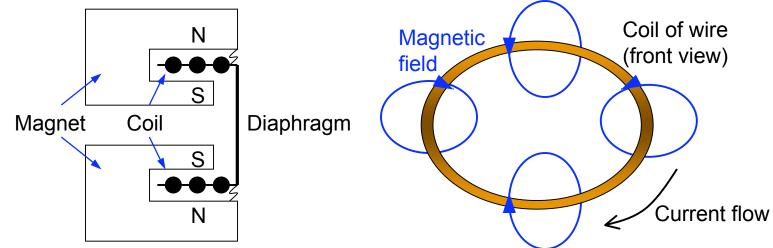
- Dynamic mics consist of a diaphragm suspended in front of a magnet to which a coil of wire is attached.
- The coil sits in the gaps of the magnet. Vibrations of the diaphragm make the coil move in the gap causing an AC to flow
- Coils of wire are used to increase the magnitude of the induced voltage and current



- The mass of the coil-diaphragm structure impedes its rapid movement at high frequencies (where there is usually low response).
- A resonant peak is usually found at around 5kHz, making it a favorite with vocalists.
- Very robust (extensively used for kick-drums)

Ribbon microphones

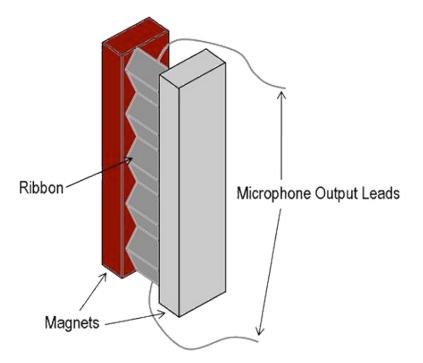
- It consists of a thin strip of conductive corrugated metal (ribbon) between magnetic plates.
- Vibration of the ribbon according to the acoustic wave induces a current
- Its electrical output is very small and needs to be stepped up by a transformer



- The lightness of the ribbon guarantees a flat frequency response for mid and high frequencies up to 14kHz. It resonates at very low frequencies (around 40Hz)
- It is very delicate and well suited for the recording of acoustic instruments

Condenser microphones (1)

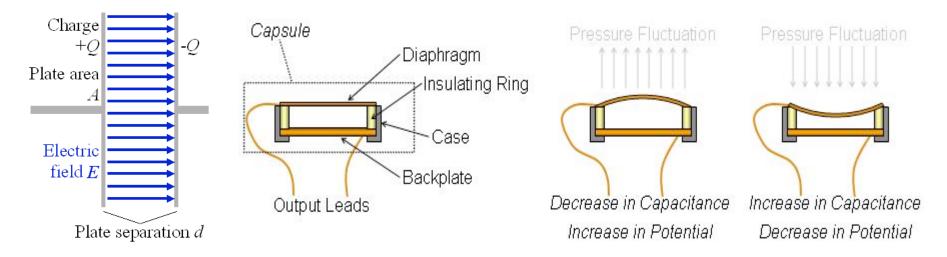- A capacitor is an electrical device able to store electrical charge between two closely-spaced conductors (plates)
- Capacitance (C) measures how much charge (Q) is stored for a given voltage (V), such that C = Q/V
- Capacitance is inversely proportional to the distance (d) between plates




 In condenser mics, the front plate is the diaphragm which vibrates with the sound. The charge (Q) is fixed, thus changes in the distance d between plates result on changes of voltage (V)

Condenser microphones (2)

- Condenser mics can be extremely high quality
- The diaphragm can be very light, rendering a flat frequency response (with a small resonance peak at above 12kHz)
- Output of condenser mics is much higher than for dynamic mics
- High output makes it more robust to noise
- To charge the capacitor a source of power is needed (usually phantom power to be discussed later in the course)
- An alternative to using a power source is to introduce a permanent electrostatic charge during manufacture, resulting on the "electret" mic.
- Electret microphones can be very small, high quality (back electrets) and cheap, e.g. Tie-clip TV microphones


Directional Response (1)

- Microphones are designed to have a directional response pattern
- This pattern is characterized by a polar diagram showing magnitude of the output (in dB) vs angle of incidence
- An omnidirectional microphone picks up sound equally in all directions
- This is achieved by opening the diaphragm at the front and completely enclosing it at the back
- At high frequencies the wavelength is comparable to the size of the capsule, resulting in a loss of gain off front center
- Smaller capsules result in better highfrequency performance
- TV tie-clip microphones are usually omni electrets

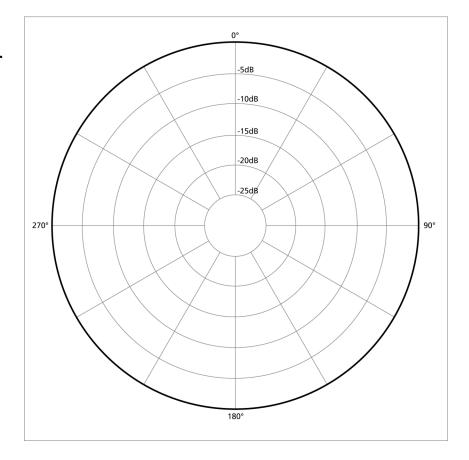


Directional Response (2)

- Figure eight or bidirectional microphones have an output close to cos(θ), where θ = angle of incidence
- This directional pattern is mostly associated with ribbon microphones (open both at the front and rear)
- The response is thus the result of the pressure difference between diaphragm front and rear (which is why response is null at 90/270°)
- The long wavelengths at low frequencies (resulting in small phase differences) cause a reduction of the output
- Because of the ribbon's shape, ribbon mics have a better polar response when upright or upside down, than when positioned horizontally

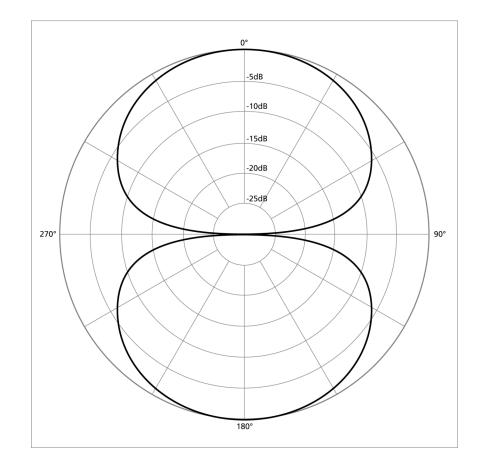

Directional Response (3)


- Cardiod microphones result from the combination of omnidirectional and bidirectional patterns
- Their output is close to $1 + \cos(\theta)$
- They are unidirectional
- The response is obtained by leaving the diaphragm open at the front while using acoustic labyrinths in the rear to cause differences of phase and amplitude in the incoming sound
- Mid frequency response is usually very good
- At low-frequencies it tends to omni
- At high frequencies it becomes too directional
- This is common to dynamic cardioids
- Top range condenser cardioids behave much more ideally

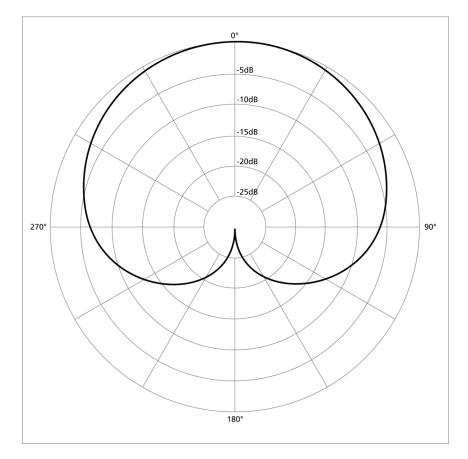

Directional Response (4)

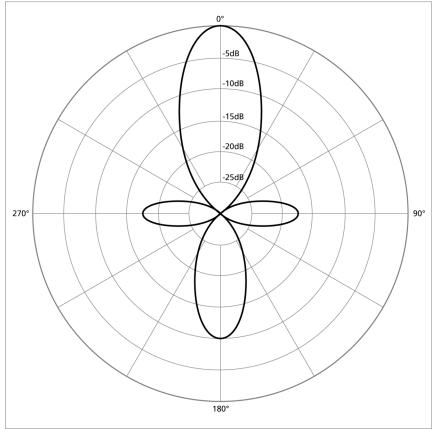- There are a number of specialized microphones such as so-called shotgun microphones or parabolic microphones which are highly directional
- A shotgun mic, for example, is cardiod with a long barrel with openings aimed at causing canceling phase differences





Characteristics of microphones

- Professional microphones have a low-impedance usually around of 200 ohms - this enables the use of long leads
- Another important characteristic is sensitivity, i.e. a measure of the electrical output (in volts) per incoming SPL
- Sensitivity is usually given in terms of a reference SPL, e.g. 94 dB or 1 Pascal (Pa).
- Condenser microphones (5-15 mV/Pa) are more sensitive than moving coils (1.5-3 mV/Pa) and ribbons (1-2 mV/Pa)
- More amplification is needed for moving-coils and ribbons (which are thus more susceptible to interference). Also, low-sensitivity mics need high-quality (low noise) amps and mixers.
- All microphones generate some noise. This is usually expressed in "A-weighted" self-noise (given in dBA).
- High-quality condenser and moving-coil mics achieve self-noise of 17-18dBA. Ribbon mics' noise can be of the order of 23dBA, which means that for quite signals low-noise amps need to be used. A self-noise in the region of 25dBA results in poor performance.

Useful References

- Francis Rumsey and Tim McCormick (2002). "Sound and Recording: An Introduction", Focal Press.
 - Chapter 3: Microphones
- For a quick reference on coils and electromagnetism see: Marshall Brain. "How Electromagnets works". <u>http://science.howstuffworks.com/electromagnet4.htm</u>
- Microphone photos, ribbon, condenser mic and polar diagrams from:
- <u>http://en.wikibooks.org/wiki/Acoustics/Microphone Design and Operation</u>
- <u>http://en.wikipedia.org/wiki/Microphone</u>

Loudspeakers

Juan P Bello

Outline


- 1. Loudspeaker Types
- 2. Loudspeaker Enclosures
- 3. Multiple drivers, Crossover Networks
- 4. Performance Measurements


Loudspeakers

- Microphone: acoustical sound energy → electrical energy
- Loudspeaker: electrical energy → acoustical sound energy

Moving-Coil

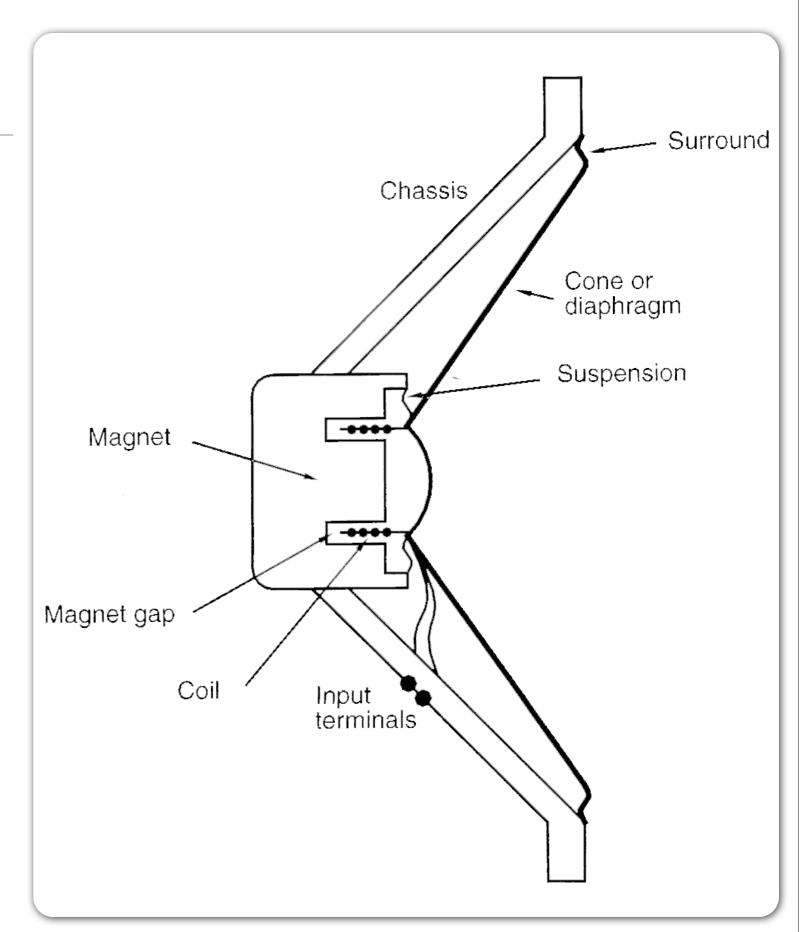- Backwards dynamic mic
- Most common: transistor radios, PAs, studio monitors
- Permanent magnet with wire coil inside ring-shaped gap
- Magnet attached to speaker cone
- Electrical input → A/C current
 in coil → diaphragm vibration
 → sound waves
- Omnidirectional pattern




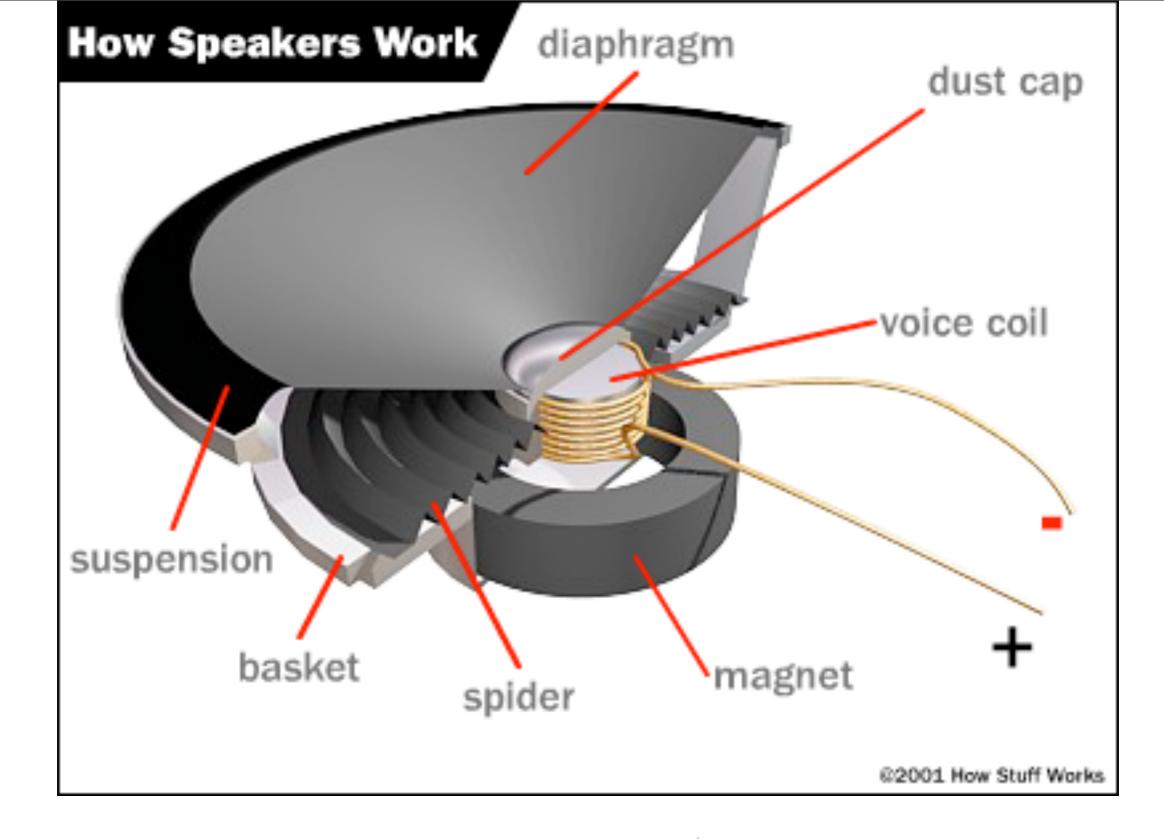

Moving Coil in Action


Electrostatic

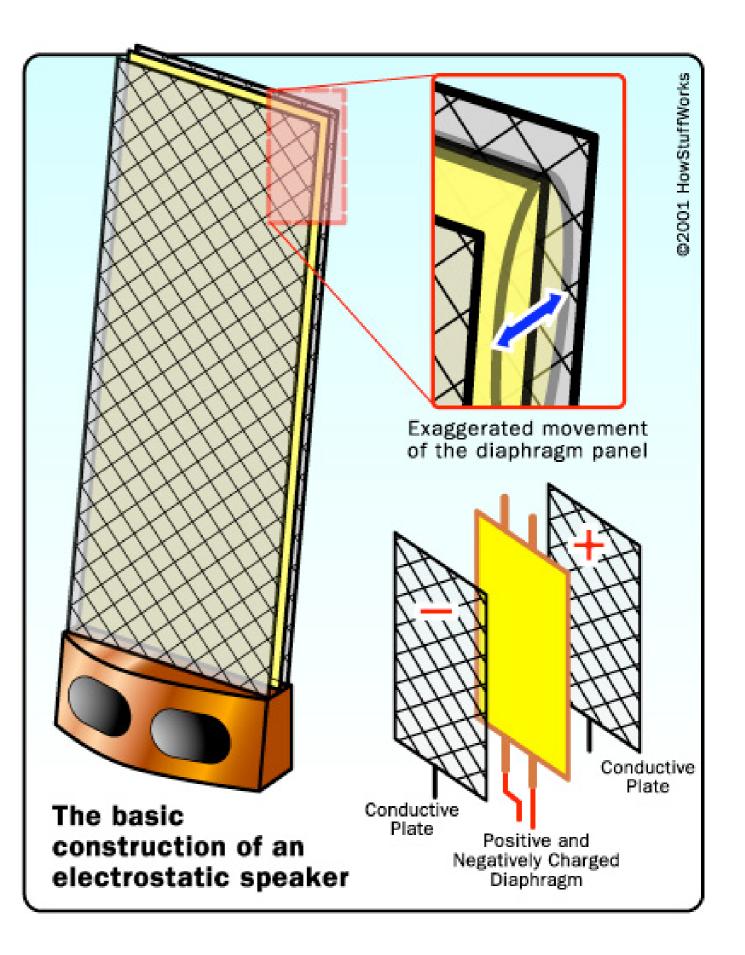- Backwards condenser mic
- Large, flat diaphragm between two oppositely charged plates (+) and (-)
- Electrical input to diaphragm alternates its charge, causing vibration.
- Expensive and harder to manufacture, usually lacking in bass response
- Figure 8 pattern



Ribbon

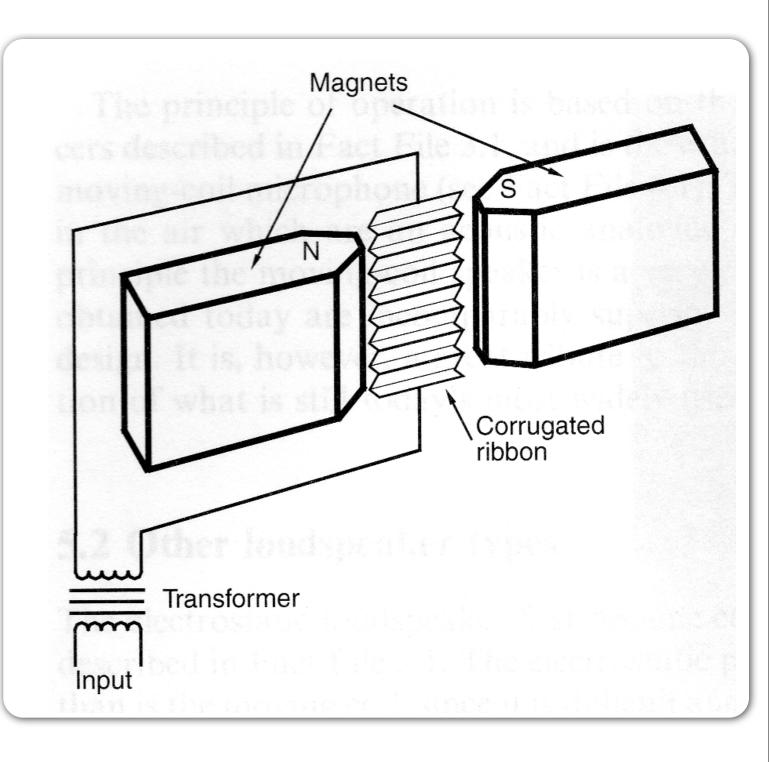
- Backwards ribbon mic
- Ribbon suspended between N pole and S pole magnets
- Electrical input applied to ends of ribbon induces alternating magnetic field, causing vibration
- Also more expensive to produce, low impedance and acoustical output
- Figure 8 pattern



Free-cone Dynamic Speaker Issues

frequencies

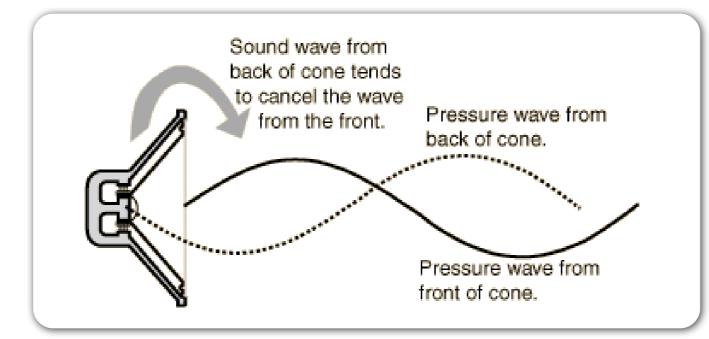
 Back-to-front cancellation: sound wave emitted from rear of driver is opposite in phase (180°) to sound wave emitted from front, more prevalent at lower



- Free-cone resonance: speaker cone will vibrate more strongly at its natural "resonant frequency"
 - Causes distortion of signal: "ringing", "boominess"


Speaker Enclosures

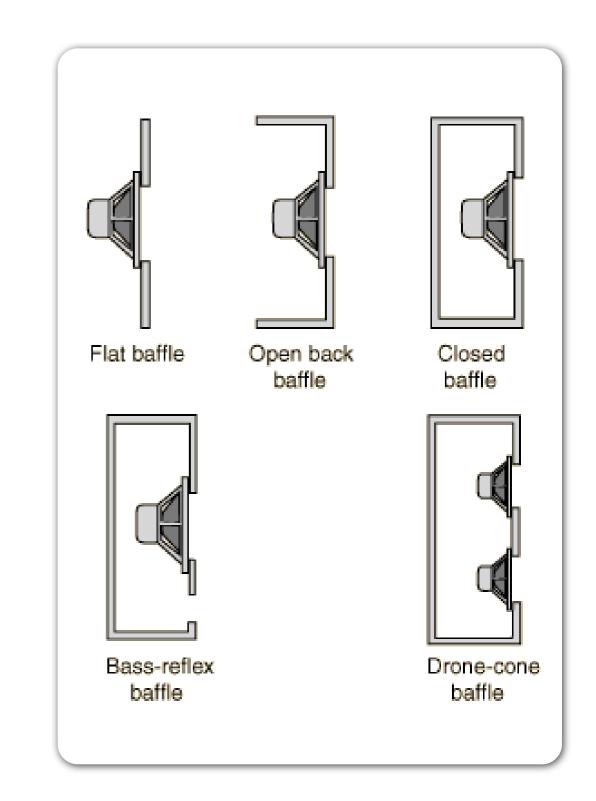- Designed to reduce the free-cone problems of cancellation and resonance
- Also referred to as "baffles" or "cabinets"
- Several types: two of the most common are the "sealed" enclosure and the "bass-reflex" enclosure



Closed-box Enclosures

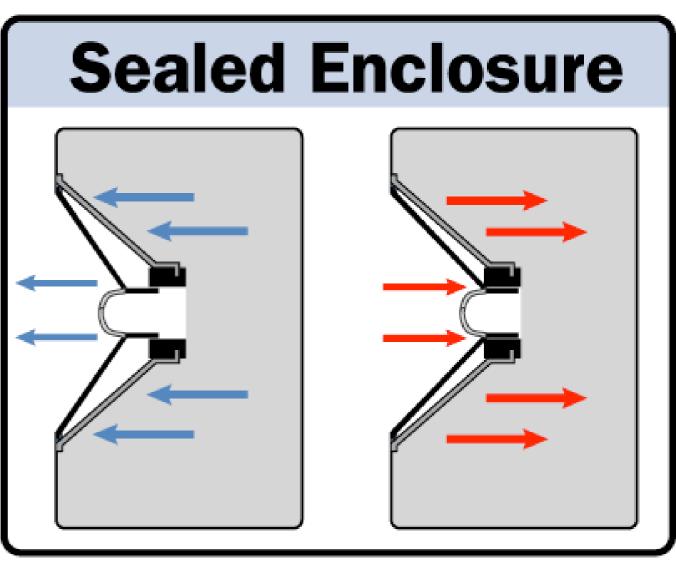- Completely sealed, usually contains sound-absorbing material inside
- Soundwaves emitted from rear of driver do not reach open air
- Cheaper to manufacture, more common




© 2001 How Stuff Works

Bass Reflex Enclosures

- Air inside bass port resonates at specified low frequency
- Reduces movement of speaker cone at bass port frequency \rightarrow increases efficiency and low frequency output
- Frequencies below resonant frequency are not acoustically loaded, can cause overexcursion of the speaker cone


Bass Reflex Enclosure

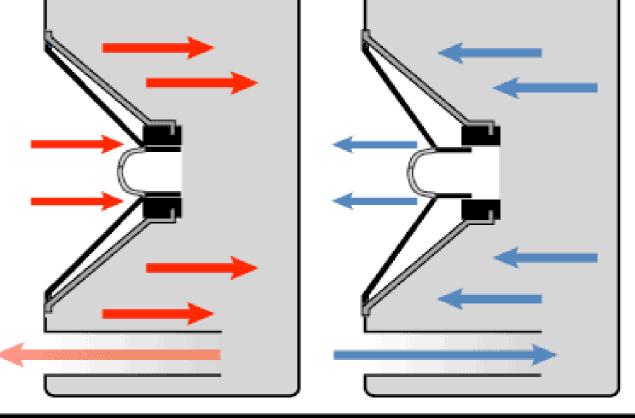



© 2001 How Stuff Works

Horn-loading

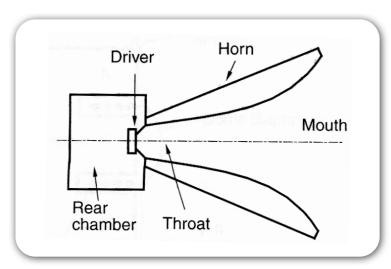- Placing horn in front of diaphragm
- Usually has limited frequency range and uneven response
- Long-throw horn
 - Concentrates sound in the forward direction
 - Used in P.A.'s
 - Acoustical lens: diffracts sound over wider angle (better for people close to the speakers)
- Re-entrant horn
 - Driver facing backward, horn much shorter
 - Often used in hand-held horns, subway



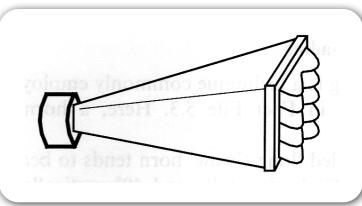

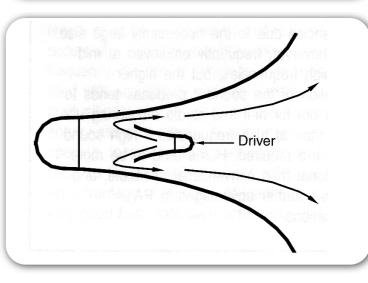


Multiple-Driver Systems

- A single driver is not adequate for producing frequencies across the entire audible spectrum
- Tweeter small, light, very responsive
 - 3 kHz 20 kHz
 - Often uses convex "dome" construction
- Bass/mid driver larger, heavier, less responsive
 - 30 Hz 3 kHz




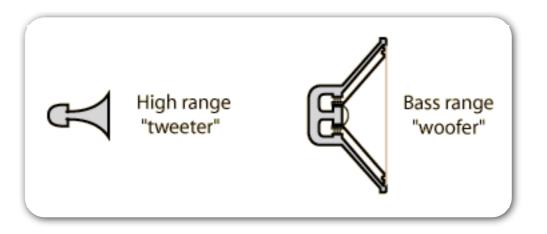- Require more power to drive greater mass
- Require "crossover" network to route frequency signals to the right driver




"Passive" Crossover Network

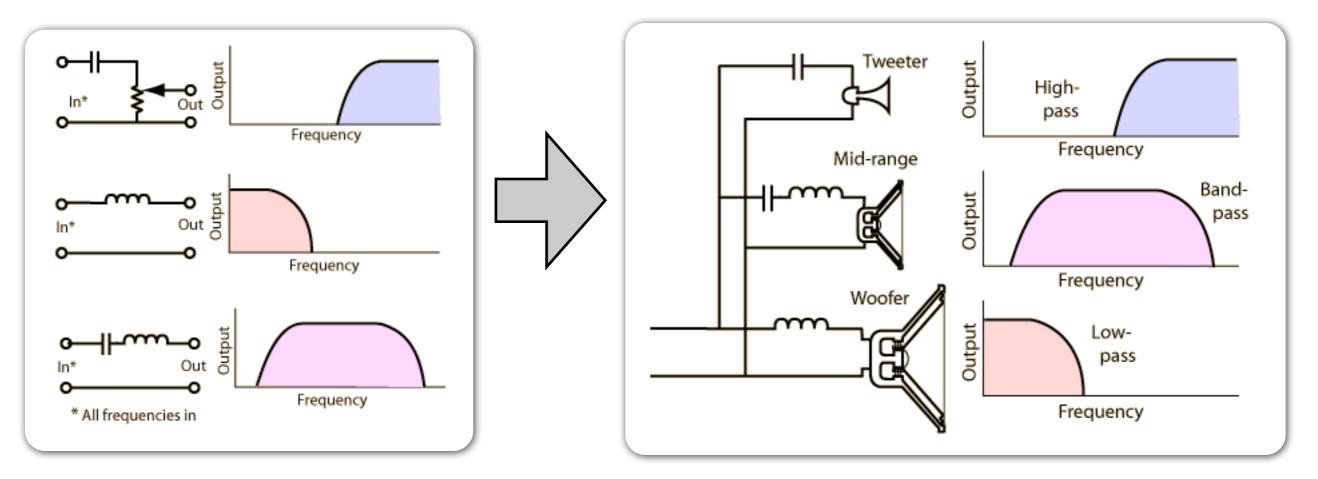- Uses passive components to divide signal: resistors, capacitors, inductors
- Hi-pass filter: capacitor with lower impedance for high frequencies
- Low-pass filter: inductor with lower impedance for low frequencies
- Band-pass filter: Capacitor and inductor in series




"Active" Crossover Network

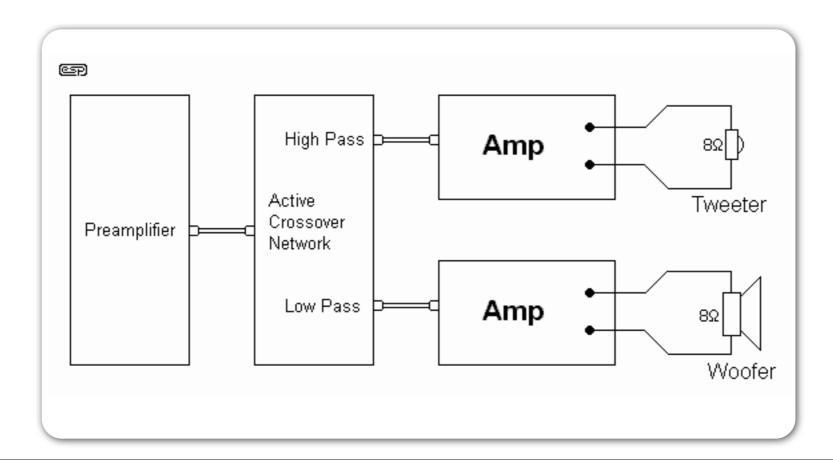- Uses "active" electronic circuitry (i.e. transistors, valves) to divide audio signal
- Each driver has own power amplifier
- Downsides: more expensive, complex
- Benefits: Lower distortion, greater flexibility of design, better control of frequency response, clearer highs, tighter lows



- Impedance standard is 8 Ω , but varies over frequency
- Most notable is the "bass hump" located at the system resonant frequency
 - Other dips/peaks due to inductive/capacitive elements in the crossover and drivers
- A bass-reflex enclosure
 - Significantly lowers the impedance at the **bass port** resonant frequency
 - But introduces a peak at the bass driver free-cone resonant frequency
- \bullet Other standard loudspeaker impedances include 4 Ω and 15 Ω
 - Lower resistance: Harder to drive, draw more current
 - Higher resistance: Easier to drive, draw less current → but less power

Sealed Enclosure

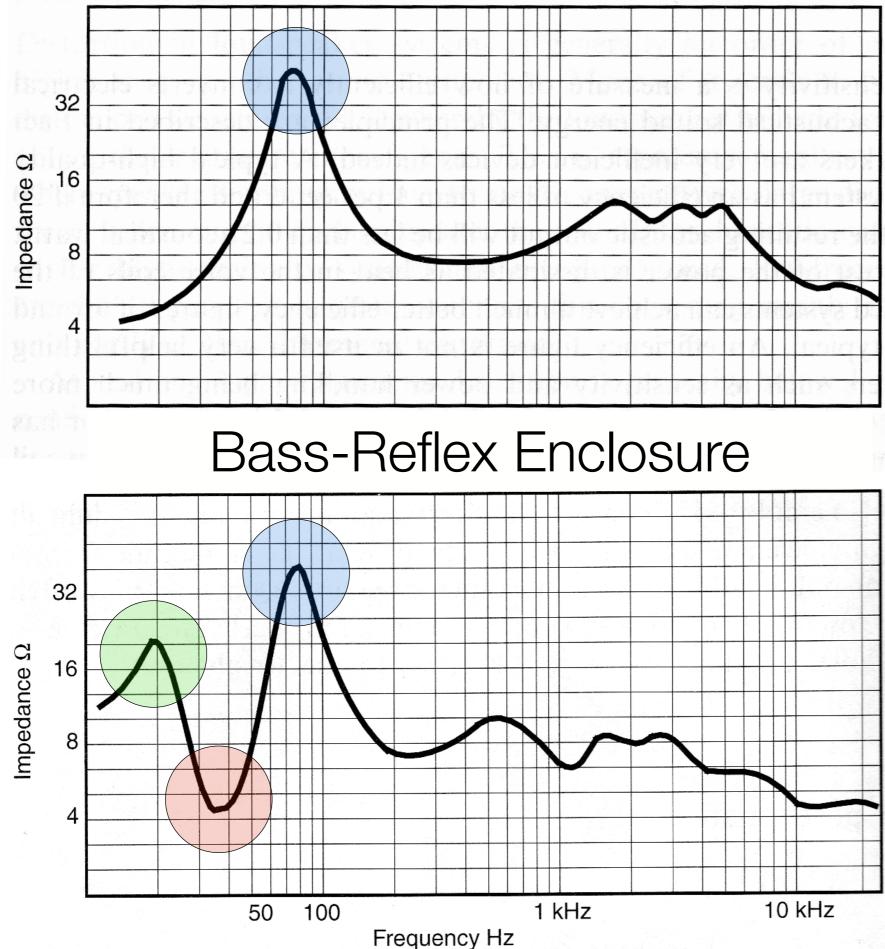

Cabinet Resonance 70 Hz

Bass Port Resonance 40 Hz

Bass Driver Free-cone Resonance 20 Hz

- Sensitivity: the effectiveness in converting electrical sound energy → acoustical sound energy
 - Most energy lost to heat, efficiency can range from 1% (typical hi-fi speaker) to 10% (horn-loaded system)
 - Standard measurement: 1 W input, 8 Ω resistance, SPL measurement 1m from speaker, i.e. 86 dB W⁻¹
- Distortion: tends to be 2nd-harmonic distortion producing frequencies octave higher.
 - At lower freq \approx 10%, mid-high freq \approx 1%
 - Usually not perceptually relevant

- Sensitivity: the effectiveness in converting electrical sound energy → acoustical sound energy
 - Most energy lost to heat, efficiency can range from 1% (typical hi-fi speaker) to 10% (horn-loaded system)
 - Standard measurement: 1 W input, 8 Ω resistance, SPL measurement 1m from speaker, i.e. 86 dB W⁻¹
- Distortion: tends to be 2nd-harmonic distortion producing frequencies octave higher.
 - At lower freq \approx 10%, mid-high freq \approx 1%
 - Usually not perceptually relevant

- Sensitivity: the effectiveness in converting electrical sound energy → acoustical sound energy
 - Most energy lost to heat, efficiency can range from 1% (typical hi-fi speaker) to 10% (horn-loaded system)
 - Standard measurement: 1 W input, 8 Ω resistance, SPL measurement 1m from speaker, i.e. 86 dB W⁻¹
- Distortion: tends to be 2nd-harmonic distortion producing frequencies octave higher.
 - At lower freq \approx 10%, mid-high freq \approx 1%
 - Usually not perceptually relevant

• Frequency Response

- Ideally: 20 Hz to 20 kHz, flat response
- Typical systems experience bass roll-off around 100 Hz
- A good system may have only ±3 dB fluctuation in the rest of the spectrum
- Power Handling: # watts speaker can handle before unacceptable distortion
 - Speaker rated at 30 W, sensitivity of 86 dB W⁻¹
 - 10 log(30 W/1 W) = 15 dB, 86 dB + 15 dB =101 dB SPL (1 m from speaker)
- Directivity: angle of coverage of loudspeaker output
 - As waveforms increase in frequency, they become smaller relative to the speaker and enclosure size
 - Harder to diffract around the back of the enclosure → foward-directional
 - Increase in off-axis phase cancellation → narrower spread

ିରୁ: ଜୁନ 250Hz 1111 1 ÷. 1212 2 Ŷ \$ Increasing forwarddirectionality

Ф.

ŝ

Ś

\$


 \ll

 $\mathcal{Q}_{\mathcal{X}}$

39

272

۶.,

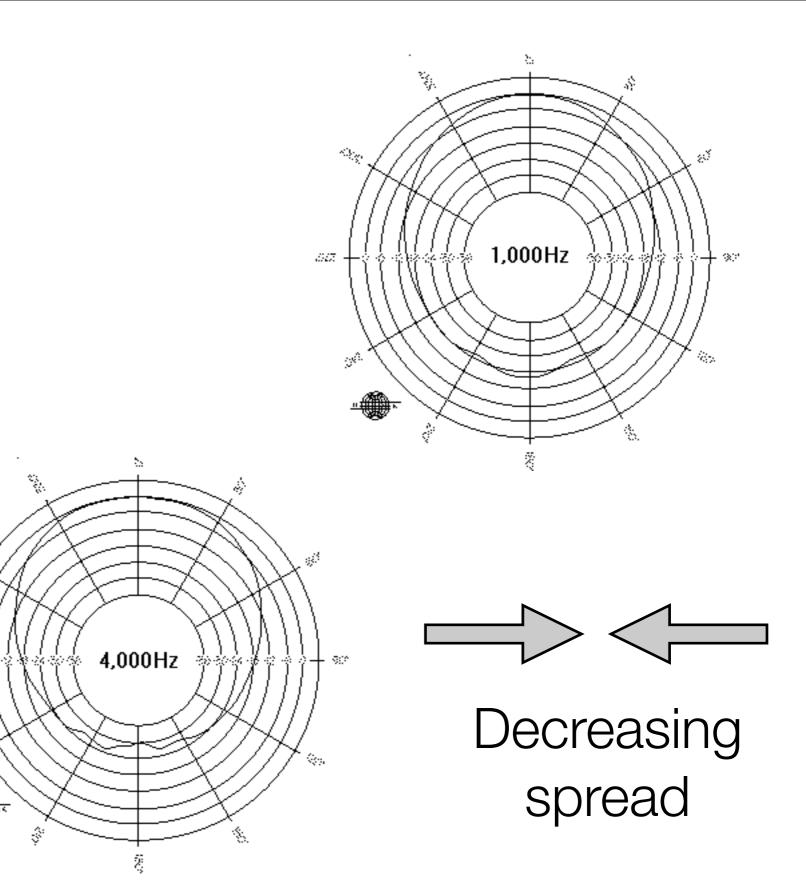

References

- Francis Rumsey and Tim McCormick (2002). "Sound and Recording: An Introduction", Focal Press.
 - Chapter 4: Loudspeakers
- Images and diagrams from:
 - Francis Rumsey and Tim McCormick (2002). "Sound and Recording: An Introduction", Focal Press.
 - http://hyperphysics.phy-astr.gsu.edu/hbase/audio/spk.html
 - http://electronics.howstuffworks.com/speaker.htm
 - http://www.mcsquared.com/speakers1.htm

GOVERNMENT OF TAMILNADU DIRECTORATE OF TECHNICAL EDUCATION CHENNAI – 600 025

STATE PROJECT COORDINATION UNIT

Diploma in Electronics And Communication Engineering

Course Code: 1040 M - Scheme

e-TEXTBOOK on TELEVISION ENGINEERING

VI Semester DECE

Convener for ECE Discipline:

DR.M.JEGANMOHAN, M.E., MBA., Ph.D., (Management)., Ph.D., (Engg)., M.I.S.T.E.,

Principal, Govt. Polytechnic College, Uthappanaickanoor, Usilampatti, Madurai – 625 536

Team Members for Television Engineering

1. Mrs.R.Mini,M.E.,

HOD/ECE, Latha Mathavan Polytechnic College, Kidaripatti,Madurai-625301

2. Mrs.R.Menaka, M.E.,

Senior Lecturer/ECE, Latha Mathavan Polytechnic College, Kidaripatti,Madurai-625301

3. Mrs.R.Rajameenal,B.E.,

Lecturer/ECE, Latha Mathavan Polytechnic College, Kidaripatti,Madurai-625301

Validated by

Dr. Mohamed Mansoor Roomi, M.E., Ph.D

Asst Professor(sel grade)/ECE department, Thiagarajar college of Engineering, Madurai – 625 015

GOVERNMENT OF TAMILNADU DIRECTORATE OF TECHNICAL EDUCATION CHENNAI – 600 025

STATE PROJECT COORDINATION UNIT

Diploma in Electronics And Communication Engineering

Course Code: 1040 M - Scheme

e-TEXTBOOK on TELEVISION ENGINEERING

VI Semester DECE

Convener for ECE Discipline:

DR.M.JEGANMOHAN, M.E., MBA., Ph.D., (Management)., Ph.D., (Engg)., M.I.S.T.E.,

Principal, Govt. Polytechnic College, Uthappanaickanoor, Usilampatti, Madurai – 625 536

Team Members for Television Engineering

1. Mrs.R.Mini,M.E.,

HOD/ECE, Latha Mathavan Polytechnic College, Kidaripatti,Madurai-625301

2. Mrs.R.Menaka, M.E.,

Senior Lecturer/ECE, Latha Mathavan Polytechnic College, Kidaripatti,Madurai-625301

3. Mrs.R.Rajameenal,B.E.,

Lecturer/ECE, Latha Mathavan Polytechnic College, Kidaripatti,Madurai-625301

Validated by

Dr. Mohamed Mansoor Roomi, M.E., Ph.D

Asst Professor(sel grade)/ECE department, Thiagarajar college of Engineering, Madurai – 625 015

34081 – TELEVISION ENGINEERING

UNIT 1-TELEVISION FUNDAMENTALS

Monochrome TV: Basic block diagram of Monochrome TV transmitter and Receiver – Scanning process – horizontal, vertical and sequential scanning – flicker – interlaced scanning (qualitative treatment only) – need for synchronization – blanking pulses – Aspect ratio– Resolution – Types – vertical and horizontal resolution – video bandwidth – composite video signal (CVS)– CVS for one horizontal line – Definitions for Vertical sync pulse, Serrated vertical pulse, Equalizing pulse – Positive & Negative modulation - TV Standards – List of Types of TV standards. Color T.V. Fundamentals: Additive mixing of colors –Types – color perception – Chromaticity diagram – Definition for Luminance, Hue Saturation and Chrominance Formation of chrominance signal in PAL system with weighting factors.

UNIT 2-CAMERA AND PICTURE TUBES

CAMERA TUBE: Characteristics – Types of camera tube – working principle of Vidicon and Plumbicon camera tube, CCD camera – Video processing of camera pick up signal – Block diagram and Principle of working of color TV camera tube.

PICTURE TUBE : Construction and working of Monochrome picture tube – screen phosphor – screen burn – Screen Persistence - Aluminized screen – Types of color picture tubes -construction and working principle of Delta gun and Trinitron Color picture tubes – Automatic degaussing.

UNIT 3-TELEVISION TRANSMITTER

Types –Comparison - Principle – Block diagram of Low level IF Modulated TV transmitter –Visual Exciter – Aural Exciter – principle of working of CIN Diplexer –Block diagram of color TV transmitter – color compatibility – PAL color coder –functional blocks and working of each block – Merits and demerits of PAL system.

UNIT 4- TELEVISION RECEIVER

Block diagram of Monochrome Receiver – functions of each block – Need for AGC – Advantages of AGC – Video amplifier requirements –High frequency & Low frequency compensation – Block diagram of PAL color Receiver – Need for sync separator – Basic sync separator circuits– Vertical sync separation & Horizontal sync separation – AFC – Need for AFC – Horizontal AFC – Hunting in AFC – Anti Hunt network.

UNIT 5-ADVANCED TELEVISION SYSTEMS

Block diagram of a digital color TV receiver – Remote control IR transmitter and receiver – Closed Circuit TV system–Applications of CCTV – scrambler – necessity - basic principle- types Descrambler block diagram - Telecine equipment – Digital CCD Telecine system -Introduction to High definition TV (HDTV) and 3DTV. Blue Ray Disc(BD)- The DVD player – Block diagram- Desirable Features & outputs of DVD players-DVD player Models - USB flash drive(pen drive).

CONTENTS

SYLLABUS

UNIT – I

UN11 - 1	
TELEVISION FUNDAMENTALS	5-26
UNIT – II	
CAMERA AND PICTURE TUBES	27-42
UNIT – III	
TELEVISION TRANSMITTER	44-53
UNIT – IV	
TELEVISION RECEIVER	54-72
UNIT – V	

ADVANCED TELEPHON	E SYSTEMS	73-88
-------------------	-----------	-------

UNIT – I TELEVISION ENGINEERING

1.1 TV FUNDAMENTALS


INTRODUCTION:

Television means Tele + Vision, i.e., Television is used to see the picture telecast from long distance.

In TV transmission both picture and sound are transmitted. For picture AM Modulation is used and for sound FM modulation is used.

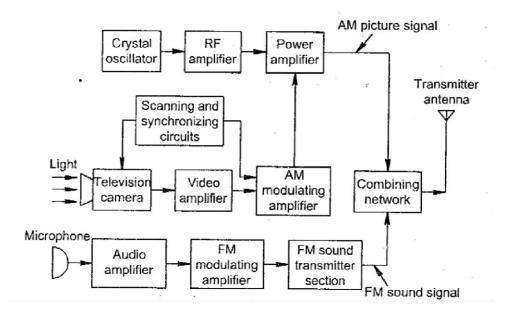1.1.1 BASIC BLOCK DIAGRAM OF TV TRANSMISSION:

The simplified block diagram of a Monochrome TV Transmitter is shown.



It consists of Television Camera, Video amplifier, AM Modulating amplifier, Audio amplifier, FM Modulating amplifier, FM sound transmitter, Crystal oscillator, RF amplifier, Power amplifier, Scanning and Synchronizing Circuits, Combining network, Transmitting antenna and Microphone.

• TELEVISION CAMERA:

Its function is to convert optical image of television scene into electrical signal by the scanning process.

• VIDEO AMPLIFIER:

Video amplifier amplifies the video signal.

• AM MODULATING AMPLIFIER

The video signals are amplified by the modulating amplifier to get the modulated signal.

• AUDIO AMPLIFIER

Audio amplifier amplifies the electrical form of audio signal from the microphone.

• FM MODULATING AMPLIFIER:

Sound signal from audio amplifier is frequency modulated by FM Modulating amplifier.

• FM SOUND TRANSMITTER:

FM modulated amplified signal is transmitted through this FM sound transmitter to transmitting antenna through the combining network.

• CRYSTAL OSCILLATOR:

Crystal Oscillator generates the allotted picture carrier frequency.

• **RF AMPLIFIER:**

RF amplifier amplifies the picture carrier frequency generated by crystal oscillator to required level.

• POWER AMPLIFIER:

Power amplifier varies according to the modulating signal from AM modulating amplifier.

1.1.2 SCANNING AND SYNCHRONIZING CIRCUITS

Scanning is the process where picture elements are converted into corresponding varying electrical signal

COMBINING NETWORK

Combining network is used to isolate the AM picture and FM sound signal during transmission.

TRANSMITTING ANTENNA:


Transmitting antenna receives the AM picture signal and FM sound signal from combining network for radiation as electromagnetic waves.

MICROPHONE:

Converts sound associated with picture being televised into proportionate electrical signal.

1.1. 3 SIMPLE BLOCK DIAGRAM OF TV

RECEPTION BASIC MONOCHROME TV

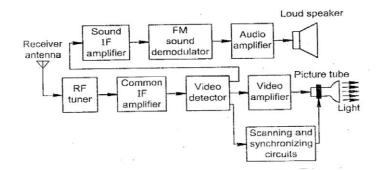

RECEIVER

Block diagram of a monochrome TV receiver is shown. It consists of RF Tuner, Receiver antenna, common IF amplifier, video detector, video amplifier, scanning and synchronizing circuits, sound IF amplifier, FM Sound demodulator, Audio amplifier, Loud Speaker, Picture tube.

RF TUNER:

RF Tuner selects the desired channel frequency band from the receiving antenna.

RECEIVER ANTENNA:

Receiver antenna intercepts the radiated RF signals and sends it to RF Tuner.

COMMON IF AMPLIFIER:

There are 2 or 3 stages of IF amplifiers.

VIDEO DETECTOR:

Used to detect video signals coming from last stage of IF amplifiers.

VIDEO AMPLIFIER:

It amplifies the detected video signal to the level required.

SCANNING AND SYNCHRONIZING CIRCUITS:

Scanning is the process where picture elements are converted into corresponding varying electrical signals.

SOUND IF AMPLIFIER:

Detected audio signal is separated and selected for its IF range and amplified.

FM SOUND DEMODULATOR:

FM Sound signal is demodulated in this stage.

AUDIO AMPLIFIER:

FM demodulated audio signal is amplified to the required level to feed into the loud speaker.

LOUD SPEAKER:

Loud Speaker converts FM demodulated amplifier signal associated with picture being televised into proportionate sound signal.

PICTURE TUBE:

In picture tube the amplified video signal is converted back into picture elements.

SCANNING:

Scanning is the process used to convert the optical into electrical signal. Fastest movement of electron beam on the image is called scanning.

1.2 SCANNING PROCESS:

Scanning process is a technique similar to reading of written information on a page starting at the top left and processing line by line downwards to the end at the bottom right.

Scanning is done frame by frame. Each frame consists of 625 horizontal lines. Each frame is scanned at a rate of 25 frames / sec.

Scanning types,

1.Horizontal Scanning

2.Vertical Scanning

3.Sequential (or) Progressive Scanning


4.Interlaced Scanning.

1.3 HORIZONTAL SCANNING (H-SCANNING)

Movement of electron beam from left to right on the screen is known as trace period. When the beam returns quickly from right to left is called retrace or fly back.

Trace and retrace period together in horizontal direction is known as HorizontalScanning.

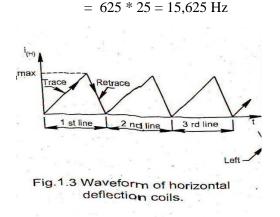
Horizontal frequency = Number of lines in a Frame * Number of frames/sec



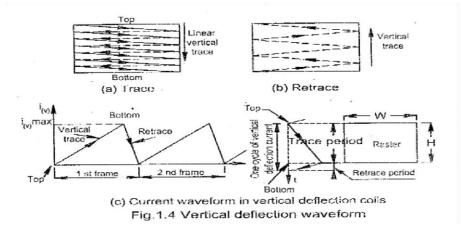1.4 VERTICAL SCANNING (V – SCANNING)

Movement of electron beam in vertical direction. Movement of electron beam from top to bottom is called trace. Movement of beam from bottom to top of the frame is called retrace.

Vertical frequency = Number of frames $/\text{sec} = 25 \text{ H}_{Z}$



1.5 SEQUENTIAL (OR) PROGRESSIVE SCANNING:

Sequential or progressive Scanning is the process in which both horizontal and vertical directions are scanned simultaneously to provide complete pictures. Horizontal lines are scanned one by one. So complete picture will be scanned through this type.

1.6 FLICKER:

The sensation produced by incident light on the nerves of the eyes retina does not cease immediately. It persists for about 1/25th of a second (.062 Sec.) This storage characteristic is called as persistence of vision of eye.

Flicker means if the scanning rate of picture is low, the time taken to move one frame to another frame will be high. This results in alternate bright and dark picture in the screen. This is called "Flicker".

To avoid flicker, the scanning rate of the picture should be increased i.e. 50 frames/Sec.

1.7 INTERLACED SCANNING:

To reduce flicker, the vertical scanning is done 50 times per second in TV system. However only 25 frames are scanned per sec.

In interlaced scanning the 625 lines are grouped into two fields. They are called as even field and odd field. Each field contains 312.5 lines. Even field contains even numbered lines and odd field contains odd numbered lines.

During first scanning line numbers 1, 3, 5 are scanned. During next scan, line numbers 2, 4, 6.... are scanned. That is alternate lines are scanned every time. So to cover each frame, scanning is

done two times. Here the vertical rate of scanning is increased twice. So it will reduce flicker.

Interlaced scanning is shown. Now the vertical frequency is 50 Hz. But there is no change in horizontal frequency.

Horizontal frequency = Number of lines in a Frame * Number of frames/sec

$$= 312.5 * 50 = 15,625 \text{ H}_{Z}$$

1.7.1 SCANNING PERIODS:

Useful video signals are obtained during the trace period only. So the trace time is larger than the retrace time.

HORIZONTAL:

Tracing = 52 μ s

Retracing = $12 \,\mu s$

Total time period = $64 \ \mu s$.

VERTICAL:

Tracing = 18.722ms

Retracing = 1.27ms

Total time period = 20ms. Horizontal frequency = 15,625 H2

Horizontal time = 1/T = 1/15,625 = 64s.

Vertical Frequency = 50 Hz Vertical Time

= 1/50 = 20 ms

Number of Horizontal lines lost during Vertical retrace = Vertical retrace time


One horizontal time

$$\frac{1.28 \text{ ms}}{648} = 20 \text{ lines}$$

So 20 lines are lost per field and in total 40 horizontal lines are lost during the scanning of each Frame.

=

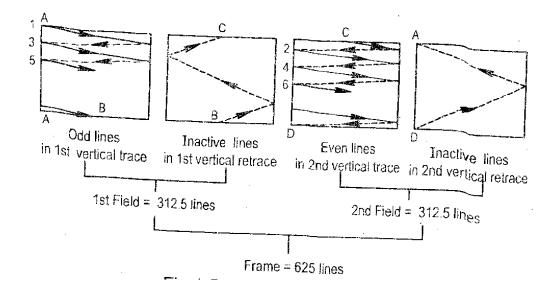Active number of lines (Na) = 625 - 40 = 585 lines.



Detailed structure of interlaced scanning is shown. This is also called as 2: 1 interlaced scanning.

1.8 NEED FOR SYNCHRONIZATION:

At any time the same co-ordinate will be scanned by the electron beam in both the camera tube and picture tube. Otherwise distorted picture will be seen on the screen. So synchronization between the transmitter and receiver is needed. For that we are using Sync pulses.

At the receiver side these pulses are identified, separated and used for triggering the oscillator

circuit.

Horizontal Sync pulse time period	$=$ 4.7 μ Sec.
Horizontal Sync pulse Frequency	=15,625 Hz.
Vertical Sync pulse time period	$= 160 \mu \text{Sec.}$
Vertical Sync pulse frequency	= 50 Hz.

1.9 BLANKING PULSES :

The video signal obtained during the horizontal and vertical retrace are not useful one. So there is no need to transmit them.

So to make the retrace signal invisible we are using blanking pulses.During horizontal blanking, horizontal retrace is blanked. This is 19% of horizontal time period.

Horizontal blanking = $64 * .19 = 12 \mu$ Sec.

Remaining 52 v Sec contains picture information and this is called as active line period. For a single line one blanking pulse is needed. So for 1 sec, 15,625 blanking pulses are needed.

In vertical retrace, for one frame two vertical blanking pulse is needed. So in 1 sec, 25 frames are scanned and so 50 V blanking pulses are needed.

Vertical blanking = 20 H = $20 \times 64 \mu$ Sec. = 1280μ Sec.

1.10 ASPECT RATIO:

The ratio between width to height of rectangle picture frame adopted in TV system is known as aspect ratio.

Aspect ratio = $\frac{\text{Width}}{\text{Height}}$ = $\frac{4}{3}$ or 4: 3

Reasons for having this ratio is,

- 1. Most of the objects are moving only in horizontal plane.
- **2.** Our eye can see the movement of object comfortably only in horizontal plane than in vertical plane.
- 3. The frame size of motion picture already existing is having the aspect ratio of 4 : 3

1.11 HORIZONTAL AND VERTICAL RESOLUTION

The ability of the image reproducing system to resolve the fine details of the picture distinctly in both horizontal and vertical direction is called as "resolution".

• VERTICAL RESOLUTION:

The ability to resolve and reproduce fine details of picture in vertical direction iscalled as Vertical resolution.

Vertical resolution (VR) = No. of active lines * Kell factor or resolution factor

= Na * k= 585.69 = 400Lines

• HORIZONTAL RESOLUTION :

The ability of the system to resolve maximum number of picture elements along the scanning determines the horizontal resolution.

Horizontal resolution = VR * Aspect ratio = 400 * 4/3= 534 Pixels

1.12 VIDEO BANDWIDTH :

Video Bandwidth = One horizontal line

One horizontal line tracing

$$\frac{267}{52 * 10^{-6}} = 5 \text{ MHz}$$

Video Bandwidth = Horizontal Resolution = 534 = 5 MHz 2* One Horizontal line scan $2*52*10^{-6}$

1.13 POSITIVE AND NEGATIVE TRANSMISSION:

=

POSITIVE TRANSMISSION (POSITIVE MODULATION)

In this type of transmission, if the brightness of picture increases, then video signal amplitude also increases. So peak white corresponds to 100% modulation level. And sync level corresponds to minimum level.

• NEGATIVE TRANSMISSION (NEGATIVE MODULATION)

In negative transmission, if the brightness of the picture increases, then video signal amplitude decreases. So the peak white corresponds to near zero level.

1.13.1 ADVANTAGES OF NEGATIVE TRANSMISSION:

 Due to noise pulses, the video signal amplitude increases and produce black dots on the screen. This will create much low disturbance compared to white dots produced in positive modulation.
 Since most of the video signal are white, the video signal is low and transmitted power is less.
 The sync pulse level at 100% are used at the receiver as AGC reference levels.


1.13.2 COMPARISON OF POSITIVE AND NEGATIVE TRANSMISSION

POSITIVE MODULATION	NEGATIVE MODULATION	PARTICULARS
White dots	Black dots	Noise
High	Low	Transmitting – power
Low	High	Efficiency
100%	10 %	White level
25%	75 %	Black level
28 %	78 %	Blanking level
0 %	100 %	Syno pulse level

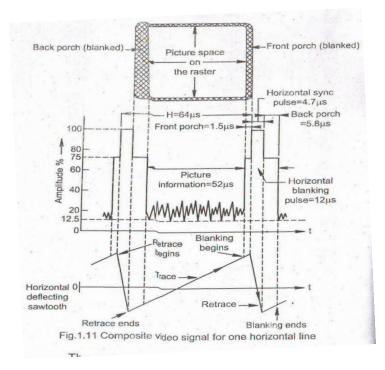1.14 COMPOSITE VIDEO SIGNAL (CVS)

CVS consists of,

- Camera signal corresponding to the picture to be transmitted.
- Blanking pulses to made the retrace invisible.
- Sync pulse to synchronize the transmitter and receiver.



Details, Total amplitude is 100%

Y-axis Amplitude:

Extreme White level = 10%Tolerance $\pm 2.5\%$

Black level = 70 % amplitude. Blanking retrace period amplitude increase to 70 %. But actually, blanking pulse of amp 75 % used

Blanking Pulse = 75% amplitude Sync Pulse = 75% to 100% amplitude

X- axis Time details

Horizontal tracing time	=	52 v Sec.
Horizontal retracing time	=	12 v Sec.
H – Sync pulse time	=	4.7 v Sec.

Difference between black level and blanking level is called as Pedestal.

Average value of video signal is DC component. Distance between DC Component and pedestal is called as pedestal height.

• FRONT PORCH:


Rising edge of sync pulse and blanking does not coincide. The time difference between the raising edge of sync and blanking pulse is called as 'Front Porch''. It is 1.5 vs, \pm .34 is tolerance. If front porch is not their sync. Pulse is build at varying fixed level and varying brightness level.

• BACK PORCH:

Difference between the failing edge of sync pulse and blanking pulse is called back porch.

- 1. It allows horizontal fly back.
- 2. Used as reference level to preserve DC component.
- 3. Used to send colour burst signal in colour Transmission.
- 4. Used as AGC reference level in receiver circuits.

1.15 VERTICAL SEPRATED SYNC PULSE:

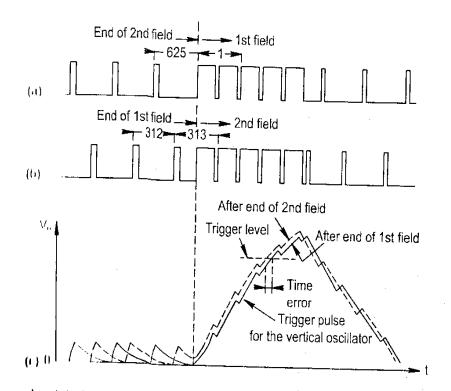

Hig 1 12 Integrating waveforms (a) pulses at the end of 2nd (even) field
 (b) pulses at the end of 1st (odd) field (c) integrator output.

Here, vertical sync pulse of duration 160 s is divided into 5 pulses of duration 32 that too 4.7 on and 27.3 OFF period. This process is called as "serration". This 4.7 sON is separated to have horizontal synchronization and it is given to differentiator the serrated pulses are given to integrator to get it as a single sync pulse.


But here for odd and even fields their occurs time error due to trigger level in both fields. Because of charging and discharging of capacitor in the integrator.

The time error due to trigger level of fields is called as "Half line discrepancy" occurs. To avoid half line discrepancy we are adding the equalizing pulses.

Time error is because for second field in capacitor residual potential is zero. But for odd field, charging occurs of first field i.e., 312.5 lines. So there is some residual voltage and half line discrepancy occurs.

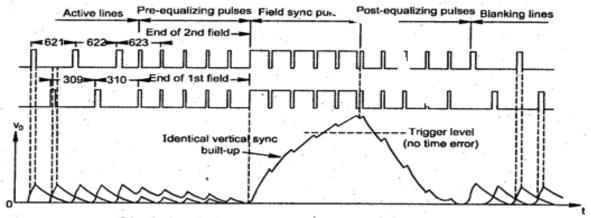1.16 EQUALISING PULSES:

To avoid half line discrepancy due to time error in trigger level, equalizing pulses are used.



Identical vertical sync voltage built-up across the integrating capacitor

These pulses are having duration of 2.3 vsec ON period and 27.4 vsec OFF period. Due to these pulses time error is completely avoided. The pulses added before the vertical sync pulse are called as "pre-equalising pulse and that added after the vertical sync pulses are called as post equalising pulses. Since the pulses are having a short duration 2.3 vsec the capacitor is charged to only small value. So before the start of vertical sync, during both field the capacitor is discharged to zero level.

Similarly due to post-equalising pulses this capacitor is discharged quickly. If the discharge is slow than the trailing edge, of integrator may false trigger the oscillator. The structure of pre and post equalising pulses are shown.

1.17 LIST OF TV STANDARDS

- i) FCC (Federal Communication Commission
- ii) NTSC (National Television system Committee)
- iii) CCIR (International Radio Consulative Committee)
- iv) SECAM (Sequential Couleures A Memory)

1.18 COLOUR TV FUNDAMENTALS:

In system we are sending only the luminance information. But in colour system we have to send information about the colours also. All colour TV system are based on the principle of our eye. Here wavelength unit is Arm strong. Visible spectrum – 4000 A^{\circ} to 7000 A^{\circ}.

 $1A^{o} = 10^{-10}m$ $1nm = 10A^{o}$


The three basic colors are called as primary colors. They are Red, Green and Blue. To get different color shading we have to mix primary colors. We have two types of mixing

- 1. Additive Mixing
- 2. Subtractive Mixing.

1.19 ADDITIVE MIXING:

In this method two or three primary colours are mixed together to form a new color. By mixing primary colours with different intensities we can obtain all types of colours.

Fig shows the method of additive mixing. By mixing 30% Red, 59% Green and 11% blue we can get white color

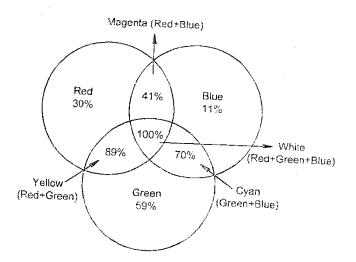

 $Y=0\%\,+\,59\%9{+}11\%\,B$

Red + Blue = Magenta (41%).

Blue + Green = Cyan (70%)

Red + Green = yellow (89%)

1.20 COMPLEMENTARY COLOUR:

Color obtained by mixing only two primary colours is called as complementary colours.

Primary	Comple	ementary
Red + Green	=	Yellow
Red + Blue	=	Magenta
Blue + Green	=	Cyan

1.21 SUBTRACTIVE MIXING.


In Subtractive mixing, the reflecting properties of colour pigments are used. A colour pigment can absorb all the colour wavelength except its characteristic colour wavelength. Its characteristic colour frequency alone is reflected. If we are mixing two or three colour pigments, then a color wavelength common to them only reflected. This method of mixing is generally used in colour printing and colour painting. By mixing primary colours, black colour is got.

Different colours are obtained by subtracting primary and secondary colours from white. So this is called as subtractive mixing.

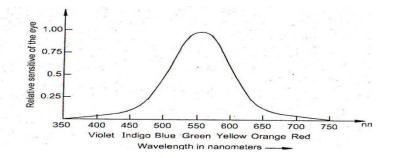1.22 COLOUR PERCEPTION:

The retina on the backside of our eye has light sensitive organs. They can be able to sense the light variations. Also the retina is connected to optical centre of the brain optical nerves.

We have two types of light sensitive organs. They are called rods and cones. Rods are used to identify brightness variations. Cones are used to identify color information. The colours are transferred to optical nerves. They are then mixed together to identify the original colour.




1.23 CHROMATICITY DIAGRAM:

Chrominance or chromaticity diagram is a graphical representation of primary colours and all other colours in a space co-ordinate. Based on principle of tristimulus value, white color is formed by mixing 30% red, 59% green and 11% blue.

Below Fig is a two dimension graph representing hue and saturation on x-y plane. In 3D representation 2 axis is used to identify the brightness of the color.

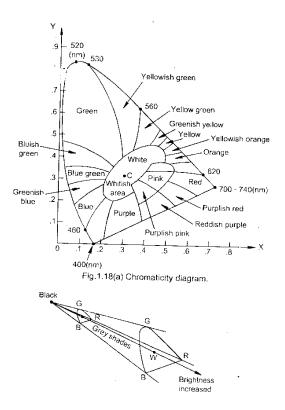Chromaticity diagram is in shape of horse shoe. On the three corners we have primary colours and on perimeter different colours are available. On moving towards centre pure colours are mixed with white and desaturated. Point 'C' represents white color. This point is at co-ordinate of x = 31, y = .32. Sunlight, sky light and day light are all different forms of white light.



1.23.1 ADVANTAGES:

Using this diagram we can identify the color obtained by additive mixing process. If bright increases, Z axis also increase and chrominance diagram becomes enlarged in 3D representation.

1.24 LUMINANCE, HUE AND SATURATION:

All the colours are having the following three characteristics. 1. Hue, 2. Saturation, 3.Luminance.

• LUMINANCE:

It is the amount of light intensity as perceived by the eye regardless of the colour. It is also called as brightness signal, y signal, and white signal.

• HUE (TINT)

It is the predominant spectral colour. For example, green leaf has a green hue and red apple has red hue.

• SATURATION:

It will indicate the spectral purify of colour. i.e., it will indicate how much white mixed with a particular colour.

• CHROMINANCE:

Hue and Saturation together are called as chrominance or chroma signal.

1.25 FORMATION OF CHROMINANCE SIGNAL IN PAL SYSTEM WITH WEIGHTING FACTOR:

PAL system u or v signals.

Es: Yellow colour,

$$y = R + G$$

 $U = -.29 + (-.15)$
 $= -.44$
 $V = .61 + (-.52) = .09$

Yellow colour chrominace signal

$$C = \sqrt{u^{2} + v^{2}}$$

= $\sqrt{(-.44)^{2} + (.09)^{2}}$
C = $\pm .44$

Yellow colour y signal value,

$$y = R + G$$

= .3 + .59 = .89

Table of PAL system.

S.No.	Colour	Basic Colour	Y	U	V	С
1.	White	R1G1B	1	0	0	0
2.	Yellow	R14	.89	44	.09	±.44
3.	Cyan	G1B	0.7	.15	6	±.63
4.	Green	G	0.59	29	52	± .59
5.	Magenta	R. 4	.41	.29	.51	±.59
6.	Red	R	.3	15	.61	±.63
7.	Blue	В	.11	.44	.1	±.44
8.	Black	-	0	0	0	0

REVIEW QUESTIONS

PART-A

- 1. Define television (TV) or what is TV?
- 2. Define scanning.
- 3. Define scanning process.
- 4. Mention the value for horizontal frequency.
- 5. Mention the value for vertical frequency.
- 6. Define flicker.
- 7. How many number of horizontal lines lost during vertical retrace?
- 8. How many active lines are there in interlaced scanning?
- 9. List the value for H-sync pulse period.
- 10. List the value for V-sync pulse period.
- 11. Mention the H-sync pulse frequency.
- 12. Mention the v-sync pulse frequency.
- 13. Mention the H-blanking period.
- 14. Mention the v-blanking period.
- 15. What is the vertical resolution factor?
- 16. Define interlaced scanning.
- 17. Define resolution.
- 18. Mention video bandwidth frequency.
- 19. Define front porch.
- 20. Define back porch.
- 21. What is vertical serrated sync pulses?
- 22. What is serration?
- 23. What is half line discrepancy error?
- 24. Define equalizing pulse.
- 25. List some TV standards.
- 26. What is additive mixing?
- 27. What is subtractive mixing?
- 28. What is color perception?
- 29. List out the advantage of chromaticity.
- 30. Define luminance.
- 31. Define Hue (tint).
- 32. Define saturation.

PART-B

1.Define video bandwidth.

2.Compare different TV standards.

3. What is horizontal scanning?

4. What is vertical scanning?

5.Explain sequential or progressive scanning.

6.Define blanking pulses.

7.Define aspect ratio.

8.Explain the reason for having this ratio as aspect ratio?

9.Define horizontal and vertical resolution.

10.Define positive and negative transmission.

11.Mention the advantage of negative transmission.

12.Compare positive and negative transmission.

13.Explain CVS?

PART - C

1. With neat block diagram explain the working of TV transmitter.

2. With neat block diagram explain the working of TV receiver.

3. Explain interlaced scanning in detail.

4. Explain the CVS for one horizontal line in detail.

5. With neat block diagram explain the working of vertical serrated sync pulses in detail.

6. With neat block diagram explain the working of equalizing pulses in detail.

7. Explain additive mixing.

8. Explain subtractive mixing.

9. Explain the chromaticity diagram in detail.

UNIT II CAMERA AND PICTURE TUBES

2.1 CAMERA TUBES:

INTRODUCTION:

A camera tube is an important unit that is used to convert the optical image into electrical signal.

T.V. Camera tubes use photo emission or photo conduction principle for converting the optical source.

2.2 CHARACTERISTICS OF CAMERA TUBES:

1. LIGHT TRANSFER CHARACTERISTIC:

It gives the relation between light falling on the camera tube and the electrical current produced.

2. SPECTRAL RESPONSE:

It is the ability of the camera tube to response equally to all colours like the human eye.

3. SENSITIVITY:

Good camera tubes have high sensitivity. It is the ability to respond for even very low illumination.

4. DARK CURRENT:

Even if there is no illumination on the face plate of a camera tube, there is a small amount of signal, current flow in the output circuit. This current is called 'Dark Current'.

5. LAG CHARACTERISTICS:

It is the inability of photo sensitive layer to follow faster changes in illumination on the camera tube.

6. **RESOLVING POWER:**

Number of black and white lines of resolution in the picture increased the signal current produced is not able to full changes in the black and white level.

2.3 TYPES OF CAMERA TUBES:

1. BASED ON PRINCIPLE:

Three photo electric effects are used for converting variations of light intensity electrical variations.

- 1. Photo emissive camera tubes.
- 2. Photo conductive camera tubes.
- 3. Photo voltaic camera tubes.


2. BASED ON TARGET PLATE :

1. Videocon 2. Plumbicon 3. Saticon 4. Newicon 5. Chalnicon 6. Silicon diode array.

2.4 VIDICON CAMERA TUBE

A small size camera tube that operate on the principle of Photo Conductivity.

• CONSTRUCTION:

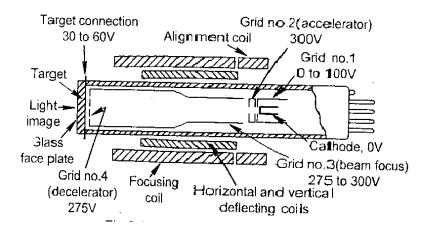

TARGET PLATE OR FACE PLATE:

It consists of thin photo conductive layer of either selenium or antimony. This is deposited on transparent conducting film coated on inner surface of face plate. This conductive coating is known as signal electrode or plate.


SCANNING SECTION:

Beam that emerges from the electron gun is focused on the surface of photo conductive layer by combined action of uniform magnetic field of an external coil and electrostatic field. Deflection is obtained by vertical and horizontal deflecting coils.

2.4.1 ELECTRON GUN SECTION:

Heater, Cathode, Control grid, focussing coils and accelerating anodes form the electron sun section. Focussing coils are used to focus e^{-n} beam.

• WORKING:

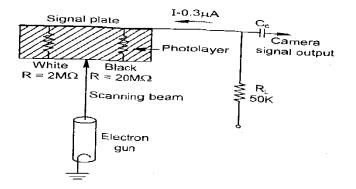


with light focused, the photon energy enables more electrons to go to conduction band and this reduces resistivity. When bright light falls on any area of photo conductive coating, resistance across the thickness of that portion gets reduced to about $2 * 10^6$. Thus with target, each point on sun side of photo layer assumes a certain potential with respect to dc supply, depending on its resistance to signal plate.

As electrons beam scans, sufficient number of electrons on photo layer reduce the potential towards zero potential. Remaining electrons are not deposited on target, return back and not utilized. However sudden changes in potential, while scan causes current flow producing varying voltage across

 R_L . The current in R_L and Voltage_{se} across R_L are directly proportional to light intensity variations on the scene. Video signal developed across R_L is very small in amplitude. It is therefore amplified by amplifiers it leaves the camera tube.

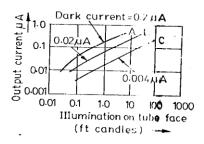2.4.2 LIGHT TRANSFER CHARACTERISTICS:

Each curve represents the characteristic curve of a particular dark current. By adjusting the target voltage, both dark current and sensitivity are increased.



ADVANTAGES:

- 1. High resolution
- 2. Long life, small size and low cost.
- 3. Gamma Cancellation circuit is not necessary.


DISADVANTAGES:

- 1. High dark current.
- 2. Poor sensitivity
- 3. Image lag is more.

2.5 PLUMBICON

Many of the drawbacks of videocon tube are removed in plumbicon tube. It has very fast response and produces high quality pictures even at low light. It has small size and light weight.

• CONSTRUCTION:

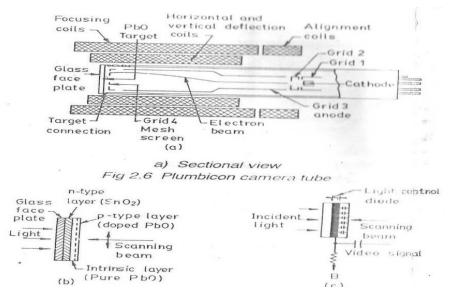

Construction is similar to vidicon except target plate and output signal.


The target plate acts as a PIN semi conductor diode. The inner surface of glass plate is coated with a transparent conducting layer of S_{no2} .

• **PRINCIPLE OF WORKING:**

In plumbicon each element is considered as a capacitor in series with a reverse biased light dependent diode.

The conductive coating of Sno2 is connected to a supply of 40V through a load resistor. The PIN diode is reverse biased and its resistance is high. So charge on capacitor is not discharged and no current flow. Whenever light is falling on target plate, the resistance of PIN diode decrease due to photo excitation of semi conductor junction. The current and output voltage taken across RL is directly proportional to incident light intensity on target plate.

• LIGHT TRANSFER CHARACTERISTICS:

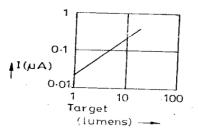

Output current Vs target illumination is shown. Here slope of response curve is higher than videocon tube. Spectral response is very close to that of human eye.

• ADVANTAGES:


1. Reduced lag. 2. Higher sensitivity. 3. Medium size and compact.

• DISADVANTAGES

1. High Cost 2. Spectral response in poor for red colour.

	COMPARSION OF VARIOUS CAMERA TUBES					
S.N	PARAMETERS	VIDEOCON	PLUMBICON	SATICON	NEWVICON	CHALNICON
S.N 1. 2.	Photo electric conversion Material used in Target plate	Photo conductive Antimony or selenium compound	Photo conductive Tin oxide SnO2 lead mono oxide + Pure PbO2	Photo conductive Selenium + Arsenic + Tellurium	Photo conductive Tin oxide + 2nse+znTe + CdTe+Sb2S3(a imoni tri sulphate)	Photo Tin oxide + Cdse + cdsep3+As2s3
3.	Sensitivity	Good	Better	Good	Very high	Good
4.	Dark Current	High	Low	Low	High	Low
5.	Speed	Severe lag	Reduced Lag	High Lag	High lag	High Lag
6.	Resolution at 400 line (5MHz)	55 %	40-50%	High	High	High
7.	Spectral Response	Good	Poor in Red	Good	Good	Very Good
8.	Gamma	0.4 to 0.9	0.9 to 1	0.9 to 1	_	_
9.	Operation	Simple	Simple	Simple	Setting the target voltage is tedious.	Simple
10.	Cost	Cheaper	Costlier	Low cost	Medium	Medium
11	Size	Small compact	Medium	Medium	Medium	Medium

2.6 CCD IMAGE SENSOR

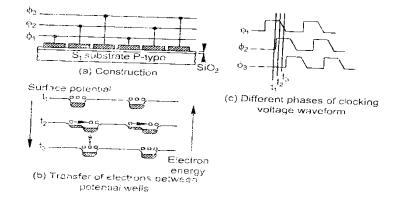

These sensors are operating on the principal of charge coupled devices. Here a large number of CCD array are formed together to construct the image plate.

P-type substrate, a thin layer of silicon dioxide is formed. Then by masking and etching process, an array of metal electrodes are formed. Large number of smalls MOS capacitors are formed on the surface of the substrate. By the application of small positive potential at the gate, every third electron is connected to common conductor.

The spot under each metal electrode serve as a light sensitive element. These electrons are collected in the potential well and represent the optical image. The charge stored in one element is transfered to next element by applying more positive voltage to the next gate.

The charge movement takes place. Like this the charge is moved to the end. It is collected to form the signal current. The one dimensional array as explained about is used to represent one scanning line. These lines are independently addressed and output is read out using the address register and drive phases.

ADVANTAGE

- 1. Good image quality.
- 2. Not troubled by noise.
- 3. No need of electron gun and beam.

LIMITATIONS

- 1. Requires external processing unit.
- 2. Relatively high power consumption.
- 3. Expensive.


APPLICATION

- 1. Barcode scanners.
- 2. Cam coders.
- 3. Fax machine.

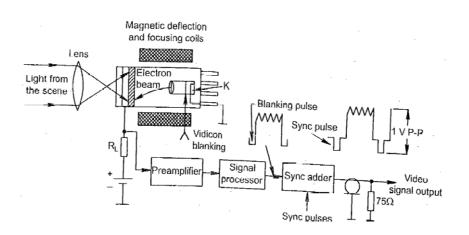2.7 VIDEO PROCESSING OF CAMERA PICKUP SIGNAL

The optical image is focused by the lens on the glass face of target plate.

The lens regulates the light, by the iris build into the lens housing. The output of video signal is taken across the load resistor.



• IMPORTANT WORKS:

- Amplify the weak, low voltage signal from the load resistance R_L.
- Addition of blanking pulses.
- Addition of sync pulse.

The signal current or voltage across the load resistance R_L . So a pre-amplifier is used at the first stage. The output terminal of camera tube to avoid external interferences.


In second stage we are using signal processor to add a blanking Rise during the horizontal and vertical retrace intervals.

Sync adder circuit is used to add the synchronizing pulses. The output waveform has a voltage of about IV p-p across 75 ohms as shown.

That is located at some distance from the Camera.

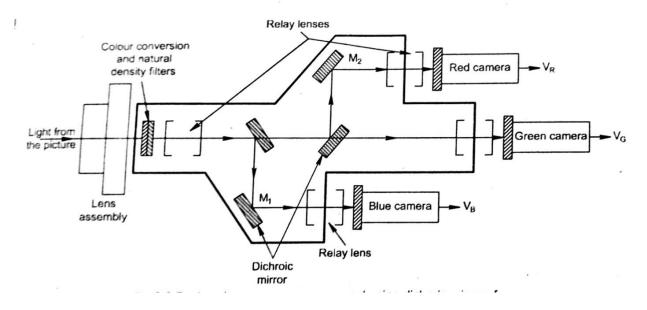2.8 PRINCIPLE OF WORKING & BLOCK DIAGRAM OF COLOUR TV CAMERA

A colour camera tube is used to split the optical image into primary colours. A special type of mirror called dichroic mirror is used.



That is red dichroic mirror reflect red colour and allow other colours to pass through it. The scene is focused by the zoom lens package on the dichroic mirrosetup. Then they are passed through the colour filters. These filters can provide precise primary colour images. Each camera tube develops video signal voltage, proportional to the colour intensity received by it.

A video pre amplifier amplifies V_R , $V_B V_G$ signals. In the output stage a resistance network is used to generate the luminance (y) signal and colour signal.

The resistance values are so related, such that Y=0.3R+0.59G+0.11B. If only red colour light is focused, then we have only red camera output V_R .

Then, $y = \frac{30}{(30+70)} * V_R = .3 V_R$.

2.9 PICTURE TUBES

• SPECIFICATIONS:

The size of picture tube in general denotes the diagonal length. The size of the picture tube ranges from about 1" (2.5 cm) to 30" (76 cm) or more.

Most of the commonly used tubes in B/W TV and colour TV are 51 cm and 36 cm screen size.

Tube 500 AmP4 has a diagonal length of 500 mm (20"). The last alphabet 'P' specifies the screen phosphor.


2.9.1 MONOCHROME PICTURE TUBE SPECIFICATION:

The commonly used picture tubes manufacture in India and marketed by Bharat Electronics Ltd., are 310 C1p4, 470C1p4 and 610C1p4, 590 Cp4. Picture tube employs electrostatic focusing and electromagnetic deflection.

• CONSTRUCTION AND WORKING PRINCIPLE OF MONOCHROME PICTURE TUBES

The picture tube is used to convert the video signal into optical signals.

• CONSTRUCTION:

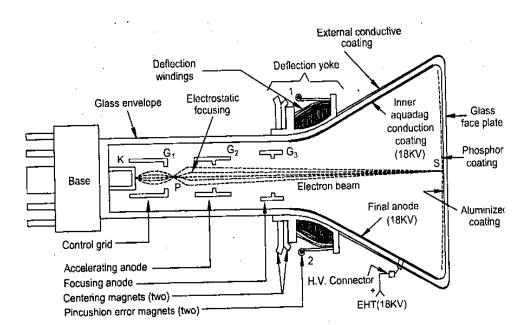

Mainparts :

- Electron gun
- Focusing anode
- Deflection Coils
- Final anode.
- Phosphor screen
- External conductive Coating.

Eg:

• ELECTRON GUN

The electron gun unit consists of Cathode, control grid and accelerating anode.

It is indirectly heated by a filament Thoriatedm Tungsten or borium and strontium oxides are having low work function and so release a sufficient number electrons of when heated.

The control grid is used to control the flow of electrons from the cathode. It is also in the form of cylinder, end for flow of electrons.

Screen grid is maintained at 400V and focusing grid is maintained at 600V. Through this

base pin only the hated voltage for different grids are supplied.

• FOCUSSING ANODE

Electro static method is used to focus the electrons beam. The positive potential at the accelerating anode is extended. This is considered as first lens action. Screen grid and focus grid forms the second lens system. The focus anode is larger in diameter and also its potential is higher than the first anode.

The voltages given to the grid are so selected that the second convergence point is on the screen picture tube.

• DEFLECTION COILS

Electromagnetic system is used to deflect electrons beam in horizontal and vertical direction. The picture tube produces horizontal deflection and another pair of coil placed left and right produces vertical deflection.

The two pair of coils are collectively called as deflection yoke. In deflection yoke, centering magnet and pin cushion magnet are also provided for centering electrons beam. At the movement of electrons beam at corners.

• FINAL ANODE.

To provide sufficient velocity and energy for electrons beam a final anode is included in the tube. This aquadong coating is provided with a high voltage of 10KV or more. The secondary electrons emitted from the screen are attracted by these coating.

• PHOSPHOR AQUADAG SCREEN

Phosphor chemicals are light metals such as zinc and cadmium in the form of sulphate, sulphide and phosphate compounds. The atoms while hitting the coating, hitting spot fluorescence emit light.

• EXTERNAL CONDUCTIVE COATING.

Aquadag is also coated on the outer surface of the glass bell. A spring clip used to connect this coating with the chassis ground. A.C. ripples in high voltage and provide a perfect higher voltage.

• WORKING PRINCIPLE:

An a.c. supply of 6.3 V is given to the heater filament. This filament heats cathode and cathode emits electrons. The number of electrons in the beam is controlled. The accelerating anode increase the velocity of moving electrons A point and strike the phosphor coating on the screen. The aquadog coating inside the tube is given a high voltage in order of to 15 kv. Because of the deflection coil current the beam is deflected both in horizontal and vertical direction. The useful video signal is given to the cathode or control grid. It's called contrast control and brightness control Due to persistence of vision of eye, the viewer accumulates all picture elements as a whole picture.

2.9.2 PHOSPHOR SCREEN:

The phosphor chemicals are light metal such as zinc and cadmium in the form of sulphate. The kinetic energy of the moving electrons in the beam are transformed to the atoms in the phosphor coating. External conductive coating is also outer the surface of the glass bell. Decay time of phosphors used in picture tubes is approximately 5 ms in monochrome picture tube.

2.10 SCREEN BURN:

It is a defect in picture tube due to electrons. But the EHT voltage is present for long time. Because of absence of deflection field there electrons continues to strike. This defect can be overcome.

2.11 ALUMINIZED SCREEN:

A very thin coating of aluminium is provided on the back surface of the screen phosphor on all modern picture tubes. The aluminium coating is connected to high voltage anode coating. Aluminium coating reflects light from the screen.


2.12 TYPES OF COLOUR PICTURE TUBES:

The screen of colour picture tube is coated with three different colour phosphor. However the three colour phosphor are separated from each other physically.

Three types of picture tubes are

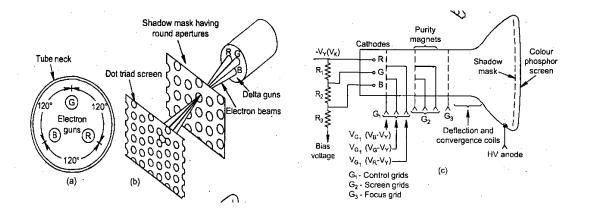- 1. Delta gun picture tube.
- 2. Precision In Line or Gun In Line picture tube.
- 3. Trinitron picture tube.

• CONSTRUCTION AND WORKING PRINCIPLE OF DELTA GUN PICTURE TUBES



DELTA GUN

Radio Corporation of America developed this tube. Arranges in delta shape.

MAIN SECTION

Electron gun consists of three electron guns spaced equally at 120 Screen and shadow mark section.

• WORKING PRINCIPLE

The video signals corresponding to each primary colour are given to the three electrons gun. The axis of even electrons beam are adjusted by the purity magnet. And during this time other triode are by the mask.

The overall colour depends upon the phosphor which are being energised and the intensity of each beam.Red and green beams are 'ON', screen become yellow.


• DRAWBACKS OF DELTA GUN TUBE:

Convergence is difficult.

Focus cannot be sharp over the entire screen, electron transparency of the mask.

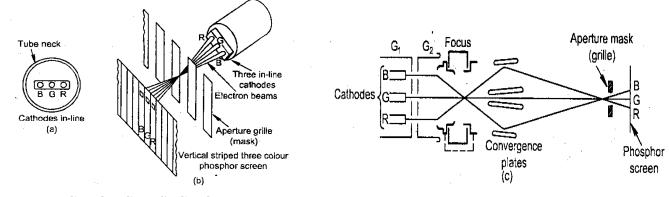2.13 TRINITRON COLOUR PICTURE TUBE:

This type of tube was developed by Sony corporation of Japan. These tubes are having a single gun with three in-line cathodes.



• ELECTRON GUN SECTION:

Here their is only one electrons gun, but with three cathode for each primary colour, screen and mask construction. The outer plates are supplied with above 450V less than the final anode voltage.


Four convergence plates are used. Since green beam is in centre, it passes through the centre plate. But red and blue beams pass between other plates. Since centre plate are connected internally to final anode, zero potential is found between these plates. So green beam is not affected by convergence voltage.

Due to voltage difference, an electronic force is developed and converging action taken place. So convergence is done for red and blue beams.

• ADVANTAGES:

- 1. Construction is simple.
- 2. Brightness is more.

2.14 AUTOMATIC DEGAUSSING:

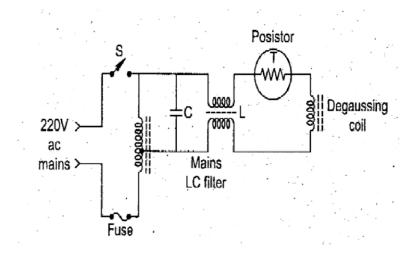

Degaussing means demagnetizing. It is the process of removal of magnetic flux from magnetized parts in TV. Steel Chasis and internal frames that hold mask are subject to induced magnetization, whenever picture tube is switched off.

These induced magnetic fields can affect the electron beam path and produce errors in colour purity. To prevent such effect picture tubes are magnetically shielded. For this a thin silicon steel is housed around belt of tube. Mask structure and shield material have non zero retentivity and so they get weakly magnetized by magnetic field of earth.

Automatic degaussing circuit is shown. When the receiver is switched 'ON', a strong main current passes through the degaussing coil. After a few seconds this current is dropped to very low level.

REVIEW QUESTIONS

PART-A

1. What is camera tube?

2. What is picture tube?

3. Mention the characteristics of camera tube.

4. Define spectral response of a camera tube.

5. Define sensitivity.

6. Define dark current.

7. Define lag characteristics.

8. Define resolving power.

9. Mention the types of camera tubes.

10. Mention the specification of picture tube.

11. What type of focusing and deflection is used in monochrome picture tube.

12. Mention the types of color picture tube.

13. Define degaussing

PART-B

1.What is screen burn?

2.Explain aluminized screen.

3.Explain automatic Degaussing

PART-C

1. With neat block diagram explain the working and construction of Videocon camera tube.

2. With neat block diagram explain the working and construction of plumbicon camera tube.

3. Compare various camera tube

4. With neat block diagram explain the working and construction of CCD image sensor.

5. Explain with neat diagram the video processing of camera pickup signal.

6. With neat block diagram explain the working of colour TV camera.

7. With neat block diagram explain the working of monochrome picture tube.

8. With neat block diagram explain the working of delta gun picture tube.

9. With neat block diagram explain the working of Trinitron picture tube.

UNIT - III TELEVISION TRANSMITTER

3.1 TWO TYPES OF MODULATION

1. HIGH LEVEL MODULATION:

In this, both the audio and video signals are amplified to the required level before modulation.

2. LOW LEVEL MODULATION:

In this, the signal is modulated before amplification.

• ADVANTAGES OF LLM (Low Level Modulation)

- 1. Simplicity of design.
- 2. Ease of operation.
- 3. Good linearity.
- 4. Superior performance.


3.2 Comparison between high level modulation and low level modulation

S.No	High level modulation	Low lelvel modulation
1	Both audio and video signals are amplified to required level before modulation	Both audio and video signals are amplified to required level after modulation
2	Transmitter power high	Transmitter power is low
3	Difficult to design and operation	Simple is design and operation

• Principles


A television transmitter both audio and video signals using a channel bandwidth of 7 MHz. The two outputs, one from picture signal transmitter and the other from sound signal transmitter are combined in suitable network and then fed to a common antenna network for transmission.

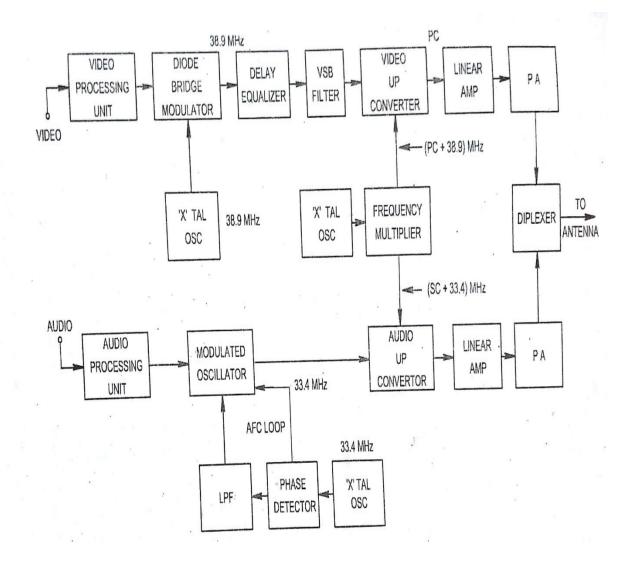3.3 BLOCK DIAGRAM OF LOW LEVEL IF MODULATED TV TRABSMITTER



In this video modulation is done at IF frequency of 38.9 MHZ and sound modulation is done at IF frequency of 33.4 MHZ. Both video and sound IF UP converted after modulation. A VSB filter is also included at lower IF power level. After up conversion they are given to lines, amplifier for power amplification and then it is connected to the diplexer unit.

3.4 VISUAL EXCITER:

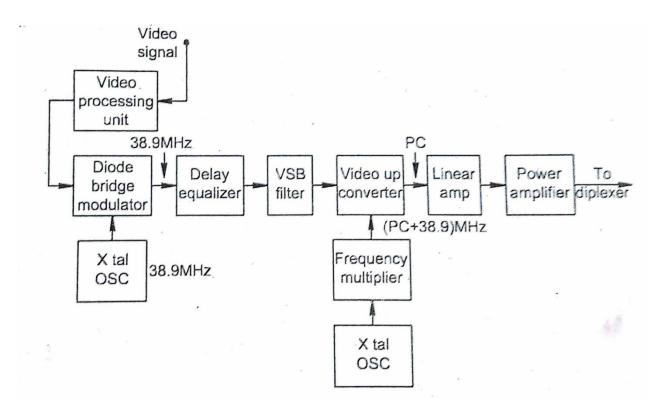


Visual exciter deals with circuits related to video signals. It consists of video processing unit, video modulator, VSB filter, Delay equalizer, Frequency up converter, Linear and power amplifier.

VIDEO PROCESSING UNIT:

In video processing unit, the Camera output signal having IVP-P amplitude is converted into standard form by eliminating hum and noise. Also after proper amplification sync pulses and blanking pulses are added to the Camera signal to get CVS.

VIDEO MODULATOR:

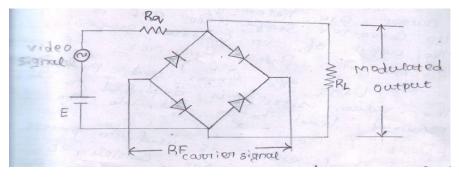

A bridge diode modulator or a diode balanced modulator is used for LLM. In diode bridge modulator, the diodes are switched ON and OFF by the carrier voltage (Ec cos wct) convert by the positive and negative half cycles. During the positive half cycle of carrier signal, R_L is short circuited. So output across R_L is zero. During negative half cycle, R_L is series with RS. So output is proportional to the potential divider ratio formed by R_S and R_L .

Instantaneous amplitude of output voltage is,

RL

 $e_0 = \dots (E_0 + E_m Sinw_m t) Cos w_c t$ RS+RL

= A₀ (1+ m Sinw_mt) Cos w_ct

From the above equation, the video signal is amplitude modulated by the carrier signal.

VSB FILTER:

It consists of four sections of LPF networks. This is used to attenuate the frequencies beyond 1.5 MHZ.

DELAY EQUALIZER:

This is used to avoid the phase distortions.

FREQENCY UP CONVERTER:

The VSB filter output and crystal oscillator output are heterodyned in the frequency UP converter stage. The BPF is used at the output of UP converter stage.

LINEAR AND POWER AMPLIFIER:


Using the linear and power amplifier, the video signal is amplified to the required level before fed into the diplexer.

3.5 AURAL EXCITER:

Aural exciter is used to process the audio signal. This section consists of, Audio processing unit, Audio modulator, Audio UP converter, Linear and power amplifier. Block diagram of aural exciter is show

46

Block Diagram of Aural Exciter

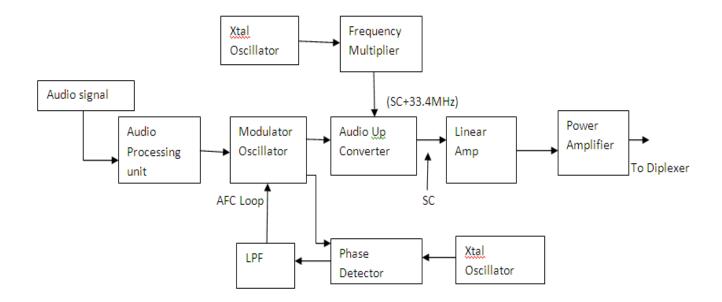

AUDIO PROCESSING UNIT:

In this section, pre emphasis circuit and amplifier are used to improve the signal to noise ratio and amplify the audio signal to the required level.

AUDIO MODULATOR:


Audio modulator has two inputs, one is from the video processing unit and the other is from crystal oscillator. These two frequencies are given to Varactor diode in parallel with LC tank circuit. The output is sound IF of 33.4 MHZ.

If there is any change in sound IF, the phase detector produces an error voltage. This voltage is given to the varactor diode to correct sound IF. Here the audio signal is frequency modulated.

AUDIO UP CONVERTER:

The output of audio modulator and crystal oscillator are heterodyned to produce the required audio signal output.

3.6 LINEAR AND POWER AMPLIFIER:

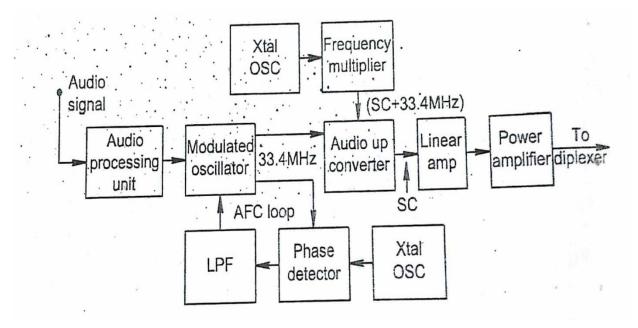

Using the linear and power amplifier the audio signal is amplified to the required level and is fed into the diplexer unit along with the video signal.

3.7 CIN DIPLEXER (CONSTANT IMPEDANCE NOTCH)

Working Principle of CIN Diplexer

Diplexer acts as the combining network, which is used to combine the audio and video signals without mixing i.e. it provides isolation between the two inputs.

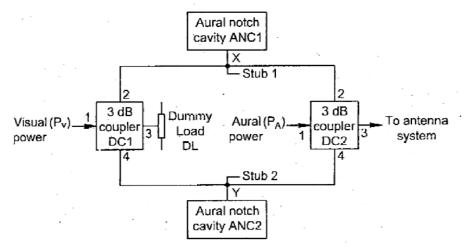


Fig.3.4 Block diagram of CIN diplexer

It consists of,

- 1. Two 3db Directional Couplers (DC)
- 2. Two Aural Notch Cavities (ANC)

These two 3db directional couplers are joined using Co-axial transmission line and two ANC's are connected in parallel with co-axial line.


Dc1, and Dc2 has 4 ports. Port 1 is the input port and other 3 are output ports.Visual power is fed into port 1 of Dc1. This signal passes through port 2 and port 4 of Dc1 with 90° phase shift. Port 3 connected with dummy load to avoid leakages.

These two signals are passed through co-axial line to port 2 and port 4 of DC_2 . These two are added up and taken from port 2 of Dc_2 .

Audio power is fed into port 1 of Dc2, this signal divided equally into port 2 and port 4 of Dc2 with 90° phase shift. They are passed to ANC1 and ANC2 and reflected to come back to port 2 and 4 of Dc2.

The reflected signals are added and taken from Port 3 of Dc2. After this processing the audio and video signal fed to common antenna without mixing.

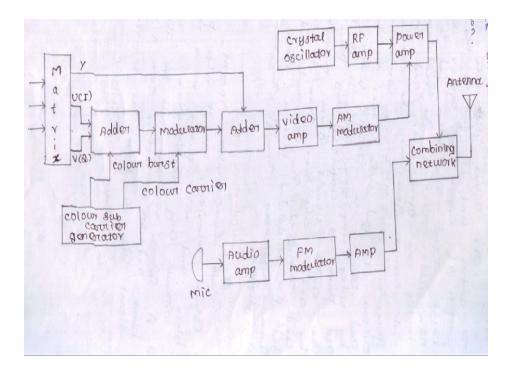3.8 BLOCK DIAGRAM OF COLOUR TV TRANSMITTER



The gamma corrected R.G, and B signals are given to the matrix network to form the Y, u and v signals.


The colour difference signals are fed to adder then fed to the modulator. Some samples of colour sub carrier called as colour burst signal is also fed to the modulator using the adder circuit. The modulator take two inputs one from adder and other from colour sub carrier generator. The sub carrier generator generates 4.43 MHZ of carrier signal. Then the output is fed into adder to combine Y signal and chrominance signal. Video signal is amplified by video amplifier and it is AM modulated and power is amplified by power amplifier. The audio signals from microphone are amplified by audio amplifier then it is FM modulated and amplified. The FM modulated sound signal and AM modulated picture signal is fed into common antenna through the combining network, adiplexer.

3.8.1 COLOUR COMPATIBILITY:

Colour compatibility means,

- 1. Colour television signal must produce a normal black and white picture on a monochrome receiver without any modification.
- 2. A colour receiver must be able to produce black and white picture from a normal monochrome signal. This is known as reverse compatibility.

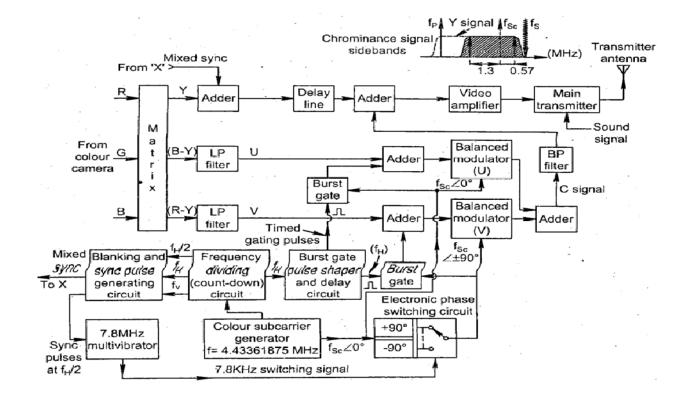3.9 PAL COLOUR CODER (FUNCTIONAL BLOCKS AND WORKING OF EACH BLOCK, OUTPUT WAVEFORMS OF DIFFERENT STAGES)



The gamma corrected R.G and B signals are given to matrix network and Y, R-y and B-y signals are formed. Bandwidth of R-y and B-y is restricted to 1.3 MHZ using LPF.

Sync and blanking pulses are added with Y signal. A delay line is inserted in the path of Y signal, because the colour difference signals (R-y) (B-y) take some time to process these signals. So to avoid this delay, a delay line is used in Y signal path.

The colour difference signals from filter are fed to balanced modulator. The output of filter and subcarrier oscillator is fed to balanced modulator, subcarrier generator is used to generate 4.43 MHz of carrier signal.

This carrier signal is directly fed to 'U' modulator, \pm but for 'v' moulduator $\pm 90^{\circ}$ phase shifted carrier signal is provided on alternate lines b y the use of 7.8 KHz switching circuit .

The DSBSC signal of U and V modulators are added together to yield the quadrature amplitude modulated chrominance signal. Then it is passed through a BPF to remove harmonics of subcarrier frequency. Then this filtered output is fed to adder to combine the Y and C signals.

The colour burst signal is also fed into the modulators along with U and V signals through adders. Before feeding this burst signals into U and V adders these are passed though separate burst gate. Each burst gate is controlled by delayed pulse at line frequency (fH).

These pulses are appeared during back porch period. During this interval 'U' modulator gets a burst with 90° phase shift, while V modulator gets burst with $\pm 90^{\circ}$ phase shift on alternate lines. At the output of modulators, the two burst signals are combined and produce the subcarrier burst at $+45^{\circ}$ on one line and -45° on the next line with reference to 'U' phase.

The CCVS formed is fed into the main transmitter. The frequency modulated sound signal is also combined to picture signal to diplexer and is fed into common antenna.

• Merits of Pal system

- i) Differential phase error have been successfully eliminated
- ii) Eliminate the hue errors, so manual hue control becomes unnecessary
- iii) More picture details because greater number of scan lines
- iv) Wider luminance signal bandwidth
- v) Higher gamma ratio
- vi) Easy studio mixing greater resolution

• Demerits of pal system

- i) The use of phase alternation by line technique is more complicated and expensive, becuse it needs a delay line in the receiver.
- ii) This system present problems in magnetic recording
- iii) More flicker because lower frame rate
- iv) Lower signal to noise ration
- v) Loss of colour editing accuracy
- vi) Variable colour saturation

REVIEW QUESTION

$\mathbf{PART} - \mathbf{A}$

- 1. List the types of modulation used in TV transmission.
- 2. What is diplex?
- 3. List out sections (components) in low level IF modulation.
- 4. List out the sections in aural exciter.
- 5. List out the sections in visual exciter.
- 6. What is the function of TV transmitter?
- 7. Mention the colour sub carrier frequency of PAL colour system.

PART - B


- 1. Compare high level and low level modulation.
- 2. What is high level modulation and low level modulation?
- 3. List out the advantages of LLM.
- 4. With neat diagram explain video modulator.
- 5. Explain colour compatibility and reverse compatibity.
- 6. List the merits (advantages) of PAL system.
- 7. List the demerits (disadvantages) of PAL system.

PART-C

1. With neat block diagram explain the working of low level IF modulated TV transmitter.

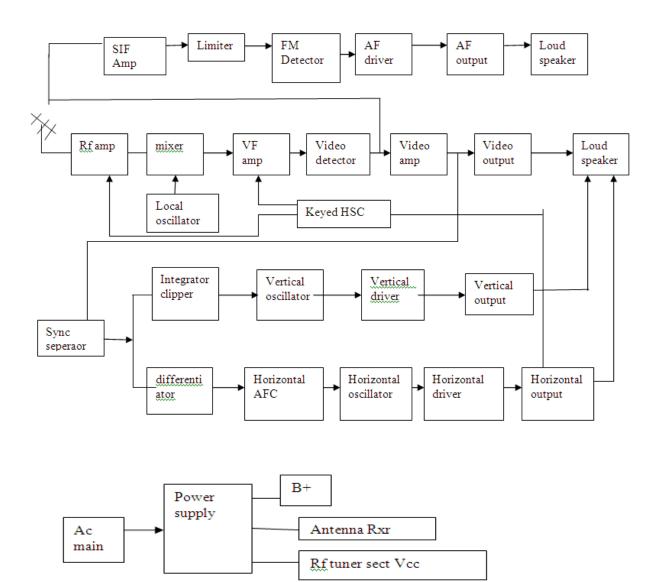- 2. With neat block diagram explain the working of aural exciter.
- 3. With neat block diagram explain the working of visual exciter.
- 4. With neat block diagram explain the working of CIN diplexer.
- 5. With neat block diagram explain the working of colour TV transmitter.
- 6. With neat block diagram explain each functional block of PAL colour system.





- Video signal and AGC section
- Audio signal section
- Synchronous separator section
- Oscillator section
- ➢ EHT section

4.2 Function of various blocks

4.2.1 Antenna section:

- To receive the TV signals, antenna is mounted at the top of a building. Converts the received electromagnetic waves into electrical signals.
- A half wave length antenna is mostly used for UHF band channels. Normally yagi
- antenna is used in TV receiver.

4.2.2 RF tuner section:

- RF amplifier, mixer and local oscillator are collectively called as RF tuner.
- The other input to the mixer is fed from a local oscillator
- Used to select the desired band and channel.

Picture 1F =38.9MHZ Sound 1F=33.4MHZ

4.2.3 Video signal and AGC section:

- The video section consists of 1F amplifier video detector, video amplifier and picture tube.
- So a video amplifier is used at the output of video detector.
- So an automatic gain control (AGC) circuit is used to automatically control the gain of the amplifiers.

4.2.4 Audio signal section:

- In this section we have audio IF amplifier, FM demodulator audio amplifier and loud speaker.
- A loud speaker is used for the reproduction of sound.

4.2.5 Sync separator section:

- This section consists of a sync separator integrator and differentiator
- So the output of sync separator contains both the horizontal and vertical sync pulses.
- The differentiated horizontal sync pulses of line frequency are used to trigger the horizontal oscillator.

4.2.6 Horizontal and vertical oscillator section

- Vertical section consists of vertical oscillator output amplifier and vertical deflection coil.
- Similarly the horizontal is synchronized by the trigger pulses from the differentiator.

EHT section (Extra High Tension section)

- In this section only the high voltage needed by final anode is developed.
- Using the damper diode section boosted B⁺ supply is taken out.

4.3 Need for AGC:

- The amount of signal received depends on the transmitter power.
- AGC also permits increase in gain for weak signals. It is achieved by delaying the application of AGC.
- Flutter in the picture due to passing aero planes and other folding effects are reduced.
- Separation of sync pulses becomes easy.
- AGC bias voltage in a D.C voltage proportional to strength of input signal. This bias voltage is received from output of video detector after rectification.
- This AGC bias voltage change the gain of IF and RF amplifiers in accordance with amplitude and maintain the output of video signal as constant amplitude.
- By using AGC amplitude of video signal at output of video detector is constant irrespective of variation of input signal.

4.4 Advantages of AGC:

- Intensity and contrast of the picture. Once set with manual controls remain almost constant.
- Contrast in the reproduced picture does not change much when the receiver is switched from one channel to another.
- Amplitude and cross modulation distortion on strong signal is avoided due to reduction in gain.
- Fading and flutter decreases.
- Controls sound signal level.
- Sync pulses can be separated easily.

4.5 Video amplifier requirements and response curve requirements:

Requirements:

To produce a satisfactory image on the screen of picture tube, video amplifier must meet the following requirements

4.5.1 Gain

Video signal at output of video detector is very low (2vp-p). To increase the required contrast level in screen, video signal must be increased to high level of 80vp-p. For this video amplifier is needed.

4.5.2 Bandwidth:

Frequency response of video amplifier must be 0HZ to 5MHZ. Then only picture without distortion will be seen in screen. For this video amplifier is used.

4.5.3Frequency distortion:

The inequality gain at different frequency components of the signal is called frequency distortion. Excessive frequency distortion cannot be tolerated because it changes picture information.


In poor high frequency response, rapid changes between black and white for small adjacent picture elements in horizontal line cannot be reproduced. This result in loss of horizontal details. Low frequency range is required for sharpness of picture. To avoid frequency distortion video amplifier is needed.

4.5.4 Phase distortion:

In video amplifiers, phase shift implies time shift, which in turn means position shift in the reproduced picture image. So to avoid phase distortion the video amplifier should not change the phase of the frequency component. So to avoid phase distortion video amplifier is needed.

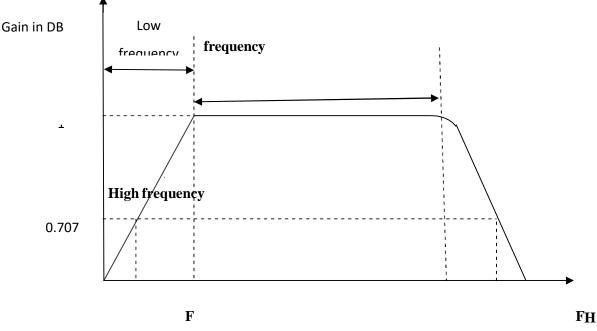4.5.5 Amplitude distortion (non linear distortion):

When different amplitude components get different amplifications. Then amplitude distortion occurs. To avoid this, video amplifier is needed.



4.5.6. Frequency response curve:

- From the response curve, we find that the gain of amplifiers is reduced very much for low frequency and high frequency.
- So HF and LF compensations are necessary for a video amplifier circuit.


4.7 HF AND LF COMPENSATION TECHNIQUES:

4.7.1 High frequency compensation: (HF compensation)

- Shunt peaking.
- Series peaking.
- Combination peaking.

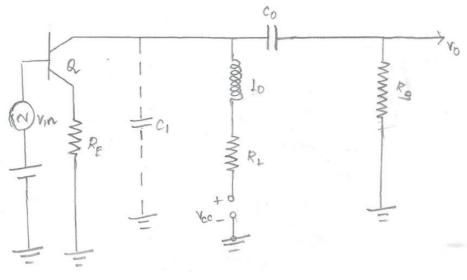
4.7.1.1 Shunt peaking

- Here the peaking coil L_0 is connected in shunt to the video amplifier.
- C1 is stray capacitance. This reduces gain at high frequency,.
- So peaking coil will resonate with C_1 and increases the gain at high frequency.




Shunt peaking

Shunt peaking:

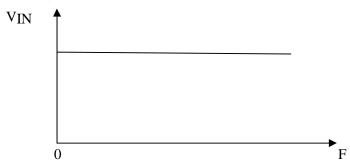


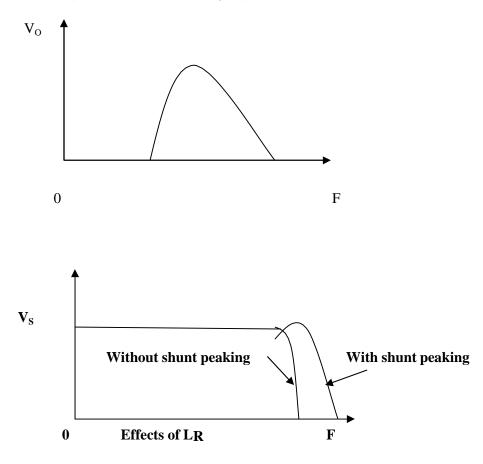The response curve of C and $L_{\rm O}$ in peaking




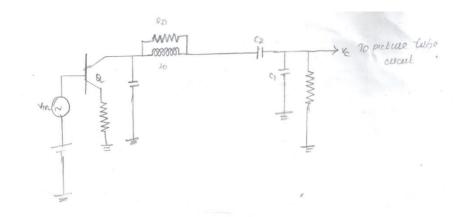4.7.2 Series peaking


- The peaking coil L_0 is connected in series with the signal path. C is divided in to Cin and Cout.
- The reduced shunt capacitance across R_L . A damping resistor R_d in shunt with its peak coil is used to prevent any oscillation in the coil.



Video amplifier with series peaking

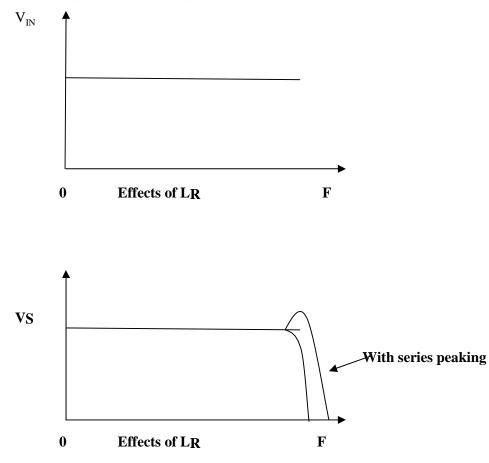


4.7.3 Combination peaking:

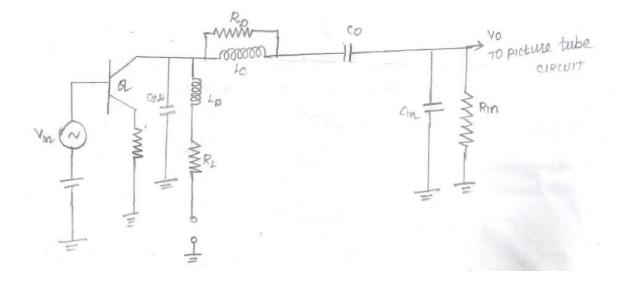

• To improve gain in high frequency combination of both series and shunt peaking are used.e

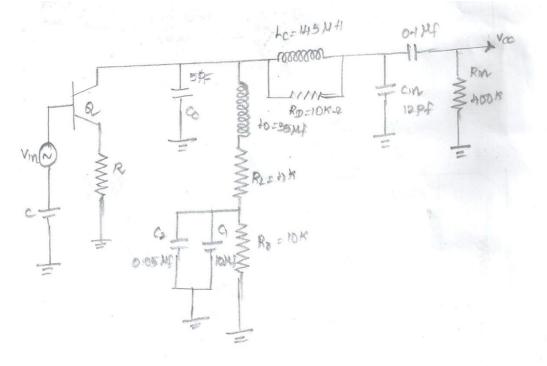
4.8 LOW FREQUENCY COMPENSATION; (LF COMPENSATION)

Coupling and by pass capacitors reduces gain at low frequency. R_f , C_f components is connected to B^+ Supply line. This increases gain at low frequency and phase distortion is reduced.



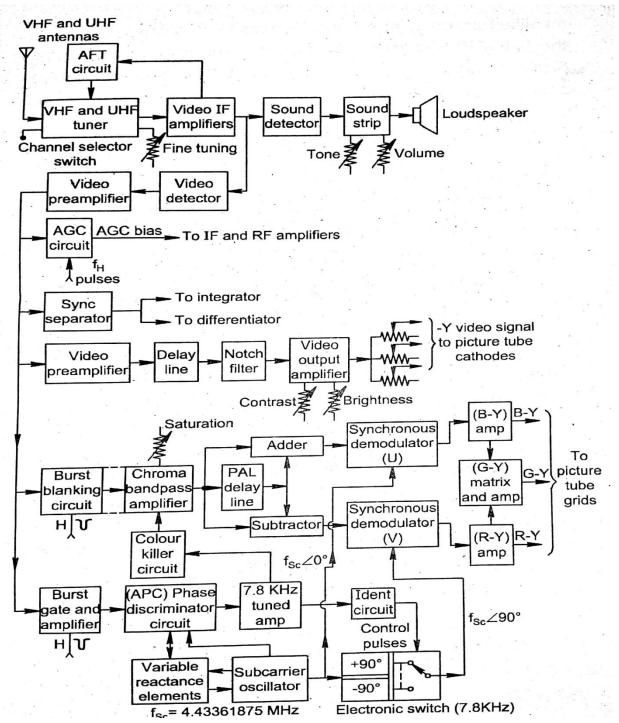4.9 PAL COLOUR RECEIVER:

The colour TV receiver is similar to the monochrome system expect that here we have a colour demodulator section.



4.9.1 The sections of the PAL colour receiver are

- 1. Colour chroma section
- 2. Colour band pass amplifier
- 3. Burst gate
- 4. Colour killer circuit
- 5. Colour subcarrier oscillator
- 6. PAL delay line and discrimination
- 7. Matrix network

Signal from antenna is selected by the tuner and converted to video and sound IF. It is amplified by the IF amplifier and detected by video amplifier. Inter carrier sound IF is sent to sound IF section and audio signal is produced. Video is amplified and sent to CRT and vertical & horizontal sync pulses are separated and transmitted to respective sections.

4.9.2 Monochrome and tuner section:

- The RF tuner is used to select the RF signal for different channel from the antenna.
- The sync pulses for horizontal and vertical oscillator are separated by the sync separator and its associated circuit.

4.9.3 Chrome band pass amplifier:

- This section consists of a chroma filter and two stage chroma amplifiers.
- In this section we have a color control. This control adjusts the gain of the band pass amplifier.

4.9.4 Colour burst gate:

• Separates colour burst signal and gives it to phase discriminator.

4.9.5 Colour killer:

- Zero and the output of 7.8 KHZ tuned amplifier also falls to zero.
- The colour killer turns off the chroma amplifier stage.

4.9.6 PAL Delay line stage:

- The purpose of this section is to delay the signal by about 64 micro seconds.
- The normal (U-V) and delayed (U+V) signals are simultaneously available.

Separation of U and V signals:

At the adder circuit

(U-V)+ (U+V) =2U (U+V)+ (U-V) =2U

At the subractor circuit

(U-V)-(U+V) = -2V(U+V)-(U-V) = 2V For adder and subractor 64 microns seconds delay signal needed. To provide this PAL delay line is needed.

4.9.7 Colour subcarrier oscillator:

• Keeping colour bunt as reference produce carrier signal of 4.43 MHZ.


4.9.8 Matrix network:


To generate (R-Y) (B-Y) and (G-Y) colour signals from U, V&Y signals matrix network is needed.

4.10 Need for synchronization pulse separator:

- The horizontal and vertical sync pulses exist in the top 25 percent of the composite video signal.
- At the output of video detector we have composite signals that contain video information and sync information for triggering of oscillator only sync pulses are needed.
- The sync separator separates both the horizontal and vertical sync pulses from the composite video signal.
- By using differentiator circuits, horizontal sync pulses (15625 HZ) are separated and by using integrator, vertical sync pulses (50HZ) are separated. They are used for triggering corresponding oscillators.

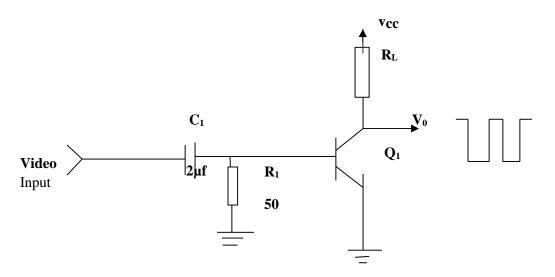4.11 Basic principle of synchronization pulse separator:




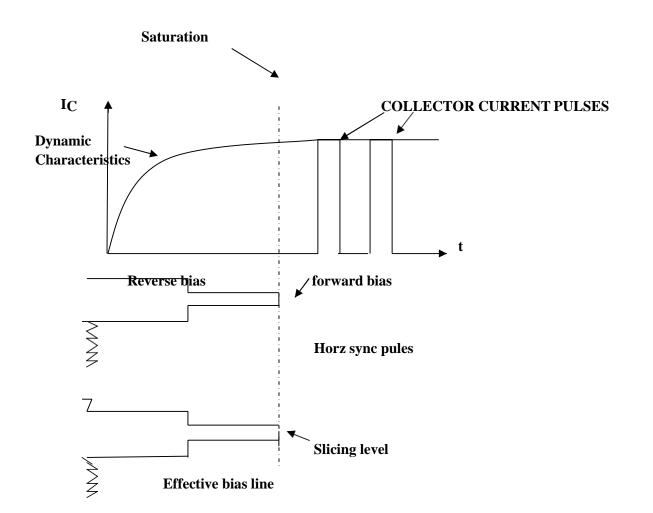

- The basic principle of merely biasing the devices used in sync separator the composite video signal makes current flow in the device.
- In self biasing the DC bias voltage is produced by the input AC signal itself.
- The transistor is operating the class 'C' mode. Input stage provides necessary DC bias voltage.
- R&C is used to provide the self bias between base and emitter of the transistor.
- Emitter circuits conduct heavily and changes the capacitor 'C'. This negative voltages then reverse bias the emitter bias base junction.
- The peaks of consecutive input video signal discharge through RC .discharge only 10% between the peak input signals.
- So the output of transistor we have only the separated sync pulses. These are shown clearly.

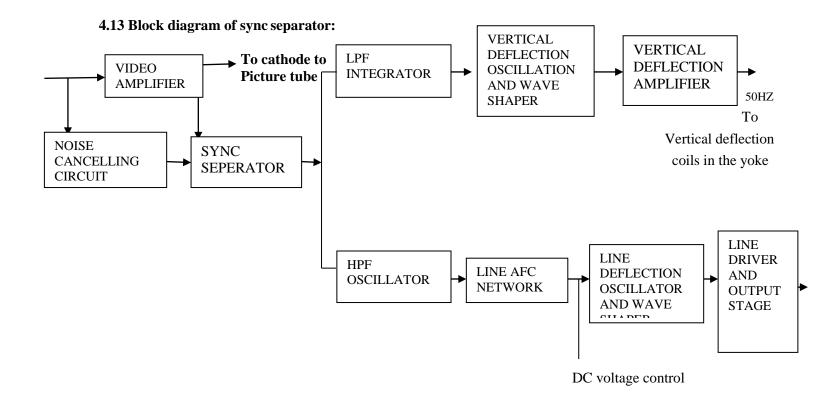4.12 Condition must be satisfied

- β of the transistor should be large.
- Output leakage current must be small.
- The time constant RC must be long.
- A low power transistor can be used, since the transistor is off for most of the period.



The video signal from the video amplifier is fed to the sync separator circuit.


- At the output of sync separator we have a train of horizontal and vertical sync pulses.
- After the proper amplification they are fed to vertical deflection coil.
- Similarly the horizontal deflection oscillator is triggered by the differentiator output.
- To maintain the horizontal frequency at constant value an automatic frequency circuit is used in horizontal deflection section.

4.14 Separator (Vertical and Horizontal Sync)

4.14.1 Vertical sync separator: (INTEGRATOR CIRCUIT) LPF

- The resistor R, capacitor C forms a low pass filter which act as an integrator circuit.
- The time constant RC is chosen to be much larger than the width of separated vertical pulses.
- Usually about 10 times the serrated pulse width is sufficient when the horizontal sync pulses and equalizing pulses are applied to integrator.

Integrator circuit:

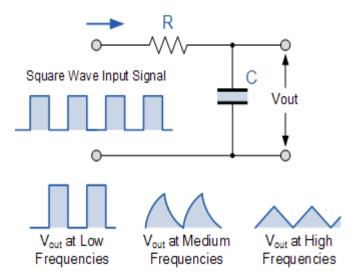


- The C charges and discharges quickly and the duration of ON period of these pulses are very less compared to time constant RC.
- The capacitor is charged for a period of 27.3 micro seconds and discharge for a period of only 4.7 micro seconds. This process is repeated.
- So, once a again capacitor is charged for 27.3 micro seconds and discharges for only 4.7 micro seconds this process is repeated.
- Due to this the voltage across the capacitor is gradually increased with small spikes super imposed on it.
- If vertical sync pulses has passed then the integration capacitor discharge almost to zero.
- In general a time constant of 50µs to 60µs is set for the integrator circuit.

4.15 Horizontal Synchronous Separator: Differentiator (HPF)

- When the leading edge of incoming pulse train is applied to RC, the output waveS follows almost the shape of input leading edge.
- When the flat top rectangular wave is reached, no further charging with time constant.

- Since the time constant is very short compared to input pulse, discharge completes before trailing edge of input pulse occurs.
- When trailing edge input pulse occurs it produces another pulse of opposite polarity to that of first pulse.

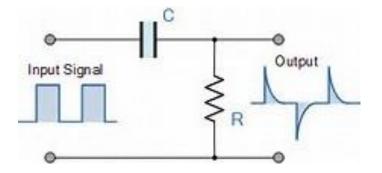• Since horizontal frequency is very high this will be affected by noise so horizontal AFC is provided.




4.16 Automatic frequency control: (AFC)

Noise pulses which arrive during intervals between sync pulses tend to trigger the drive oscillators prior to their proper time. Picture rolls vertically upwards or downwards in vertical oscillator is so triggered and a series of lines will be jumped up in horizontal oscillator causing tearing of picture. This system is automatically controlled by using AFC circuits. AFC means **Automatic Frequency Control**. To maintain synchronization AFC is needed.

4.17 Need for AFC:

AFC means automatic frequency control. Horizontal and vertical sync pulses are separated using HPF and LPF.Vertical sync pulse frequency is 50HZ. So it is not affected by noise pulses. But horizontal sync pulses frequency is 15625 HZ. So it is affected by noise pulses. This causes out of synchronization. So to maintain constant frequency AFC is needed.

4.18 Block diagram of horizontal AFC:

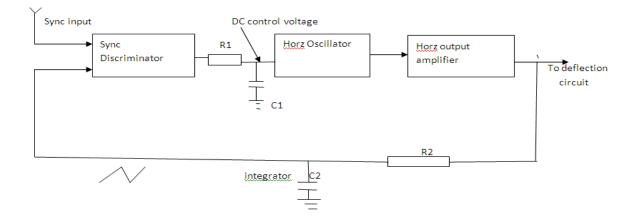


It consist of

- 1. Sync discriminator.
- 2. Horizontal oscillator.
- 3. Horizontal output amplifier.

The horizontal synchronization voltage and fraction of horizontal output voltages are given to sync discriminators terminals. It detects difference frequency and develops dc output voltage proportional to difference voltage. This DC voltage is fed to large time constant filter and output of which is used to control the oscillator frequency. The capacitor in the LPF terminates the effect of noise pulses.

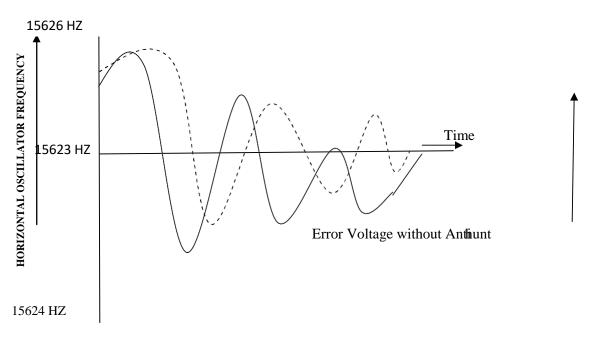
4.19 Hunting in AFC:

The low power frequency followed by differentiator controls the performance of AFC. If time constant is too large control is sluggish. If time constant is low oscillator is hunt while returning to the correct frequency. Excessive hunting in AFC circuit appears as "WEAVING" or "GEAR-TOOTH" effect on picture. Hunting in AFC is shown.




Because of hunting effect horizontal frequency deviates from correct values. To prevent this hunting double section filter is used.

4.20 ANTI-HUNT network:

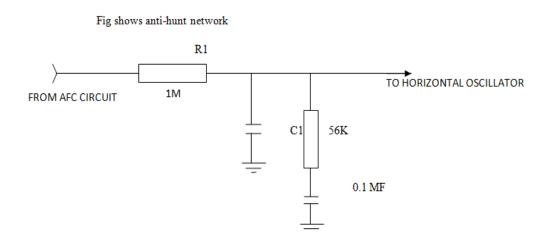

R1C1 time constant of 5ms is large enough to filter noise, horizontal sync and fly back pulses effects. Second section R2C2 in series is known as "ANTI HUNT" network.

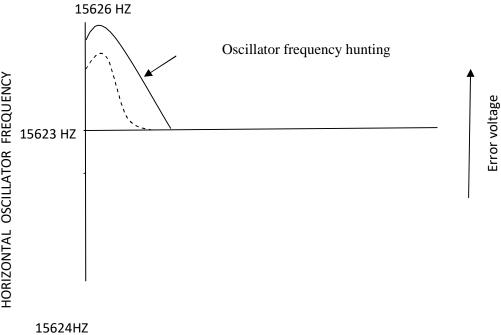In anti hunt network R2 act as a damping resistance across C1 making output voltage more resistive and less capacitive. Because of addition of anti hunt network the time delay in charge of control voltage is reduced.



REVIEW QUESTION

PART-A

- 1. List out the sections (components) of monochrome TV receiver.
- 2. List out the values of picture IF and sound IF in TV transmission.
- 3. What is AGC?
- 4. List out the sections of PAL color receiver.
- 5. What is sync separator?
- 6. What is the function of colour killer section?
- 7. What is AFC?

- 8. Why AFC is used in horizontal section?
- 9. What is an antenna?
- 10. Mention the types of FM sound detectors?

PART-B

- 1. Explain the need of AGC.
- 2. List the advantages (merits) of AGC.
- 3. Mention the video amplifier requirements.
- 4. Explain the need for sync pulse separator.
- 5. With neat diagram explain integrator (vertical) or (LPF) working in details.
- 6. With neat diagram explain differentiator (or) HPF working in details.
- 7. Explain the need for AGC.
- 8. What is hunting in AFC?
- 9. What is anti hunt network?
- 10. What is the compensation technique employed to extend the bandwidth of an amplifier?


PART-C

- 1. With neat block diagram explain the working of monochrome TV receiver.
- 2. With necessary diagram explain the HF and LF compensation technique.
- 3. With neat block diagram explain the working of PAL color receiver.
- 4. With neat block diagram explain the working of basic principle of sync pulse separator.
- 5. With neat block diagram explain the working of sync separator.
- 6. With neat block diagram explain the working of hunting in AFC.
- 7. Explain the anti hunt network in detail.
- 8. Explain the requirement of video amplifier in detail.

UNIT V ADVANCED TELEVISION SYSTEM

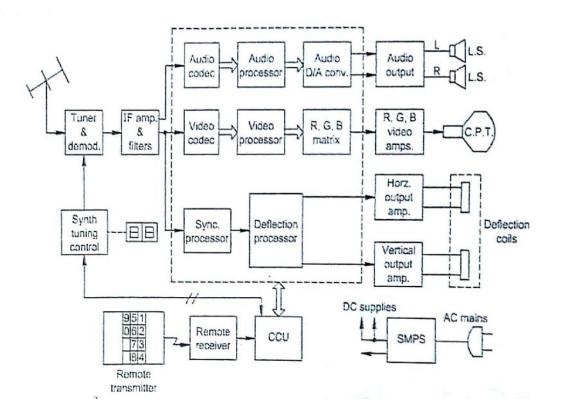5.1 Block diagram of digital colour TV receiver:

- Digital television means the digital processing of TV signal both at the transmitter and at the receiver.
- The luminance and chrominance signal process are in digital form.
- The central control unit is a microcomputer based device used to control and coordinate all circuit in this receiver.
- The main block used in digital receivers are,
 - 1) Video codec
 - 2) Video processor
 - 3) Deflection processing unit
 - 4) Audio codec
 - 5) Audio processor
 - 6) Central control unit



5.1.1 Video codec:

The signal from the IF stage is converted to analog CVS by the high speed flash A/D converter into 8 bit digital signal and given to video processor.

5.1.2 Video processor:

The output of video codec is separated into two channels – luminance and chrominance. Brightness and contrast of luminance signal are adjusted in accordance with user's settings. Chrominance signal is encoded to relative weightage of red, green and blue.

These signals are then given to video codec. The D/A converter in video codec convert it to analog form. By the delay line technique and demodulation R,G,B signals are obtained amplified and applied to corresponding guns.

5.1.3 Deflection processing unit:

This unit senses the standard TV signals and synchronizes the vertical and horizontal sweep generators and amplified and given to corresponding deflection yokes.

5.1.4 Audio codec:

This samples the input signal to produce 1 bit data stream and convert this into 16 bit resolution stream. This is given as input to audio processor.

5.1.5 Audio processor:

The input signal is split into two channels. Then the stereo balance, tone, loudness, and other necessary function are controlled.

5.1.6 Central control unit (CCU):

It is a microcomputer based device used to control and coordinate all circuits in the receiver. It is supported by an EEPROM, a timer, a control bus and circuits to decode user commands.


5.1.7 Merits of digital receiver:

- Resolution is high
- No interference of electrical appliances
- Synchronization is better.
- Picture in picture is possible.
- Improved reception in for fringe areas.

5.2 Remote control circuit:

- To operate the various receiver controls from a distance by the viewer, he is provided by the remote control circuits.
- The main function done by it are changing the channels, varying the sound level, turning ON and OFF the TV set, contrast level.
- Two signaling methods used for remote control.
 - 1) By ultrasonic waves
 - 2) By infrared wave using LED'S.
- We have 11 buttons for channels selection, one for VCR connection. Power ON / OFF button, volume control, color control are provided.
- The remote transmitter is somewhat directional since we are using the infrared waves.
- We can operate within 7 meters and at a radians of 30° from the receiver point, labeled for remote operation.


5.3 Remote control IR transmitters:

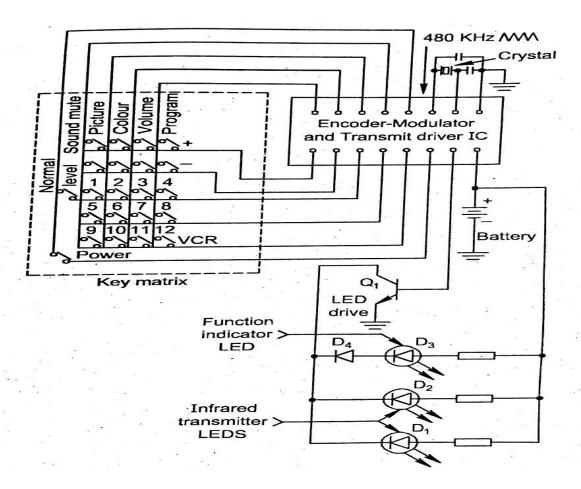

• To achieve all the necessary basic function 24 different commands are needed. So 24 different pulse patterns are generated. The modulator IC (encoder) performs the main function.

- The waves are modulated through a 480 KHZ carrier by one of the 24 pulse pattern.
- If any one of the key is pressed, it produces a distinctive pulse train which modulates the crystal controlled 480KHZ carrier.
- After proper amplification, it is fed to LED driver (Q1). The output of the Q1 drives the infrared LED D1 and D2 then the IR signal is transmitted.
- Then the function indicates LED D3 comes to ON state.
- If the LED is not glow on depression of a button then it indicates that the battery is to be replaced.

5.4 Remote control IR receiver:

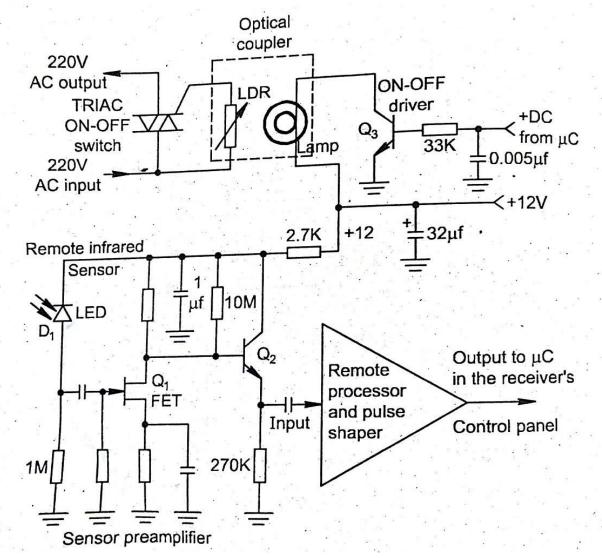

- A simplified circuit diagram used for the synthesis of remote control receiver.
- The remote infrared sensor D1 is used to pick up the pulse modulated infrared signals send by the IR transmitter.

- The A.C signal picked up by D1 is fed to the FET Q1 for some amplification.
- The output of Q1 is given to emitter follower Q2 through remote processor and given to pulse shaper. Here signal is amplified and then demodulated.
- Demodulated distinct pulses belong to distinctive function.
- This is given to microcontroller.
- This microcontroller on receiving different pulses produces different output necessary to perform the ordered function.

For example:


- The power ON/OFF button is pressed it is demodulated by the receiver then the micro computer output at the receiver is a positive voltage.
- Positive voltage through a 33k resistor turns 'ON' the transistor Q3and operates the opto coupler and lamp is now glowing.
- The resistance of LDR decreases. Due to the resistance 220 V A.C applied to the gate of the transmitter, theTRIAC comes to ON state, so the TV receiver is switched ON.
- To turn the receiver OFF the ON button of the transmitter is pressed once again.
- The positive voltage to the base of Q3 is removed the TRIAC is deactivated and so the lamp goes OFF in the opto coupler unit.
- So the AC supply to the receiver is cutoff. The above sequence is repeated for successive depression of the ON/OFF button.

Similarly several different circuits are employed at the output of microcontroller to achieve different functions like volume control, color control and contrast control etc.

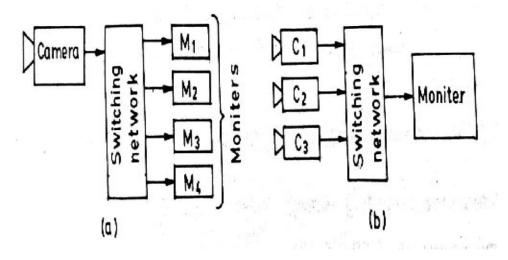5.5 CCTV (closed circuit television system):

If a single camera output is given to TV receiver through cable or the output of many cameras is connected to a TV monitor, then the system is called CCTV system.

Two types of switching network are made possible between the camera and TV monitor. This makes us to select the camera / monitor. Both CCTV systems is shown,



In diagram (a) a single camera(C) is connected to many monitors (M) through switching network (SN).in this we can see a single program in monitors at many places.

In diagram (b) many cameras(C) are connected to single monitor (M) through switching network. In this at single place, we can see many programs happening at different places.

5.5.1 Application of CCTV:

- 1. Education lecture classes and demonstration experiments.
- 2. Business used to keep on eye over customer and sales personal
- 3. **Home** seeing the caller before opening the door.
- 4. Industries for remote inspection of objects in place where human resources cannot be used.
- 5. Aerospace & oceanography: To see the inaccessible objects or places.
- 6. **Medicine:** To visualize the surgery.

5.6 Scrambler-Necessity-Basic Principles

This channel provided by the cable TV owners to its customers is of two types.

They are

- 1. Basic services
- 2. Premium services

Several basic channels and local TV programmes offered by cable companies for a minimum charge level is called basic services.

For new movies, sports etc., separate channels are provided with additional charges called as premium services.

Cable TV connections provided for viewing premium services with additional chargesis called as Conditional Access System (CAS).

In TVs provided with CAS connection only premium service programmes to be received.

For TVs provided with basic services connections premium services channel follow certain methods different from basic services. This is called scrambling. Equipments used for scrambling is called as scrambler.

5.7 Types of scrambling:

1) TRAP:

Here the signal is blocked by inserting and interfering carrier in the pay channel and notching it out.

2) Sync suppression scrambler:

Here the sync details from RF signal is removed and transmitted. So in basic services channels without H and V sync pulses pictures cannot be reproduced. Without sync pulses reference for AGC is also not provided. Without AGC bias contrast is overloaded.

So the picture continuously rolls with horizontal tearing of video signal.

3) Data encryption method:

In this method the audio and video signals are converted to digital forms. They are encoded using digital signal processing method. This is called as data encryption.


4) Baseband scrambling:

In this method the polarity of the randomly selected H- line is inverted. Line code for that particular H- line is transmitted with the video band.

5.8 Descrambler:

For channels that are scrambled, the signal cannot be reproduced normally. For that descrambler are needed. Signals that are scrambled is descrambled by an equipment is called descrambler. This process is called descrambling.

Descrambler block diagram:

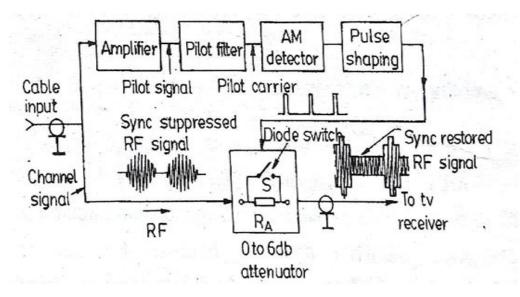

- Descrambler reverses the effect of scrambling at the head end of the cable system. Simple sync suppression scrambling and descrambling method is mostly used.
- In this sync signals from the final output is removed and this information is sent through a pilot carrier.
- for this purpose a pilot carrier signal having a frequency lower than that of the selected channel is used.


• Channel signal in the pilot signal is separated by the tuned amplifier.Pilotfilter, filters the sync details from the pilot carrier. AM detector demodulates this. In the demodulated signal timing information needed for synchronization is available. For proper shaping, pulse shaping is provided. Keyed RF alternator is provided for mixing the sync signal with channel signal. Alternator is represented by resistor Ra.Keying by pass action is provided by diode. This is represented by's'.

5.9 Telecine equipment:

In cinema cameras 24 frames per second is used. But for television 25 frames / second is used. So the pictures taken by movie camera is used for TV broadcast means, then it should be first converted to TV standards. The equipment used for this purpose is called telecine equipment.

510 Digital CCD telecine equipment:

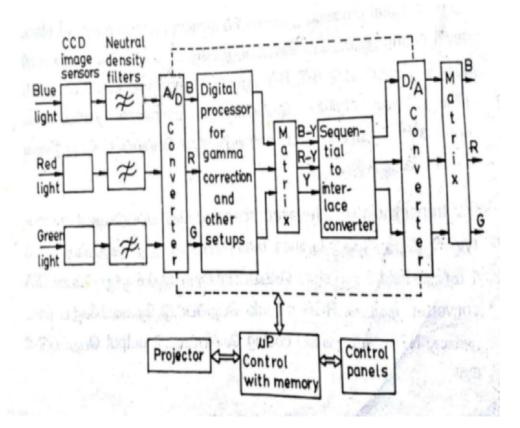Telecine equipment using CCD sensors that operate digitally is called as digital CCD telecine equipment. Block diagram is shown below.



Cine film is illuminated by slit of light. This represents H- line in TV scanning. By using dichroic prismatic splitters this light is separated to basic colors R,G and B. then it is given to separate CCD image sensors.

To correct the RGB sensitivity from the three CCD sensors, neutral density filters are used. The linear array in each CCD sensors contains 1024 elements. This represents H-line. By charge transfer method, the information's are moved in H – direction. Then H- scanning takes place. Then this is given to A/D converter and converted to digital signal.

Then by digital processing gamma correction and black level clamp is done. Then this is given to matrix network to produce B-Y, R-Y, and Y signals. Then it is digitized and separated to luminance and chrominance signal and stored in memory. This will be in sequential.

In TV transmission interlaced scanning is used. So from memory lines are read and stored in field 1 and field 2. Then this is given to D/A convertor, then the RGB signals are got and coded to required system (PAL and NTSC) and the output is got.

5.11 Introduction to high definition TV:

High definition television (HDTV) provides a resolution that is substantially higher than that of standard definition television. In HDTV, recent digital techniques are used for processing television signals. The aim of this HDTV are given below,

- I. Improvement in both vertical and horizontal resolution of the reproduced picture by approximately 2:1 over existing standards.
- II. Much improved color reproduction.
- III. Higher speed ratio at least 5:3 and
- IV. Stereophonic sound

Their implementation result is a picture quality as clear as obtained from 35mm cine films and sound as good as from digital audio discs.

HDTV may be transmitted in various formats.

- i. $1080p \rightarrow 1920 \ge 1080p : -2.1 \text{ megapixel (MPx) per frame}$
- ii. $1080i \rightarrow 1920 \ge 1080i : -2.1 \text{ megapixel (MPx) per frame}$
 - \rightarrow 1440 x 1080i: 1.6 megapixel (MPx) per frame
- iii. $720p \rightarrow 1280 \ge 720p : -0.9$ megapixel (MPx) per frame

The letter 'P' stands for progressive scan while 'I' indicates interlaced. Interlaced is fine for still and slow moving images. Progressive is fine for high speed video.


5.12 3D TV:

The two dimensional (length and breadth) pictures as we see on the television receiver screen look flat because these lack depth. However in three dimensional (3-D) appears to have all the qualities of a live scenes as viewed with natural vision. The 3-D picture scenes to extend beyond the screen at its back and also in the front.

The block schematic of a possible 3D picture and stereo sound receiver is shown in figure.

The RF amplifier in the tuner has a bandwidth of over 12 MHZ and enough gain to feed sufficient amplitude of RF signal to the mixer (converter) circuits for easy separation of USB and LSB modulation components. The two RF sideband signals are separated by BP filters for feeding to corresponding mixer circuits. The USB IF signal is derived from the RF LSB signal by beating with the carrier equal to (fc –IF) MHZ. from this stage onwards the two IF signals are processed separately, as in a conventional colour TV receiver to obtain the right and left channel RGB video signals.

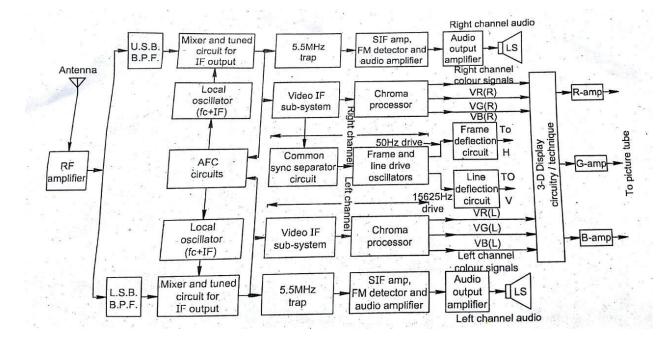The sync pulses are obtained from the composite video signal produced through video IF subsystems. On clipping and processing, these are fed to the vertical and horizontal(line) oscillator circuits for synchronizing, to obtain a steady raster. The right and left channel 5.5 MHZ SIF signals are separated by trap circuits and demodulated in the usual way to feed the two stereo sound loudspeakers.



5.13 BLUE RAY:

5.13.1 Introduction:

Blue ray (or) Blue Ray disc is a next generation digital video disc. It is optical disc storage medium. It was introduced in 1996. It can, record, store, rewrite and play back high definition(HD) video and digital audio as well as large amounts of data.

A single layer BD can store up to 25GB of data and a double layer can store up to 50GB of data.


5.13.2 Disc parameter:

Parameters	
Disk diameter	120 mm
Disk thickness	1.2 mm
Laser wavelength	405 nm
Numerical aperture	0.85
Minimum pit length	0.138µm
	36 Mb/sec
Data rate	
Number of sides	One or two
Number of data layers	One or two
Data capacity	Single layer : 25 GB
	Double layer : 50 GB

The following table shows the characteristics of BD.

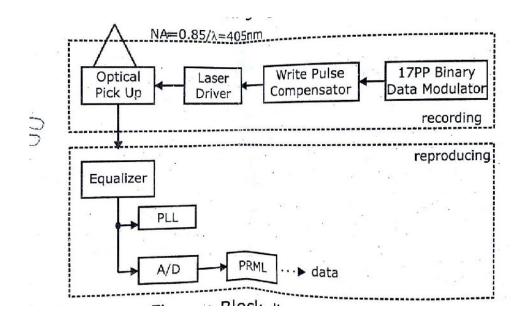5.13.3 RECORDING AND PLAY BACK PRINCIPLES:

The recording and play back principle is described in the following figure



• Recording:


The binary data modulator encodes the NRZI signal according to the 17PP rule. The encoded signal is sent to a write pulse compensator. In which the signal is modulated to multi-pulse. The modulated pulse waveform is sent to a laser driver circuit. The laser driver circuit modulates the power of laser beam to record data on Blue – Ray disc.

• Playback:

To playback the recorded data, the reproduced signal through an equalizer is given to the Phase Locked Loop (PLL). The output of the equalizer is also given to the analog to digital (A/D) converter. The (A/D) converter converts the signal to digital. It is at the clock timing of PLL. Then the signal is passed through a PRML channel to correct the initial bit error. The output is the NRZI signal. It is sent to the subsequent digital signal processing unit.

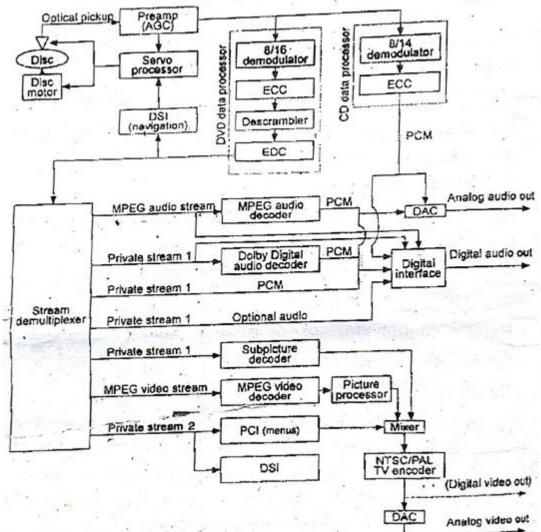5.14 Block diagram of DVD player:

Important sections and their working is explained below.



5.14.1 Optical pickup section:

Using disc motor, DVD rotates. Laser pickup assembly identities the pits and lands in the tracks of rotating disc and gives the corresponding output voltage. DSI (data search information) navigate according to user requirement and gives servo signals for motor rotation according to read data.

5.14.2 DVD data processor:

DVD is modulated with 8 to 16 coding. This is demodulated and compared with details in ECC (Error Correction Code) and it is corrected if there is any error.

After that this is descrambled and verified using EDC(Error Detection Code)

While recording datas are multiplexed and stored. For demultiplexing, it is sent to stream demultiplexer.

5.14.3 CD Data Processor:

DVD player can read CD also. In CD data is modulated by 8 to 14 methods. After demodulation by using ECC. It is verified and the output data is sent to analog and digital output.

Stream demultiplexer:

In DVD at end of each sector EDC will be there. Using this, data is verified and sent to stream demultiplexer. Here all data (audio, video, subtitles) are multiplexed.

Here except MPEG audio / video others are marked as private stream.

By using remote control particular data is selected by using navigation manager data is operated. That selected data is sent to the respective decoders.

5.14.4 Decoding Section:

For each stream there will be distinctive decoders. By using decoders decoding is completed. If digital output is needed it is directly taken as digital and if analog output is needed by using DAC, analog output is taken.

5.14.5 Abbreviations used in block diagram:

ECC:Error Correction Code.

EDC: Error Detection Code

PCM: Pulse Code Modulation

PCI: Presenting Control Information

DSI: Data Search Information

5.15 Desirable features and output of DVD player:

- Since there is no physical content with the disc as it revolves the quality of pictures and sound in DVD.
- Movies on DVD can be seen in wide screen format and we can get an experience of watching in a cinema theatre.

Capacity:

- Single layer DVD hold over a 2 hours and dual layer hold 4 hours over.
- Still picture accompanied by hundreds of hours of audio and next.

Noise

• Most of the LD player make a whirring noise

Video

• DVD use digital video technique

Availability:


• DVD player and disc are available for purchase and rental in thousand of output in internet.

Price:

• Low cost DVD player are cheaper than the cheapest LD player. Most movies on DVD less than on LD.

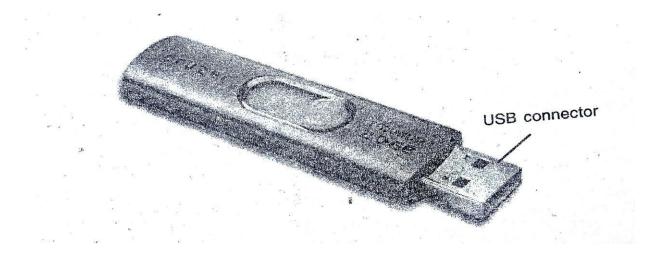5.15 USB flash drive (PEN DRIVE)

USB flash drive is a small portable flash memory card. This can be plugged into computer USB ports and function like a portable hard drive. This drive is otherwise called thump drive or jump drive or pen drive or key drives. These drives were introduced by IBM in December 2000. The figure given below show the structure of a flash drive.



A flash drive consists of a flash memory chip (EEPROM) protected inside a plastic metal. The USB connector is in one side and is protected by a removable cap. Most of the flash drives are preformatted with FAT or FAT 32 file systems. Each sector is of 512 bytes and the first sector contains a master boot record and partition table.

Therefore flash drive can be partitioned as hard drives. Flash drives are available is various capacities such as 1 GB, 2GB, 4GB etc.

5.15.1 Features:

- I. Flash drives are resistance to scratches and other mechanical damage.
- II. It is very small, so it can kept inside the user's pocket.
- III. Storage capacity is higher than a DVD.
- IV. It can be used as audio player.
- V. It uses less power than hard disk.
- VI. The user can insert the flash drive into the computer and use it immediately.

REVIEW QUESTION

$\mathbf{PART} - \mathbf{A}$

- 1. What is scrambling?
- 2. What is descrambling?
- 3. What is CCTV?
- 4. List out some models of DVD.
- 5. Expand HDTV, CCTV and DVD.
- 6. List out the types of scrambling method.

PART-B

- 1. List out some applications of CCTV.
- 2. Explain the types of scrambling.
- 3. List out some features of DVD.
- 4. Explain CCTV in detail.
- 5. What is telecine equipment?

PART-C

- 1. With neat block diagram explain the working of remote control IR transmitter.
- 2. With neat block diagram explain the working of remote control IR receiver.
- 3. With neat block diagram explain the working of descrambler.
- 4. With neat block diagram explain the working of digital CCD telecine equipment(System).
- 5. With neat block diagram explain the working of 3DTV.
- 6. With neat block diagram explain the working of DVD.
- 7. With neat block diagram explain the working of blue ray disc.
- 8. Explain in detail the USB flash drive (pen drive).
- 9. With neat block diagram explain the working of digital colour TV receiver.

1.